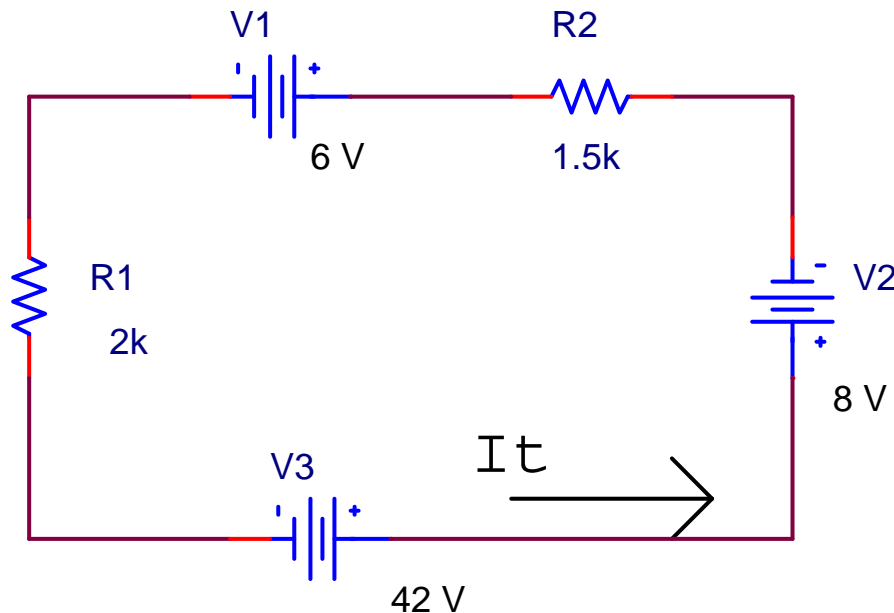


Breakout #1 – Using the same circuit

■ Questions

- ☐ Was source V1 delivering or absorbing power? How much?
- ☐ What about source V2?
- ☐ What about source V3?



Absorbed:

$$P_{V1} = 6\text{ V} \cdot 8\text{ mA} = 48\text{ mW}$$


$$P_{V2} = 8\text{ V} \cdot 8\text{ mA} = 64\text{ mW}$$

Delivered:

$$P_{V3} = 42\text{ V} \cdot 8\text{ mA} = 336\text{ mW}$$

Breakout #2

- Find V_{R1} and V_2

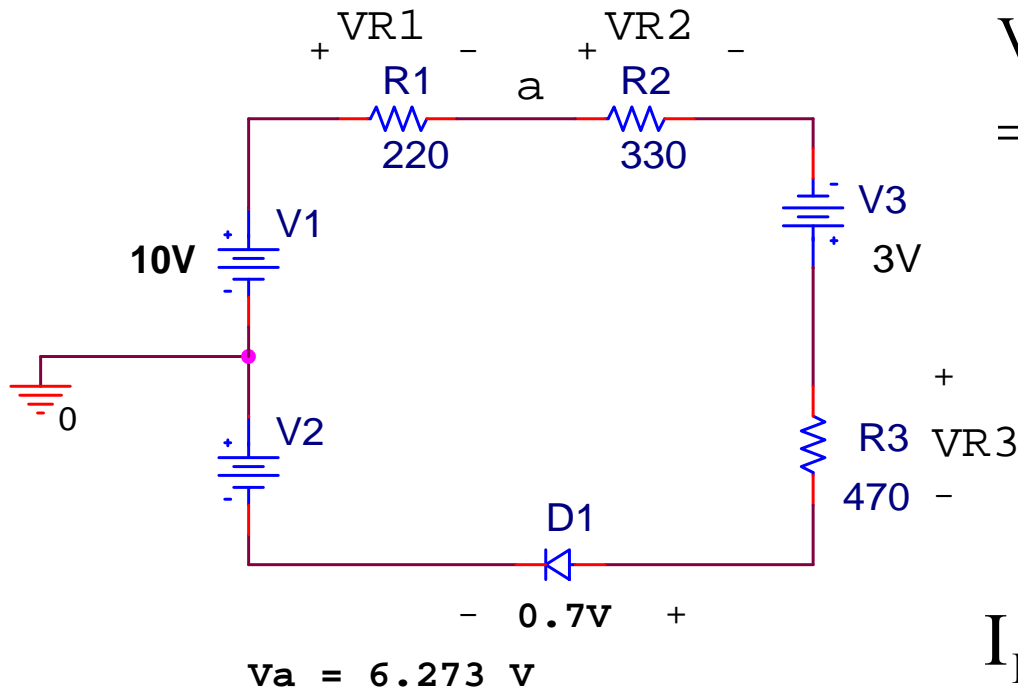

KVL:

$$V_1 - V_{R1} - V_a = 0$$

$$V_{R1} = V_1 - V_a = 10V - 6.273V \\ = 3.727V$$



$$I_{R1} = \frac{V_{R1}}{R_1} = 16.941\text{mA}$$

Left to right

Breakout #2

■ Find V_{R1} and V_2

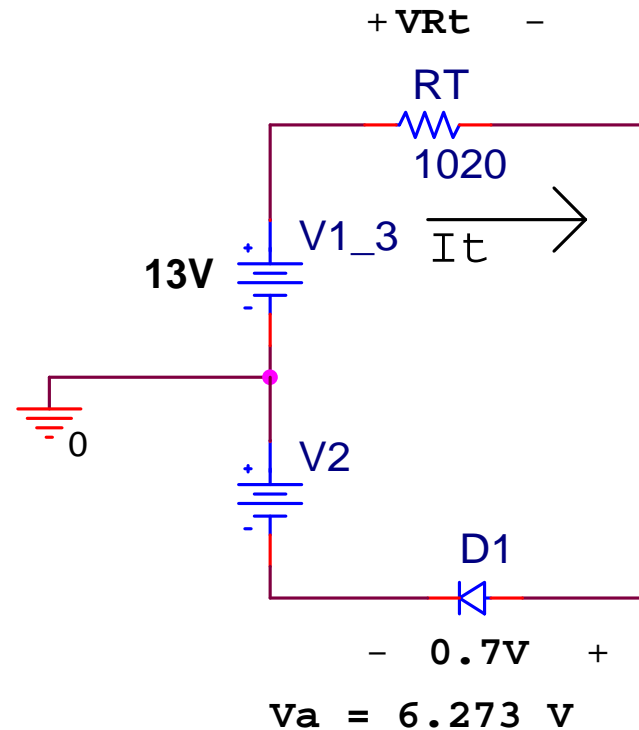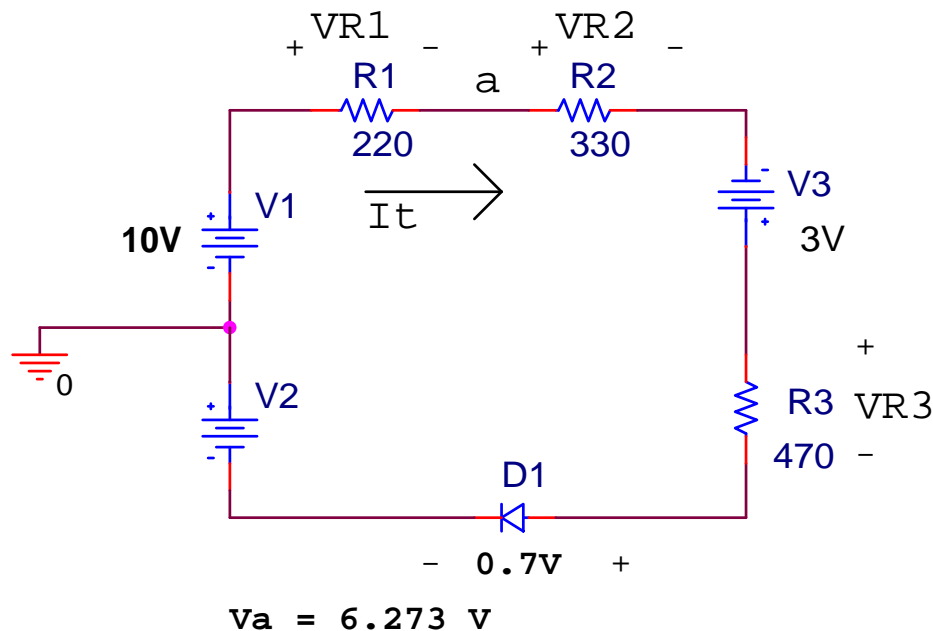
- Simplify the circuit
- Use I_T to find V_{RT} and then KVL for V_2



Breakout #2

■ Find V_{R1} and V_2

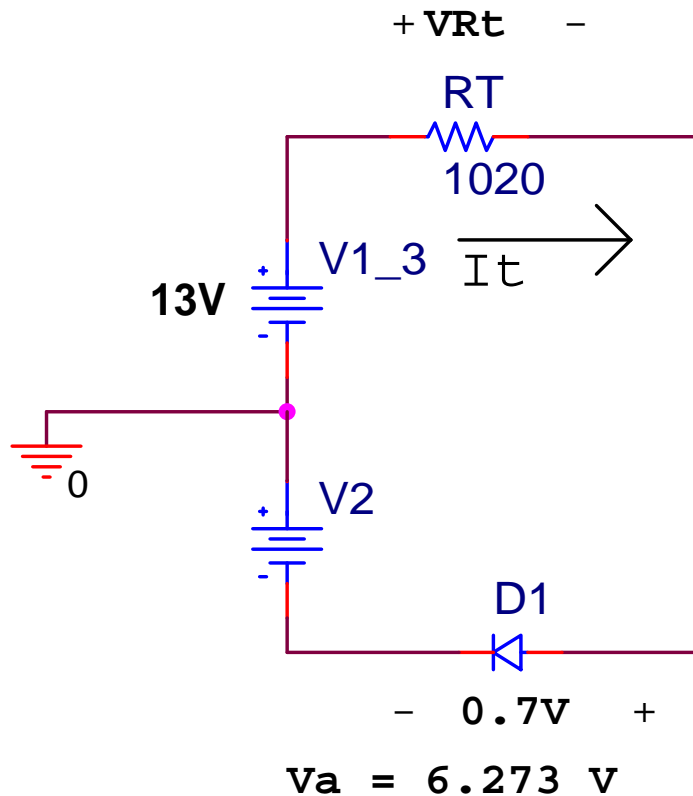- Use I_T to find V_{RT} and then KVL for V_2



$$V_{RT} = I_T \cdot R_T = 17.28V$$

KVL:

$$+13V - 17.28V - 0.7V + V_2 = 0$$

$$V_2 = 17.28V + 0.7V - 13V$$

$$= 4.98V$$