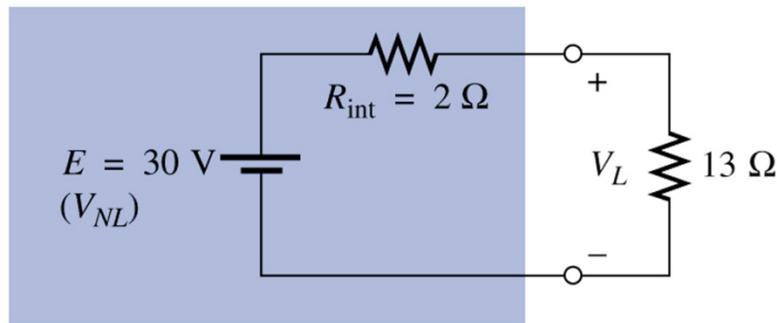


Breakout #1 – Voltage Regulation

- (a) Find the voltage across the load (full-load conditions)
- (b) Find the voltage regulation of the supply
- (c) How much power is lost due to R_{int} (under full-load)?



$$P_{R_{int}} = \frac{V_{R_{int}}^2}{R_{int}} = \frac{(30\text{ V} - 26\text{ V})^2}{2\ \Omega}$$

$$= 8\text{ W}$$


$$V_L = E \cdot \frac{R_L}{R_T} = 30\text{ V} \cdot \frac{13\ \Omega}{15\ \Omega} = 26\text{ V}$$

$$VR = \frac{V_{NL} - V_{FL}}{V_{FL}} \cdot 100\% = \frac{30\text{ V} - 26\text{ V}}{26\text{ V}} \cdot 100\%$$

$$= 15.39\%$$

Breakout #2 – Voltage Divider

- Find V_2 and V_3

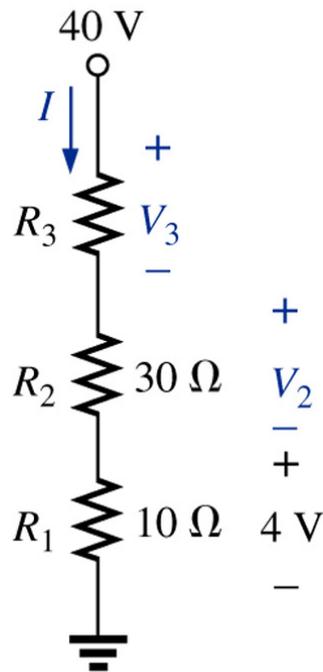

$$V_2 = 3 \cdot 4\ \text{V} = 12\ \text{V}$$

$$V_3 = 40\ \text{V} - (V_2 + 4\ \text{V}) = 24\ \text{V}$$