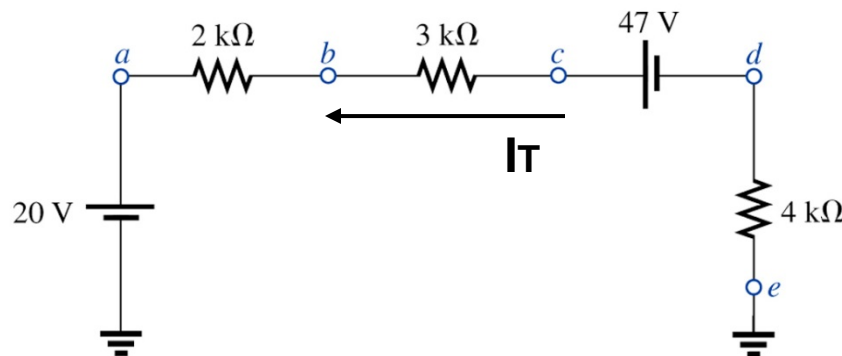


# Breakout #1

## Find

- ☐ The magnitude and direction of current flow
- ☐  $V_b$ ,  $V_c$ ,  $V_d$
- ☐  $V_{ab}$ ,  $V_{cd}$ ,  $V_{de}$



$$I_T = \frac{E_T}{R_T} = \frac{27V}{9K\Omega} = 3mA, CCW$$

$$V_b = 20V + V_{ba} \\ = 20V + I_T \cdot 2K\Omega = 26V$$

$$V_c = V_b + V_{cb} \\ = 26V + I_T \cdot 3K\Omega = 35V$$

$$V_d = V_{de} \\ = -I_T \cdot 4K\Omega = -12V$$

$$V_{ab} = V_a - V_b = 20V - 26V = -6V$$


$$V_{cd} = 47V$$

$$V_{de} = V_d - V_e = -12V - 0V = -12V$$

## Breakout #2

### ■ Find

□  $V_0$ ,  $V_2$ ,  $V_{12}$ ,  $I_i$

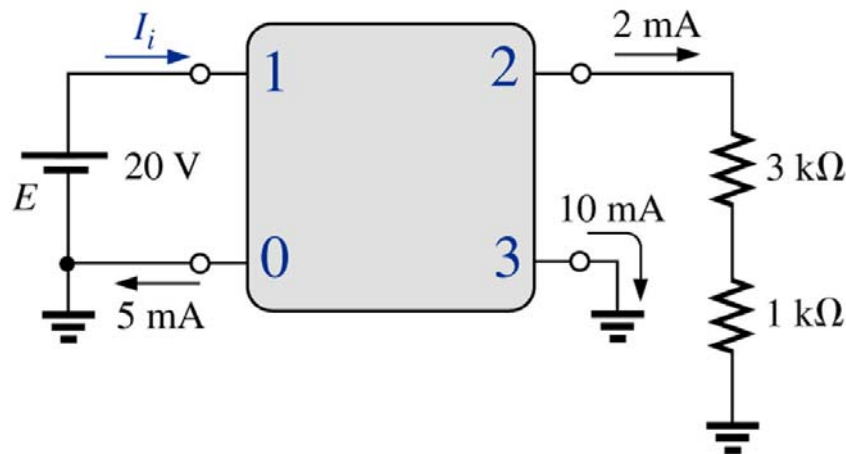

For  $I_i$ , use KCL :

$$I_i = 5 \text{ mA} + 2 \text{ mA} + 10 \text{ mA} \\ = 17 \text{ mA}$$

$$V_0 = 0 \text{ V}$$


$$V_2 = 2 \text{ mA} \cdot 4 \text{ k}\Omega = 8 \text{ V}$$

$$V_{12} = V_1 - V_2 = 20 \text{ V} - 8 \text{ V} = 12 \text{ V}$$

## Breakout #3

### Find


- RT and GT for each circuit

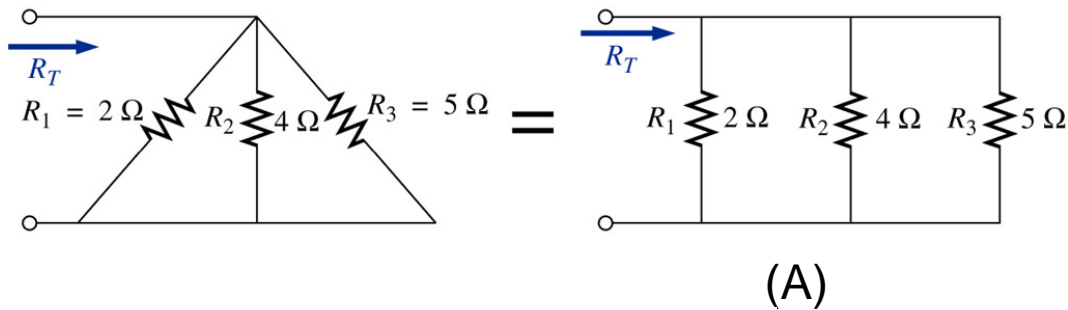

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$= 1.053\ \Omega$$
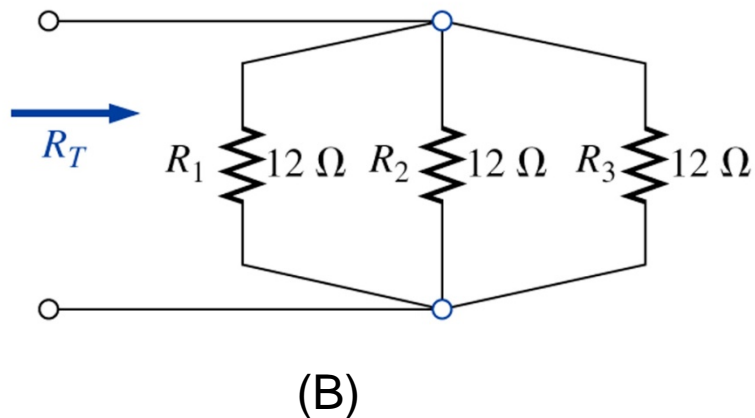
$$G_T = \frac{1}{R_T} = 0.950\ \text{S}$$



$$R_T = \frac{12\ \Omega}{3} = 4\ \Omega$$

$$G_T = \frac{1}{R_T} = 0.25\ \text{S}$$