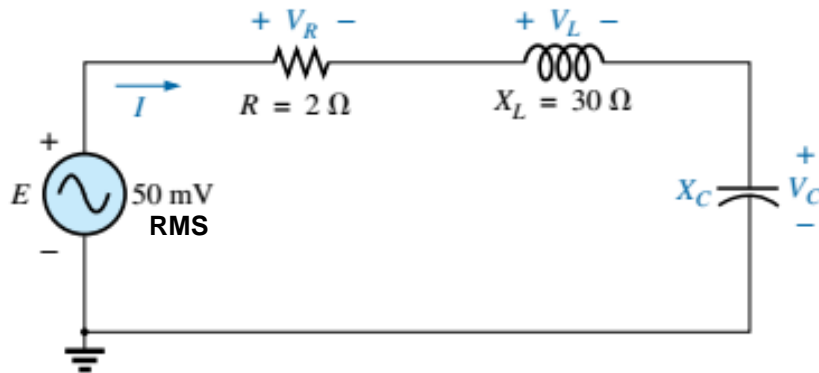



Series Resonance – In Class Problem



Find:

- a) X_C for resonance
- b) Z_T at resonance**
- c) $|I|$ at resonance
- d) $|V_R|$, $|V_L|$, $|V_C|$ at resonance
- e) Q , the quality factor
- f) The power dissipated by the circuit at resonance

Series Resonance – In Class Problem

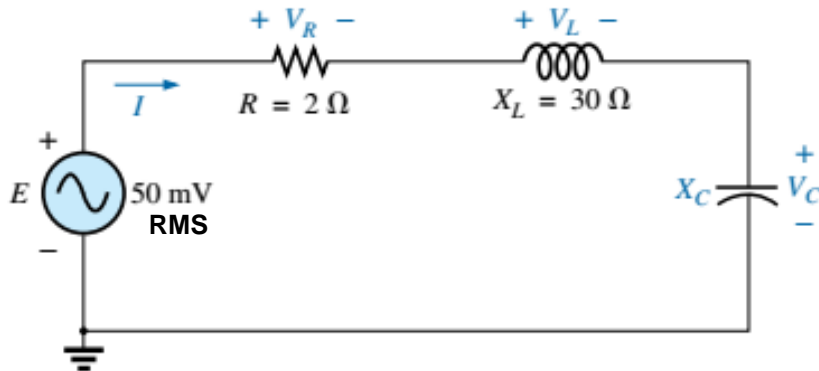

a) X_C for resonance

At f_s , $X_C = X_L = 30 \text{ Ohms}$

b) Z_T at resonance

At f_s , $Z_T = R = 2 \text{ Ohms}$

c) $|I|$ at resonance

At f_s , $I = E/R = 50\text{mV}_{\text{RMS}} < 0^\circ / 2 \text{ Ohms}$

$$I = 25\text{mA}_{\text{RMS}} < 0^\circ$$

$$\text{Or } |I| = 25\text{mA}_{\text{RMS}}$$

d) $|V_R|$, $|V_L|$, $|V_C|$ at resonance

$$V_R = (I)(R) = 50\text{mV}_{\text{RMS}} < 0^\circ$$

$$\text{Or } |V_R| = 50\text{mV}_{\text{RMS}}$$

$$V_L = (I)(Z_L) = 750\text{mV}_{\text{RMS}} < 90^\circ$$

$$\text{Or } |V_L| = 750\text{mV}_{\text{RMS}}$$

$$V_C = (I)(Z_C) = 750\text{mV}_{\text{RMS}} < -90^\circ$$

$$\text{Or } |V_C| = 750\text{mV}_{\text{RMS}}$$

e) Q, the quality factor

$$Q = X_L/R = 30 \text{ Ohms} / 2 \text{ Ohms}$$

$$\text{Or } Q = 15$$

f) The power dissipated by the circuit at resonance

$$P = |I_{\text{RMS}}|^2 R \text{ or } [(25\text{mA}_{\text{RMS}})^2][2 \text{ Ohms}] =$$

$$1.25\text{mW}$$