

# *Electrical Engineering Technology*

**Thevenin's Theorem**


**Spring 2019 (2185)**

## Thevenin's Theorem

- Introduction and Detailed Approach
- Example 1
  - Illustrative example
  - Only independent sources
- Example 2
  - Only independent sources, more complex
  - **Work as we go in your calculator**
- Example 3
  - Includes a dependent source controlled in-network
  - Requires a different method to determine **Z<sub>TH</sub>** (test source)
- In Class Problem
  - Includes a dependent source controlled out-of network
  - Use the standard approach

## Thevenin's Theorem

- Thévenin's theorem, as stated for sinusoidal ac circuits, is changed only to include the term impedance instead of resistance; that is, any two-terminal linear ac network can be replaced with an equivalent circuit consisting of a voltage source and an impedance in series.

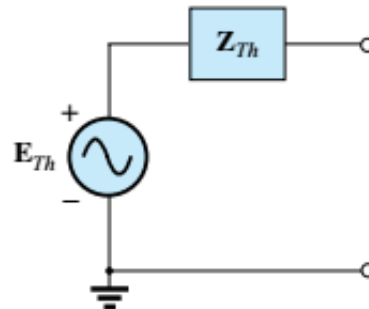

**FIG. 19.23**

*Thévenin equivalent circuit for ac networks.*

## Thevenin's Theorem - Approach

### Independent ac and dc Sources

1. *Remove that portion of the network across which the Thévenin equivalent circuit is to be found.*
2. *Mark ( A and B or a-a' ) the terminals of the remaining two-terminal network.*
3. *Calculate  $Z_{Th}$  by first setting all voltage and current sources to zero (short circuit and open circuit, respectively) and then finding the resulting impedance between the two marked terminals.*
4. *Calculate  $E_{Th}$  by first replacing the voltage and current sources and then finding the open-circuit voltage between the marked terminals.*
5. *Draw the Thévenin equivalent circuit with the portion of the circuit previously removed replaced between the terminals of the Thévenin equivalent circuit.*

**For dependent sources** – Must use an alternate method to find  $Z_{Th}$  if the controlling variable is IN the network under investigation.

## Thevenin's Theorem – Example 1 (Find the Thevenin Equivalent Circuit)

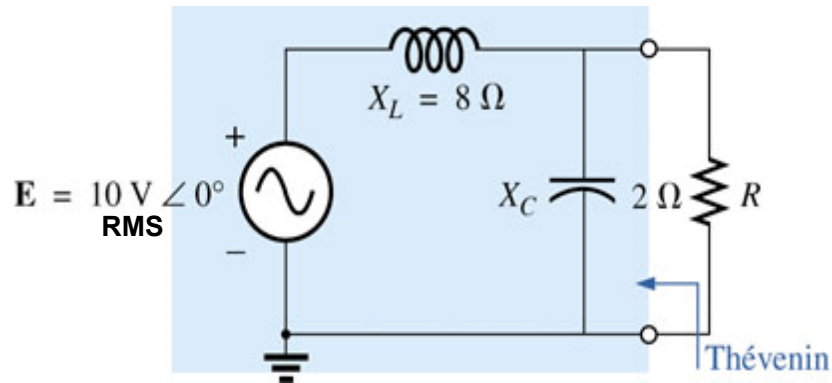


FIG. 19.24 Example 19.7.

**Steps 1,2:** Redraw and label the terminals

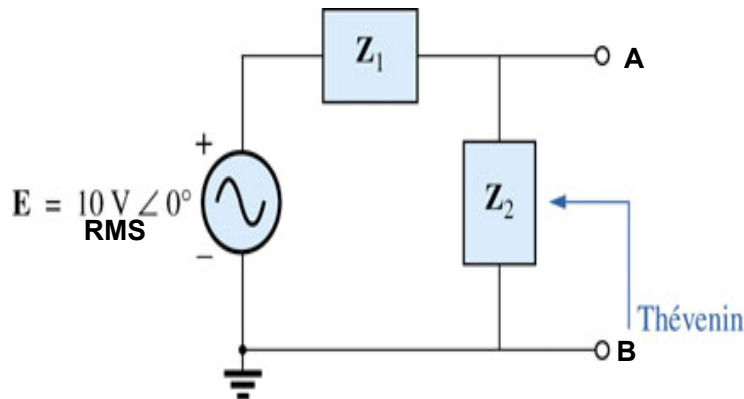


FIG. 19.25 Assigning the subscripted impedances to the network in Fig. 19.24.

$$Z_1 = jX_L = j8 \Omega$$

$$Z_2 = -jX_C = -j2 \Omega$$

**Step 3:** Find  $Z_{TH}$  (relax the independent sources)

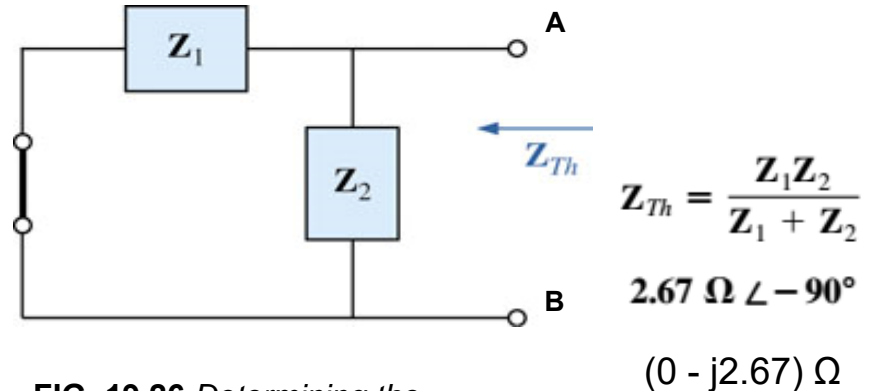


FIG. 19.26 Determining the Thévenin impedance for the network in Fig. 19.24.

**Step 4:** Find  $E_{TH}$  ( $V_{AB}$  open-circuit)

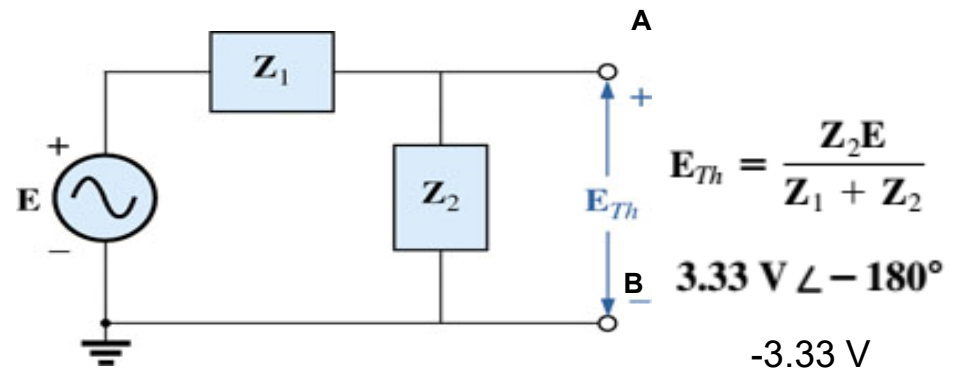


FIG. 19.27 Determining the open-circuit Thévenin voltage for the network in Fig. 19.24.

## Thevenin's Theorem – Example 1 (Find the Thevenin Equivalent Circuit)


$$Z_{Th} = 2.67 \, \Omega \angle -90^\circ$$

$$(0 - j2.67) \, \Omega$$

$$E_{Th} = 3.33 \, \text{V} \angle -180^\circ$$


$$-3.33 \, \text{V}$$

**Step 5:** Draw the Thevenin Equivalent Circuit

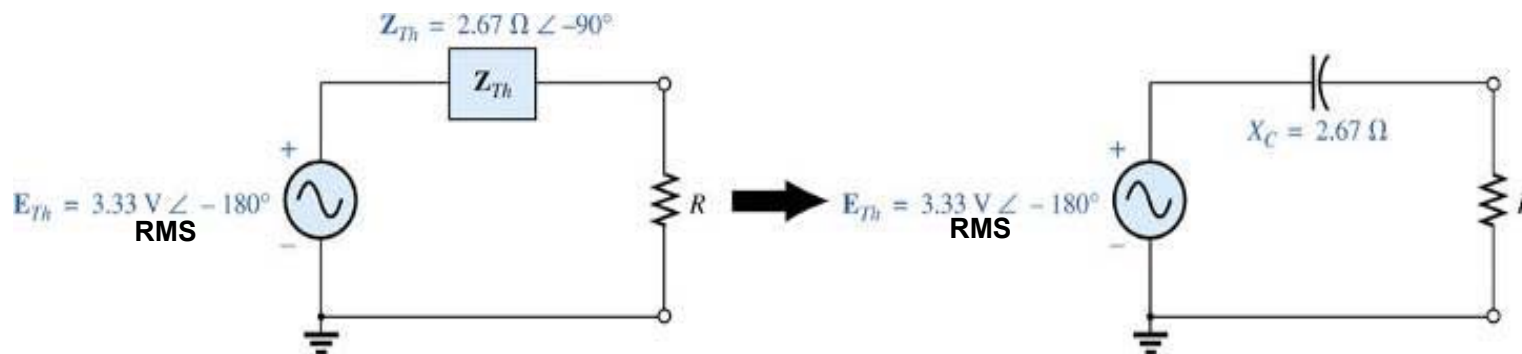


**FIG. 19.28** The Thévenin equivalent circuit for the network in Fig. 19.24.
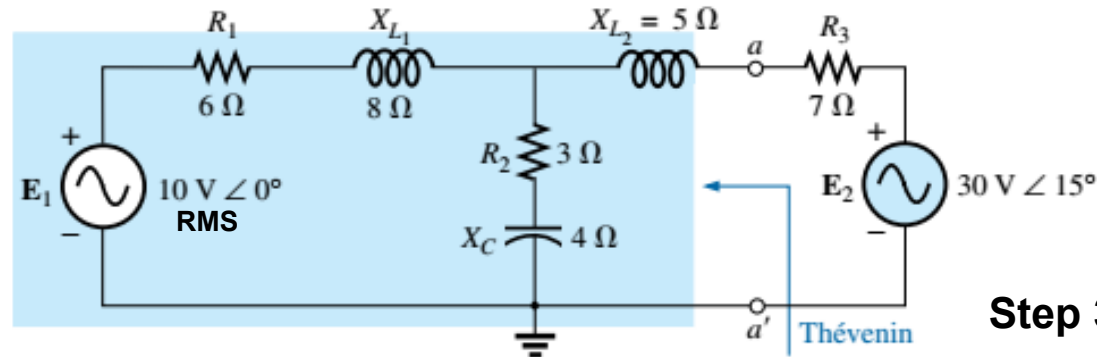
## Thevenin's Theorem – Example 2 (use your calculator)



**Find:** the Thevenin equivalent circuit looking into terminals a-a'

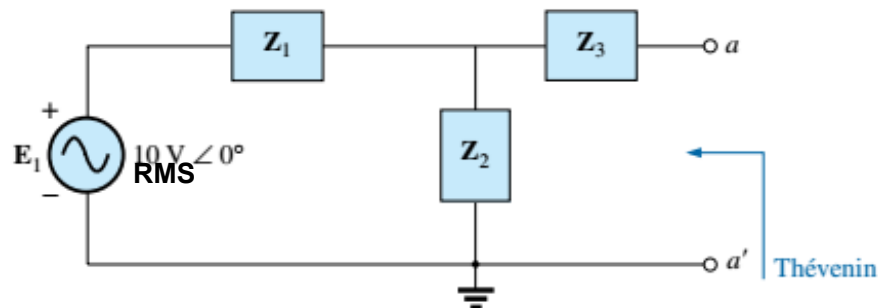**Steps 1&2:** Redraw, removing E2 and R3 (external to the network terminals), keep track of a-a'




$$Z_1 = R_1 + jX_{L1} = 6 \Omega + j8 \Omega$$

$$Z_2 = R_2 - jX_C = 3 \Omega - j4 \Omega$$

$$Z_3 = +jX_{L2} = j5 \Omega$$

**Step 3: Find  $Z_{TH}$**

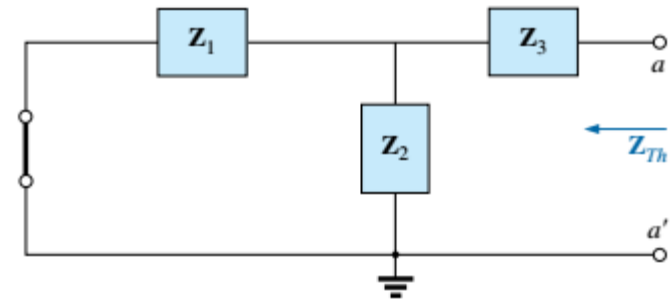


$$\vec{Z}_{TH} = (\vec{Z}_1 // \vec{Z}_2) + \vec{Z}_3$$

$$\begin{aligned} Z_{Th} &= Z_3 + \frac{Z_1 Z_2}{Z_1 + Z_2} \\ &= j5 \Omega + \frac{(10 \Omega \angle 53.13^\circ)(5 \Omega \angle -53.13^\circ)}{(6 \Omega + j8 \Omega) + (3 \Omega - j4 \Omega)} \end{aligned}$$

$$Z_{Th} = 4.64 \Omega + j2.94 \Omega$$

## Thevenin's Theorem – Example 2 (use your calculator)

**Step 4: Find  $E_{Th}$**

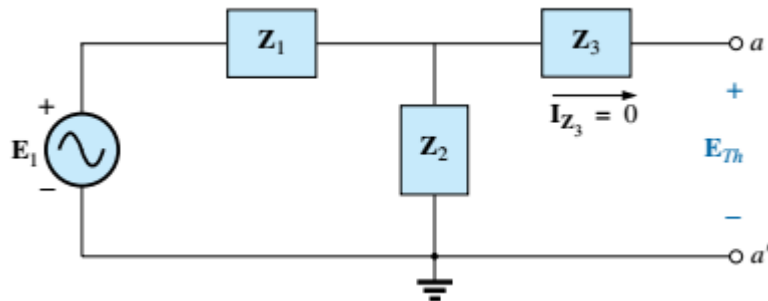

$$Z_1 = R_1 + jX_{L_1} = 6 \Omega + j8 \Omega$$

$$Z_2 = R_2 - jX_C = 3 \Omega - j4 \Omega$$



$$Z_3 = +jX_{L_2} = j5 \Omega$$

$$E_{Th} = \frac{Z_2 E_1}{Z_2 + Z_1}$$

$$= \frac{(5 \Omega \angle -53.13^\circ)(10 \text{ V} \angle 0^\circ)}{9.85 \Omega \angle 23.96^\circ}$$


$$E_{Th} = \frac{50 \text{ V} \angle -53.13^\circ}{9.85 \angle 23.96^\circ} = 5.08 \text{ V} \angle -77.09^\circ \text{ RMS}$$

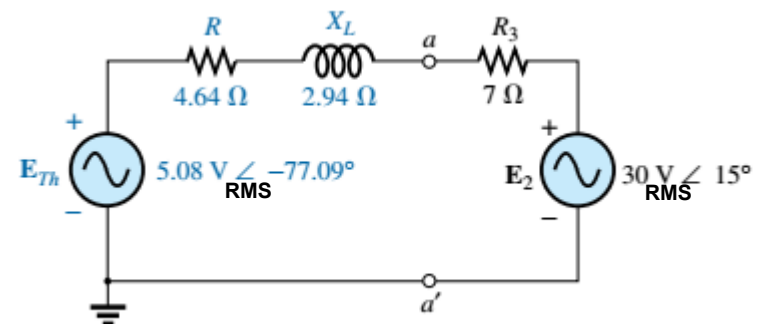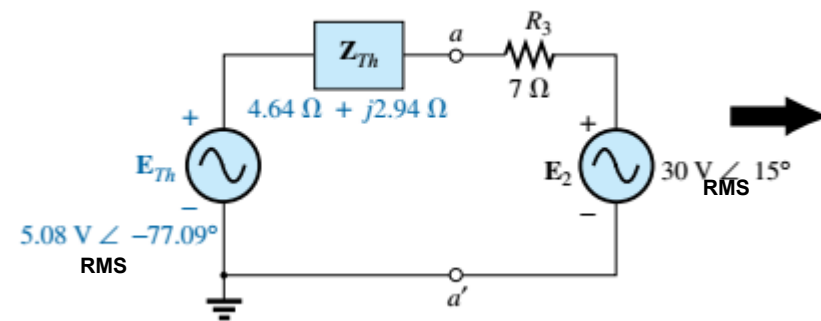**Step 5: Draw the Thevenin Equivalent Circuit**





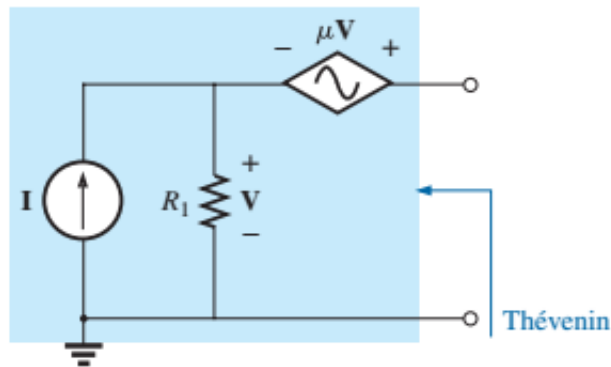
## Thevenin's Theorem – Example 3 (dependent source controlled within network)



**Note:** The network contains a dependent source that is controlled by a voltage in the network

- Find  $V_{TH}$  as usual
- Find  $Z_{TH}$  using an alternate method (test source)

**Steps 1&2:** Redraw, keep track of a-b

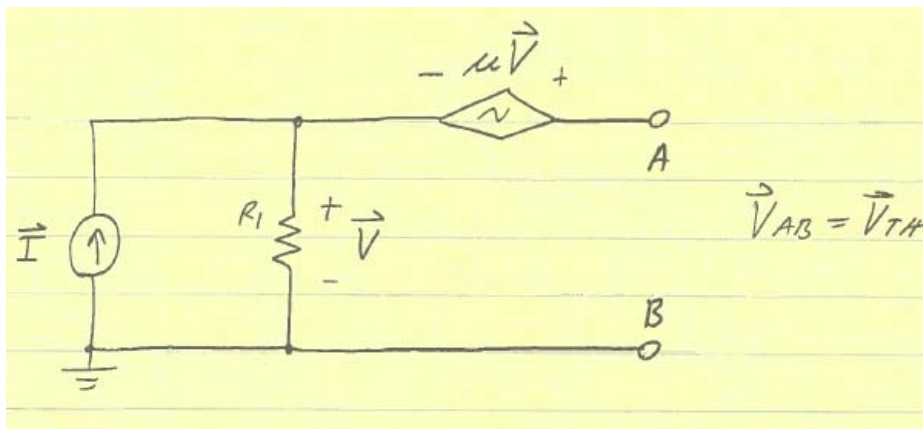

**Step 4:** Find  $V_{TH}$

$$\text{KVL: } \vec{V} + \mu\vec{V} - \vec{V}_{TH} = 0$$

$$\therefore \vec{V}_{TH} = \vec{V} + \mu\vec{V}$$


$$\text{BUT } \vec{V} = \vec{I}R_1$$

$$\therefore \vec{V}_{TH} = \vec{I}R_1 + \mu\vec{I}R_1$$

$$\text{OR } \boxed{\vec{V}_{TH} = \vec{I}R_1(1 + \mu)}$$


**Note:**  $V_{TH}$  ( $E_{TH}$ ) is a dependent voltage source itself
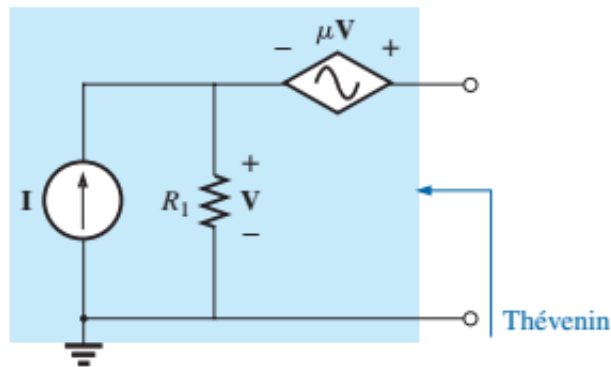
## Thevenin's Theorem – Example 3 (dependent source controlled within network)



**Step 3:** Find  $Z_{TH}$  by

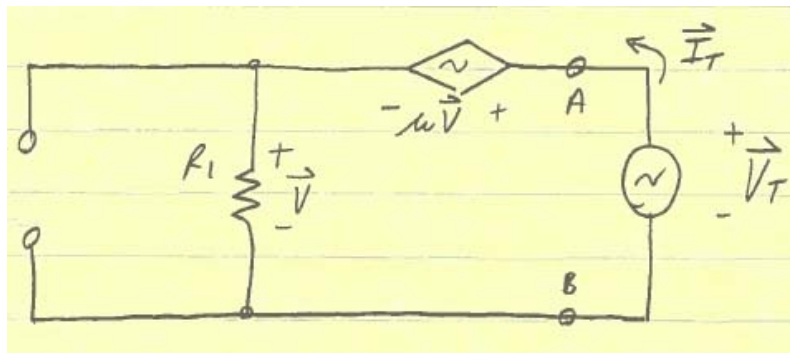- Relaxing the independent sources (I)
- Applying a test-source across a-b



$$KVL: \vec{V}_T = \mu \vec{V} + \vec{V}$$

$$BUT \vec{V} = \vec{I}_T R_1$$


$$\therefore \vec{V}_T = \mu \vec{I}_T R_1 + \vec{I}_T R_1$$

$$\frac{\vec{V}_T}{\vec{I}_T} = \mu R_1 + R_1$$


$$\vec{Z}_{TH} = \boxed{R_1(1 + \mu)}$$

$$\vec{Z}_{TH} = \frac{\vec{V}_T}{\vec{I}_T}$$

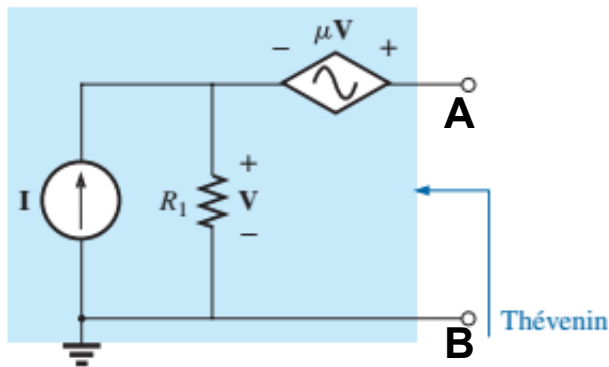
## Thevenin's Theorem – Example 3 (dependent source controlled within network)



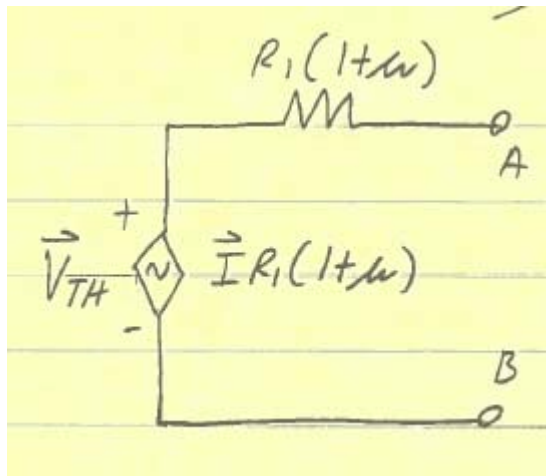Step 5: Draw the Thevenin Equivalent Circuit



## In Class Problem

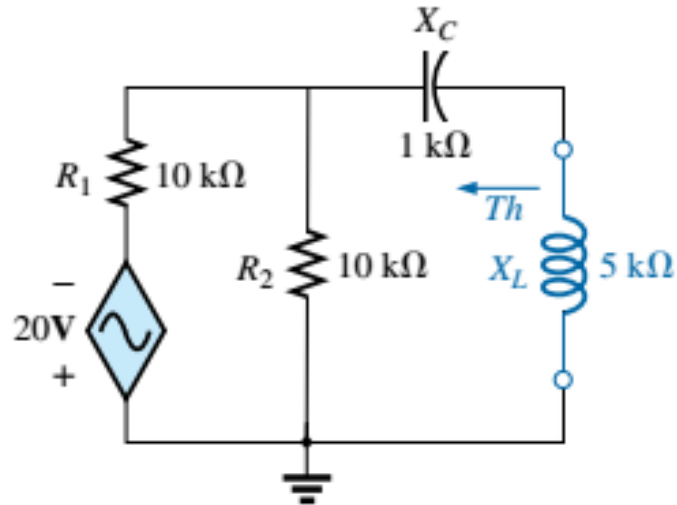

### Find:

- The Thevenin equivalent circuit for the network external to the inductor

### Approach:

- Standard Thevenin approach
  - Dependent source is controlled out of the network of interest