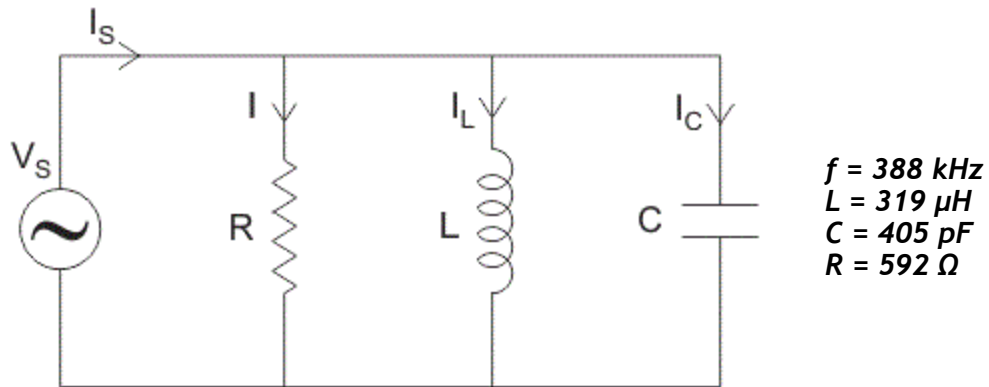


32. A 4.7 k Ω resistor has a conductance of:
- a. 213 mS
 - b. **213 μ S**
 - c. 4.7 S
 - d. 4.7 mS
33. At 62 kHz, a 527 nF capacitor has a susceptance of:
- a. 4.87 mS
 - b. 4.87 S
 - c. 205 S
 - d. **205 mS**
34. At 261 Hz, a 682 mH inductor has a susceptance of:
- a. 1.12 kS
 - b. 1.12 S
 - c. **894 μ S**
 - d. 894 mS
35. If $Z_L = (503 + 223j) \Omega$, $Y_L =$
- a. $(223 + 503j) S$
 - b. $(1.66 + 0.737j) mS$
 - c. **$(1.66 - 0.737j) mS$**
 - d. 550 S




36. Total admittance seen by the source is:

$$(1.715 \text{ mS} \angle -10^\circ) = (1.689 - j0.299) \text{ mS}$$

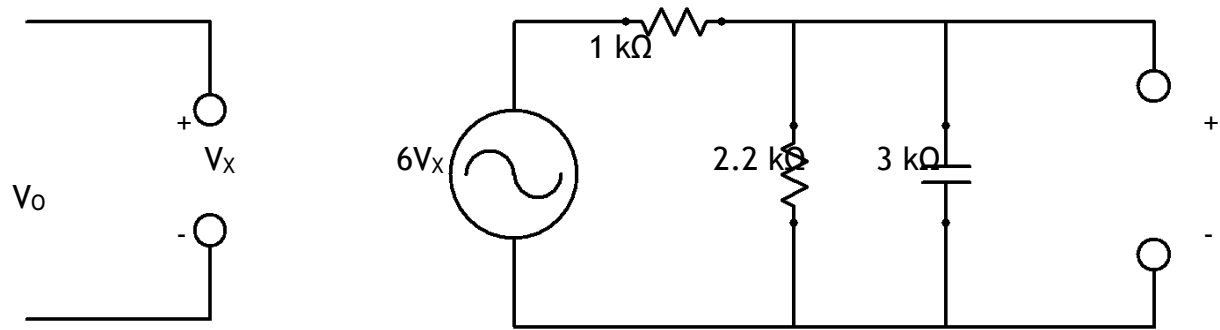37. If $I_s = (1.2 \angle 70^\circ) \text{ A}$, $I_L =$


$$(899.5 \text{ mA} \angle -10^\circ) = (0.886 - j0.156) \text{ mA}$$




38. If $V_X = (8 \angle 10^\circ) \text{ V}$, what is V_0 ?


$$(31.2 \text{ V} \angle -2.9^\circ) = (32.1 - j1.632) \text{ V}$$

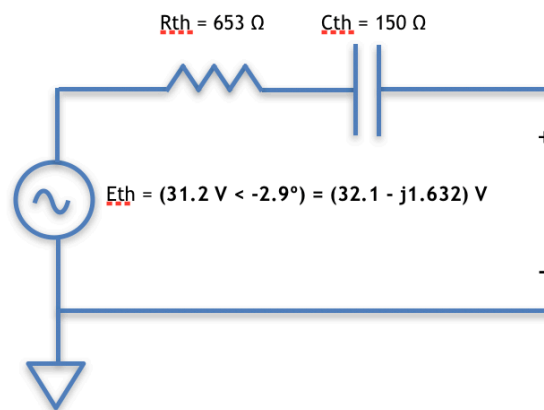39. Draw the Thevenin equivalent circuit external to V_0 , assuming $V_X = (8 \angle 10^\circ) \text{ V}$.



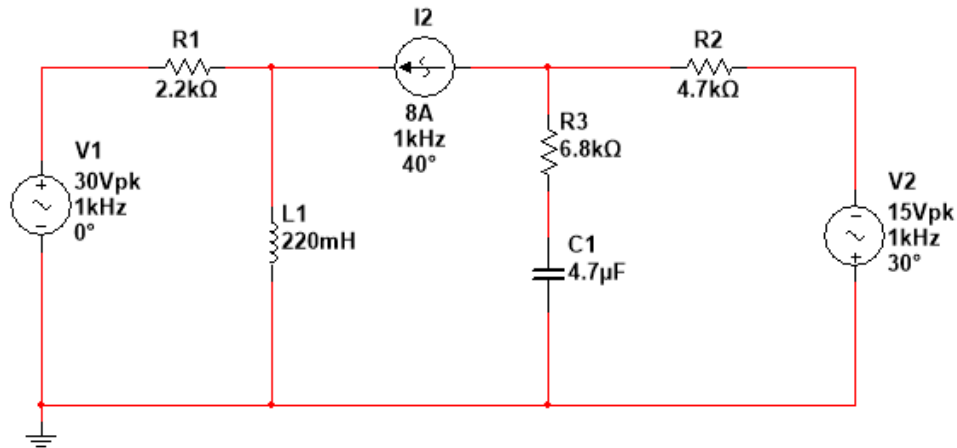


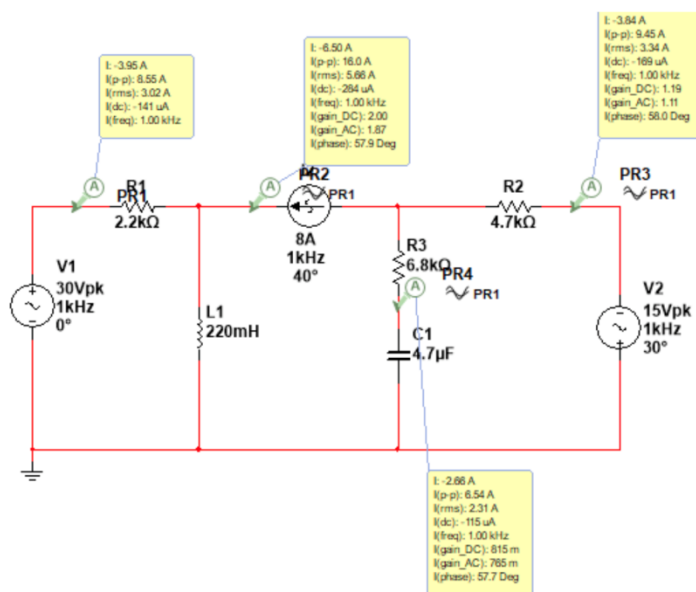40. Using mesh analysis, find the 3 loop currents for the circuit above.




41. How much power is dissipated by the 3 resistors?

108.8 kW

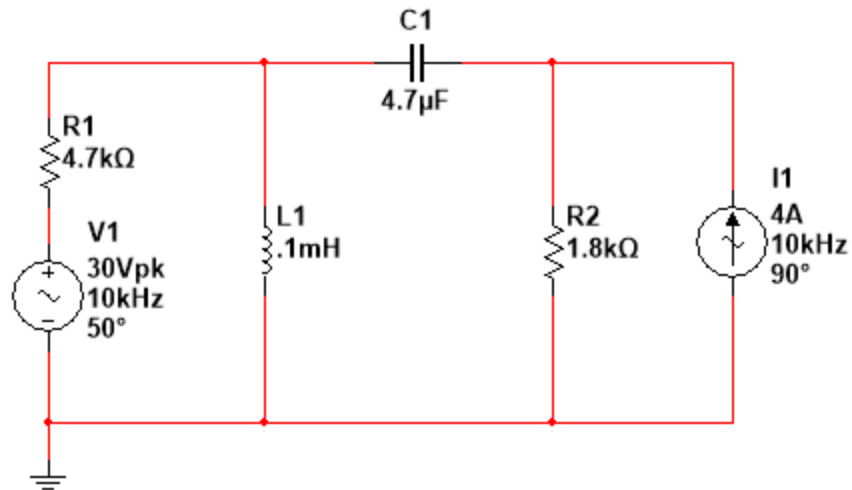


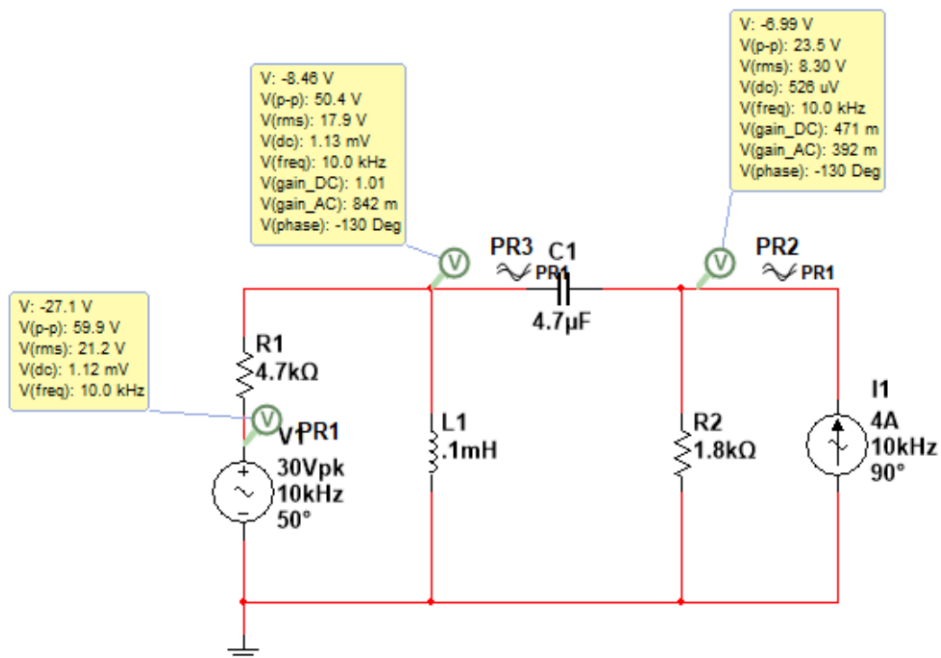42. Using nodal analysis, find the voltage at all nodes in the circuit above.



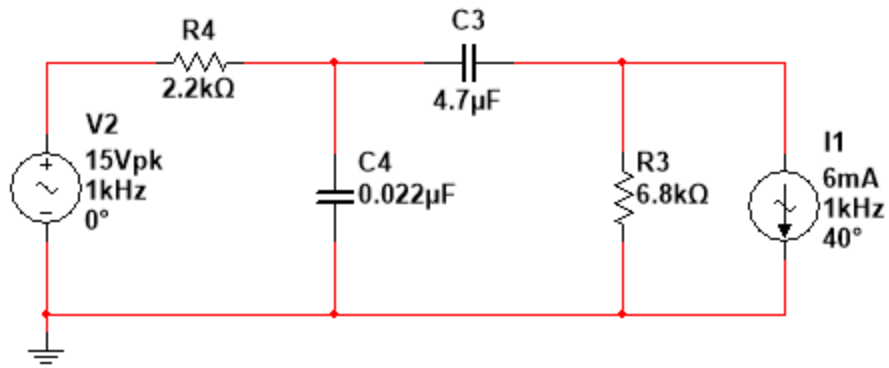43. What is the current through the capacitor C_1 ?

$$(3.972 \text{ A} \angle -40^\circ) = (3.043 - j2.553) \text{ A}$$



44. Using **superposition**, find the voltage across R_3 .


$$(7.038 \text{ V} \angle 102^\circ) = (-1.463 + j6.884) \text{ V}$$

45. How much power is supplied by the source I_1 ?

$$42.23 \text{ mW}$$

46. For the power triangle to the right, find S and θ .

$$S = (610 \angle 35^\circ) \text{ VA}$$

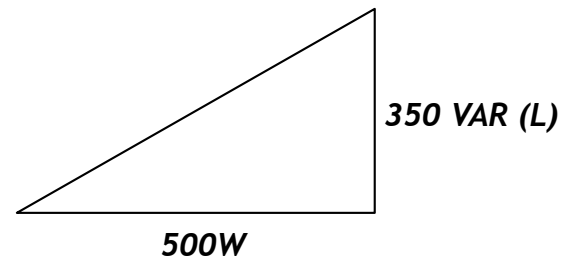


47. For the power triangle above, if the source voltage is $(120 \angle 0^\circ) \text{ V}_{\text{rms}}$, what is the source current?

$$I = S^* / V = (610 \angle -35^\circ) \text{ VA} / (120 \angle 0^\circ) \text{ V} = (5.08 \angle -35^\circ) \text{ A}$$

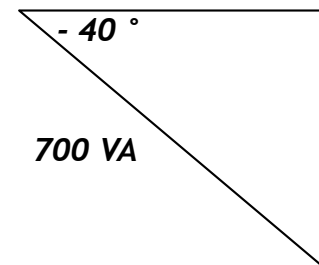48. For the power triangle to the right, find P and Q .

$$P = 536 \text{ W}$$
$$Q = 450 \text{ VAR (C)}$$




49. If the source voltage is $240 \text{ V}_{\text{rms}}$ and the frequency is 50 Hz , what value of inductor would be needed to achieve unity power factor in the system above?


$$Q_L = 450 \text{ VAR} = (240 \text{ V}_{\text{rms}})^2 / X_L$$

$$X_L = 128 \Omega = 2\pi fL$$

$$L = 407 \text{ mH}$$

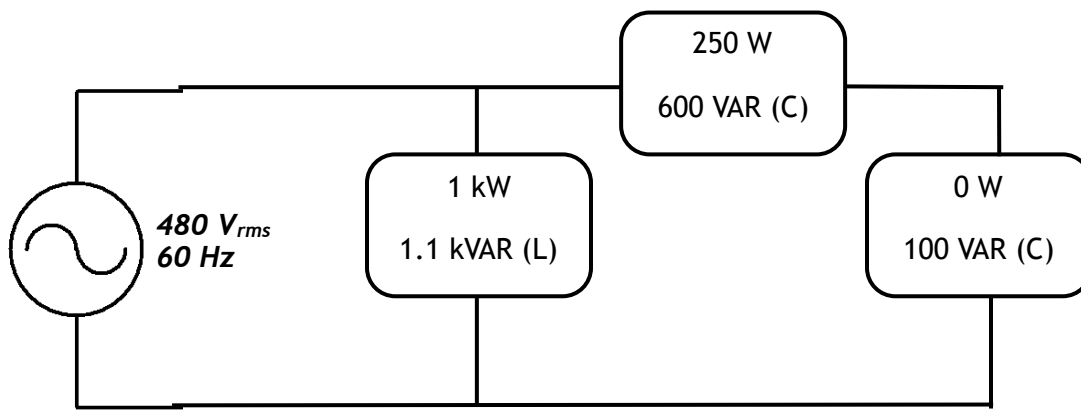

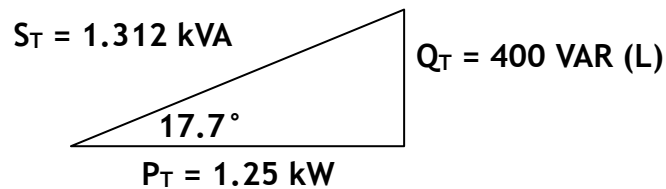50. Draw a fully-labeled power triangle for the system above (P, Q, S, θ)



51. For the 1 kW load, determine what component(s) comprise it.

$$R = (480\text{ V}_{rms})^2 / 1\text{ kW} = 230.4\ \Omega$$

$$X_L = (480\text{ V}_{rms})^2 / 1.1\text{ kVAR} = 209.5\ \Omega = 2\pi fL$$

$$L = 556\text{ mH}$$

52. What component (type and value) would be needed to correct the system power factor?

$$X_C = (480\text{ V}_{rms})^2 / 400\text{ VAR} = 576\ \Omega = 1 / (2\pi fC)$$

$$C = 1 / (2\pi * 60\text{ Hz} * 576\ \Omega) = 4.605\ \mu\text{F}$$

Changlog:

1. Answers to #35 were updated.