

1.  $5 V_{pk}$  is equivalent to:
- $7.07 V_{pk-pk}$
  - $10 V_{pk-pk}$**
  - $2.5 V_{pk-pk}$
  - $25 V_{pk-pk}$
2.  $20 V_{pk}$  is equivalent to:
- $14.14 V_{rms}$**
  - $28.28 V_{rms}$
  - $10 V_{rms}$
  - $40 V_{rms}$
3.  $V(t) = 5 \sin(377t + 30^\circ)$   
What is the peak value of  $V(t)$ ?
- $3.53 V_{pk}$
  - $2.5 V_{pk}$
  - $5 V_{pk}$**
  - $7.07 V_{pk}$
4. At 1 kHz, a  $10 \mu F$  capacitor has a reactance of:
- $6.28 m\Omega$
  - $15.9 \Omega$**
  - $159 k\Omega$
  - $159 \Omega$
5. At 60 Hz, a 22 mH inductor has a reactance of:
- $8.3 \Omega$**
  - $8.3 k\Omega$
  - $1.32 \Omega$
  - $121 m\Omega$

6. See the phasor diagram to the right. What component(s) compose  $Z_T$ ?
- a. Resistor
  - b. Inductor
  - c. Capacitor
  - d. Resistor and Inductor
  - e. Resistor and Capacitor**
  - f. Inductor and Capacitor
7. As frequency increases, the reactance of a capacitor will:
- a. Decrease**
  - b. Increase
  - c. Remain the same
  - d. It depends on other factors within the circuit
8. At DC, an ideal inductor looks like:
- a. A resistor
  - b. A capacitor
  - c. An open circuit
  - d. A short circuit**

For questions 9 thru 16, express your answer in both rectangular and polar form.  
Read these questions carefully!

$$9. \quad (6 \angle 40^\circ) + (8 - 2j) = (12.73 \angle 8.39^\circ) = (12.6 + 1.86j)$$

$$10. \quad (8 \angle 10^\circ) - (7 \angle -10^\circ) = (2.785 \angle 69.3^\circ) = (0.985 + 2.605j)$$

$$11. \quad (5 - 8j) * (5 \angle 8^\circ) = (47.17 \angle -50.0^\circ) = (30.32 - 36.13j)$$


$$12. \quad [ (-10 + j) + (4 \angle 33^\circ) ] / (-8 \angle 72^\circ) = (0.921 \angle -97.6^\circ) = (-0.121 - 0.913j)$$

$$13. \quad [ (-41 \angle -98^\circ) - (83 - 74j) ] * [ (96 \angle 53^\circ) - (64 \angle -84^\circ) ] = (20.6k \angle -166^\circ) = (-20k - 5kj)$$

$$14. \quad \frac{[ (-93 - 66j) + 10j + (37j + 51) ]}{[ (75 \angle -37^\circ) - (-47 \angle -5^\circ) - (15 \angle 4^\circ) ]} = (0.441 \angle -127^\circ) = (-0.265 - 0.352j)$$

$$15. \quad \frac{[ (-65 \angle 7^\circ) + (-78 + 13j) + (42 \angle -21^\circ) ] * [ (-5j + 94) * (-8 + 29j) ]}{[ (14 \angle -82^\circ) + (94 \angle -55^\circ) - (-23j + 86) ]} = (3.758k \angle 63.3^\circ) = (1.687k + 3.358kj)$$

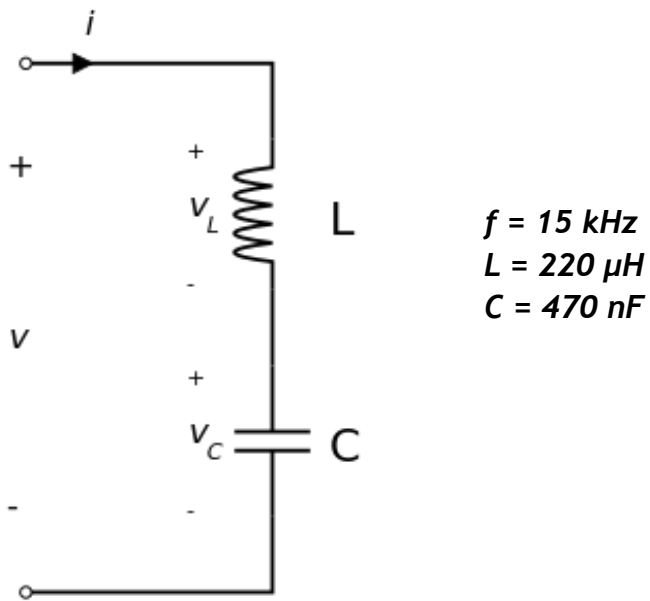
$$16. \quad \frac{[ (67 + 56j) * (-15 - 72j) ] + [ (-83 * -55j) - (-69 \angle 80^\circ) - (-50 + 77j) ]^2}{[ (10 \angle 27^\circ) + (-52 + 77j) - (92 \angle -51^\circ) ]^3} = (3.367 \angle 168^\circ) = (-3.296 + 0.689j)$$



Questions 17 thru 19 are based on the circuit above.


17. What is the total impedance of the series circuit?
- $(30.68 \angle -48^\circ) \Omega$
  - $(20.73 \angle 90^\circ) \Omega$
  - $(22.58 \angle -90^\circ) \Omega$
  - $(1.841 \angle -90^\circ) \Omega$
18. If the applied voltage is  $(8 \angle 15^\circ) \text{ V}$ , what is the current?
- $(261 \angle 63^\circ) \text{ mA}$
  - $(386 \angle -75^\circ) \text{ mA}$
  - $(354 \angle 105^\circ) \text{ mA}$
  - $(4.35 \angle 105^\circ) \text{ A}$
19. What is  $V_L$ ?
- $(90.1 \angle -165^\circ) \text{ V}$**
  - $(7.35 \angle 105^\circ) \text{ V}$
  - $(8.0 \angle -75^\circ) \text{ V}$
  - $(5.41 \angle 63^\circ) \text{ V}$

This answer was misprinted in rev A.

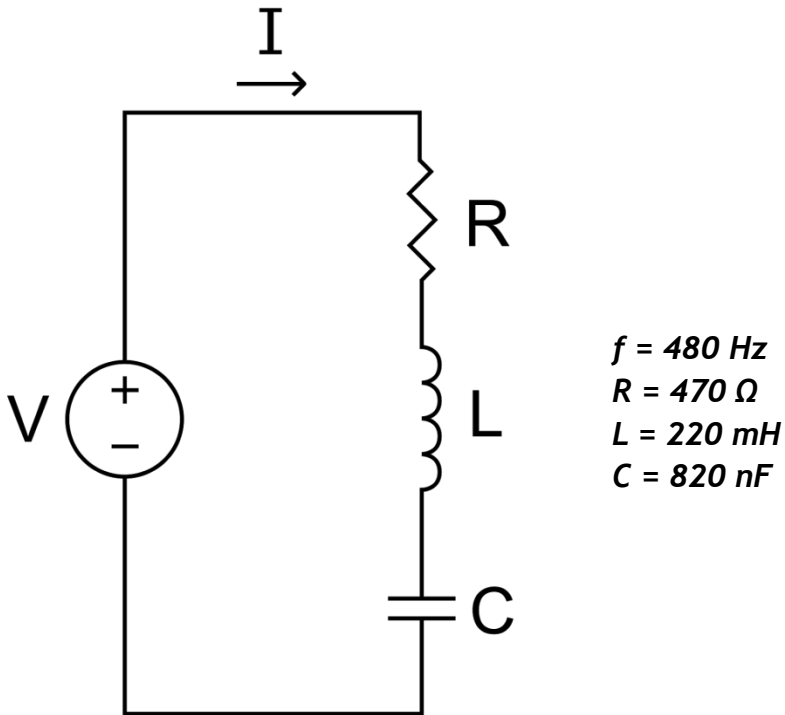

Questions 20 and 21 are based on the circuit above.

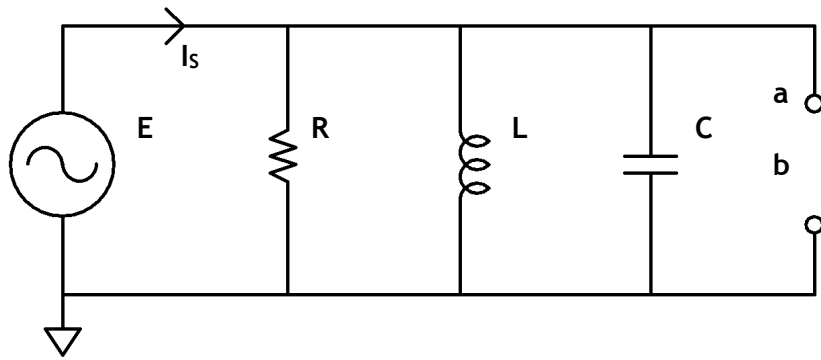20. What is the total impedance of the circuit?
- a.  $(620 \angle -40.7^\circ) \, \Omega$
  - b.  $(813 \angle 54.7^\circ) \, \Omega$
  - c.  **$(537 \angle 28.9^\circ) \, \Omega$**
  - d.  $(259 \angle 90^\circ) \, \Omega$
21. If the applied voltage is  $(120 \angle 0^\circ) \text{ V}$ , what is the voltage across the resistor?
- a.  $(876 \angle -28.9^\circ) \text{ mV}$
  - b.  **$(105 \angle -28.9^\circ) \text{ V}$**
  - c.  $(148 \angle 61.1^\circ) \text{ V}$
  - d.  $(90.4 \angle -28.9^\circ) \text{ V}$



$$\begin{aligned}
 f &= 5 \text{ kHz} \\
 R &= 771 \, \Omega \\
 L &= 60 \, \mu\text{H} \\
 C &= 663 \text{ nF} \\
 I_s &= (503 \angle 126^\circ) \text{ mA}
 \end{aligned}$$

Questions 22 thru 27 are based on the circuit above.

22. What is the total impedance seen by the source?

$$(1.962 \angle 89.9^\circ) = (0.00499 + 1.962j)$$

$$\text{was previously found to be } (1.814 \angle 89.9^\circ) = (0.0043 + 1.814j)$$

23. What is  $E_s$ ?

$$(0.987 \angle -144^\circ) = (-0.8 - 0.578j)$$

$$\text{was previously found to be } (0.912 \angle -144^\circ) = (-0.739 - 0.534j)$$

24. What is  $I_C$ ?


$$(0.021 \angle -54.2^\circ) = (0.012 - 0.017j)$$

$$\text{was previously found to be } (0.019 \angle -54.1^\circ) = (0.011 - 0.015j)$$

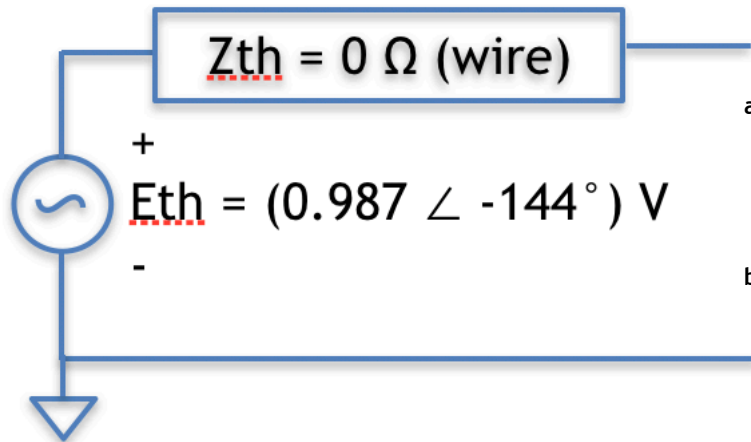25. Draw the Thévenin equivalent circuit (voltage source and series impedance).

In an effort to find  $Z_{th}$ , we must relax the voltage source. When we do this, we get a short circuit ( $0 \Omega$ ) in parallel with the rest of the components, thus  $Z_{th} = 0 \Omega$ .

In a parallel circuit, the voltage is the same across all components. This means  $E_{th} = E_s = (0.987 \angle -144^\circ) \text{ V} = (-0.8 - 0.578j) \text{ V}$ .



26. What load placed across terminals  $a$  and  $b$  would dissipate the most power?


The answer to this question is simply an ideal wire because of the lack of  $Z_{th}$ .

This was previously found to be  $(0.019 \angle 54.1^\circ) = (0.011 + 0.015j)$ .

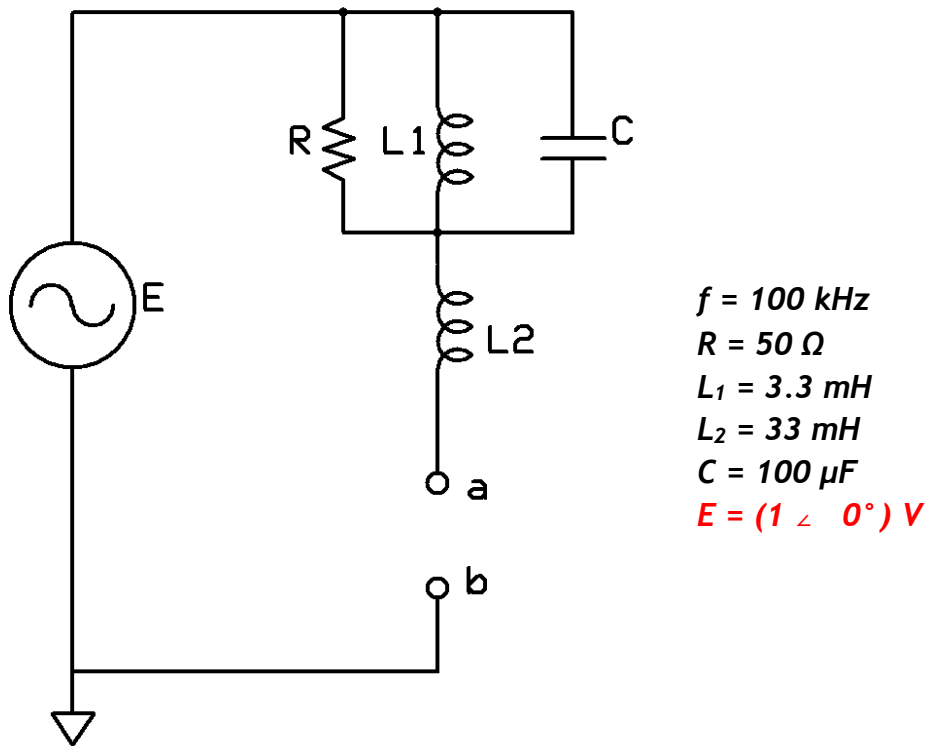27. How much average power would the load you selected in the previous question dissipate?

This is indeterminate.

This was previously found to be **37.8 W**.




Questions 28 thru 30 are based on the circuit above.

28. What is the Thévenin impedance of the circuit external to points *a* and *b*?  
 $(20.73\text{k} \angle 90^\circ) = (5.066\mu + 20.73\text{kj})$

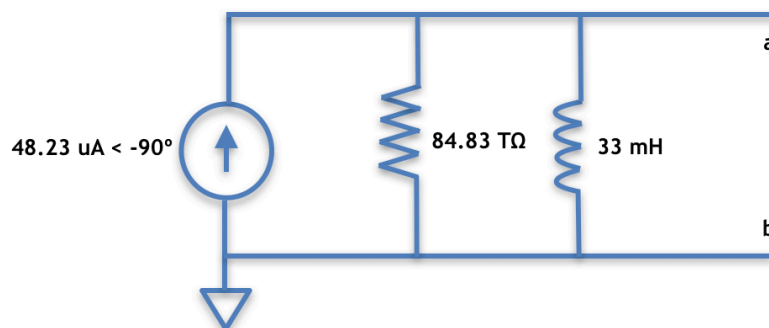29. Draw the Norton equivalent circuit for 100 kHz (current source with completely parallel components)

Norton current =  $48.23 \mu\text{A} \angle -90^\circ$





30. If a  $1\text{k}\Omega$  resistor is placed across terminals  $a$  and  $b$ , how much average power will be dissipated?

2.321  $\mu\text{W}$  by the  $1\text{k}\Omega$

31. Do you want a cookie?
- a. Yes
  - b. No
  - c. Not sure
  - d. Depends on what kind of cookie