

Parallel AC Circuits

■ Impedance and Admittance

- Relationship and intro (**Z** and **Y**)
- Admittance for the basic elements
- Impedance and admittance diagram - Example

■ Parallel Circuit Analysis

- Example using impedance
- Example using admittance
- **ICP – Parallel AC Circuit**

Impedance and Admittance

$$\text{RECALL : } \vec{Z} = R + jX$$

\swarrow IMPEDANCE \uparrow RESISTANCE \nwarrow REACTANCE

$$\vec{Y} \equiv \frac{1}{\vec{Z}} = \frac{1}{R + jX} \Rightarrow \text{Form of } G + jB$$

\swarrow ADMITTANCE (V or S) \uparrow CONDUCTANCE (V) or (S) \nwarrow SUSCEPTANCE (V or S)

A pure

RESISTANCE

$$\vec{Z} = R + j0$$

$$\therefore \vec{Y} = \frac{1}{\vec{Z}} = \frac{1}{R} = G$$

Impedance and Admittance

A pure

INDUCTANCE

$$\vec{Z}_L = 0 + jX_L$$

$$\vec{Y}_L = \frac{1}{\vec{Z}_L} = \frac{1}{jX_L} = \frac{-j}{X_L} = \left(\frac{1}{X_L}\right) \angle -90^\circ$$

B_L

A pure


CAPACITANCE

$$\vec{Z}_C = 0 - jX_C$$

$$\vec{Y}_C = \frac{1}{\vec{Z}_C} = \frac{1}{-jX_C} = \frac{j}{X_C} = \frac{1}{X_C} \angle 90^\circ$$

B_C

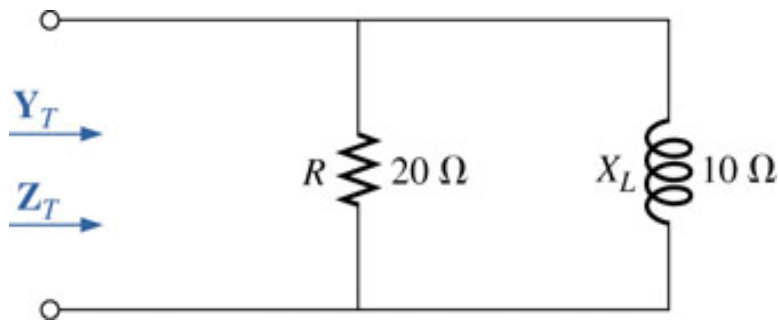Impedance and Admittance Diagrams (Find Z_T)



$$Z_T = \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_L}}$$

$$Z_T = \frac{1}{\frac{1}{20} + \frac{1}{j10}}$$

$$Z_T = (4 + j8)\ \text{Ohms}$$

Or

$$8.94\ \text{Ohms} \angle 63.4\ \text{Deg}$$


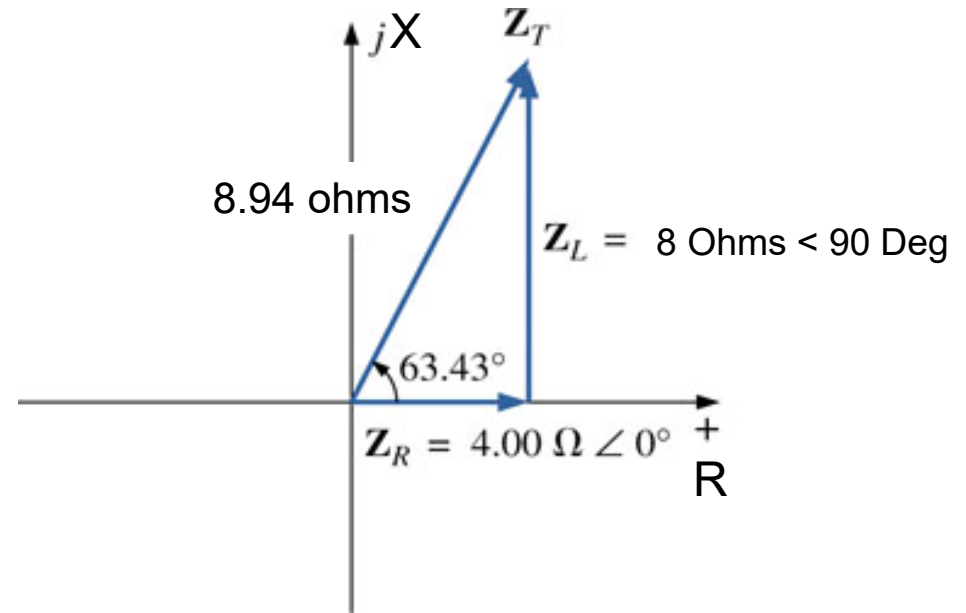


FIG. 16.4 Impedance diagram for the network in Fig. 16.3.

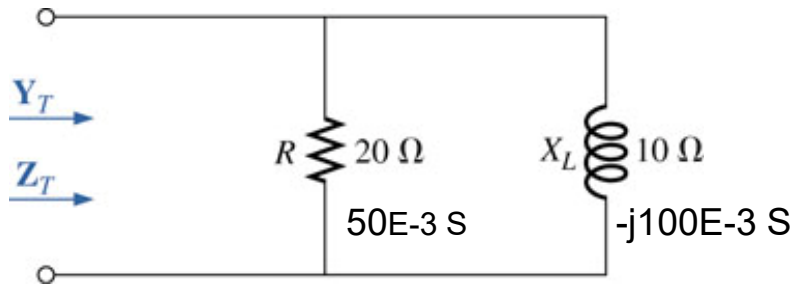Impedance and Admittance Diagrams (Find Y_T)



$$Z_T = (4 + j8)\ \text{Ohms}$$

Or

$$8.94\ \text{Ohms} \angle 63.4^\circ$$

$$Y_T = 1/Z_T$$

$$= (50\text{E-}3 - j100\text{E-}3)\ \text{S}$$

Or

$$111.8\text{E-}3\ \text{S} \angle -63.4^\circ$$

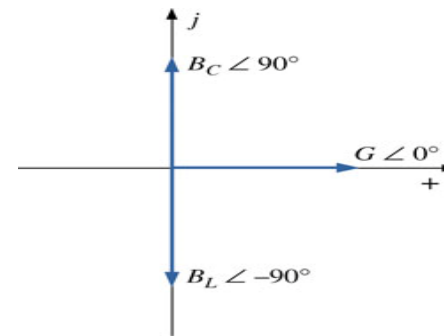


FIG. 16.8 Admittance diagram.


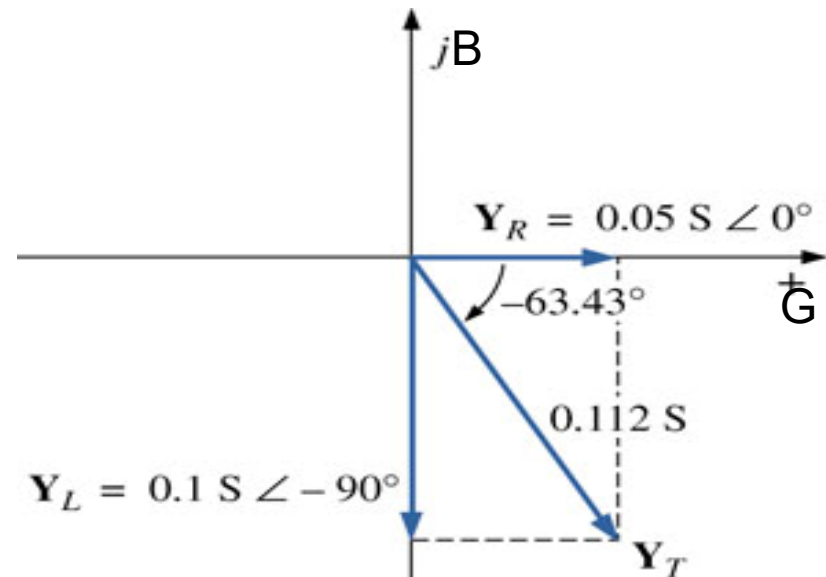


FIG. 16.9 Admittance diagram for the network in Fig. 16.3.

PARALLEL AC CIRCUIT EXAMPLE

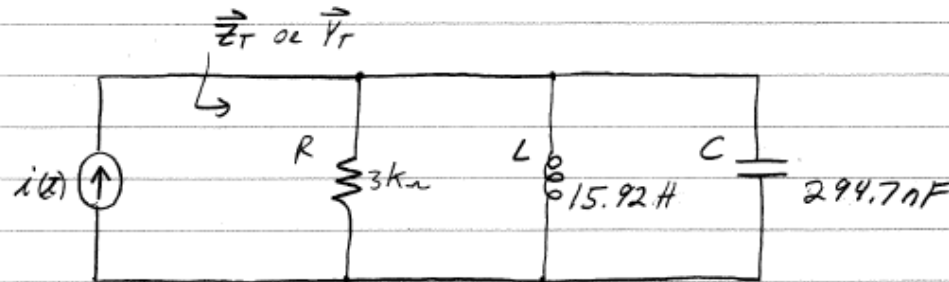

$$i(t) = 3 \sin(377t + 60^\circ) \text{ mA}$$

FIND: \vec{Z}_T , \vec{V}_T


FIND: \vec{Z}_T , \vec{V}_T

→ REORAN


$$\vec{Z}_L = j\omega L = j(377)(15.92) = j5.994\Omega$$

$$\vec{Z}_C = \frac{-j}{\omega C} = \frac{-j}{(377)(294.7nF)} = -j9k\Omega$$

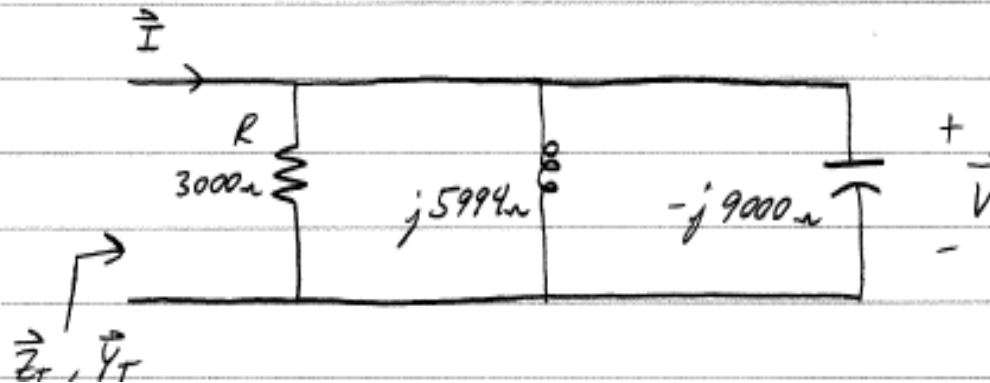Slight rounding error
(15.92H entered as
15.9H)



Parallel AC Circuit Analysis – Using Z_T


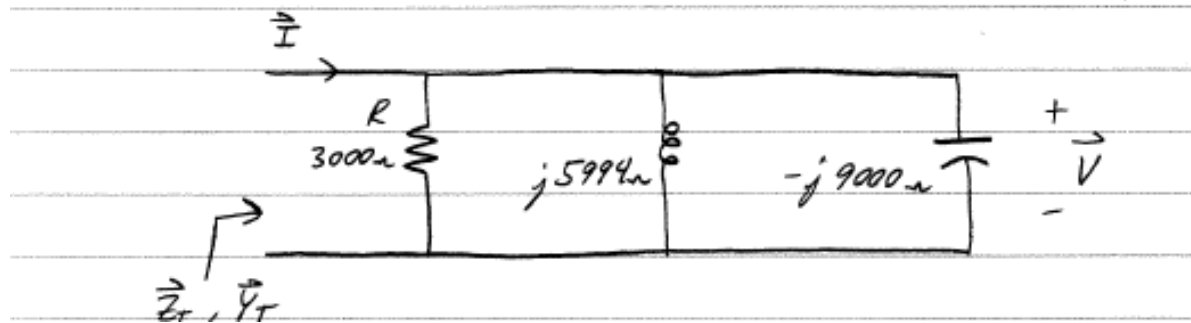


Z_T, Y_T

$$\vec{Z}_T = \frac{1}{\frac{1}{3000} + \frac{1}{j5994} + \frac{1}{-j9000}} = \boxed{\begin{array}{l} 2,918 + j487.9 \Omega \\ \text{OR} \\ 2,959 \angle 9.49^\circ \end{array}}$$

$$\vec{Y}_T = \frac{1}{\vec{Z}_T} = \boxed{\begin{array}{l} 333.3 \times 10^{-6} - j55.72 \times 10^{-6} \text{ S} \\ \text{OR} \\ 338 \mu\text{S} \angle -9.49^\circ \end{array}}$$

Parallel AC Circuit Analysis – Using Y_T

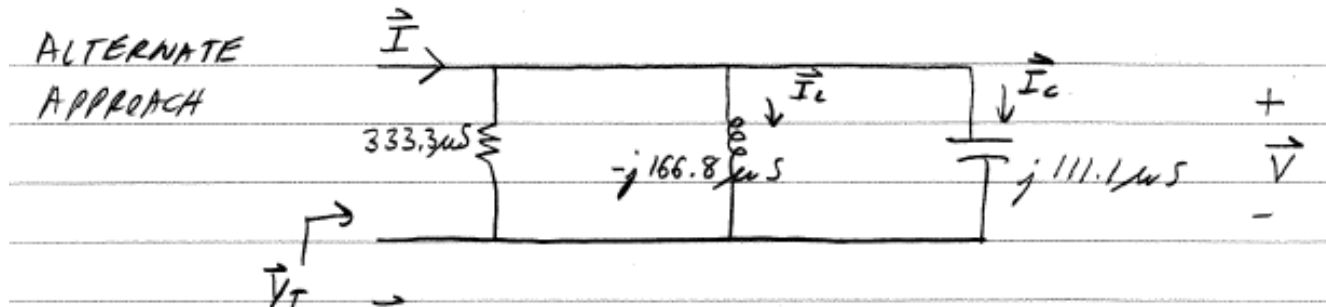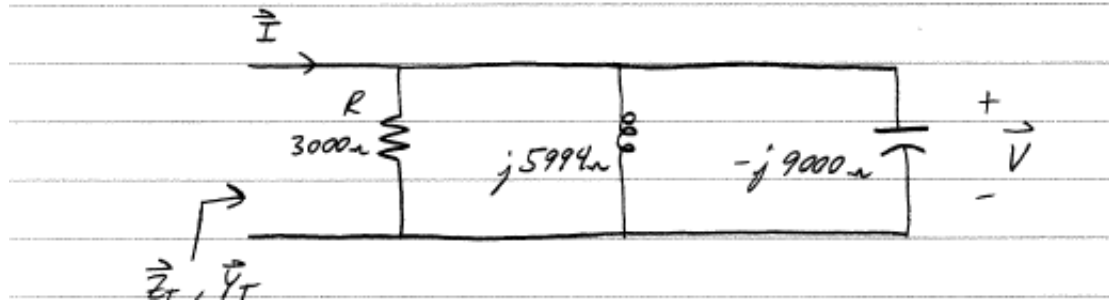


$$\vec{Y}_T = 333.3\mu S - j166.8\mu S + j111.1\mu S$$

$$\vec{Y}_T = \boxed{333.3 \times 10^{-6} - j55.7 \times 10^{-6} \text{ S}}$$


OR

$$\boxed{337.9\mu S \angle -9.49^\circ \text{ S}}$$

ADMITTANCE DIAGRAM

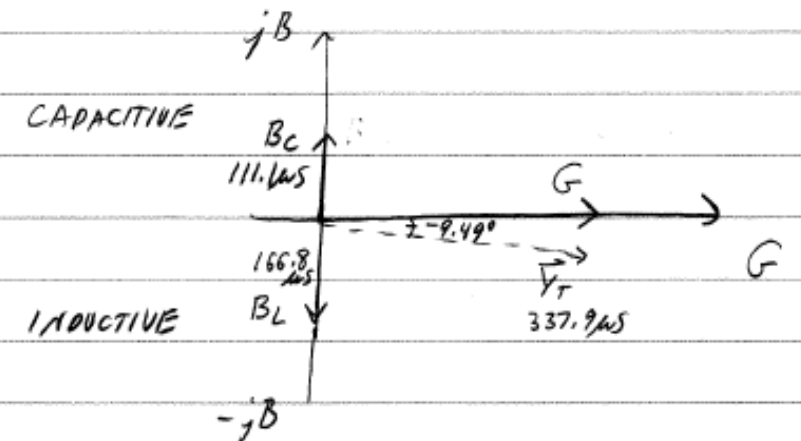

ICP – Parallel AC Circuit Analysis

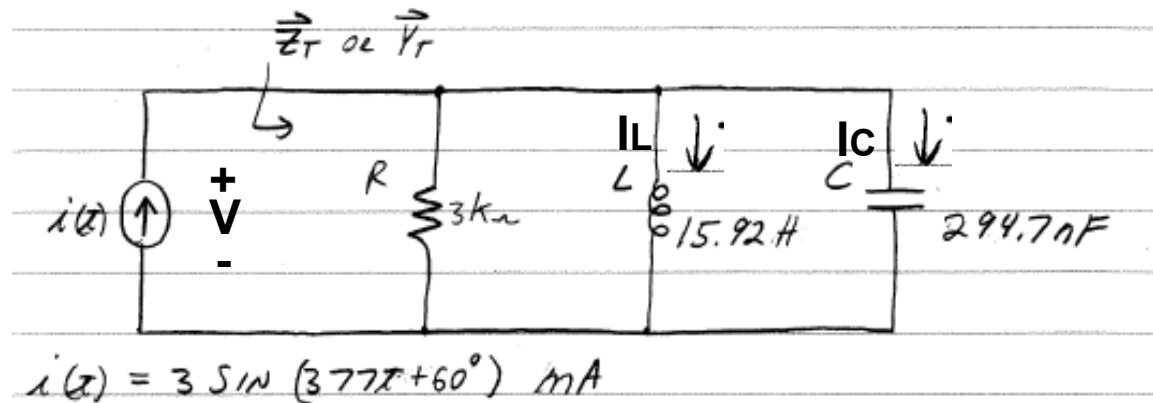

- 1 – Find the voltage V across the elements (use RMS)
- 2 – Find $v(t)$, the voltage across the elements
- 3 - Find I_L and I_C (use RMS)
- 4 - Find $i_L(t)$ and $i_C(t)$