

Average Power, Power factor, Complex Number Intro

■ **Average Power and Power Factor**

- ☐ Intro and background
- ☐ Instantaneous vs average power
- ☐ Average power delivered (R,L,C)
- ☐ Power factor definition
- ☐ **ICP – Average power and power factor**

■ **Lab #2 – Capacitor Charge and Discharge**

- ☐ Overview and prelab discussion

■ **Complex Numbers**

- ☐ Introduction and forms
- ☐ R->P, P-R conversions
- ☐ Math with complex numbers

Power Delivered to a Load by A Sinusoidal Forcing Function

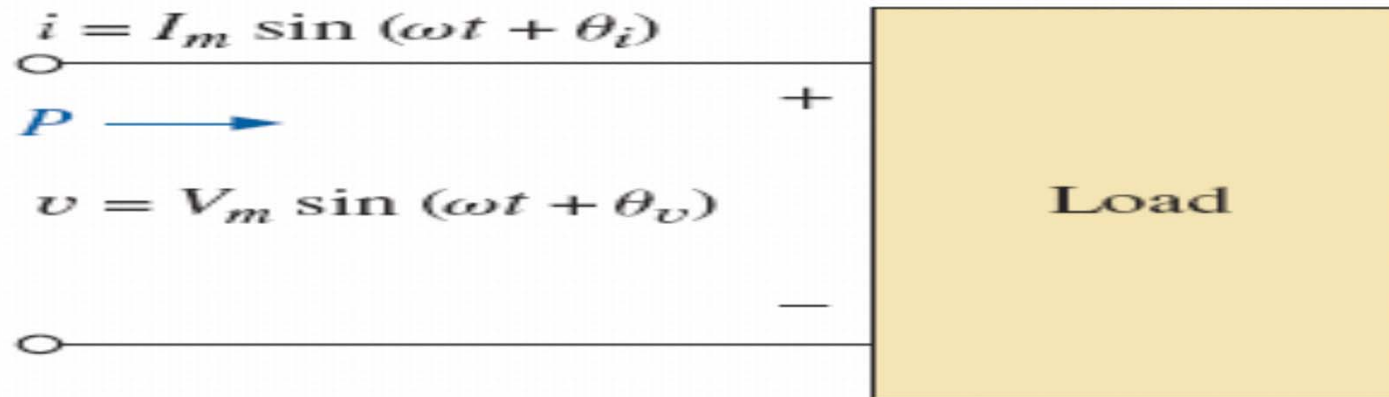


FIG. 14.28 Determining the power delivered in a sinusoidal ac network.

$$p(t) = v(t) i(t) = V_m I_m \sin(\omega t + \theta_v) \sin(\omega t + \theta_i)$$

$$\text{But: } \sin(\alpha) \sin(\beta) = \frac{1}{2} [\cos(\alpha - \beta) - \cos(\alpha + \beta)]$$

$$\therefore p(t) = \frac{V_m I_m}{2} \left[\cos(\omega t + \theta_v - \omega t - \theta_i) - \cos(\omega t + \theta_v + \omega t + \theta_i) \right]$$

$$= \frac{V_m I_m}{2} \left[\cos(\theta_v - \theta_i) - \cos(2\omega t + \theta_v + \theta_i) \right]$$

Power Delivered to a Load by A Sinusoidal Forcing Function

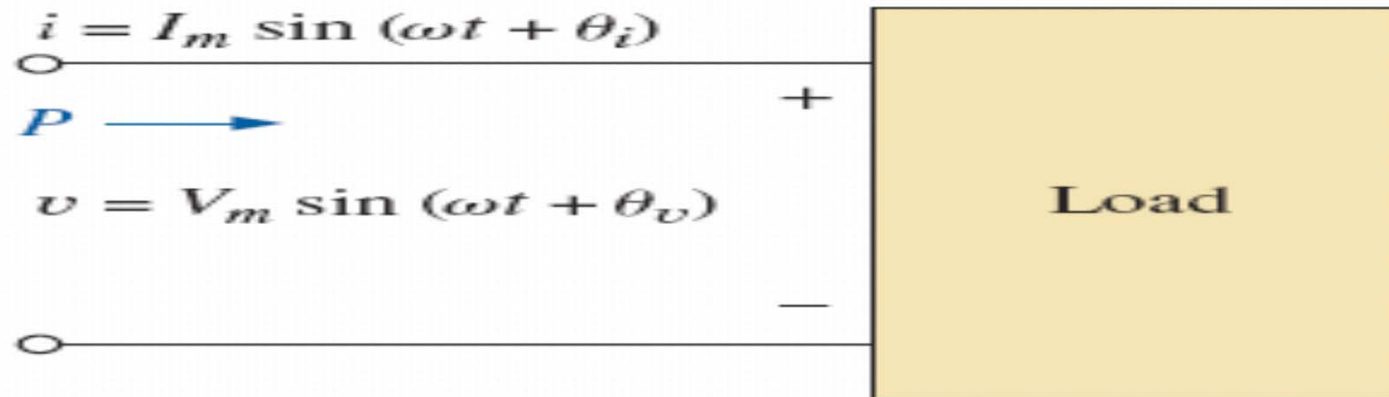


FIG. 14.28 Determining the power delivered in a sinusoidal ac network.

$$= \frac{V_m I_m}{2} \left[\cos(\theta_v - \theta_i) - \cos(2\omega t + \theta_v + \theta_i) \right]$$

OR

$$p(t) = \underbrace{\frac{V_m I_m}{2} \cos(\theta_v - \theta_i)}_{\text{FIXED}} - \underbrace{\frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i)}_{\text{TIME VARYING}}$$

Power Delivered to a Load by A Sinusoidal Forcing Function

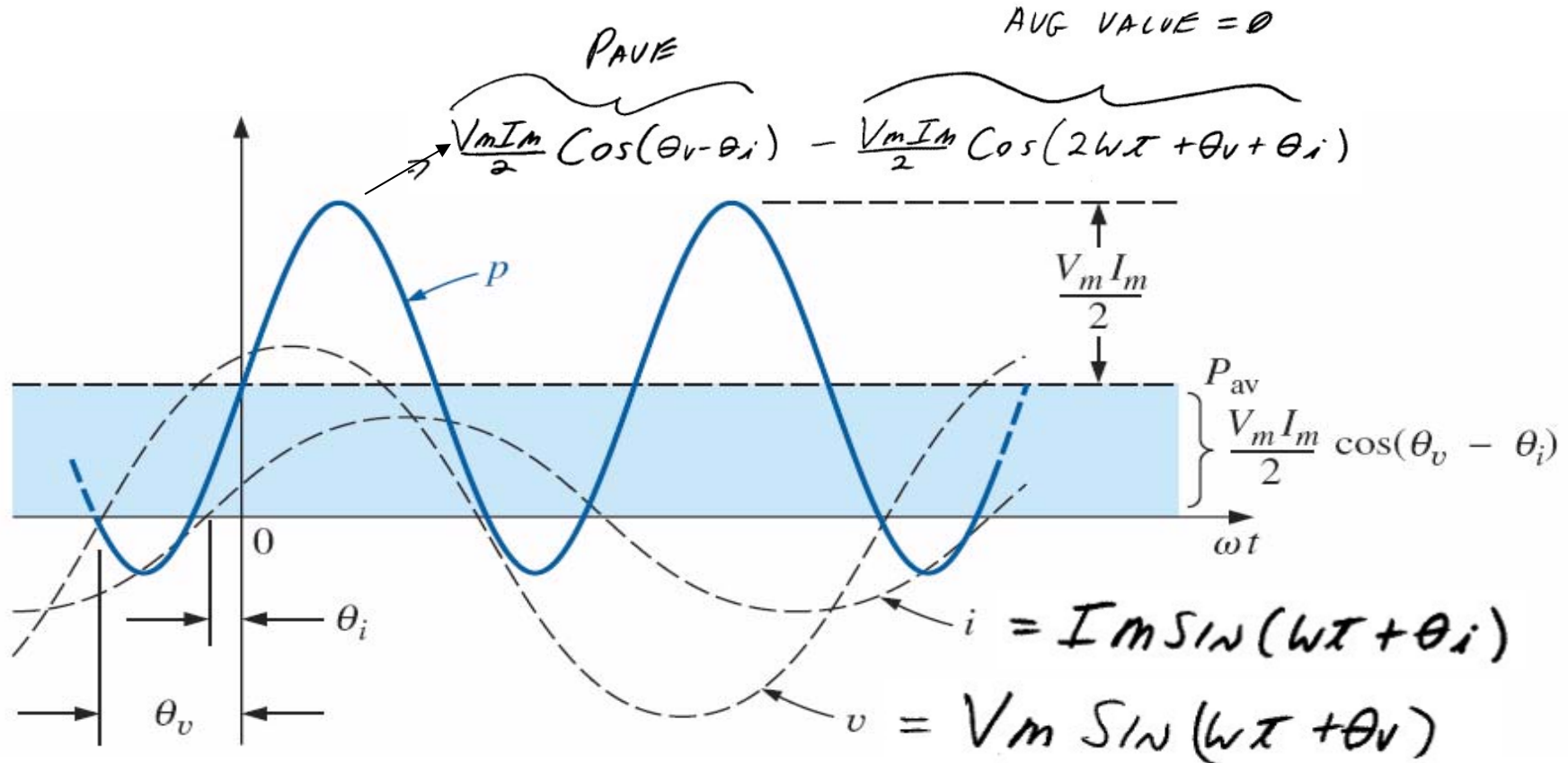


FIG. 14.29 Defining the average power for a sinusoidal ac network.

$$P_{AVE} = \frac{V_m I_m}{2} \cos(\theta) \text{ WATTS}$$

$$\theta = |\theta_v - \theta_i|$$

Average Power for R,L,C

FOR VARIOUS LOADS ° $P_{AVE} = \frac{V_m I_m}{2} \cos(\theta)$
 $\theta = |\theta_v - \theta_i|$

RESISTOR

$|\theta_v - \theta_i| = 0$, Since $v(t)$ & $i(t)$ ARE IN PHASE

$$P_{AVE} = \frac{V_m I_m}{2}$$

BUT $V_m = V_{RMS} \cdot \sqrt{2}$
 & $I_m = I_{RMS} \cdot \sqrt{2}$

∴ $P_{AVE} = V_{RMS} I_{RMS}$

OR RECALL : $I_{RMS} = \frac{V_{RMS}}{R}$

∴ $P_{AVE} = \frac{V_{RMS}^2}{R} = I_{RMS}^2 R$

INDUCTOR

$|\theta_v - \theta_i| = 90^\circ$ ∴ $P_{AVE} = \frac{V_m I_m}{2} \cos(90^\circ)$
 OR $P_{AVE} = 0W$

CAPACITOR

$|\theta_v - \theta_i| = 90^\circ$ ∴ $P_{AVE} = 0W$

* THE AVE POWER DISSIPATED BY AN IDEAL INDUCTOR OR IDEAL CAPACITOR IS 0 WATTS

POWER FACTOR

$$\text{POWER FACTOR} \equiv \boxed{F_p \equiv \cos(\theta)}$$

WHERE $\theta = |\theta_v - \theta_i|$

RECALL: $P_{AVE} = V_{RMS} I_{RMS} \cos(\theta)$

$$\therefore \boxed{\cos(\theta) = F_p = \frac{P_{AVE}}{V_{RMS} I_{RMS}}}$$

$F_p : 0 \rightarrow$ PURELY REACTIVE LOAD, NO POWER DELIVERED

$1 \rightarrow$ PURELY RESISTIVE LOAD, MAX POWER DELIVERED

WE LOOK AT THE CURRENT THROUGH THE LOAD:

\rightarrow IF $i(t)$ LEADS $v(t)$, LEADING POWER FACTOR \leftarrow

\rightarrow IF $i(t)$ LAGS $v(t)$, LAGGING POWER FACTOR

\uparrow
INDUCTIVE

\nwarrow
CAPACITIVE

ICPs – Pave and Power Factor

A CIRCUIT DISSIPATES 100W (PAVE) AT 150V (V_{EFF}) + 2A (I_{EFF}).

(1) FIND: THE POWER FACTOR

(2) IS THE LOAD RESISTIVE, REACTIVE OR BOTH? FIND $\theta = |\theta_v - \theta_i|$ IN DEGREES

(3) CAN WE TELL IF THE LOAD IS INDUCTIVE OR CAPACITIVE IN NATURE WITH THE GIVEN INFO?

Lab #2 – Capacitor Charge and Discharge



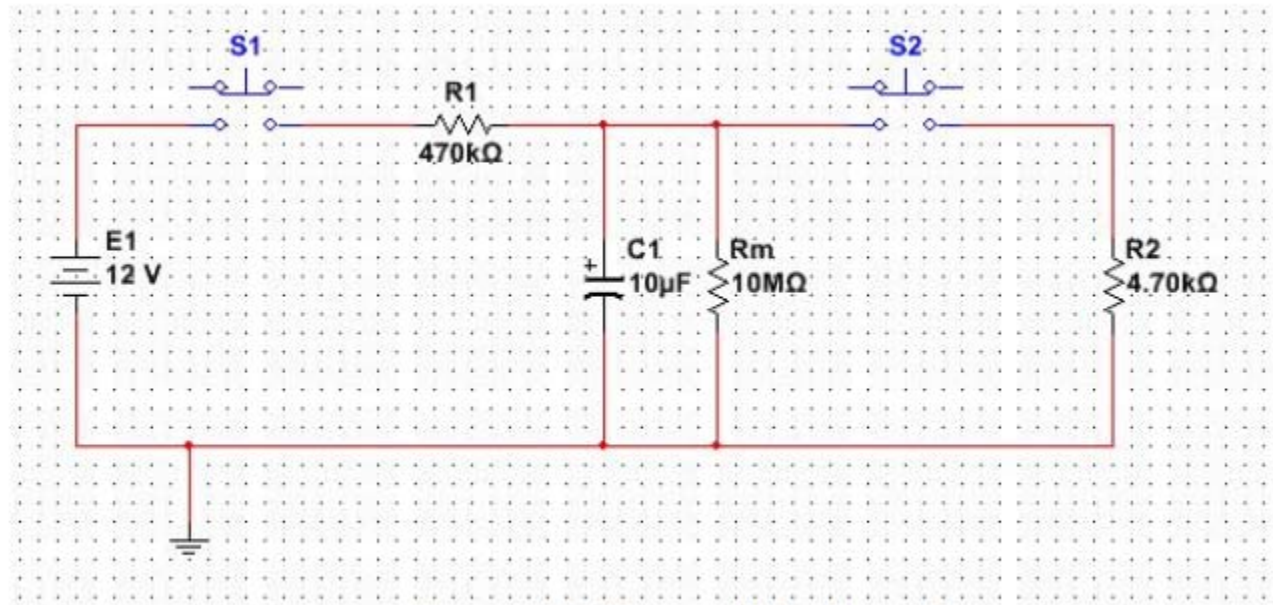


Figure 1 - RC Charge and Discharge Circuit


Charge Simulation

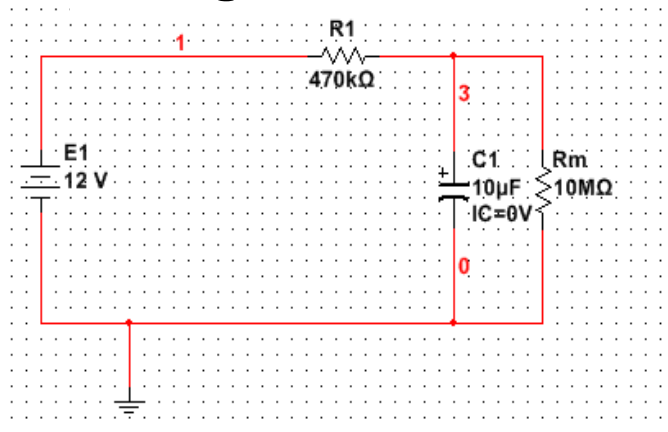


Discharge Simulation

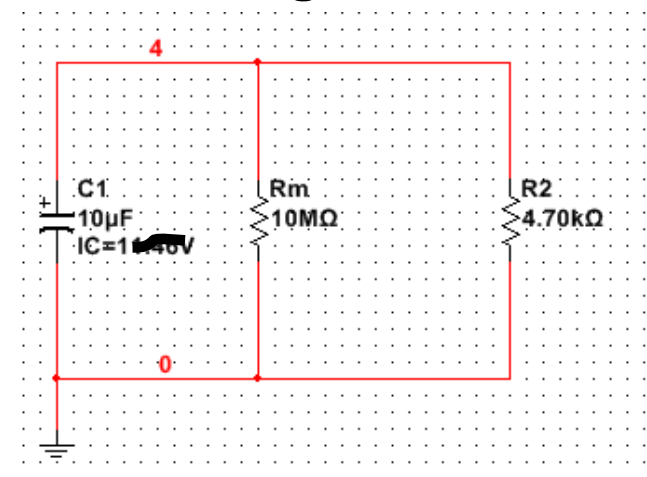


Lab #2 – Capacitor Charge and Discharge

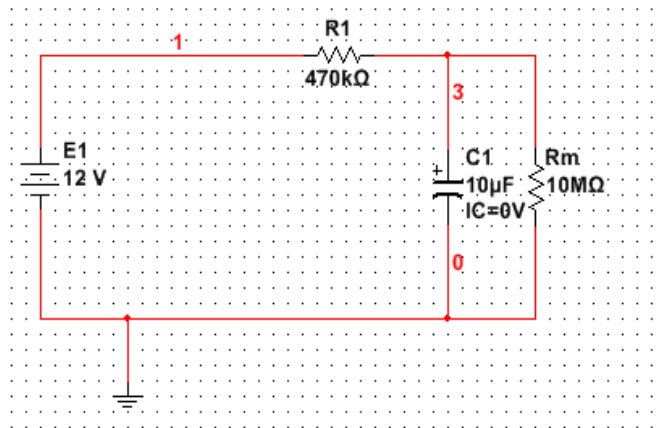


Charge Simulation

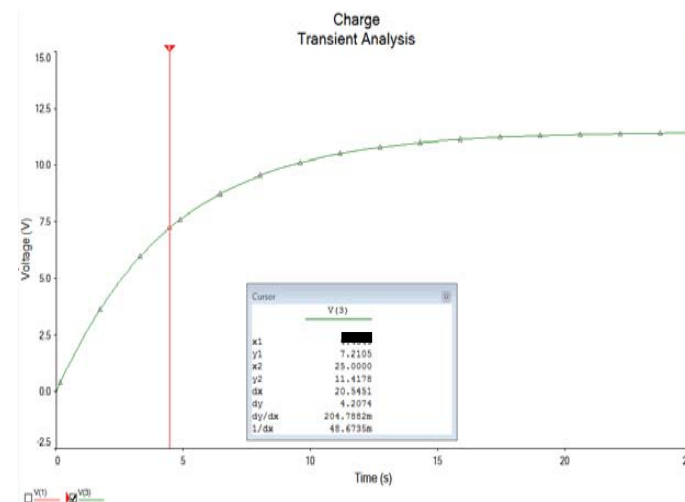

Charge in Excel


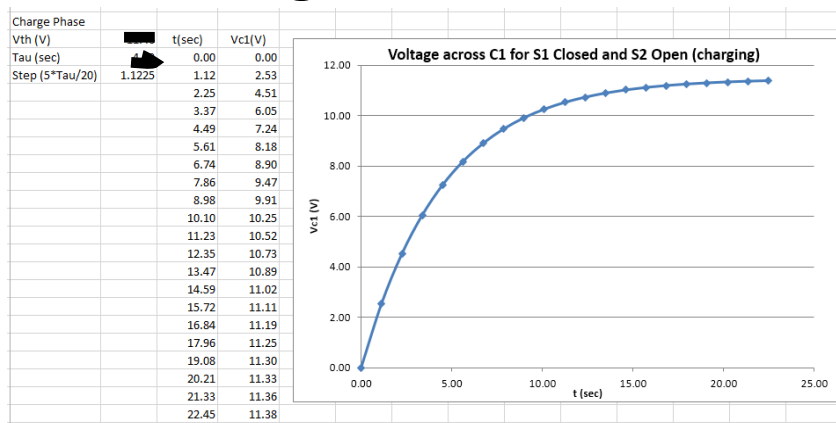


Charge in Lab

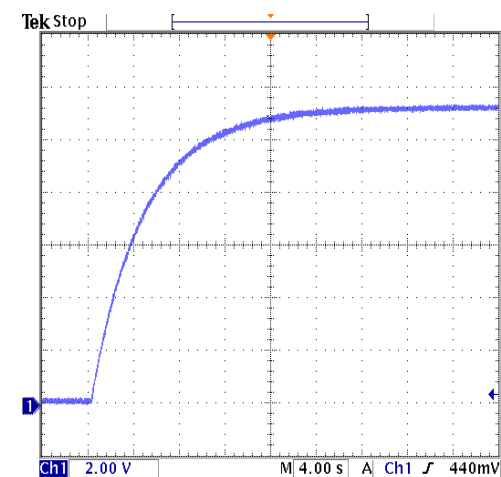


Lab #2 – Capacitor Charge and Discharge


Discharge in Simulation

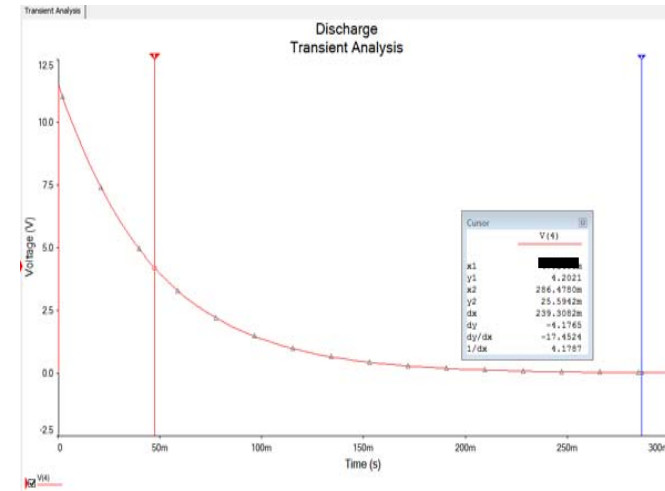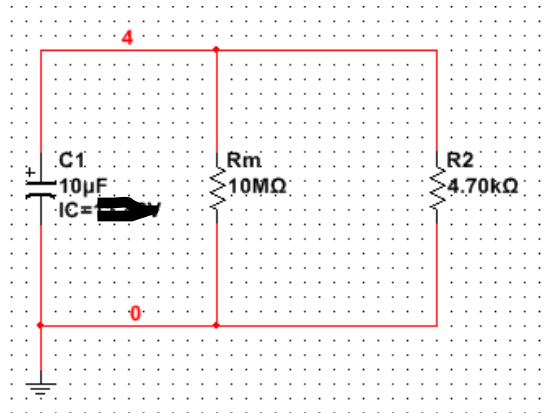

Discharge in Excel

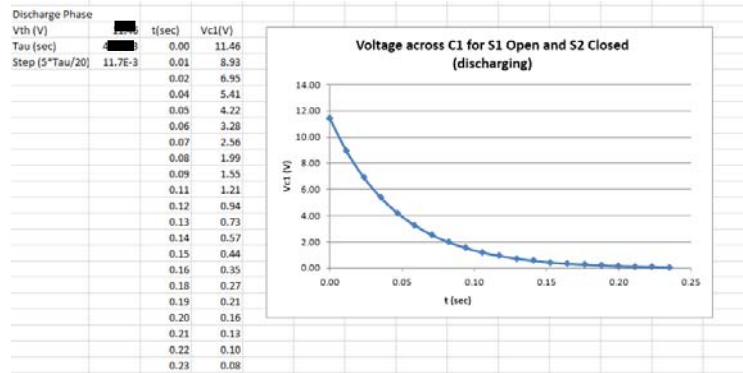

Discharge in Lab

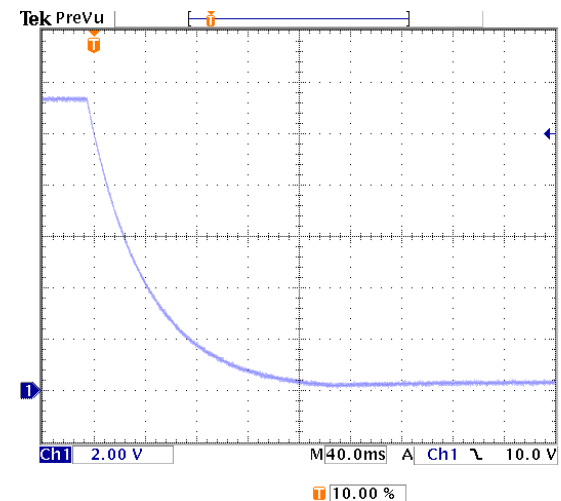


Complex Numbers – Definition and Intro

DEFINE : $j = +\sqrt{-1}$

$$\begin{aligned} j^2 &= -1 \\ j^3 &= -j \\ j^4 &= 1 \\ j^5 &= j \end{aligned}$$

COMPLEX NUMBER PLANE

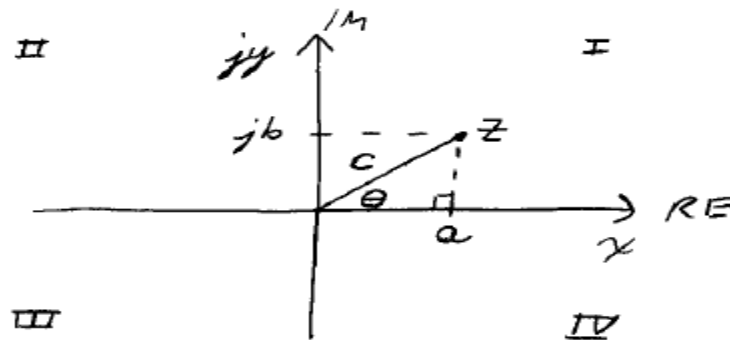


POSITIVE θ
MADE WITH THE RE
AXIS (COUNTERCLOCKWISE)

$$z = x + jy = C \angle \theta$$

\uparrow RECTANGULAR FORM \uparrow POLAR FORM

1.2 POLAR / RECTANGULAR CONVERSIONS

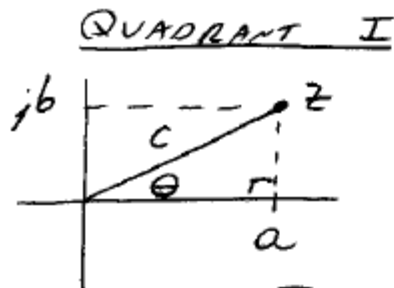

R → P

$$z = a + jb, \quad a \text{ \& b ARE POSITIVE}$$


$$z = C \angle \theta \begin{cases} C = \sqrt{a^2 + b^2}, \text{ MAGNITUDE} \\ \tan(\theta) = \frac{b}{a} \\ \theta = \tan^{-1}(b/a), \text{ ANGLE} \end{cases}$$

Complex Numbers – Definition and Intro

DEFINE : $j = +\sqrt{-1}$

$$\begin{aligned} \therefore j^2 &= -1 \\ j^3 &= -j \\ j^4 &= 1 \\ j^5 &= j \end{aligned}$$

COMPLEX NUMBER PLANE

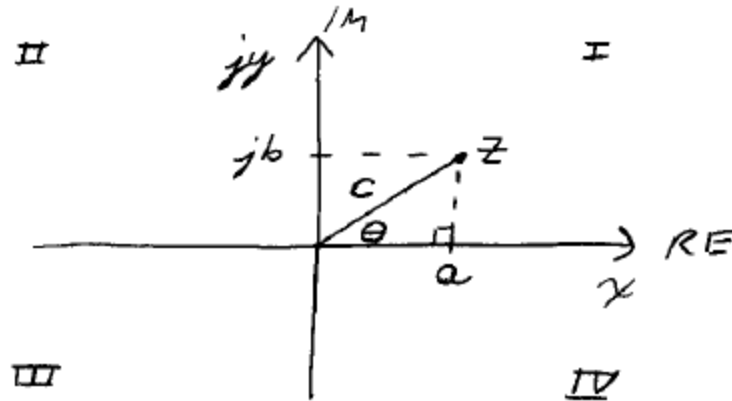

POSITIVE θ
MADE WITH THE RE
AXIS (COUNTERCLOCKWISE)

$$z = x + jy = c \angle \theta$$

\uparrow RECTANGULAR FORM \uparrow POLAR FORM

$$z = \frac{P \rightarrow R}{c \angle \theta}$$

$$\cos(\theta) = \frac{\text{adj}}{\text{hyp}} = \frac{a}{c}$$

$$\therefore a = c \cos \theta$$

$$\sin(\theta) = \frac{\text{opp}}{\text{hyp}} = \frac{b}{c}$$

$$\therefore b = c \sin \theta$$

\downarrow HAVE $\underline{\underline{z = a + jb}}$

Complex Numbers – On the Sharp EL-516

Mathematical operations (rectangular mode)

25 **MODE** **(CPLX)**

$(12 - 6i) + (7 + 15i) - (11 + 4i) =$

$\text{MODE } 3$
 $12 \text{ } - \text{ } 6 \text{ } i \text{ } + \text{ } 7 \text{ } + \text{ } 15 \text{ } i$
 $- \text{ } (\text{ } 11 \text{ } + \text{ } 4 \text{ } i$
 $) \text{ } =$

8.
+5.i


$6 \times (7 - 9i) \times (-5 + 8i) =$

$6 \text{ } \times \text{ } (\text{ } 7 \text{ } - \text{ } 9 \text{ } i \text{ })$
 $\times \text{ } (\text{ } (-) \text{ } 5 \text{ } + \text{ } 8 \text{ } i \text{ })$
 $=$

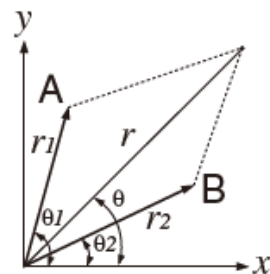222.
+606.i

Complex Numbers – On the Sharp EL-516

Mathematical operations (polar form – think VECTORS)



$$r1 = 8, \theta1 = 70^\circ$$

$$r2 = 12, \theta2 = 25^\circ$$

$$\rightarrow r = ?, \theta = ?^\circ$$

Calculator sequence: 2ndF →rθ 8 ∠ 70 + 12 ∠ 25 =

Result: 18.5408873
∠42.76427608

$$1 + i$$

$$\rightarrow r = ?, \theta = ?^\circ$$

Calculator sequence: 2ndF →xy 1 + i =

Result: 1.
+1.i

R->P Conversion

Calculator sequence: 2ndF →rθ

Result: 1.414213562
∠45.

See our text for more examples, addition/subtraction are easier in rectangular form and multiplication/division is easier in polar form