

# *Electrical Engineering Technology*

**Series Configuration and Voltage Divider**

**Spring 2019 (2185)**

## **Series Configuration and Voltage Divider**

### ■ Series Configuration

- ☐ Introduction to AC Series Circuits
- ☐ Comparison to DC Series Circuits
- ☐ RL Circuit Example
- ☐ **ICP 1 – Series RC Circuit**

### ■ Voltage Divider Rule

- ☐ Introduction
- ☐ Example
- ☐ **ICP 2 – Use voltage divider to find unknown voltages**

## Series Circuit Configuration

- Overall properties of AC series circuits are the same as those of DC series circuits if

- The source is converted to phasor form

$$V_m \angle \theta^\circ \text{ or } V_{pk} \angle \theta^\circ$$

$$V_m \sin(\omega t + \theta^\circ) \rightarrow$$

$$\frac{V_m}{\sqrt{2}} \angle \theta^\circ \rightarrow V_{rms} \angle \theta^\circ$$


- The circuit loads ( $R, L$  or  $C$ ) are converted to their respective impedances ( $Z_R, Z_L$  or  $Z_C$ )

$$\mathbf{Z}_R = R \angle 0^\circ$$

$$\mathbf{Z}_L = X_L \angle 90^\circ$$

$$\mathbf{Z}_C = X_C \angle -90^\circ$$

## Series DC Circuit

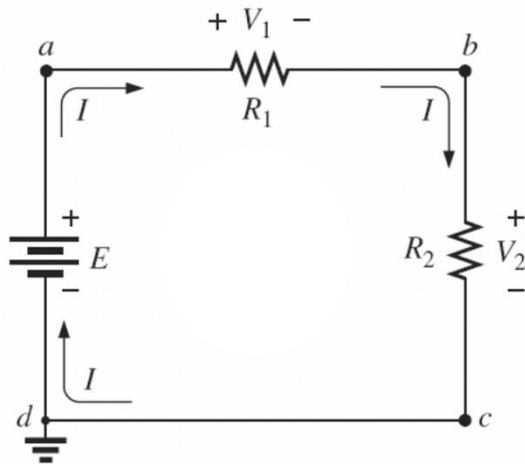

- The applied voltage of a series dc circuit will equal the algebraic sum of the voltage drops of the circuit (aka KVL)

$$E = V_1 + V_2$$


- The current is the same at every point in a series circuit

$$I = \frac{E}{R_T}$$

- The voltage across each element can be found by Ohm's law

$$V_1 = IR_1 \quad V_2 = IR_2$$

## Series AC Circuit

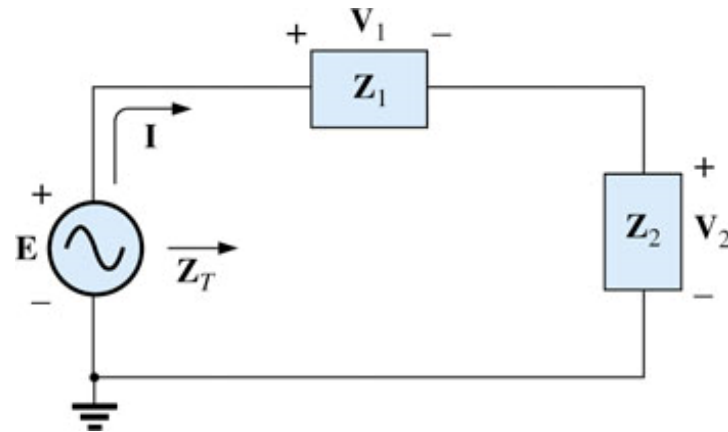


$$E = V_1 + V_2$$

$$I = \frac{E}{Z_T}$$

$$V_1 = IZ_1 \quad V_2 = IZ_2$$

## Series DC Circuit

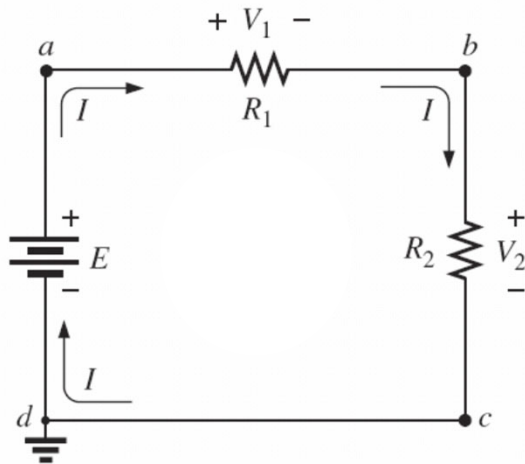


- The total resistance (impedance for AC) of a series configuration is the sum of the resistors (impedances for AC)

$$R_T = R_1 + R_2$$

- The total power delivered to the load is

$$P = EI$$

## Series AC Circuit

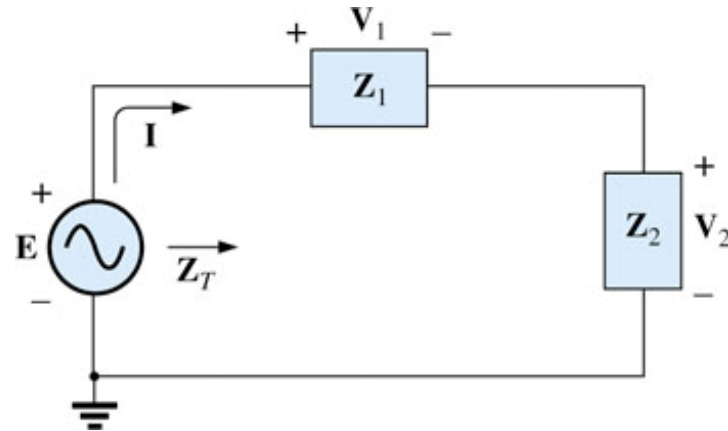

$$Z_T = Z_1 + Z_2$$

$$P = EI \cos(\theta_T)$$


$E$  and  $I$  are the effective (RMS) values

Where  $\theta_T$  is the phase angle between voltage and current

$$\theta_T = \theta_E - \theta_I$$
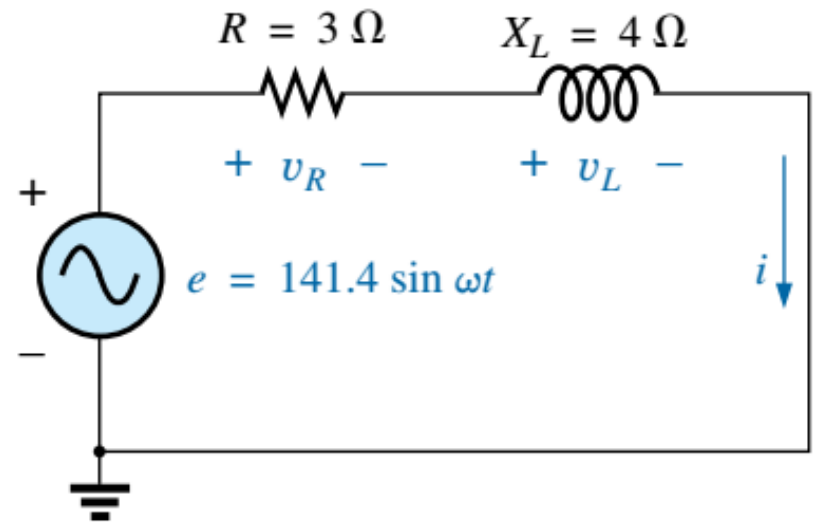
## Series RL Circuit Example

- Consider the series RL circuit below
  1. Write the voltage  $E$  in phasor form.
  2. Calculate the total impedance  $Z_T$  of the circuit
  3. Find the current  $I$  and the voltages  $V_R$  and  $V_L$
  4. Find the power delivered to the loads and the total power




## Series RL Circuit Example

- Source voltage  $e = 141.4_{pk} \sin(\omega t)$

- Sinusoidal

$$E = \frac{141.4}{\sqrt{2}} \angle 0^\circ$$

- Polar & Rectangular

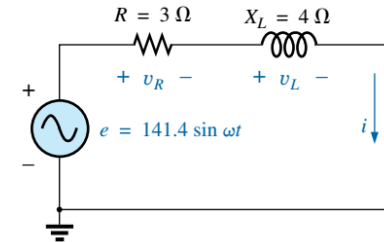

$$E = 100V_{rms} \angle 0^\circ$$

$$E = (100 + j0)V_{rms}$$

- Impedance

- Total impedance  $Z_T = Z_R + Z_L$

$$Z_R = R \angle 0^\circ \quad Z_R = 3\Omega \angle 0^\circ = (3 + j0)\Omega$$

$$Z_L = X_L \angle 90^\circ \quad Z_L = 4\Omega \angle 90^\circ = (0 + j4)\Omega$$

$$Z_T = Z_R + Z_L = (3 + j0) + (0 + j4) = (3 + j4)\Omega$$

$$Z_T = \sqrt{(3^2 + 4^2)} \angle \tan^{-1}\left(\frac{4}{3}\right) = (5\Omega \angle 53.13^\circ)$$

- Current

$$I = I_R = I_L = \frac{E}{Z_T} = \frac{100V_{rms} \angle 0^\circ}{5\Omega \angle 53.13^\circ} = (20A_{rms} \angle -53.13^\circ)$$

$$I = 20 \cos(-53.13^\circ) + j20 \sin(-53.13^\circ) = (12 - j16)A_{rms}$$

## Series RL Circuit Example

### ■ Total Power Delivered

$$P_T = EI \cos \theta_T \quad P_T = (E)(I) \cos(\theta_E - \theta_I)$$

$$P_T = (100V_{rms})(20A_{rms}) \cos(0 - (-53.13^\circ))$$


$$P_T = (100V_{rms})(20A_{rms}) \cos(53.13^\circ) = (2000 W)(0.6) = 1200 W$$

### ■ Power Factor

$$F_P = \cos \theta_T = \frac{R}{Z_T}$$

$$F_P = \cos(\theta_E - \theta_I) = \frac{R}{Z_T}$$
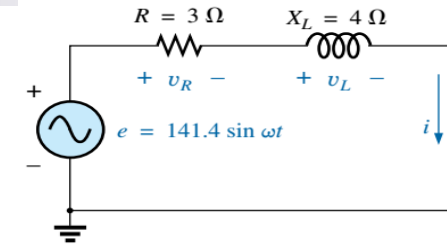
$$F_P = \cos(0 - (-53.13^\circ)) = \frac{3}{5} = 0.6 \text{ lagging (current lags voltage)}$$




Where  $\theta_T$  is the phase angle between E and I

□ Find  $V_R$ ,  $V_L$  and sum to check the input voltage



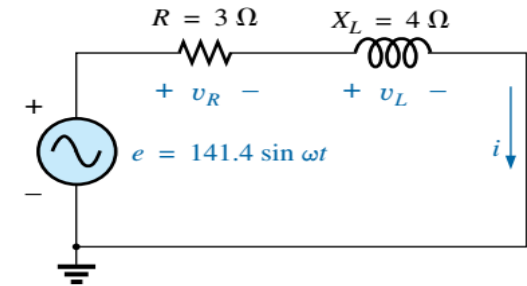
The results are summarized in the table below.



		<b>R</b>	<b>L</b>	<b>Total</b>
<b>E</b>	<b>Polar</b>	$60 V_{rms} \angle -53.13^\circ$	$80 V_{rms} \angle 36.87^\circ$	$100 V_{rms} \angle 0^\circ$
	<b>Rectangular</b>	$(36 - j48) V_{rms}$	$(64 + j48) V_{rms}$	$(100 + j0) V_{rms}$
<b>I</b>	<b>Polar</b>	$20 A_{rms} \angle -53.13^\circ$	$20 A_{rms} \angle -53.13^\circ$	$20 A_{rms} \angle -53.13^\circ$
	<b>Rectangular</b>	$(12 - j16) A_{rms}$	$(12 - j16) A_{rms}$	$(12 - j16) A_{rms}$
<b>Z</b>	<b>Polar</b>	$3 \Omega \angle 0^\circ$	$4 \Omega \angle 90^\circ$	$5 \Omega \angle 53.13^\circ$
	<b>Rectangular</b>	$(3 + j0) \Omega$	$(0 + j4) \Omega$	$(3 + j4) \Omega$
<b>P</b>		<b>1200 W</b>	$0$	<b>1200 W</b>

## ICP 1 - Series RC Circuit

- Consider the series RC circuit in Fig. 15.33, analyze the circuit similar to the RL circuit.
  1. Write the current  $\mathbf{I}$  in phasor form.
  2. Calculate the total impedance  $\mathbf{Z}_T$  of the circuit
  3. Find the voltage across the current source,  $\mathbf{V}_{in}$  and the voltages  $\mathbf{V}_R$  and  $\mathbf{V}_C$
  4. Find the power delivered to the loads and the total power delivered

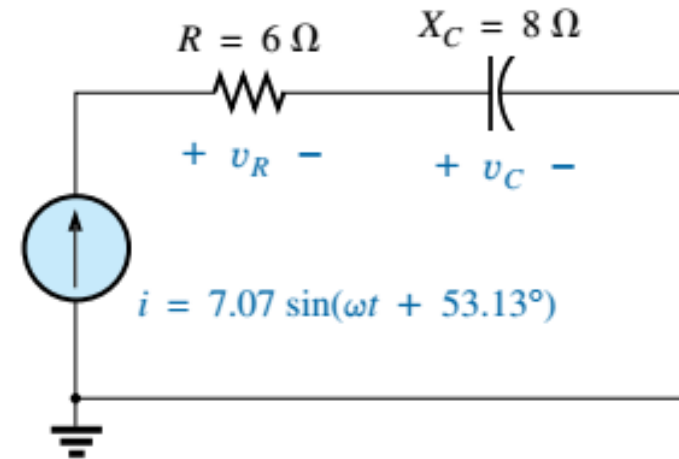

**FIG. 15.33**  
*Series R-C ac circuit.*

## Voltage Divider Rule (VDR)

- The basic format for the voltage divider rule in AC circuits is exactly the same for DC circuits (covered in Chap. 5.7)
  - VDR is used to determine the voltage across a series load without first having to determine the current through the circuit.

$$V_x = \frac{Z_x E}{Z_T}$$

where

$V_x$  is the voltage across one or more elements


$E$  is the source voltage

$Z_x$  is the impedance with unknown voltage

$Z_T$  is the total impedance of the series circuit

## Voltage Divider Rule (VDR): Example

- Using the voltage divider rule, find the voltage across each element of the circuit shown below
  - Voltage across the capacitor  $V_C$ ?
  - Voltage across the resistor  $V_R$ ?

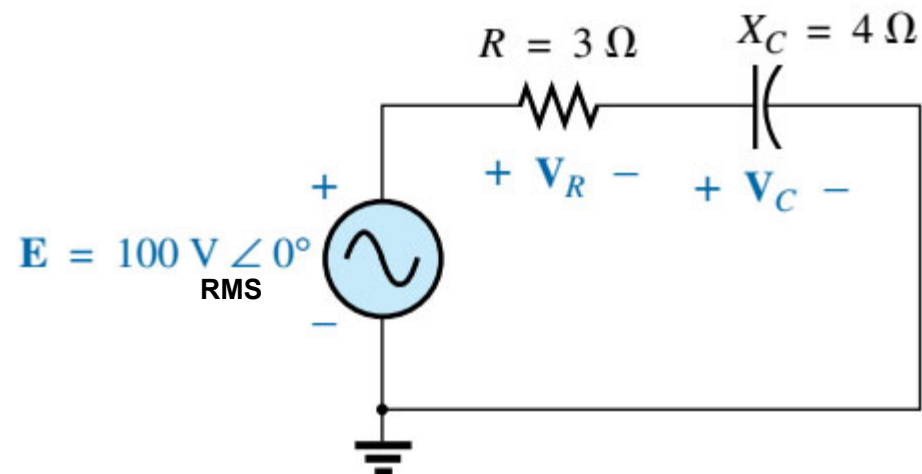


**FIG. 15.43**

*Example 15.11.*

## Voltage Divider Rule (VDR): Example

- Using the voltage divider rule, find the voltage across each element of the circuit shown below
- Voltage across the capacitor  $V_C$ ?
- Voltage across the resistor  $V_R$ ?

$$V_c = \frac{Z_C E}{Z_T} = \frac{Z_C E}{Z_R + Z_C}$$

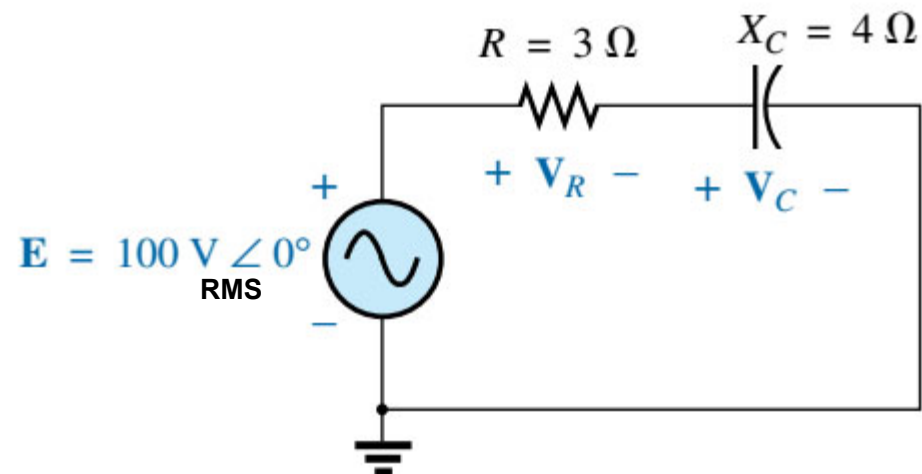

**FIG. 15.43**


*Example 15.11.*

## Voltage Divider Rule (VDR): Example

- Using the voltage divider rule, find the voltage across each element of the circuit shown below
- Voltage across the capacitor  $V_C$ ?

$$V_c = \frac{Z_C E}{Z_T} = \frac{Z_C E}{Z_R + Z_C}$$

$$V_c = \frac{400 \angle -90^\circ}{5 \angle -53.13^\circ} = 80 V_{\text{RMS}} \angle -36.87^\circ$$

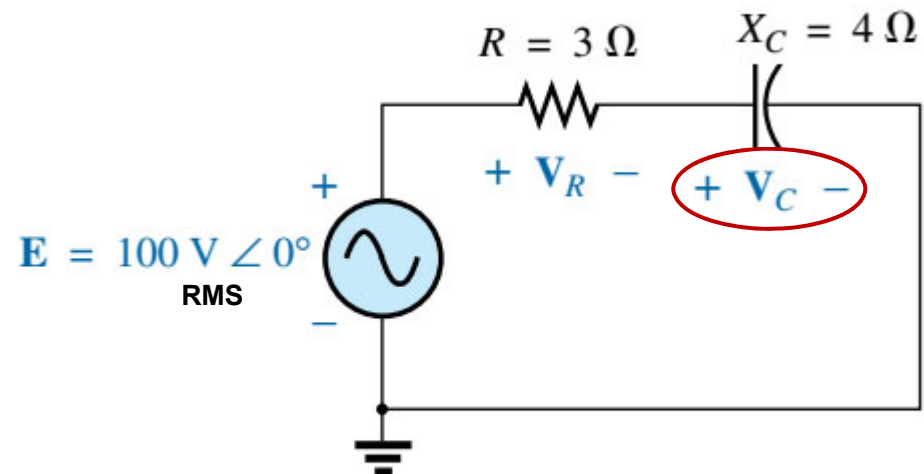

**FIG. 15.43**

*Example 15.11.*

## Voltage Divider Rule (VDR): Example


- Using the voltage divider rule, find the voltage across each element of the circuit shown below

□ Voltage across the resistor  $V_R$ ?

$$V_R = \frac{Z_R E}{Z_T} = \frac{Z_R E}{Z_R + Z_C}$$

$$V_R = \frac{300 \angle 0^\circ}{5 \angle -53.13^\circ} = 60V \angle 53.13^\circ_{\text{RMS}}$$

□ Check: Use  $V_R$  and  $V_C$  to find  $E$

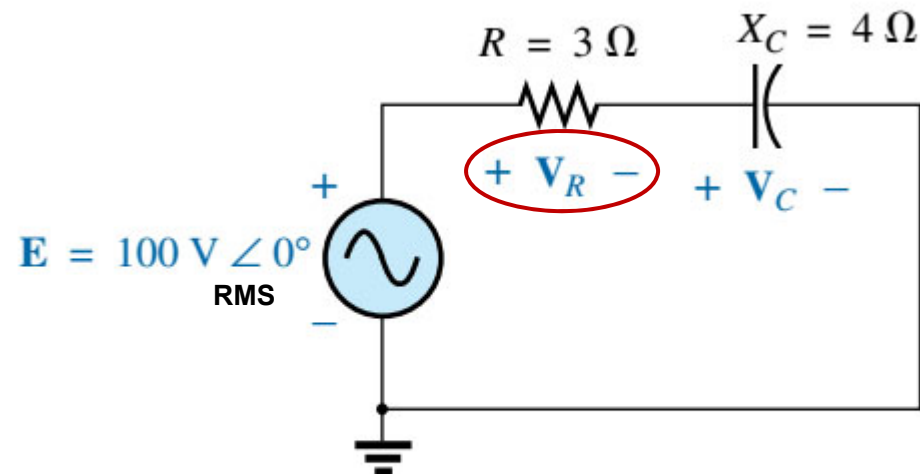


**FIG. 15.43**

*Example 15.11.*

## ICP 2 – Voltage Divider Rule

- Using the voltage divider rule, find the unknown voltages  $V_R$ ,  $V_L$ ,  $V_C$ , and  $V_1$  for the circuit shown below.

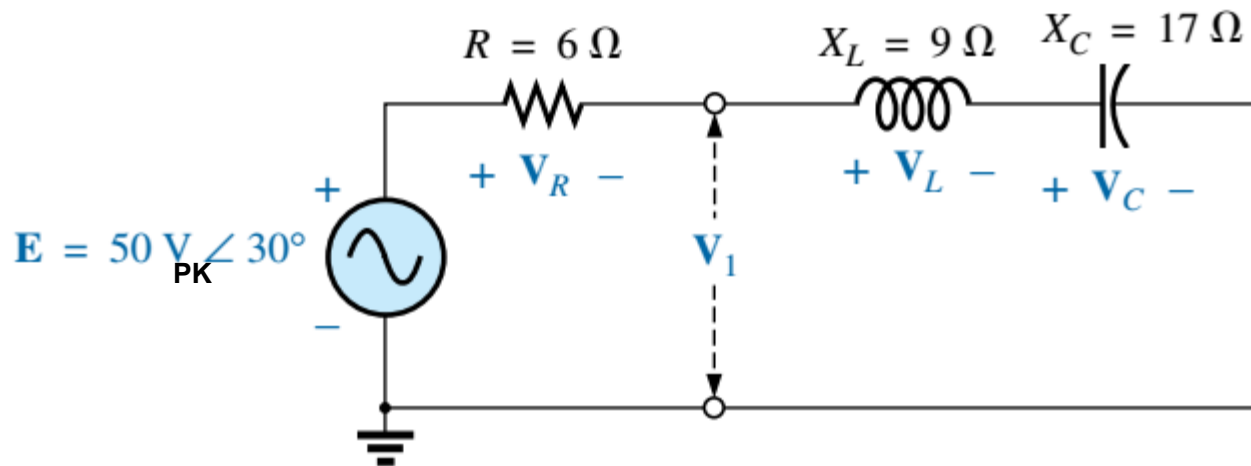

**FIG. 15.44**

*Example 15.12.*