

Electrical Engineering Technology


Series AC Circuits (continued)

Spring 2019 (2185)

Series AC Circuits (continued)

- Project #1, Week 1
 - Prelab (partial) discussion – **Z_T** for a series RL Circuit
 - Calculations
 - Simulation (interpretation of results)
- Series RC Circuit – Frequency Response
 - **ICP –In your teams**
 - Check each other's work
 - Help each other with your calculators
 - Simulation Demo (Multisim)
 - Simulation set-up
 - AC magnitude vs V_{peak}
 - Compare **Z_T** results
 - Compare **V_C** results


Project #1 – Week 1 Prelab (Partial)

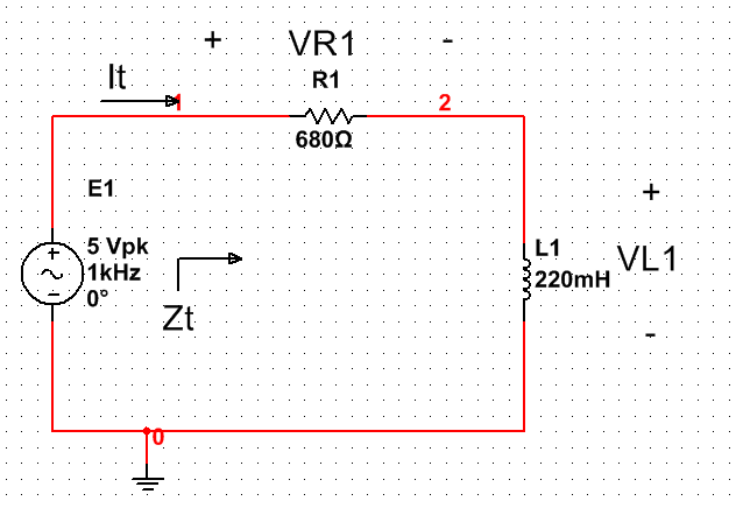

1. Calculate $\mathbf{Z_T}$ and draw the impedance diagram (one RC series circuit, one RL series circuit)
2. Using Multisim, determine $\mathbf{Z_T}$ and draw the impedance diagram
3. In lab, build the circuit, determine $\mathbf{Z_T}$ and draw the impedance diagram

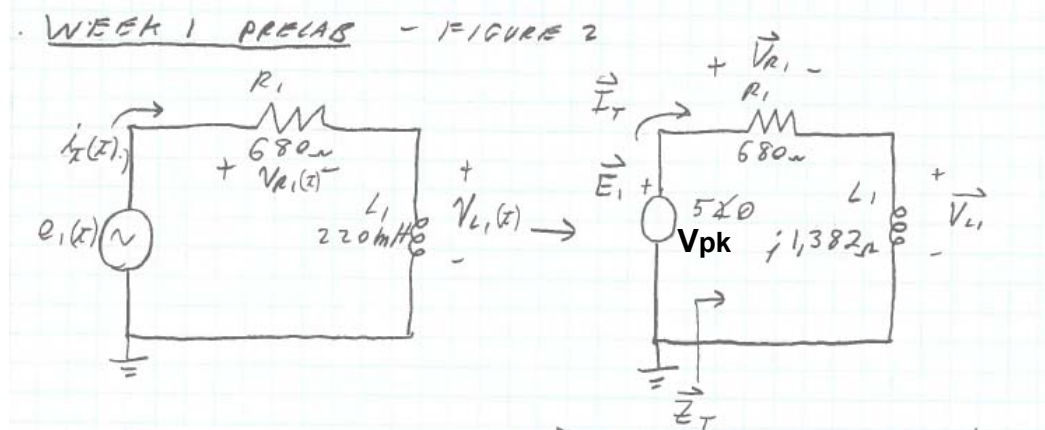1. Calculations – RL Circuit

Convert to the Phasor Domain
(R,L,C → impedance)




Calculate $\mathbf{Z_T}$

$$\vec{Z_T} = (680 + j1,382) \Omega$$


OR

$$1,540 \angle 63.8^\circ$$

Draw the Impedance Diagram

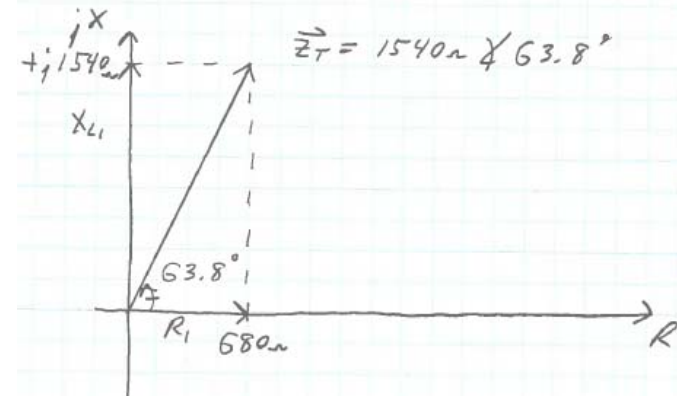

2. Simulation – RL Circuit

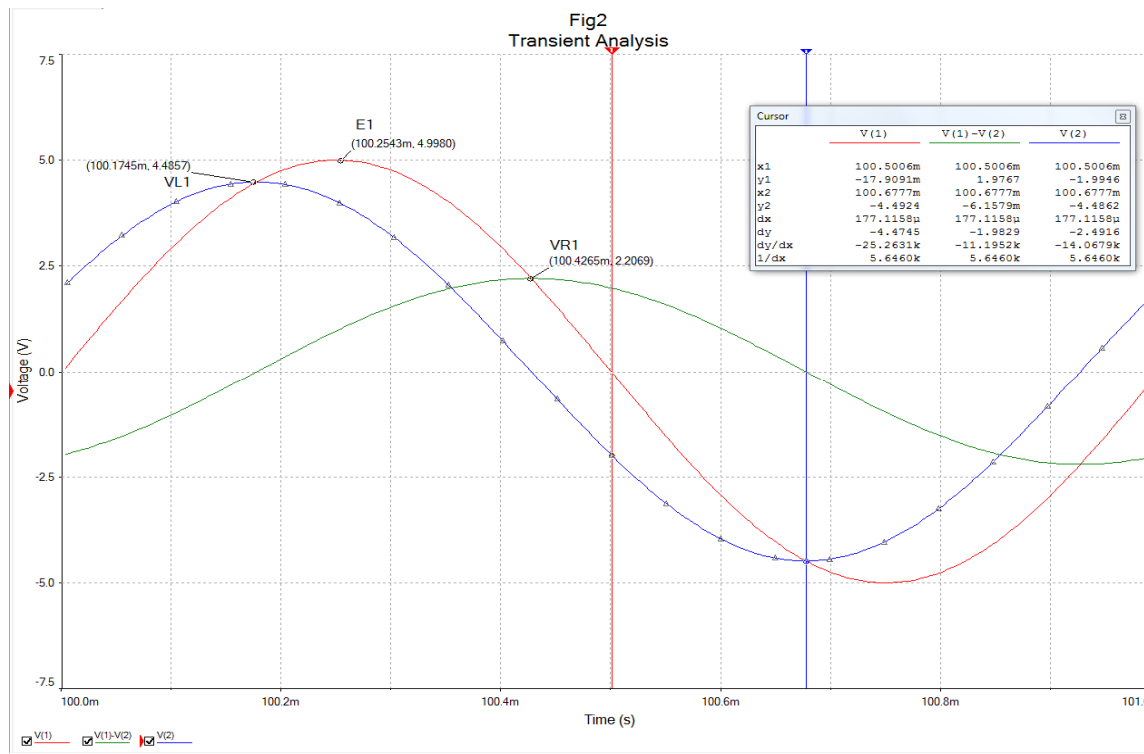

Interpret to Determine Z_T

$$\vec{Z}_T = \frac{\vec{E}_1}{\vec{I}_T}$$

$$\vec{E}_1 = 5V \angle 0^\circ$$

$$|\vec{I}_T| = \left| \frac{\vec{V}_{R1}}{R_1} \right| = \frac{2.21V}{680\Omega}$$

$$= 3.25mA_{pk}$$



$$\angle \vec{I}_T \rightarrow \vec{I}_T \text{ LAGS } \vec{E}_1 \text{ By } 177\mu\text{Sec}$$

$$\frac{177\mu\text{Sec}}{X_{OEF}} = \frac{1m\text{Sec}}{360DEG}$$

$$X = 63.7^\circ$$

$$\therefore \vec{I}_T = 3.25mA \angle 63.7^\circ$$


Draw the Impedance Diagram

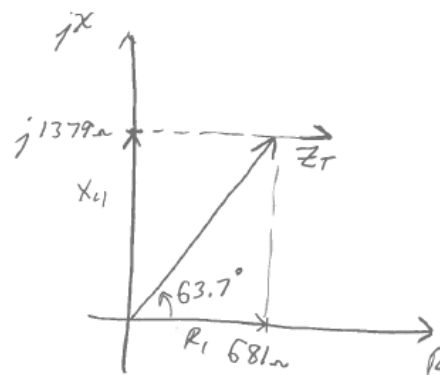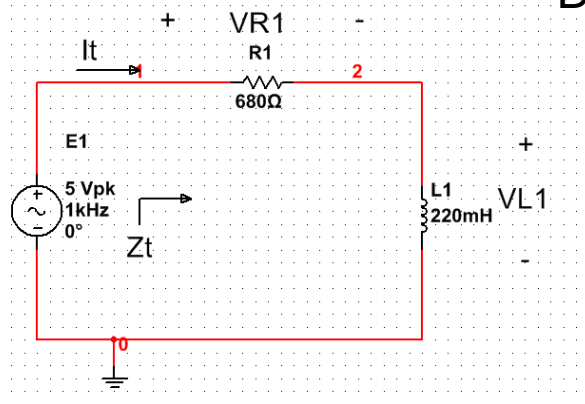

$$\vec{Z}_T = \frac{5V \angle 0^\circ}{3.25mA \angle -63.7^\circ}$$

$$\vec{Z}_T = 1,538\Omega \angle 63.7^\circ$$

Series R-C Circuit Analysis (ICP)

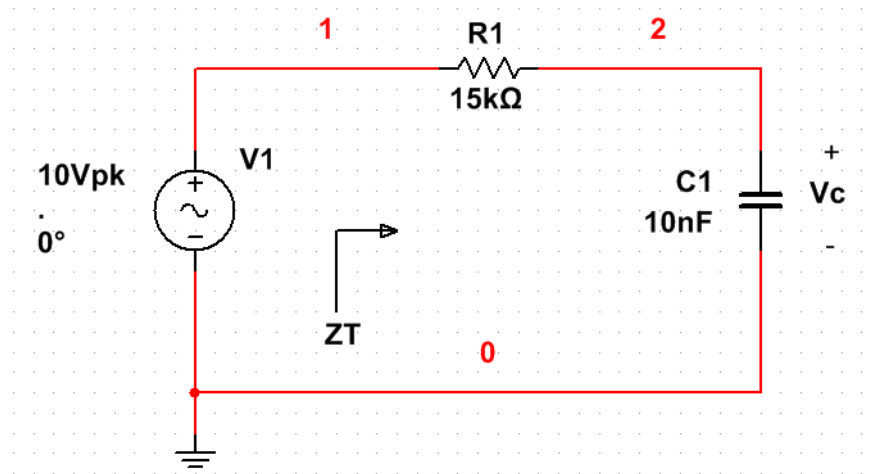


1. What is the source voltage, **V1** in phasor form?
2. Write an **equation** for the capacitive reactance, X_{C1}
3. Write an **equation** for the total impedance magnitude $|Z_T|$
4. Write an **equation** for the total impedance phase θ_T
5. Draw the impedance diagram for the circuit at 1 kHz.
6. Write an **equation** for the series current **I**
7. Find the corner frequency, f_1
8. Write an **equation** for **Vc**
9. Using your results, check the values in the table below AND complete it:

Table 1: Calculated Values for the Series RC Circuit

$f(\text{Hz})$	$X_C(\Omega)$	$Z_T(\Omega)$		$V_C(V_{pk})$	
		$ Z_T $	θ_T°	$ V_C $	θ_C°
10	$1.59 \cdot 10^6$	$1.59 \cdot 10^6$	-89.5	10	-0.54
1000					
10,000					
20,000	795.8	15,021	-3.04	0.53	-87.0


Series R-C Circuit Analysis (Z_T)

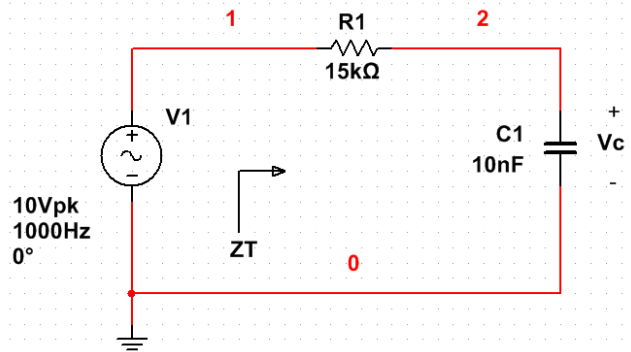


f (Hz)	$X_C (\Omega)$	\vec{Z}_T
10	1.592×10^5	$1.592 \times 10^5 \angle -89.5^\circ$
1,000	15,915	$21,870 \angle -46.7^\circ$
10,000	1,592	$15,084 \angle -6.06^\circ$
20,000	795.8	$15,021 \angle -3.04^\circ$

Multisim:

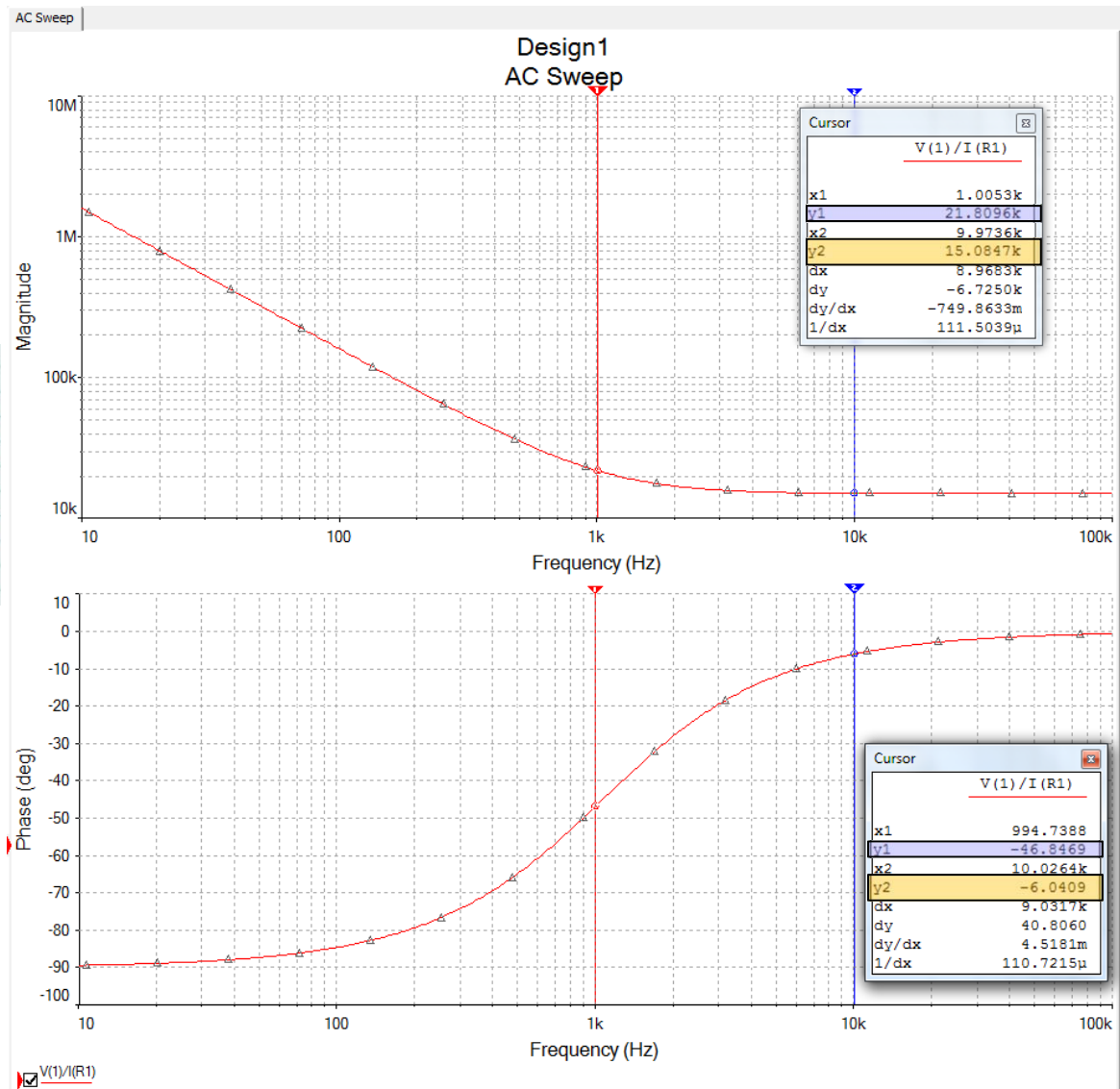- 1) Z_T magnitude and angle matches with calculations
- Simulation setup
 - Include 100 points/decade or more



Series R-C Circuit Analysis (Vc)

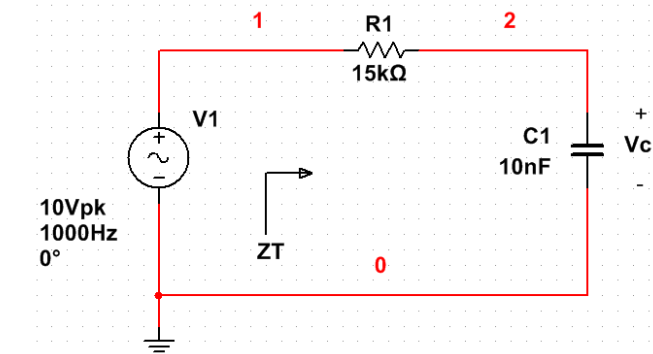

f (Hz)	$X_C (\Omega)$	\vec{V}_c
10	1.592×10^5	$10.0V_{pk} \angle -0.54^\circ$
1,000	15,915	$7.28V_{pk} \angle -43.3^\circ$
10,000	1,592	$1.06V_{pk} \angle -83.9^\circ$
20,000	795.8	$0.530V_{pk} \angle -87.0^\circ$

Multisim:

- 1) V_c magnitude and angle matches with calculations
- Simulation setup
 - Include 100 points/decade or more
 - "AC Analysis Magnitude"

