

Electrical Engineering Technology

Parallel Resonant Circuits and Simulation

Spring 2019 (2185)

Parallel Resonant Circuits and Simulation

□ Parallel Resonance (Summary)

- General circuit
- Simplified circuit ($Q \geq 10$)
- Impedance and voltage over frequency (frequency response)
- Selectivity change with varying R_L
- Summary equations from the text


□ Parallel Resonance ICP

- Calculations using the $Q \geq 10$ equivalent circuit
- Z_{TP} calculation (exact)
- I_T calculation (exact)
- V_C calculation (exact)
- Simulation results/clarifications


Parallel Resonance - Summary

General circuit

General Parallel
R-L-C Circuit

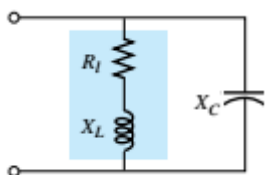

Converted to parallel equivalent

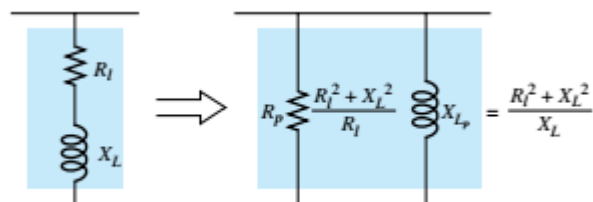

Simplified ($Q \geq 10$)


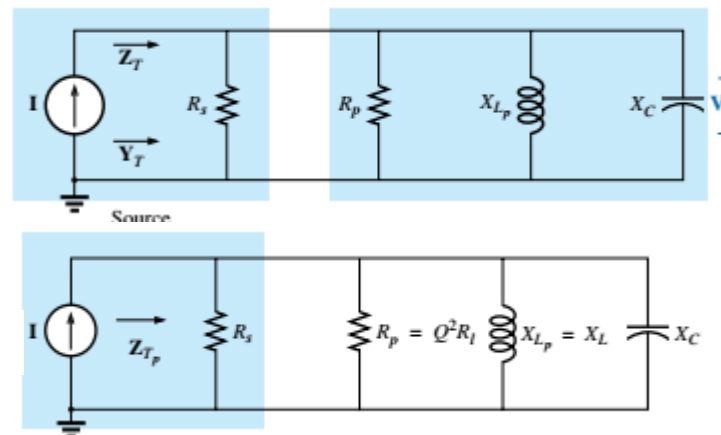


TABLE 21.2

Parallel resonant circuit ($f_s = 1/(2\pi\sqrt{LC})$).


	Any Q_L	$Q_L \geq 10$	$Q_L \geq 10, R_s \gg Q_L^2 R_L$
f_p	$f_s \sqrt{1 - \frac{R_L^2 C}{L}}$	f_s	f_s
f_m	$f_s \sqrt{1 - \frac{1}{4} \left[\frac{R_L^2 C}{L} \right]}$	f_s	f_s
Z_{Tp}	$R_s \parallel R_p = R_s \parallel \left(\frac{R_L^2 + X_L^2}{R_L} \right)$	$R_s \parallel Q_L^2 R_L$	$Q_L^2 R_L$
Z_{Tm}	$R_s \parallel Z_{R-L} \parallel Z_C$	$R_s \parallel Q_L^2 R_L$	$Q_L^2 R_L$
Q_p	$\frac{Z_{Tp}}{X_{Lp}} = \frac{Z_{Tp}}{X_C}$	$\frac{Z_{Tp}}{X_L} = \frac{Z_{Tp}}{X_C}$	Q_L
BW	$\frac{f_p}{Q_p}$ or $\frac{f_m}{Q_p}$	$\frac{f_p}{Q_p} = \frac{f_s}{Q_p}$	$\frac{f_p}{Q_L} = \frac{f_s}{Q_L}$
I_L, I_C	Network analysis	$I_L = I_C = Q_L I_T$	$I_L = I_C = Q_L I_T$

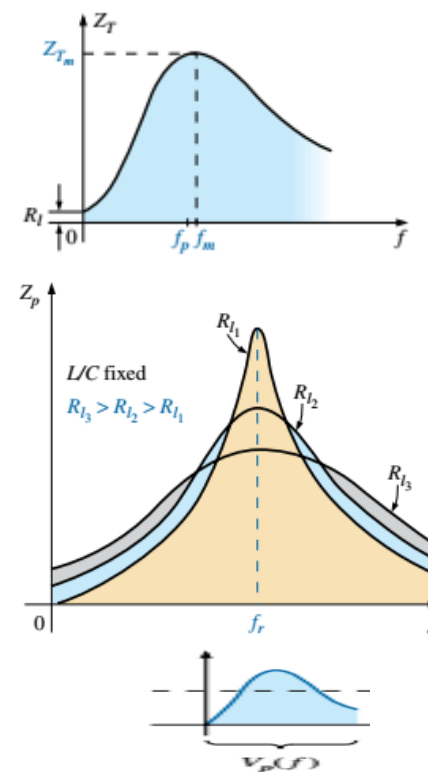

Parallel Resonance – In Class Example

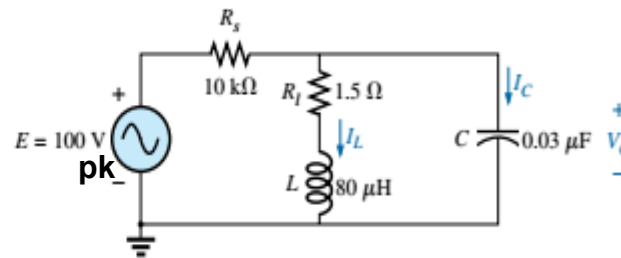18. For the network in Fig. 21.59:

- Find the resonant frequencies f_s , f_p , and f_m . What do the results suggest about the Q_p of the network?
- Find the values of X_L and X_C at resonance (f_p). How do they compare?
- Find the impedance Z_{T_p} at resonance (f_p).
- Calculate Q_p and the BW.
- Find the magnitude of currents I_L and I_C at resonance (f_p).
- Calculate the voltage V_C at resonance (f_p).



(a) f_s, f_p, f_m

$$f_s = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{(2\pi)\sqrt{(80\mu H)(0.03\mu F)}} = \boxed{102.7 \text{ KHz}}$$

$$\begin{aligned} f_p &= f_s \sqrt{1 - \frac{R_l^2 C}{L}} = (102.7 \text{ KHz}) \sqrt{1 - \frac{(1.5)^2 (0.03\mu F)}{80\mu H}} \\ &= (102.7 \text{ KHz})(0.9995) \\ &= \boxed{102.7 \text{ KHz}} \end{aligned}$$

$$\begin{aligned} f_m &= f_s \sqrt{1 - \frac{1}{4}\left(\frac{R_l^2 C}{L}\right)} \\ &= (102.7 \text{ KHz})(0.9999) \\ &= \boxed{f_m = 102.7 \text{ KHz}} \end{aligned}$$

$$f_s \sim f_p \sim f_m \Rightarrow \text{HIGH } Q \text{ (} Q > 10 \text{)}$$

Therefore, we are using the $Q \geq 10$ circuit and equations

Parallel Resonance – In Class Example

Simplified Circuit
($Q \geq 10$)

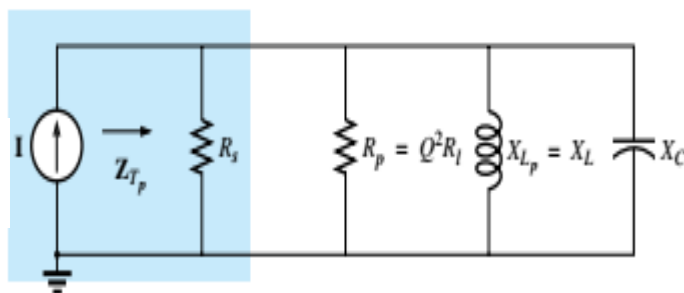


TABLE 21.2

Parallel resonant circuit ($f_s = 1/(2\pi\sqrt{LC})$).

	Any Q_l	$Q_l \geq 10$	$Q_l \geq 10, R_s \gg Q_l^2 R_l$
f_p	$f_s \sqrt{1 - \frac{R_l^2 C}{L}}$	f_s	f_s
f_m	$f_s \sqrt{1 - \frac{1}{4} \left[\frac{R_l^2 C}{L} \right]}$	f_s	f_s
Z_{T_p}	$R_s \parallel R_p = R_s \parallel \left(\frac{R_l^2 + X_L^2}{R_l} \right)$	$R_s \parallel Q_l^2 R_l$	$Q_l^2 R_l$
Z_{T_m}	$R_s \parallel Z_{R \cdot L} \parallel Z_C$	$R_s \parallel Q_l^2 R_l$	$Q_l^2 R_l$
Q_p	$\frac{Z_{T_p}}{X_{L_p}} = \frac{Z_{T_p}}{X_C}$	$\frac{Z_{T_p}}{X_L} = \frac{Z_{T_p}}{X_C}$	Q_l
BW	$\frac{f_p}{Q_p}$ or $\frac{f_m}{Q_p}$	$\frac{f_p}{Q_p} = \frac{f_s}{Q_p}$	$\frac{f_p}{Q_l} = \frac{f_s}{Q_l}$
I_L, I_C	Network analysis	$I_L = I_C = Q_l I_T$	$I_L = I_C = Q_l I_T$

Parallel Resonance – In Class Example

18. For the network in Fig. 21.59:

- Find the resonant frequencies f_s , f_p , and f_m . What do the results suggest about the Q_p of the network?
- Find the values of X_L and X_C at resonance (f_p). How do they compare?
- Find the impedance Z_{Tp} at resonance (f_p).
- Calculate Q_p and the BW.
- Find the magnitude of currents I_L and I_C at resonance (f_p).
- Calculate the voltage V_C at resonance (f_p).


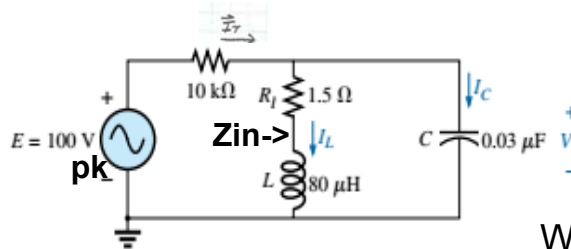


FIG. 21.59

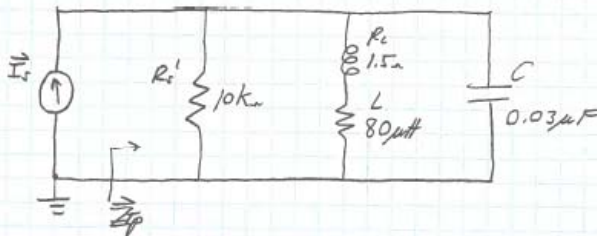Problem 18.

Where is **ZTp** in this circuit?

CONVERT \vec{E}_s, \vec{R}_s TO A PRACTICAL CURRENT SOURCE:



RECALL: $f_p = 102.7 \text{ kHz}$

@ f_p : $X_L = X_C = 51.7 \Omega$

\vec{Z}_{Tp} ($\vec{Z}_T @ f_p$):

$$\vec{Z}_{Tp} = R_s' // (R_l + jX_L) // -jX_C$$

$$= 10,000 \Omega // (1.5 + j51.7) \Omega // -j51.7 \Omega$$

$$\vec{Z}_{Tp} = \boxed{1,513 \Omega \angle -1.4^\circ}$$

At f_p :

$$\begin{aligned} \vec{Z}_{in} &= (-jX_C) // (R + jX_L) \\ &= (-j51.7 \Omega) // (1.5 + j51.7) \Omega \\ &= 1,783 \Omega \angle -1.66^\circ \end{aligned}$$

$$\begin{aligned} I_T &= E / (\vec{Z}_{in} + R_s) \\ &= 8.49 \text{ mA}_{pk} \angle 0.3^\circ \end{aligned}$$

$$\begin{aligned} V_C &= (I_T)(\vec{Z}_{in}) \\ &= 15.1 \text{ V}_{pk} \angle -1.4^\circ \end{aligned}$$

Standard circuit analysis
still works!

Very close to the value obtained using the $Q \gg 10$ circuit approximation of 1507 Ohms

Parallel Resonance – Simulation

18. For the network in Fig. 21.59:

- Find the resonant frequencies f_s , f_p , and f_m . What do the results suggest about the Q_p of the network?
- Find the values of X_L and X_C at resonance (f_p). How do they compare?
- Find the impedance Z_{T_p} at resonance (f_p).
- Calculate Q_p and the BW .
- Find the magnitude of currents I_L and I_C at resonance (f_p).
- Calculate the voltage V_C at resonance (f_p).


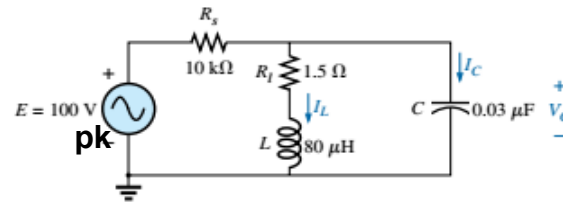
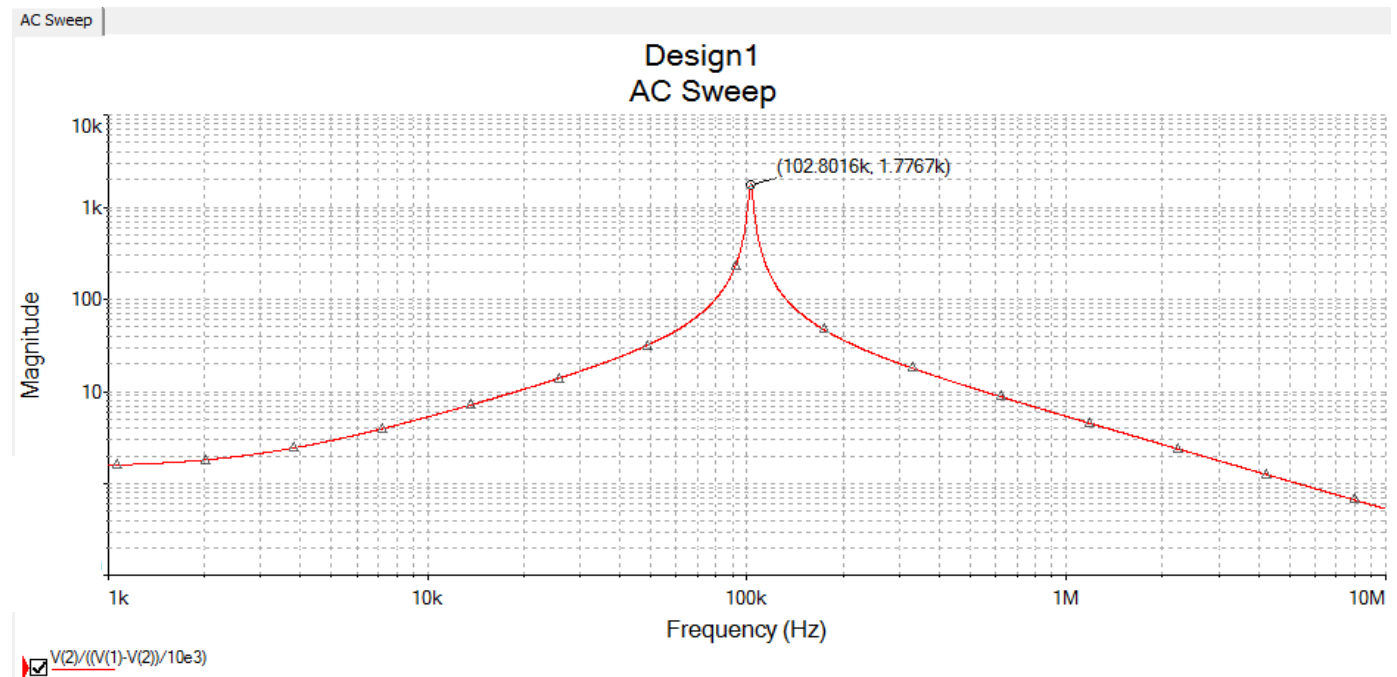


FIG. 21.59
Problem 18.


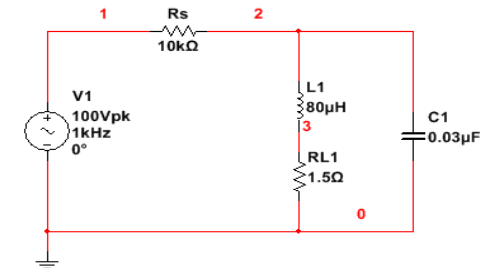


What is this the plot of?



Interpret the plot

- What is f_p ?
- What is $|Z_{TP}|$?

Parallel Resonance – In Class Example

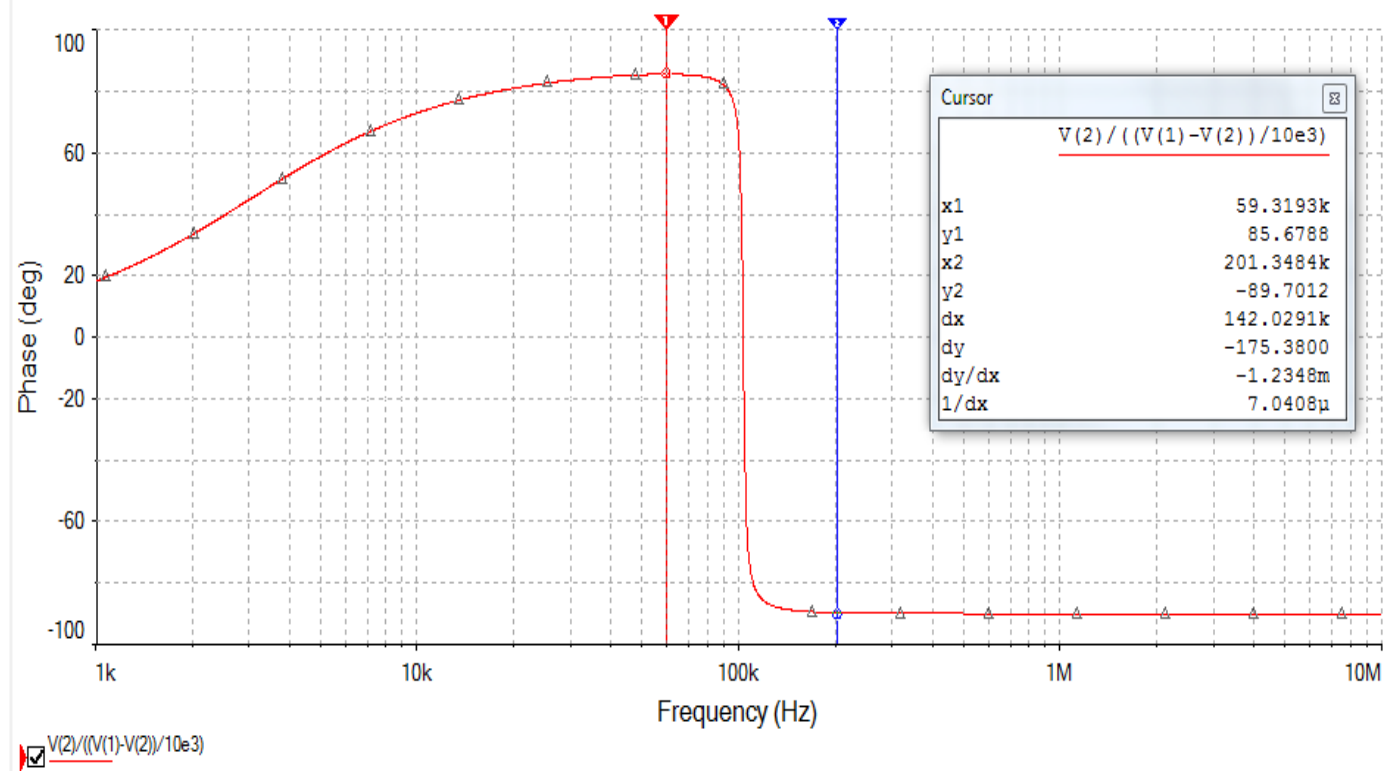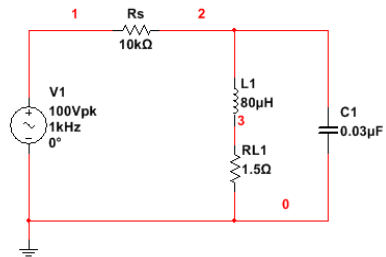



Parallel Resonance – In Class Example

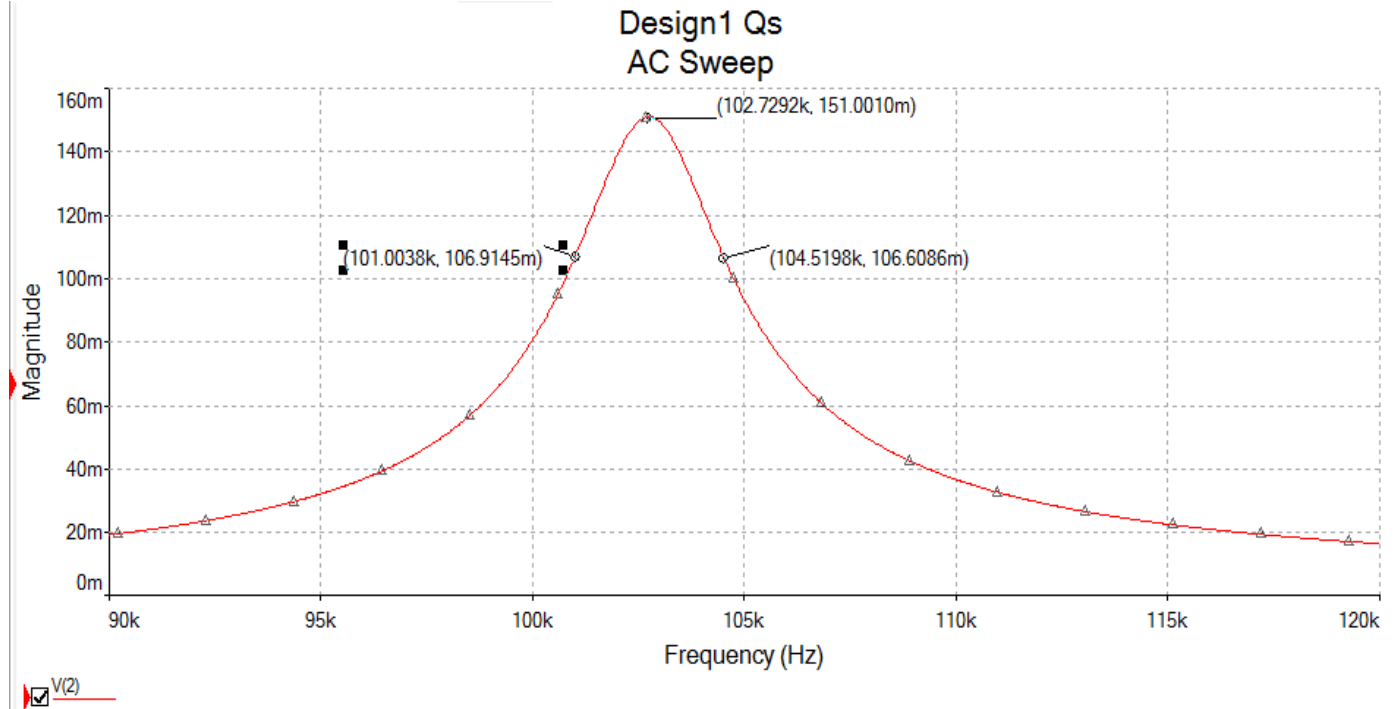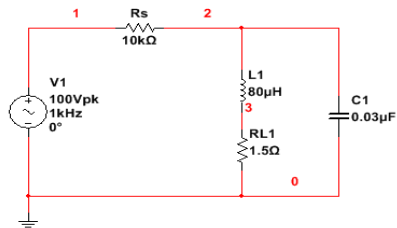

Plot of $V_2 = V_P$

- This should be 15.1V at f_p
- Why isn't it?

Parallel Resonance – In Class Example

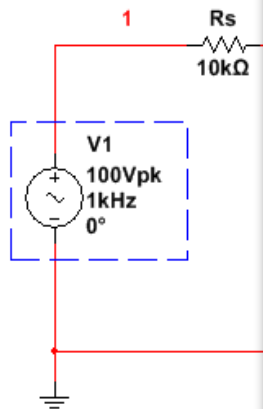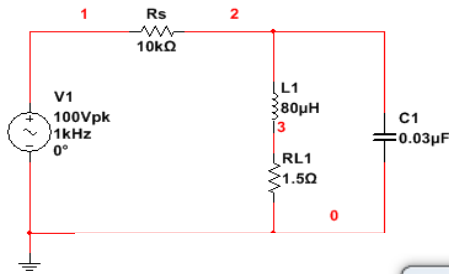

AC_VOLTAGE


Label	Display	Value	Fault	Pins	Variant
Voltage (Pk):		100			V
Voltage offset:		0			V
Frequency (F):		1k			Hz
Time delay:		0			s
Damping factor (1/s):		0			
Phase:		0			°
AC analysis magnitude:		1			V
AC analysis phase:		0			°
Distortion frequency 1 magnitude:		0			V
Distortion frequency 1 phase:		0			°
Distortion frequency 2 magnitude:		0			V
Distortion frequency 2 phase:		0			°
Tolerance:		0			%

Replace... OK Cancel Help


AC analysis magnitude is set to 1V by default

- We usually scale the result (i.e. $151\text{mV} * 100 = 15.1\text{V}$)
- We can change the number and re-simulate

Parallel Resonance – In Class Example

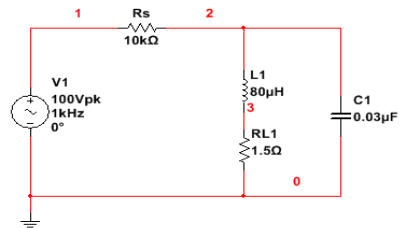

AC analysis magnitude set to 100V

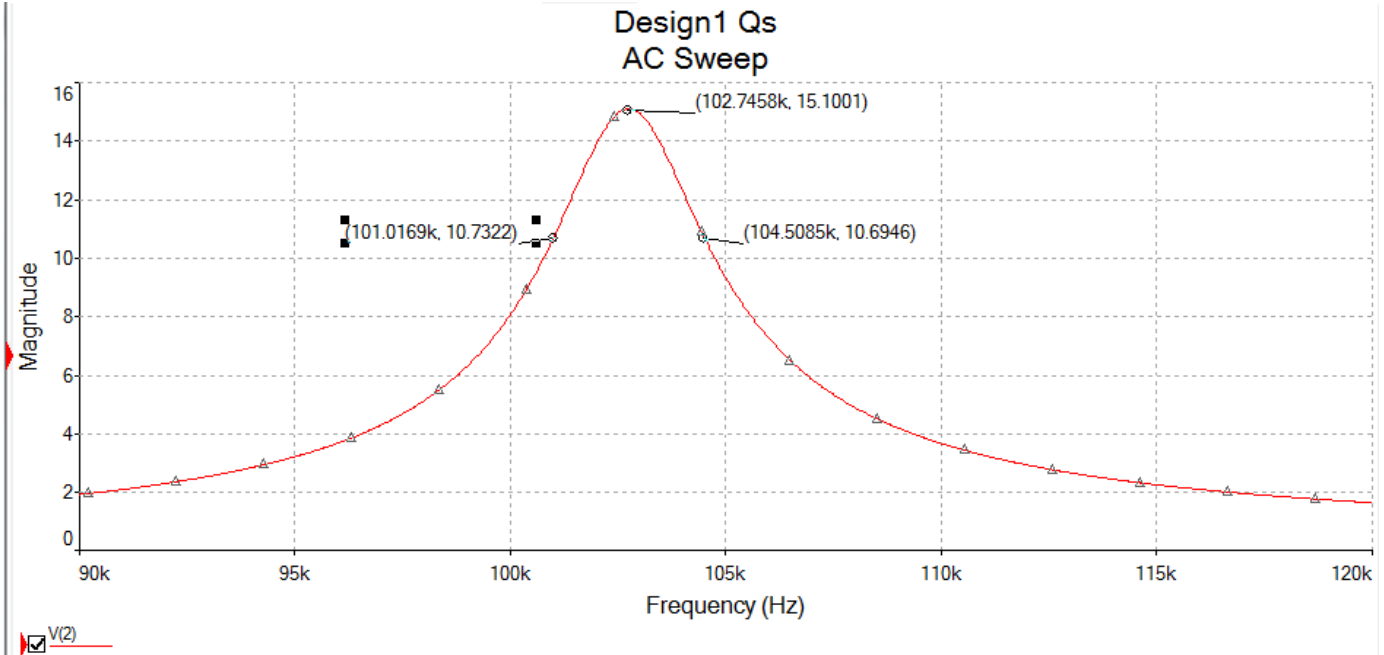

Interpret the plot

- What is V_p at f_p ?
- What is f_p ?
- What is the BW?
- What is Q_p ?