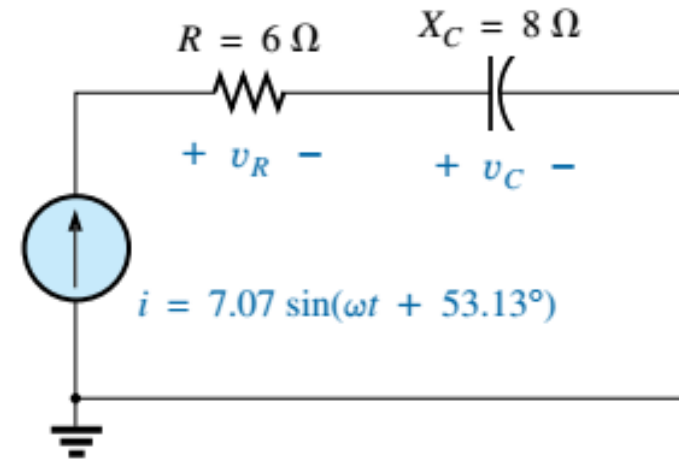


## ICP 1 - Series RC Circuit

- Consider the series RC circuit in Fig. 15.33, analyze the circuit similar to the RL circuit.
  1. Write the current  $\mathbf{I}$  in phasor form.
  2. Calculate the total impedance  $\mathbf{Z}_T$  of the circuit
  3. Find the voltage across the current source,  $\mathbf{V}_{in}$  and the voltages  $\mathbf{V}_R$  and  $\mathbf{V}_C$
  4. Find the power delivered to the loads and the total power delivered



**FIG. 15.33**  
*Series R-C ac circuit.*

Use the table below to check your analysis of the series RC circuit

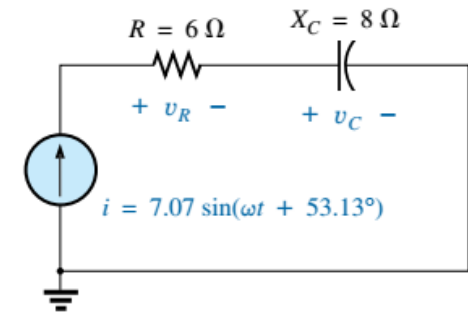


FIG. 15.33


Series R-C ac circuit.

		<b>R</b>	<b>C</b>	<b>Total</b>	
<b>E</b>	<b>Polar</b>	$30 \angle 53.13^\circ$	$40 \angle -36.87^\circ$	$50 \angle 0^\circ$	<b>V<sub>rms</sub></b>
	<b>Rectangular</b>	$18 + j24$	$32 - j24$	$50 + j0$	
<b>I</b>	<b>Polar</b>	$5 \angle 53.13^\circ$	$5 \angle 53.13^\circ$	$5 \angle 53.13^\circ$	<b>A<sub>rms</sub></b>
	<b>Rectangular</b>	$3 + j4$	$3 + j4$	$3 + j4$	
<b>Z</b>	<b>Polar</b>	$6 \angle 0^\circ$	$8 \angle -90^\circ$	$10 \angle -53.13^\circ$	<b>Ohms</b>
	<b>Rectangular</b>	$6 + j0$	$0 - j8$	$6 - j8$	
<b>P</b>		150	0	150	<b>Watts</b>

$$F_P = \cos \theta_T = \frac{R}{Z_T} = \cos(53.13) = \frac{6\Omega}{10\Omega} = 0.6 \text{ leading}$$

## ICP 2 – Voltage Divider Rule

- Using the voltage divider rule, find the unknown voltages  $V_R$ ,  $V_L$ ,  $V_C$ , and  $V_1$  for the circuit shown below.

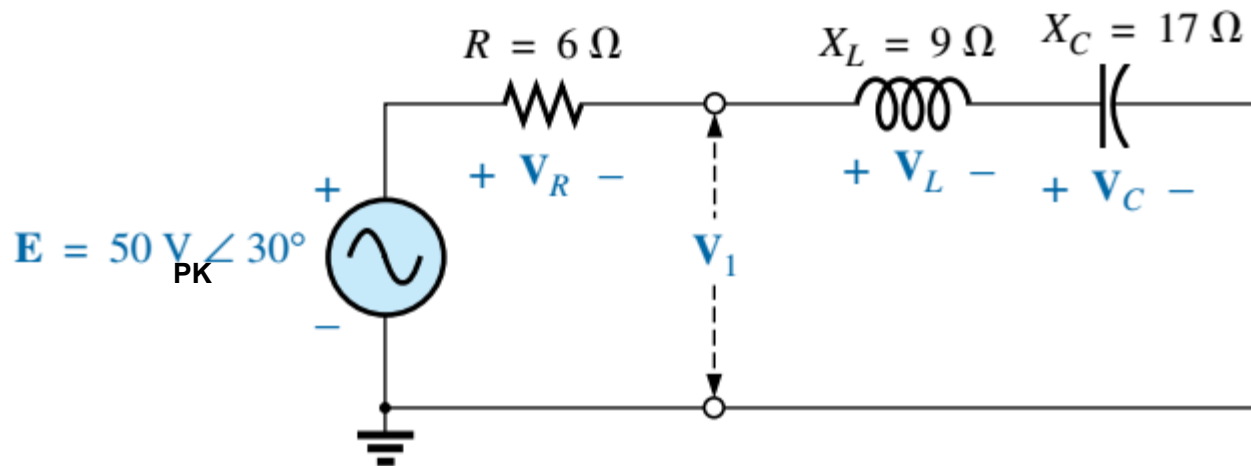

**FIG. 15.44**

*Example 15.12.*

## ICP 2 – Voltage Divider Rule

- Using the voltage divider rule, find the unknown voltages  $V_R$ ,  $V_L$ ,  $V_C$ , and  $V_1$  for the circuit shown below.

$$V_R = \frac{Z_R E}{Z_R + Z_L + Z_C} = \frac{(6\Omega \angle 0^\circ)(50V_{pk} \angle 30^\circ)}{(6\Omega \angle 0^\circ) + (9\Omega \angle 90^\circ) + (17\Omega \angle -90^\circ)}$$

$$V_R = 30V_{pk} \angle 83.13^\circ$$

$$V_L = \frac{Z_L E}{Z_T} = \frac{(9\Omega \angle 90^\circ)(50V_{pk} \angle 30^\circ)}{10\Omega \angle -53.13^\circ}$$

$$V_L = 45V_{pk} \angle 173.13^\circ$$

$$V_C = \frac{Z_C E}{Z_T} = \frac{(17\Omega \angle -90^\circ)(50V_{pk} \angle 30^\circ)}{10\Omega \angle -53.13^\circ}$$

$$V_C = 85V_{pk} \angle -6.87^\circ$$

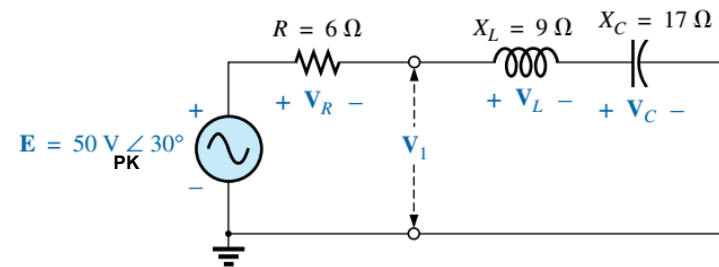


FIG. 15.44

Example 15.12.

□ Check: Sum  $V_R$ ,  $V_L$  and  $V_C$  = E, KVL


## ICP 2 – Voltage Divider Rule

- Using the voltage divider rule, find the unknown voltages  $V_R$ ,  $V_L$ ,  $V_C$ , and  $V_1$  for the circuit shown below.

$$V_1 = \frac{(Z_L + Z_C)E}{Z_T} = \frac{(9\Omega \angle 90^\circ + 17\Omega \angle -90^\circ)(50V_{pk} \angle 30^\circ)}{(10\Omega \angle -53.13^\circ)}$$

$$V_1 = \frac{(8\Omega \angle -90^\circ)(50V_{pk} \angle 30^\circ)}{(10\Omega \angle -53.13^\circ)}$$

$$V_1 = 40V_{pk} \angle -6.87^\circ$$

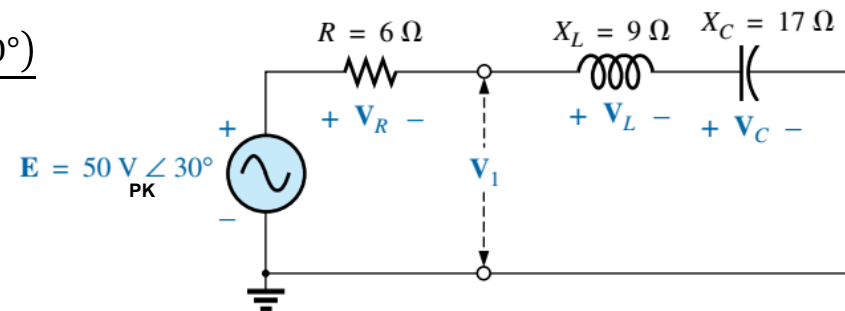

**FIG. 15.44**  
Example 15.12.