

Series-Parallel AC Networks

■ Introduction and Approach

- Introduction
- **Studying the problem**
- Complete example (Work as we go in your calculator)
- **ICP – Partial HW#6 problem**


■ Ladder Networks

- Discussion (specific case)
- Development of the approach
- Current divider – Development of the two-impedance special case

Introduction - Approach

- **In general**, when working with series-parallel ac networks, consider the following approach:
 - Redraw the network, using block impedances to combine obvious series and parallel elements, which will reduce the network to one that clearly reveals the fundamental structure of the system.
 - **1st**: Study the problem and make a brief mental sketch of the overall approach you plan to use. Doing this may result in time and energy-saving shortcuts.
 - After the overall approach has been determined, it is usually best to consider each branch involved in your method independently before tying them together in series-parallel combinations..
 - When you have arrived at a solution, check to see that it is reasonable by considering the magnitudes of the source voltage or current and the elements in the circuit.



Introduction - Approach

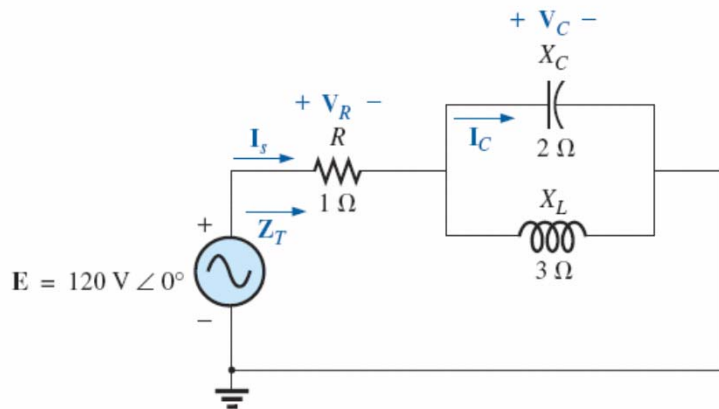

Find: Z_T , I_s , V_R , V_C , I_C

Strategy/Plan 1st

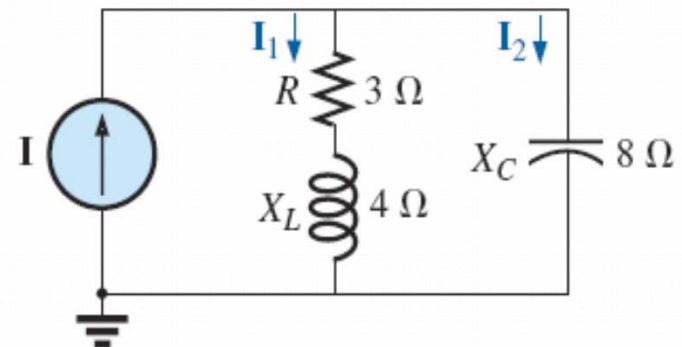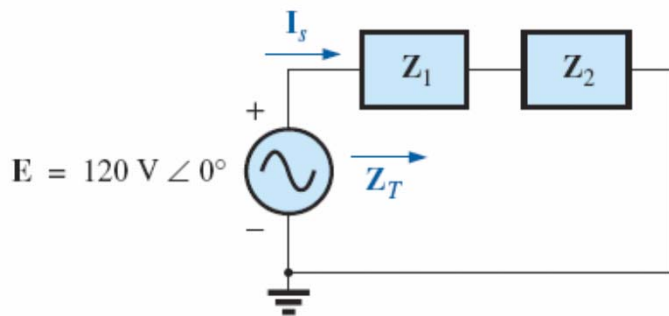
- 1) Combine L and C
- 2) Analyze the *series* circuit
 - ☐ Z_T , then I_s
 - ☐ I_C , then V_C




Find: I_1 , I_2

Strategy/Plan 1st

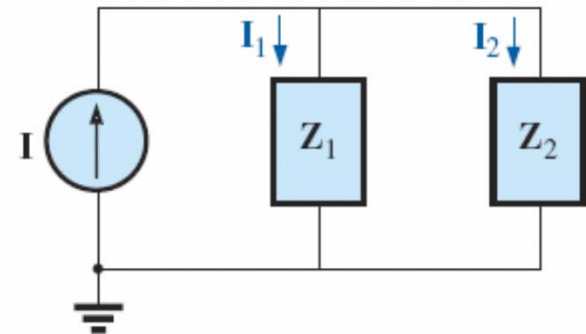- 1) Combine R and L
- 2) Analyze the *parallel* circuit
 - ☐ Use current divider



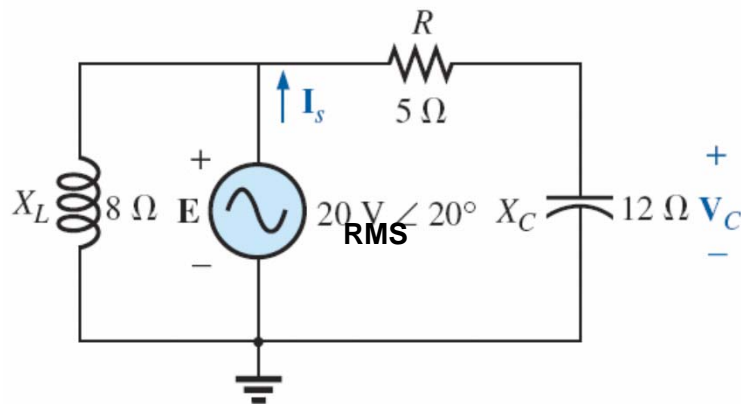Example – Work in Your Calculator as We Go



Find: I_s , V_C , FP and the average power delivered to the network


Strategy/Plan 1st

- 1) Keep each element
- 2) Analyze the *series* branch
 - ☐ V_C (voltage divider)
 - ☐ Combine R and C
- 3) Analyze the parallel circuit
 - ☐ I_s , FP, Pave

Check:

- ☐ $|V_C|$ on the order of 15 VRMS ?
- ☐ E lead I_s ?

Redrawing the circuit with the knowns:

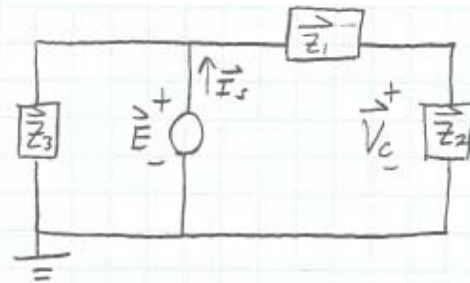

$$\vec{E} = 20 \text{ V RMS} \angle 20^\circ$$

$$\vec{Z}_1 = 5 \Omega$$

$$\vec{Z}_2 = -j12 \Omega = 12 \Omega \angle -90^\circ$$

$$\vec{Z}_3 = +j8 \Omega = 8 \Omega \angle 90^\circ$$

Finding V_C :

$$\vec{V}_C = \left(\frac{\vec{Z}_2}{\vec{Z}_2 + \vec{Z}_1} \right) \vec{E}$$


$$= 20 \text{ V RMS} \angle 20^\circ \left(\frac{12 \Omega \angle -90^\circ}{(5 - j12) \Omega} \right)$$

$$\boxed{\vec{V}_C = 18.46 \text{ V RMS} \angle -2.62^\circ}$$

Does this make sense?

Example – Work in Your Calculator as We Go

Redrawing the circuit (per the plan):

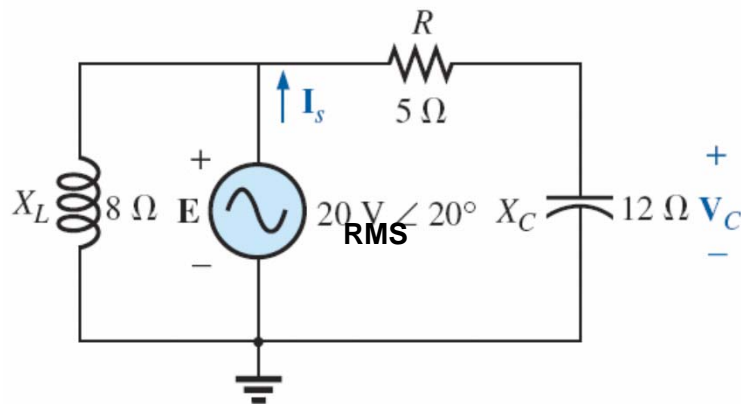


Find: I_s , V_c , F_p and the average power delivered to the network

Strategy/Plan 1st

- 1) Keep each element
- 2) Analyze the *series* branch
 - ☐ V_c (voltage divider)
 - ☐ Combine R and C
- 3) Analyze the parallel circuit
 - ☐ I_s , F_p , P_{ave}

Check:

- ☐ $|V_c|$ on the order of $15V_{RMS}$?
- ☐ E lead I_s ?

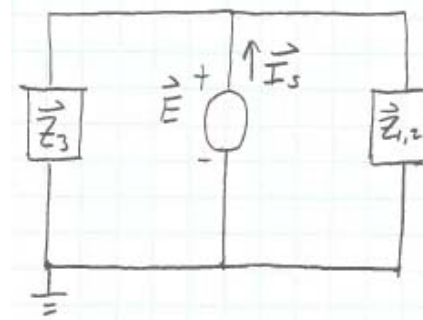

Finding I_s :

$$\vec{I}_s = \frac{\vec{E}}{\vec{Z}_{1,2} // \vec{Z}_3} = \frac{20V_{RMS} \angle 20^\circ}{16.24 \angle 61.3^\circ}$$

$$\boxed{\vec{I}_s = 1.23 A_{RMS} \angle -41.28^\circ}$$

Finding F_p :

$$F_p = \cos(\theta) = \cos(\theta_v - \theta_i)$$

$$F_p = \cos(20^\circ - (-41.28^\circ))$$


$$F_p = \cos(20^\circ + 41.28^\circ)$$

$$= \cos(61.28^\circ) = 0.48$$

Is F_p leading or lagging? Does it make sense?

LAGGING (I LAGS V)

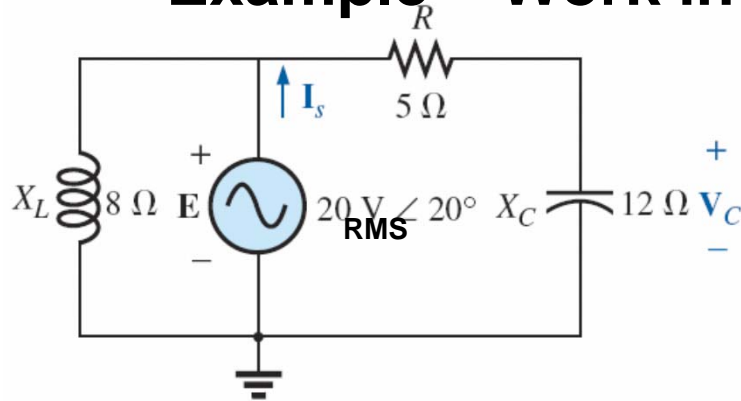
Example – Work in Your Calculator as We Go



Find: I_s , V_c , F_P and the average power delivered to the network

Strategy/Plan 1st

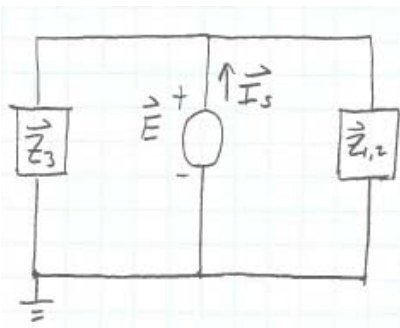- 1) Keep each element
- 2) Analyze the *series* branch
 - ☐ V_c (voltage divider)
 - ☐ Combine R and C
- 3) Analyze the *parallel* circuit
 - ☐ I_s , F_P , P_{ave}



$$P_{DELIV} = V_{RMS} I_{RMS} \cos(\theta)$$

$$= (20 V_{RMS}) (1.23 A_{RMS}) (0.48)$$

\uparrow $|\vec{E}|$ \uparrow $|\vec{I}_s|$

$$P_{DELIV} = 11.8 W$$

Is there an easy check for this number?

$$P_{DELIV} = P_R$$

$$P_R = |\vec{V}_{RMS}|^2 / R$$

$$\text{But } \vec{V}_R = \vec{E} - \vec{V}_c$$

$$\vec{V}_R = 20 V \angle 20^\circ - 18.46 V \angle 2.62^\circ$$


$$\vec{V}_R = 7.69 V_{RMS} \angle 87.4^\circ$$

$$\therefore P_R = \frac{(7.69 V_{RMS})^2}{5 \Omega}$$

$$P_R = 11.8 W$$

CHECK ☺

In Class Problem (partial HW problem)

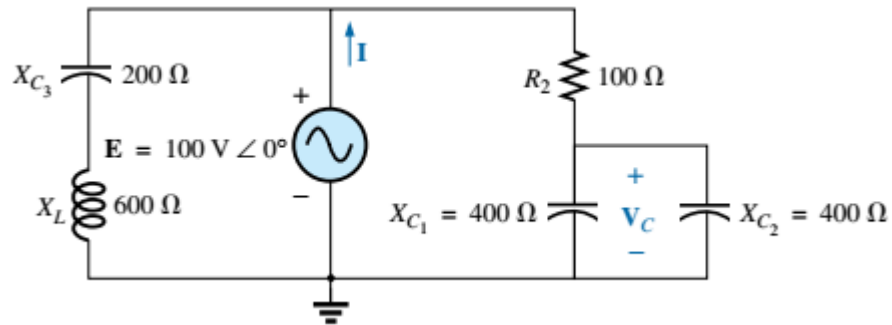


Find: I , P_{R2}

(one possible) Strategy/Plan 1st

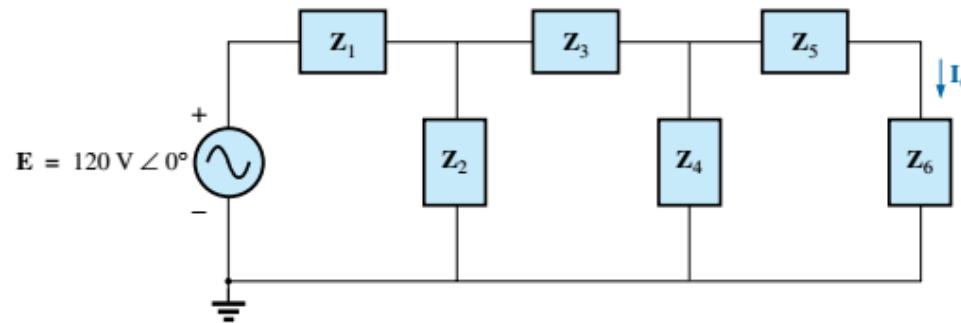- 1) Combine R_2 , C_1 , $C_2 \rightarrow \mathbf{Z_1}$
- 2) Combine C_3 , $L \rightarrow \mathbf{Z_2}$
- 3) Analyze the parallel circuit
 - ☐ I
 - ☐ P_{R2}

Ladder Networks – One Approach (same as in DC Circuits)




A specific series-parallel configuration


Analyze by:

- Collapse the circuit from the far end
- Find the source current
- Expand the circuit again, finding voltages or currents along the way
 - Successive application of voltage or current divider

Are there other approaches?

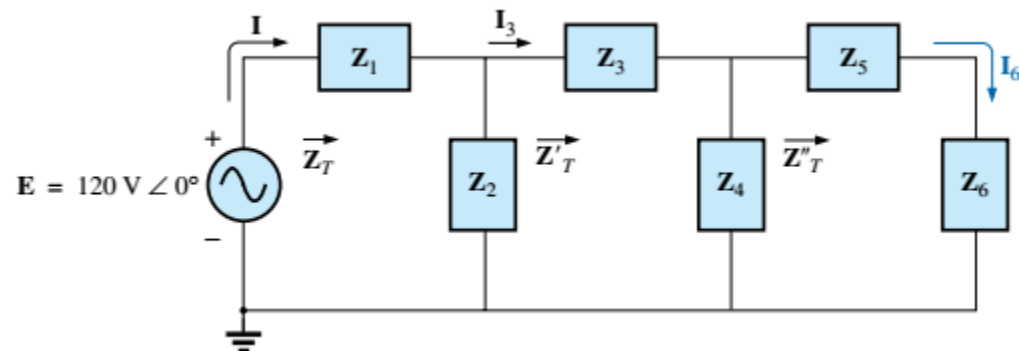

Ladder Networks – One Approach

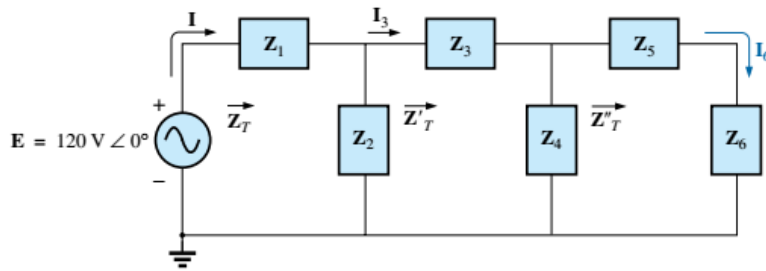

Finding \mathbf{Z}_T

$$\mathbf{Z}''_T = \mathbf{Z}_5 + \mathbf{Z}_6$$

and

$$\mathbf{Z}'_T = \mathbf{Z}_3 + \mathbf{Z}_4 \parallel \mathbf{Z}''_T$$

with

$$\mathbf{Z}_T = \mathbf{Z}_1 + \mathbf{Z}_2 \parallel \mathbf{Z}'_T$$

Finding \mathbf{I}


$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T}$$

Current Divider (special case of 2 impedances)

$$\mathbf{I}_3 = \frac{\mathbf{Z}_2 \mathbf{I}}{\mathbf{Z}_2 + \mathbf{Z}'_T}$$

$$\mathbf{I}_6 = \frac{\mathbf{Z}_4 \mathbf{I}_3}{\mathbf{Z}_4 + \mathbf{Z}''_T}$$

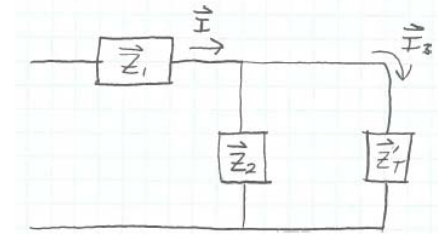Development of \mathbf{I}_3 (special case equation)



GENERAL FORM:

$$\vec{I}_x = \vec{I}_T \left(\frac{\vec{Z}_T}{\vec{Z}_x} \right)$$

HERE:

$$\vec{I}_3 = \vec{I} \left(\frac{\vec{Z}'_T \parallel \vec{Z}_2}{\vec{Z}'_T} \right)$$

$$\text{BUT } \vec{Z}'_T \parallel \vec{Z}_2 = \frac{\vec{Z}'_T \cdot \vec{Z}_2}{\vec{Z}'_T + \vec{Z}_2}$$

$$\therefore \vec{I}_3 = \vec{I} \left(\frac{\vec{Z}'_T \cdot \vec{Z}_2}{\vec{Z}'_T + \vec{Z}_2} \right) \left(\frac{1}{\vec{Z}'_T} \right)$$

$$\vec{I}_3 = \vec{I} \frac{\vec{Z}_2}{\vec{Z}'_T + \vec{Z}_2}$$