

## Series Resonance - Summary

General Series R-L-C Circuit


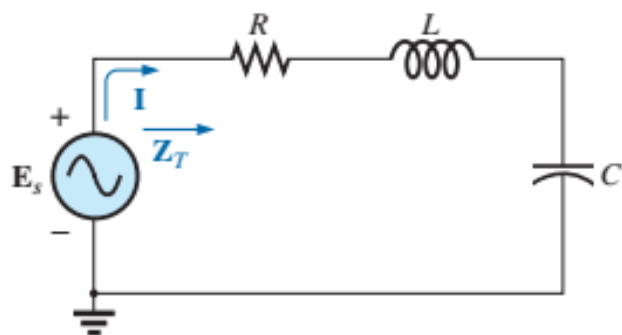
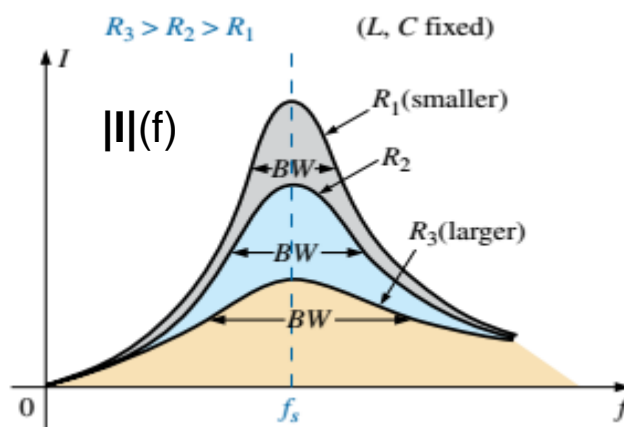
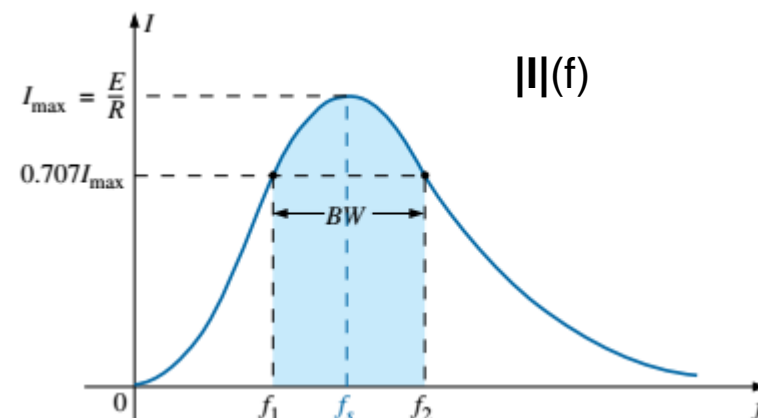


TABLE 21.1

Important equations related to series resonant circuits.

At Resonance	Additional Equations
$X_L = X_C$	$P_{\text{HPF}} = \frac{1}{2}P_{\text{max}}$
$Z_{T_s} = R$	$f_2 = \frac{1}{2\pi} \left[ \frac{R}{2L} + \frac{1}{2} \sqrt{\left(\frac{R}{L}\right)^2 + \frac{4}{LC}} \right]$
$f_s = \frac{1}{2\pi\sqrt{LC}}$	$f_1 = \frac{1}{2\pi} \left[ -\frac{R}{2L} + \frac{1}{2} \sqrt{\left(\frac{R}{L}\right)^2 + \frac{4}{LC}} \right]$
$V_{L_s} = V_{C_s} = Q_s E$	$BW = f_2 - f_1 = \frac{R}{2\pi L}$
$F_{P_s} = 1$	$f_s = \sqrt{f_1 f_2}$
$Q_s = \frac{X_L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$	

$$BW = f_s / Q_s$$

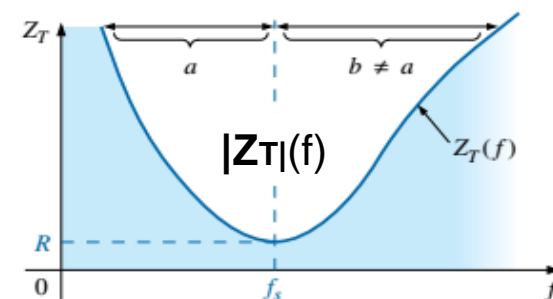

## Series Resonance – In Class problem

### Problem 9 – A Team HW Problem

- \*9. a. Design a series resonant circuit with an input voltage of  $5 \text{ V}_{pk} \angle 0^\circ$  to have the following specifications:
- Peak current of 500 mA at resonance
  - Bandwidth of 120 Hz
  - Resonant frequency of 8400 Hz
- b. Find the value of  $L$  and  $C$  and the cutoff frequencies.

#### Approach:

- Draw the circuit
- List the knowns
- List the unknowns (to solve for)
- Develop a strategy