

Phasors and Impedance

■ Phasor Representations

- ☐ Introduction for voltage and current
- ☐ Phasor arithmetic (addition)
- ☐ Peak vs RMS Values
- ☐ **ICP 1 – Phasors (conversion and arithmetic)**

■ Impedance for the Basic Elements

- ☐ Resistors
- ☐ Inductors
- ☐ Capacitors
- ☐ **ICP 2 – Impedance (Find Z, find the component given Z)**

■ Lab #3 – Prelab Discussion and Demo

- ☐ Finding the impedance of and current through a series circuit
- ☐ Using Multisim to verify your results

PHASOR REPRESENTATION FOR $v(t)$, $i(t)$

$$\left. \begin{aligned} \text{RECALL: } v(t) &= V_m \sin(\omega t + \theta) \\ i(t) &= I_m \sin(\omega t + \theta) \end{aligned} \right\} \text{SAME FREQUENCY}$$


- WE NEED A CONVENIENT WAY TO REPRESENT VOLTAGE, CURRENT & IMPEDANCE
 - > ALL HAVE MAGNITUDE & PHASE
 - > SAME FREQUENCY FOR A GIVEN CIRCUIT/ PROBLEM
- SINCE ONLY MAGNITUDE & PHASE ARE PARAMETERS, WE DEFINE VOLTAGE, CURRENT & IMPEDANCE PHASORS:

$$A \sin(\omega t + \theta) \longrightarrow A \angle \theta, \text{ FOR VOLTAGE OR CURRENT}$$

$$V_m \sin(\omega t + \theta) \longrightarrow \vec{V} = V_m \angle \theta$$

$$I_m \sin(\omega t + \theta) \longrightarrow \vec{I} = I_m \angle \theta$$

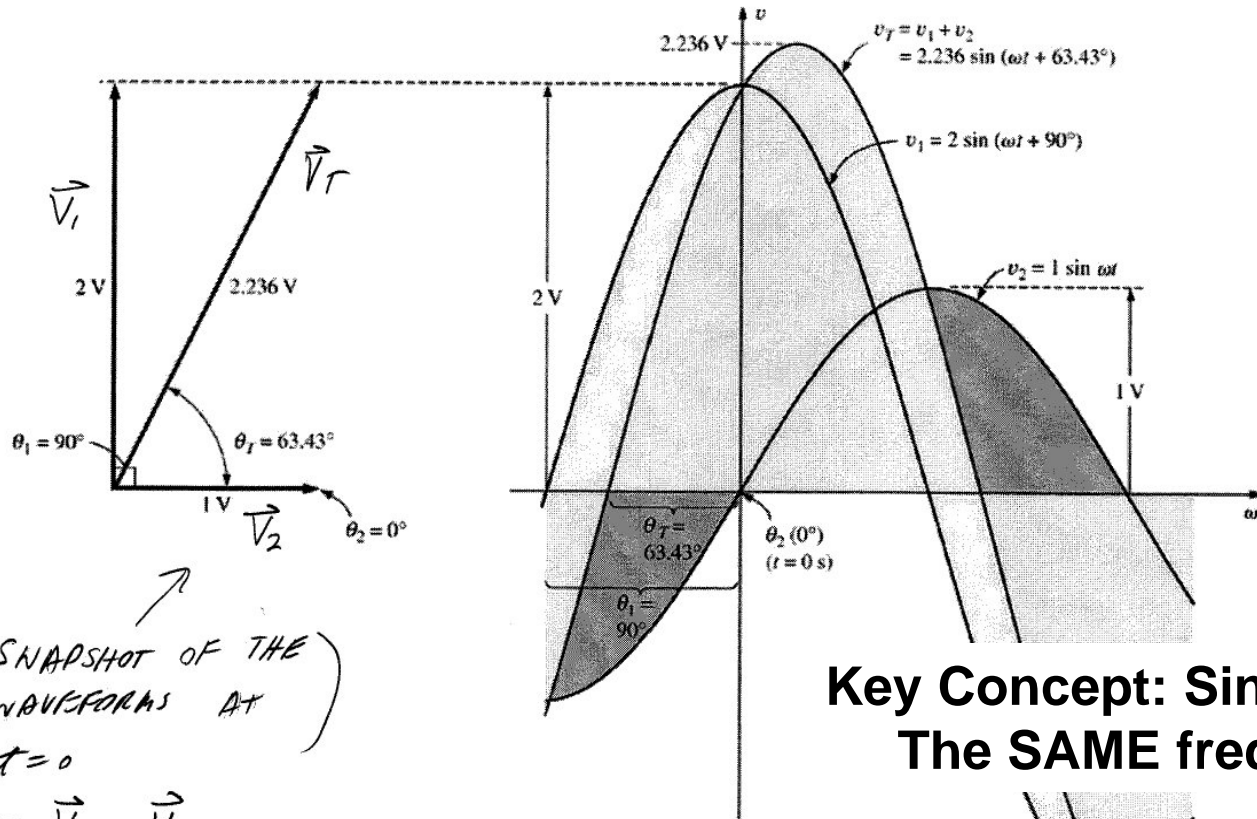Using Phasor Representation to Add Sinusoids



(SNAPSHOT OF THE
WAVEFORMS AT
 $t = 0$)

$$\vec{V}_T = \vec{V}_1 + \vec{V}_2$$

$$= 2 \angle 90^\circ + 1 \angle 0^\circ$$

$$\boxed{\vec{V}_T = 2.236 \text{ V} \angle 63.44^\circ}$$

**Key Concept: Sinusoids of
The SAME frequency**

Using Phasor Representation to Add Sinusoids

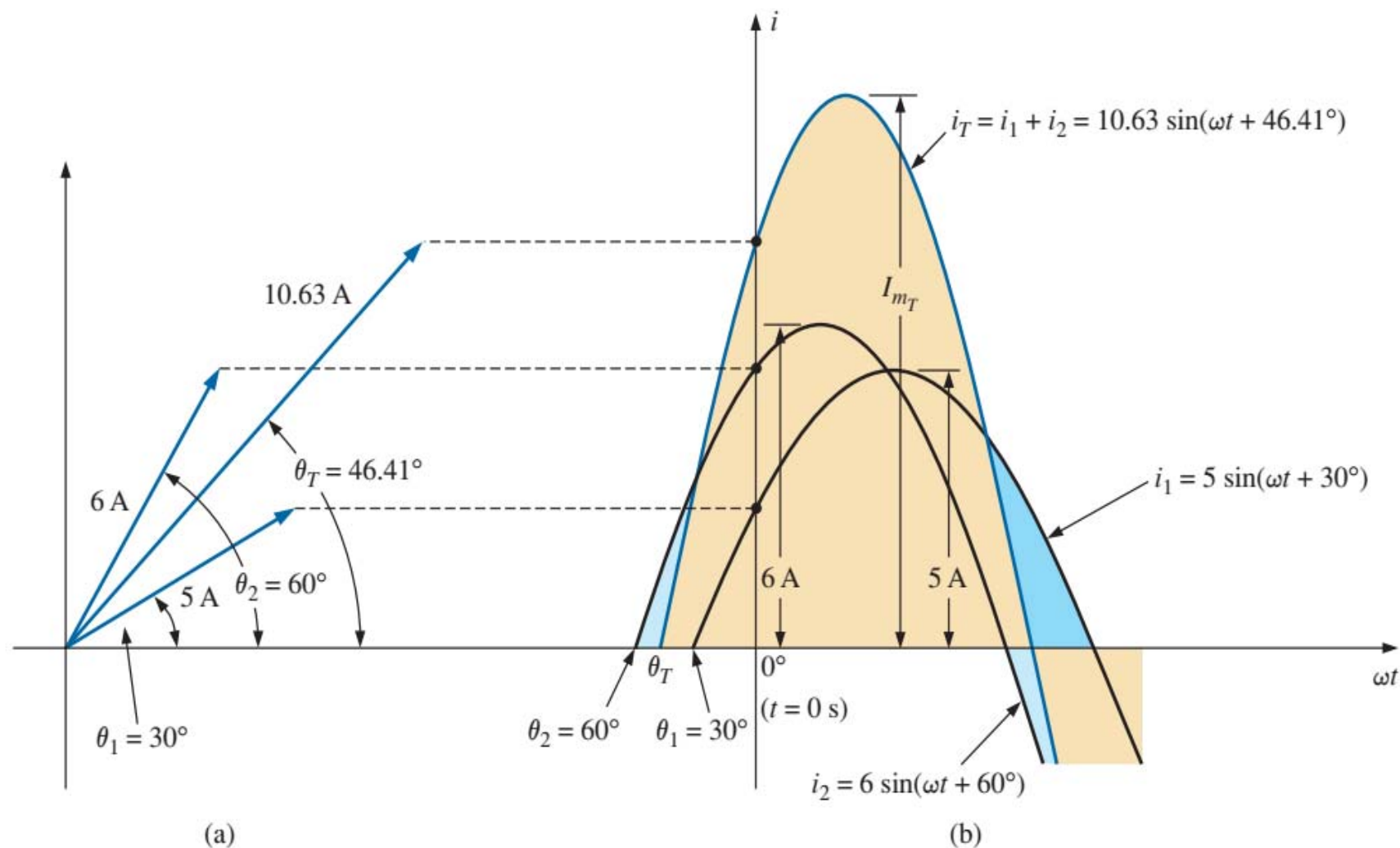


FIG. 14.68

Example 14.27

Phasor Representation for Voltage and Current

FOR THE TEXT :

$$V_m \sin(\omega t + \theta) \rightarrow \vec{V} = \left(\frac{V_m}{\sqrt{2}} \right) \angle \theta$$

$$I_m \sin(\omega t + \theta) \rightarrow \vec{I} = \left(\frac{I_m}{\sqrt{2}} \right) \angle \theta$$

↑
RMS VALUES

EXPRESS IN PHASOR FORM

$$v(t) = 42 \sin(377t + 0^\circ) \quad V$$

Or 42Vpk $\angle 0^\circ$

$$\vec{V} = \left(\frac{42}{\sqrt{2}} \right) V_{rms} \angle 0^\circ$$

* YOU MUST USE
RMS DESIGNATOR *

$$\boxed{\vec{V} = 29.7 V_{rms} \angle 0^\circ}$$

$$v(t) = 3.6 \times 10^{-6} \cos(754t - 20^\circ)$$

Or 3.6E-6Vpk $\angle 70^\circ$

$$\vec{V} = \frac{3.6 \times 10^{-6}}{\sqrt{2}} V_{rms} \angle 70^\circ$$

$$\boxed{\vec{V} = 2.55 \mu V_{rms} \angle 70^\circ}$$

EXPRESS AS A SINE WAVE $\omega / f = 60 \text{ Hz}$

If 120Vpk, we would have:
120 sin(377t) V

$$\vec{V} = 120 V \angle 0^\circ \rightarrow 120 V_{rms} \angle 0^\circ, \text{ TEXT}$$

$$\therefore v(t) = 120 \sqrt{2} \sin(377t + 0^\circ)$$

$$\boxed{v(t) = 169.71 \sin(377t) \quad V}$$

ICP Set 1 – Phasors

Use PEAK Values for your voltage and current phasors and make sure you
LABEL your phasors properly

1 - Express the following in phasor form:

- a) $230 \sin(\omega t + 30^\circ) \text{ V}$
- b) $10 \sin(\omega t - 90^\circ) \text{ A}$

2 - Express the following as sinusoids at $f = 1\text{kHz}$:


- a) $I = 10\text{E-}3\text{A}_{\text{pk}} < -80^\circ$
- b) $V = 169\text{V}_{\text{pk}} < 45^\circ$
- c) $V = 10\text{V}_{\text{RMS}} < 23^\circ$

3 - Find $v(t) = v_1(t) + v_2(t)$ if

$v_1(t) = 10 \sin(\omega t + 10^\circ)$ and $v_2(t) = 5 \sin(\omega t - 10^\circ)$

Impedance - Resistors

RECALL :

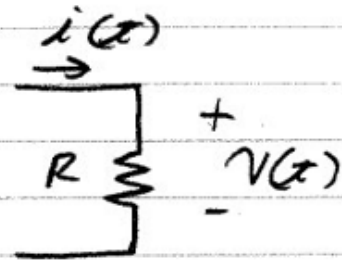

$$v(t) = V_m \sin(\omega t) \quad V$$

$$i(t) = I_m \sin(\omega t) \quad A$$

$$I_m = \frac{V_m}{R}$$


IN PHASOR FORM :

$$\vec{V} = V_m \angle 0^\circ$$

$$\vec{I} = I_m \angle 0^\circ = \frac{V_m}{R} \angle 0^\circ$$

$$\therefore \frac{\vec{V}}{\vec{I}} = \frac{V_m \angle 0^\circ}{\frac{V_m}{R} \angle 0^\circ} = \boxed{\begin{matrix} R \angle 0^\circ \\ \text{OR} \\ R + j0 \end{matrix}} \quad \leftarrow \vec{Z}$$

Impedance - Inductors

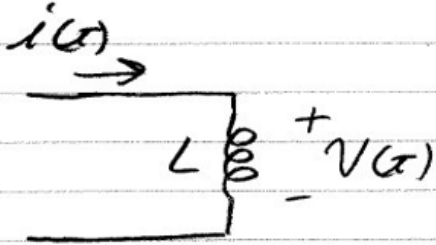

$$i(t) = I_m \sin(\omega t) \quad A$$

$$V(t) = \omega L I_m \sin(\omega t + 90^\circ) \quad V$$

$$\vec{I} = I_m \angle 0^\circ$$

$$\vec{V} = \omega L I_m \angle 90^\circ$$


$$\therefore \frac{\vec{V}}{\vec{I}} = \frac{\omega L I_m \angle 90^\circ}{I_m \angle 0^\circ} =$$

\vec{Z}



$$\begin{array}{c} \omega L \angle 90^\circ \\ \text{OR} \\ j\omega L \\ \text{OR} \\ jX_L \end{array}$$

Impedance - Capacitors

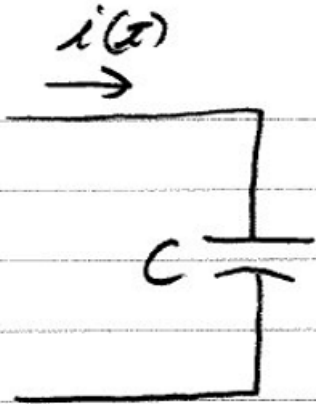

$$v(t) = V_m \sin(\omega t) \quad V$$

$$i(t) = \omega C V_m \sin(\omega t + 90^\circ) \quad A$$

$$\vec{V} = V_m \angle 0^\circ$$

$$\vec{I} = \omega C V_m \angle 90^\circ$$

$$\therefore \frac{\vec{V}}{\vec{I}} = \frac{V_m \angle 0^\circ}{\omega C V_m \angle 90^\circ}$$

$$= \frac{1}{\omega C} \angle -90^\circ$$

OR

$$X_C \angle -90^\circ$$

OR

$$\frac{-j}{\omega C} \Rightarrow -j X_C$$


ICP Set 2 – Impedance

1 – Find the impedance of:

- a) A 1000 Ohm resistor
- b) A 100mH inductor at 60 Hz
- c) A 100mH inductor at 2.5kHz
- d) A 0.1uF capacitor at 60 Hz
- e) A 0.1uF capacitor at 2.5kHz

2 - If a component has an impedance of $4\angle 90^\circ$ Ohms at $f=400\text{Hz}$, find the component type and value

Lab #3 Prelab (Partial)

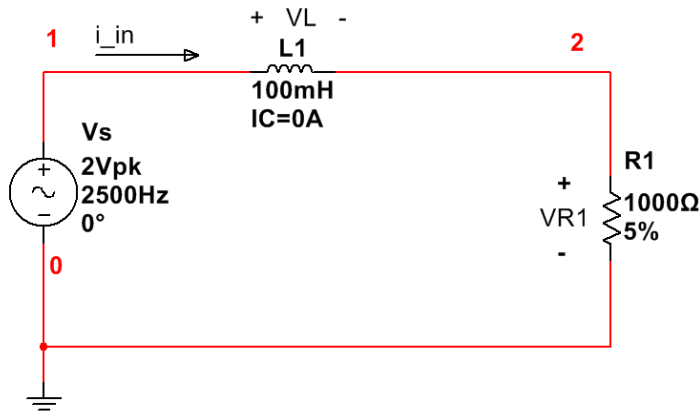


$$Z_{L1} = \omega L_1 < 90^\circ = 1,571 \text{ Ohms} < 90^\circ$$

$$Z_{R1} = R_1 < 0^\circ = 1000 \text{ Ohms} < 0^\circ$$

$$Z_T = Z_{L1} + Z_{R1} = 1862 \text{ Ohms} < 57.5^\circ$$

$$I_{in} = V_s / Z_T = (2V_{pk} < 0) / (1862 \text{ Ohms} < 57.5^\circ)$$

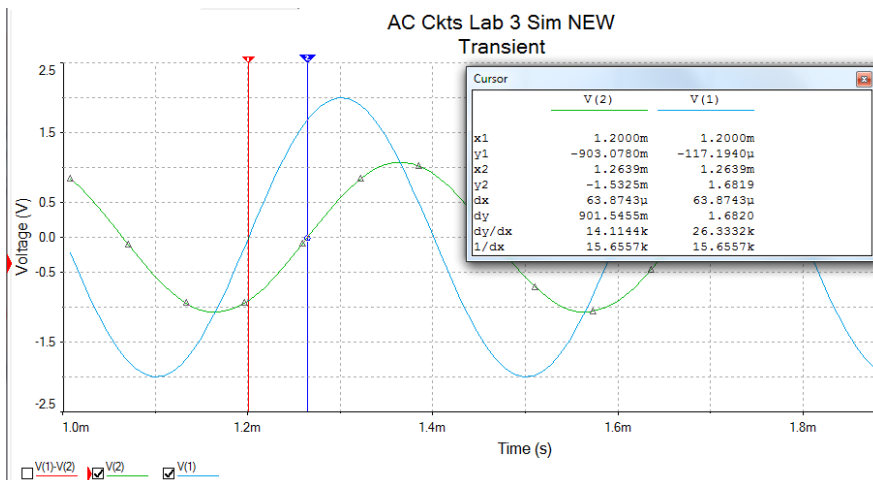1. Find the impedance of each component
2. Use Ohm's Law for phasors to determine $i_{in}(t)$, $V_L(t)$ and $V_{R1}(t)$
3. Verify your results by simulating the circuit in Multisim



$$I_{in} = V_{R1} / 1000 = 1.07V_{pk} / 1000 \text{ Ohms, lags } V_s \text{ by } 63.9\mu\text{Sec}$$

$$I_{in} = 1.07\text{mA}_{pk} < -57.5^\circ$$

$$i_{in}(t) = 1.07\text{E-}3 \sin(15,708t - 57.5^\circ) \text{ A}$$