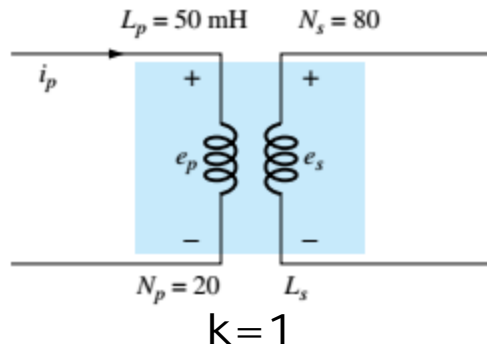



## Transformer Intro – In Class Problem



**Find:**

- a)  $L_s$  if  $M = 200 \text{ mH}$
- b)  $e_p$  and  $e_s$  if the flux linking the primary coil changes at a rate of  $0.08 \text{ Wb/s}$
- c)  $e_p$  and  $e_s$  if  $i_p$  changes at a rate of  $0.3 \text{ A/ms}$

## Transformer Intro – In Class Problem

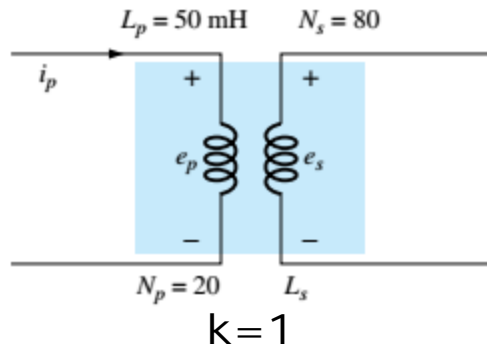

$$M = k \sqrt{L_p L_s}$$

$$200 \text{ mH} = (1) \sqrt{(50 \text{ mH})(L_s)}$$

$$\therefore L_s = 800 \text{ mH}$$

$$e_p = N_p \frac{d\phi}{dt}$$

$$= 20 \left( 0.08 \frac{\text{wb}}{\text{s}} \right)$$

$$e_p = 1.6 \text{ V}$$

$$e_s = k N_s \frac{d\phi}{dt}$$

$$= (1)(80) \left( 0.08 \frac{\text{wb}}{\text{s}} \right)$$

$$e_s = 6.4 \text{ V}$$

NOTE:  $\frac{N_s}{N_p} = \frac{80}{20} = 4$

$\frac{e_s}{e_p} = \frac{6.4 \text{ V}}{1.6 \text{ V}} = 4$

SAME (LOSSLESS) XFMR  $k=1$

$$e_p = L_p \frac{di_p}{dt}$$

$$= 50 \text{ mH} \left( \frac{0.3 \text{ A}}{1 \text{ ms}} \right)$$

$$e_p = 15 \text{ V}$$

$$e_s = M \frac{di_p}{dt}$$

$$= 200 \text{ mH} \left( \frac{0.3 \text{ A}}{1 \text{ ms}} \right)$$

$$e_s = 60 \text{ V}$$

AGAIN:  $\frac{60 \text{ V}}{15 \text{ V}} = 4$ , TURNS RATIO