

Impedance Diagrams

- Impedance Diagrams
 - For the basic elements
 - For a series circuit
 - **ICP 1 – Impedance Diagrams**
- Lab #3 – Prelab Discussion and Demo
 - Simulation demo
 - Finding $v_L(t)$

Impedance Diagram – for R, L, C

- Now that an angle is associated with resistance, inductive reactance, and capacitive reactance, each can be placed on a complex plane diagram.

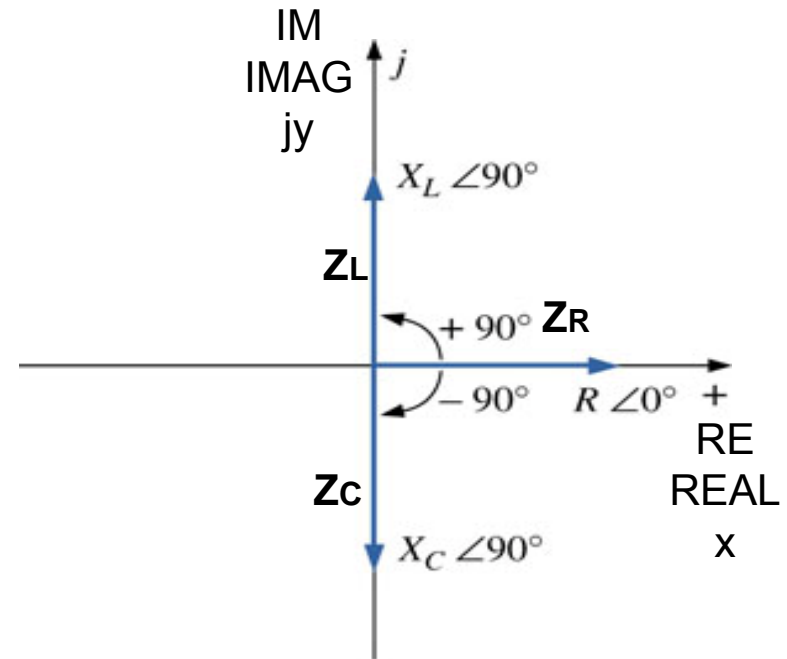


FIG. 15.20 Impedance diagram.

Impedance Diagram – For a Series R-L Circuit

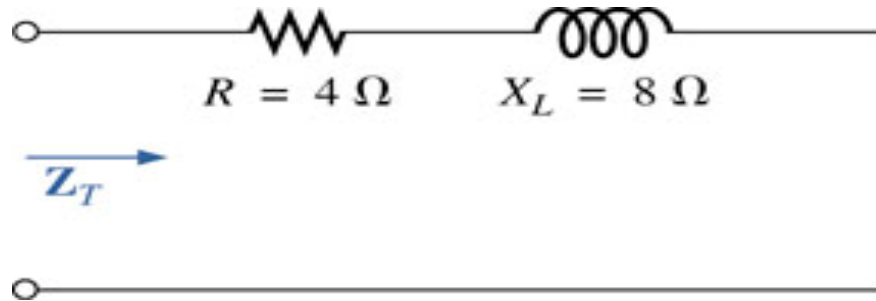


FIG. 15.24 Example 15.9.

Note: You are given X_L

What's the magnitude and angle of Z_T ?

$$Z_T = 4 + j8 = 8.94 \angle 63.4^\circ$$

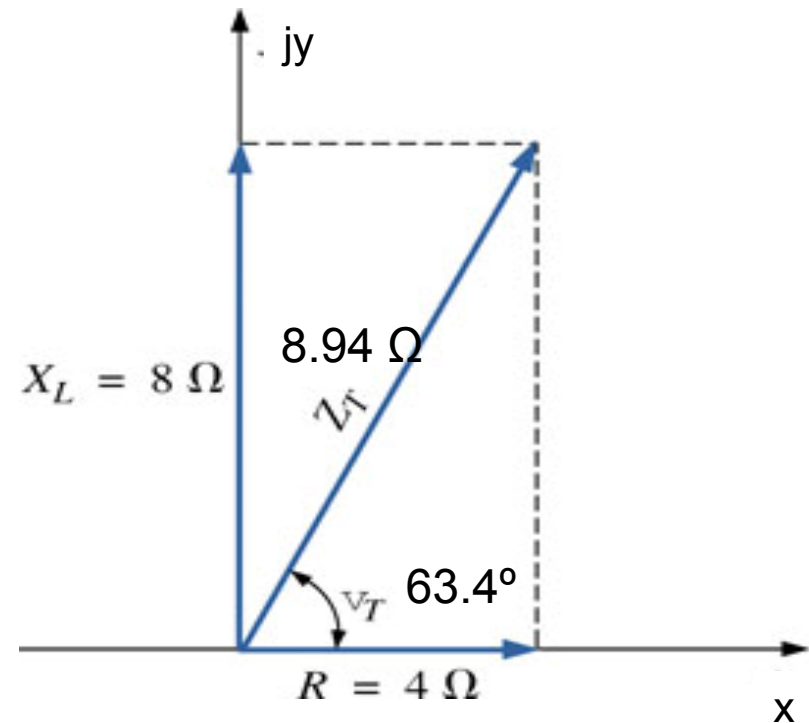


FIG. 15.25 Impedance diagram for Example 15.9.

Impedance Diagram – For a Series R,L,C Circuit

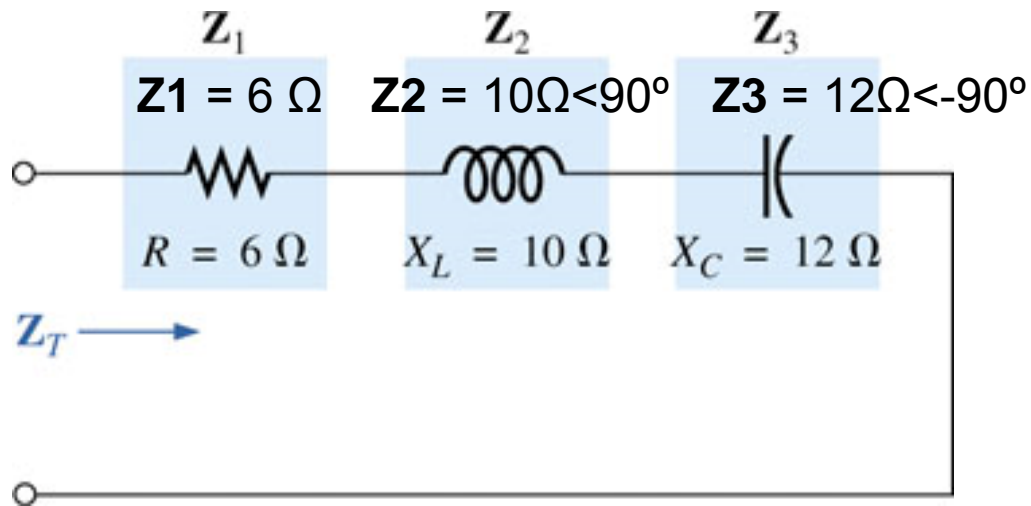


FIG. 15.26 Example 15.10

What's the magnitude and angle of Z_T ?

$$Z_T = 6 + j10 - j12 = 6 - j2$$

$$6.32 \angle -18.4^\circ$$


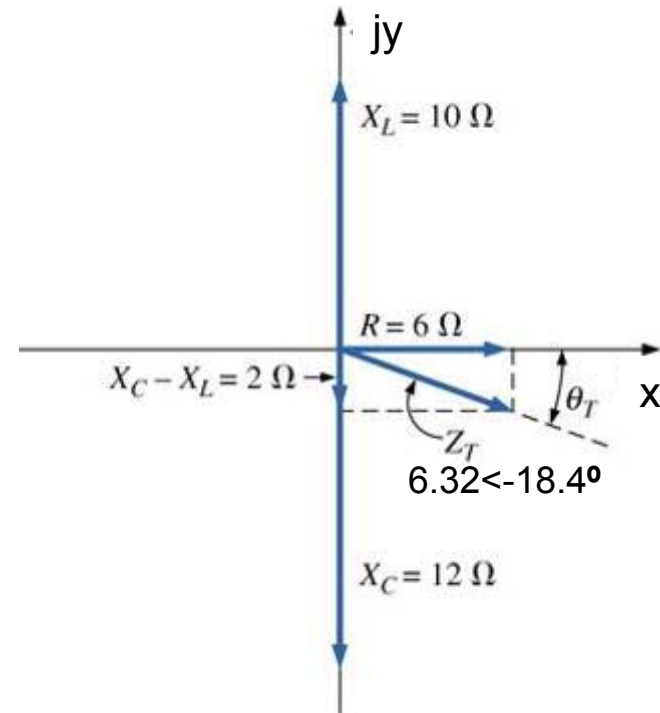


FIG. 15.27 Impedance diagram for Example 15.10.

ICP Set 1 – Impedance Diagram


1 - Find Z_T (in rectangular form) for:

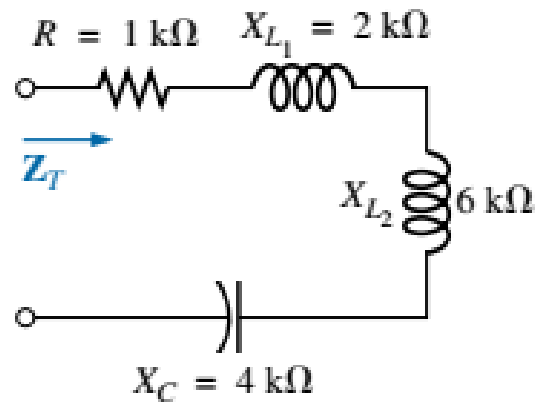

2 - Express your answer in polar form (angle in degrees):

3 - Draw the impedance diagram for the circuit shown:

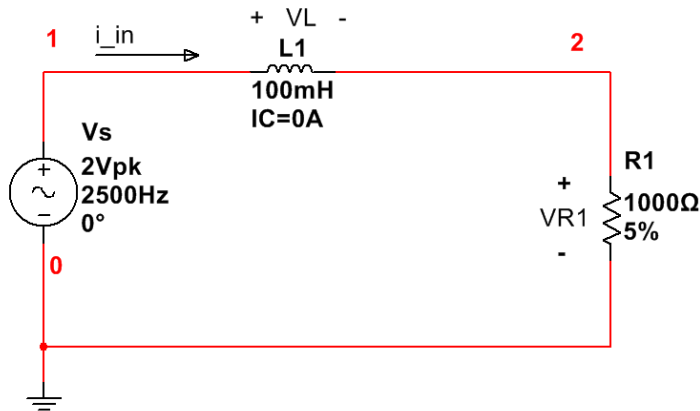Recall (from Wednesday) - Lab #3 Prelab (Partial)




$$Z_{L1} = \omega L_1 < 90^\circ = 1,571 \text{ Ohms} < 90^\circ$$

$$Z_{R1} = R_1 < 0^\circ = 1000 \text{ Ohms} < 0^\circ$$

$$Z_T = Z_{L1} + Z_{R1} = 1862 \text{ Ohms} < 57.5^\circ$$

$$I_{in} = V_s / Z_T = (2V_{pk} < 0) / (1862 \text{ Ohms} < 57.5^\circ)$$

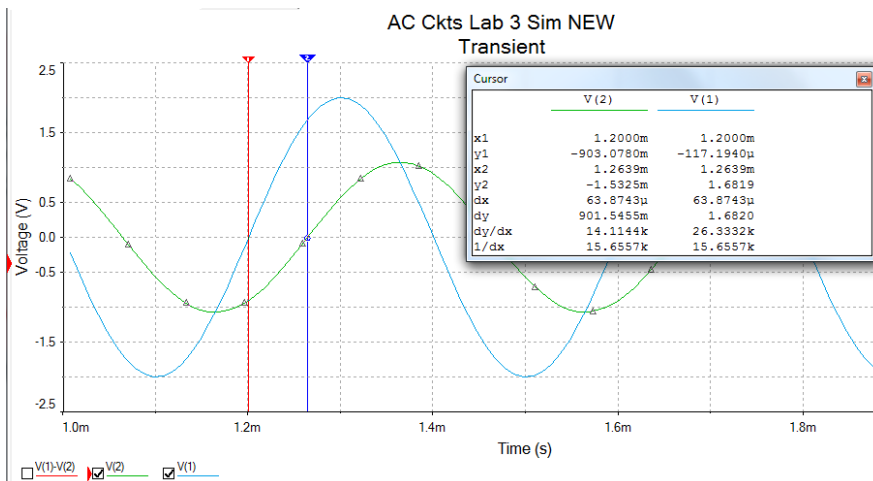1. Find the impedance of each component
2. Use Ohm's Law for phasors to determine $i_{in}(t)$, $V_L(t)$ and $V_{R1}(t)$
3. Verify your results by simulating the circuit in Multisim




$$I_{in} = V_{R1} / 1000 = 1.07V_{pk} / 1000 \text{ Ohms, lags } V_s \text{ by } 63.9\mu\text{Sec}$$

$$I_{in} = 1.07\text{mA}_{pk} < -57.5^\circ$$

$$i_{in}(t) = 1.07\text{E-}3 \sin(15,708t - 57.5^\circ) \text{ A}$$

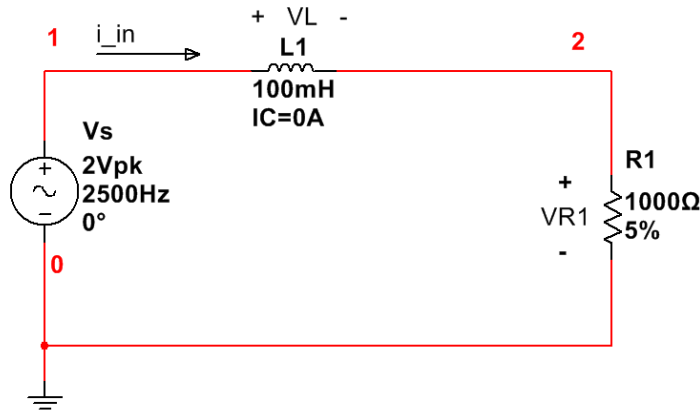Lab #3 Prelab (Partial – Simulating on Multisim)




1. Find the impedance of each component
2. Use Ohm's Law for phasors to determine $i_{in}(t)$, $V_L(t)$ and $V_{R1}(t)$
3. Verify your results by simulating the circuit in Multisim

What is V_L (magnitude and angle)?

V_L leads V_s by 35.99 μ Sec or 32.4 Deg

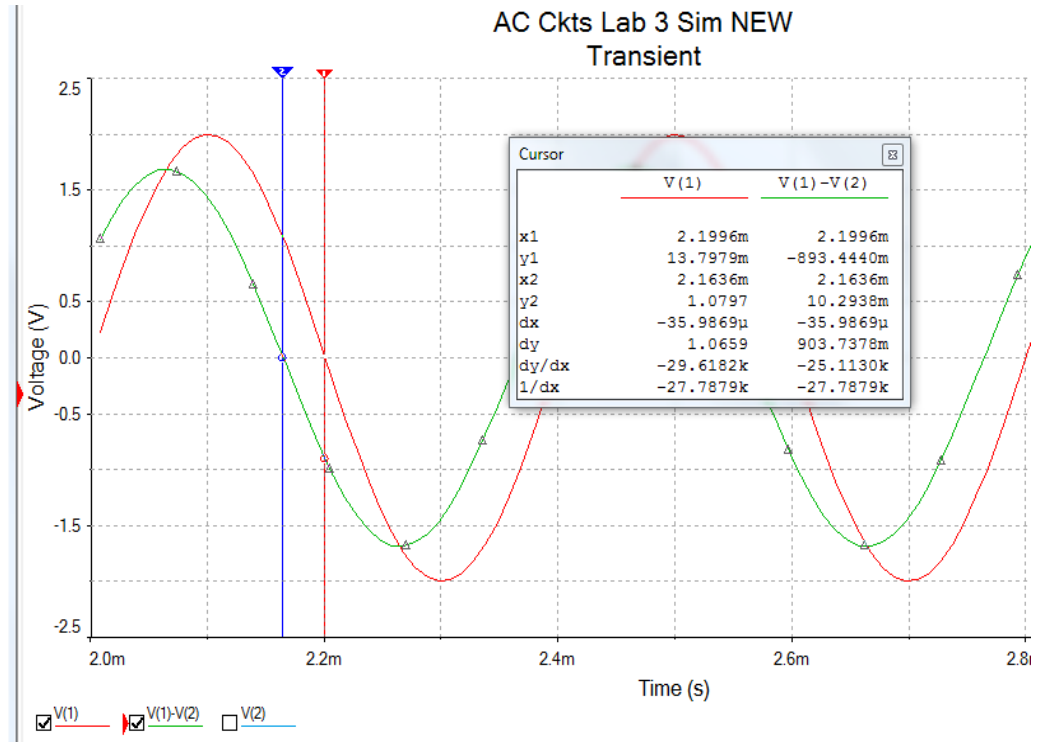Therefore, $V_L = 1.68V_{pk} < 32.4 \text{ Deg}$



Also from the simulation: $V_1 = 2V_{pk}$, $V_1 - V_2 =$
Hence $V_L = 1.68V_{pk}$

$V_L = 1.68V_{pk} < 32.4 \text{ Deg} \rightarrow 1.68 \sin(15,708t + 32.4 \text{ Deg}) V$