

# Norton's Theorem and Max Power Transfer

## □ Norton's Theorem


- Introduction and general approach
- Source conversion approach
- Example
  - Only independent sources
  - Use your calculator
- Example 2
  - Includes a dependent source controlled in-network
  - Requires a different method to determine  $Z_N$  (test source)

## □ Maximum Power Transfer Theorem

- Statement and discussion
- **In class problem**

## Norton's Theorem

- Norton's theorem allows us to replace any two-terminal linear bilateral ac network with an equivalent circuit consisting of a current source and an impedance.
- The Norton equivalent circuit, like the Thévenin equivalent circuit, is applicable at only one frequency since the reactances are frequency dependent.

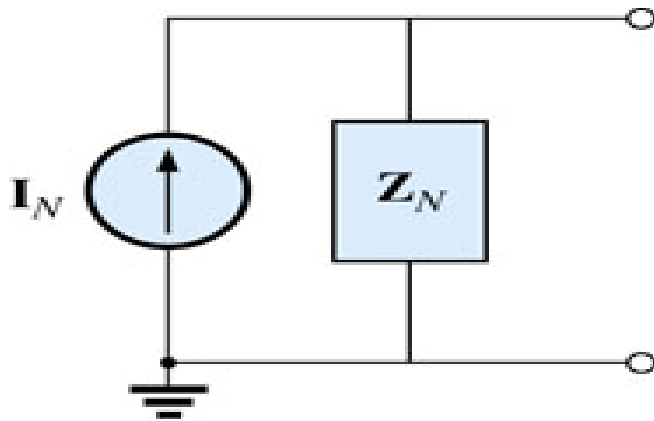


**FIG. 19.60** The Norton equivalent circuit for ac networks.

## Norton's Theorem - Approach

- 1. Remove that portion of the network across which the Norton equivalent circuit is to be found.*
- 2. Mark ( A and B or a-a' ) the terminals of the remaining two-terminal network.*
- 3. Calculate  $Z_N$  by first setting all voltage and current sources to zero (short circuit and open circuit, respectively) and then finding the resulting impedance between the two marked terminals.*
- 4. Calculate  $I_N$  by first replacing the voltage and current sources and then finding the short-circuit current between the marked terminals.*
- 5. Draw the Norton equivalent circuit with the portion of the circuit previously removed replaced between the terminals of the Norton equivalent circuit.*


**For dependent sources** – Must use an alternate method to find  $Z_N$  if the controlling variable is  $I_N$  in the network under investigation.

## Norton's Theorem – Source Conversion

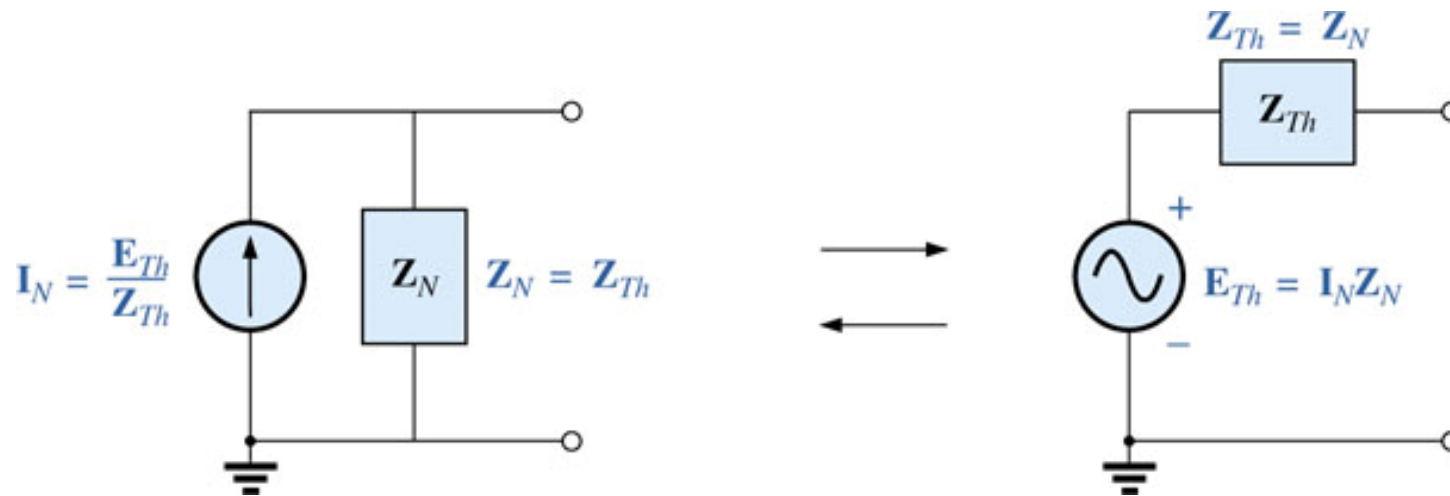


**FIG. 19.61** Conversion between the Thévenin and Norton equivalent circuits.
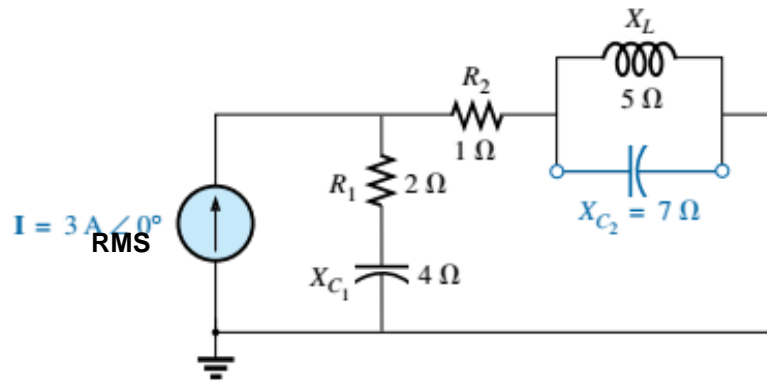
## Norton's Theorem – Example (use your calculator)




**Find:** the Norton equivalent circuit external to capacitor,  $C_2$

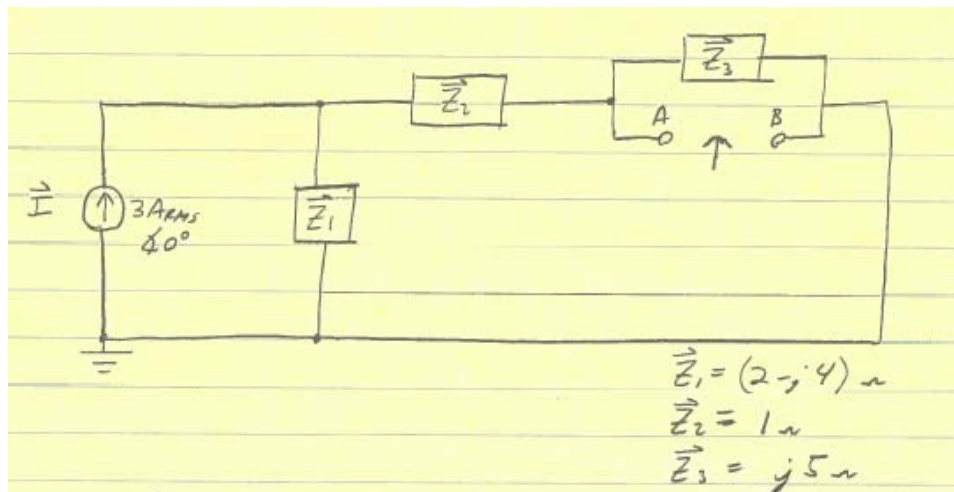**Steps 1&2:** Redraw, removing  $C_2$  (external to the network terminals), keep track of A-B



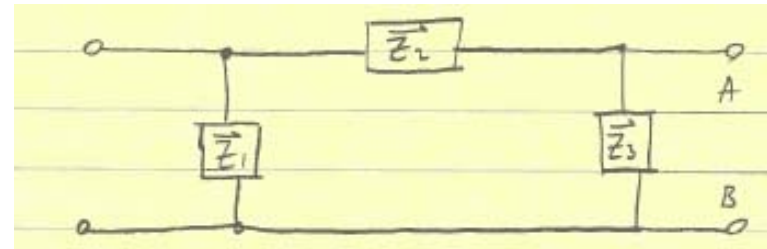**Step 3: Find  $Z_N$**   
(Remove independent sources,  
 $Z_N = Z_{TH} = Z_{ab} \text{ o/c}$ )




$$\vec{Z}_N = (\vec{Z}_1 + \vec{Z}_2) \parallel \vec{Z}_3$$

$$= (3 - j4) \Omega \parallel (j5 \Omega)$$

$$\boxed{\vec{Z}_N = (7.5 + j2.5) \Omega}$$

## Norton's Theorem – Example (use your calculator)

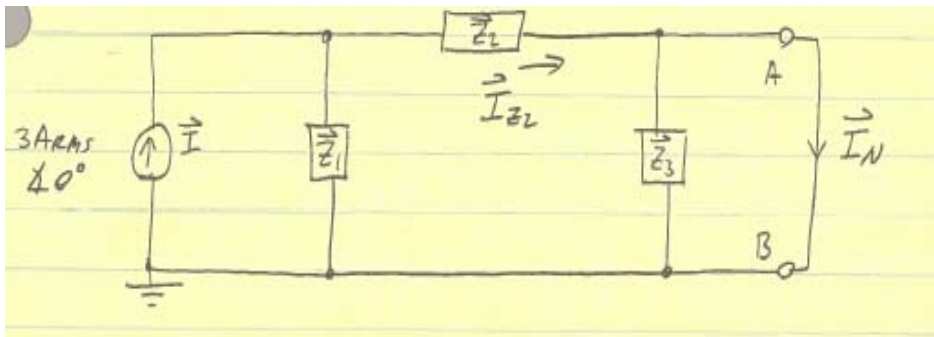**Step 4: Find  $I_N$  (I<sub>AB</sub> s/c)**





$$\vec{I}_N = \vec{I}_{Z_2} = \vec{I} \left( \frac{\vec{Z}_1}{\vec{Z}_1 + \vec{Z}_2} \right)$$


$$= 3A_{rms} \angle 40^\circ \frac{(2-j4)\Omega}{(3-j4)\Omega}$$

$$\boxed{\vec{I}_N = 2.68A_{rms} \angle -10.31^\circ}$$

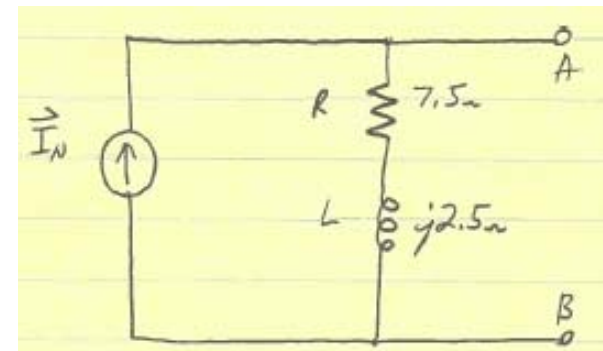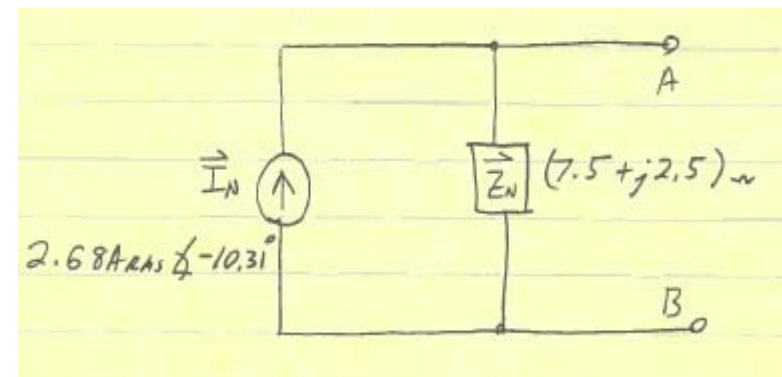**Step 5: Draw the Norton Equivalent Circuit**


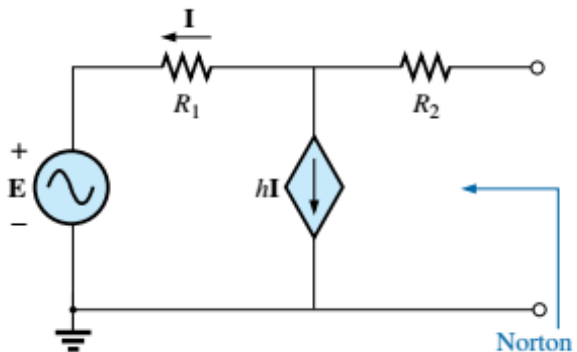
## Norton's Theorem – Example 2 (dependent source controlled within network)



Step 4: Find  $I_N$


$$\text{KVL (outer): } \vec{E} + \vec{I}Z_1 - \vec{I}_N Z_2 = 0 \quad (1)$$

$$\text{KCL } 0 = \vec{I} + h\vec{I} + \vec{I}_N \quad (2)$$

**Note:** The network contains a dependent source that is controlled by a current in the network

- Find  $I_N$  as usual
- Find  $Z_N$  using an alternate method (test source)

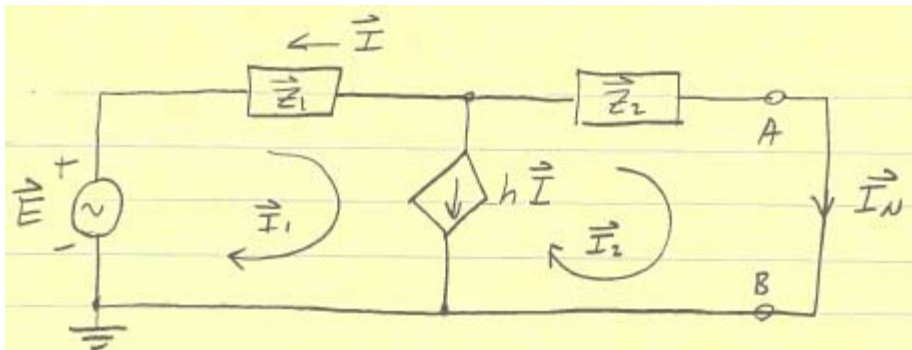**Steps 1&2:** Redraw using impedance boxes (keep track of terminals A-B)



Solving (1) for  $I$ :

$$\vec{I}Z_1 = \vec{I}_N Z_2 - \vec{E}$$

$$\therefore \vec{I} = \frac{\vec{I}_N Z_2 - \vec{E}}{Z_1}$$

Into (2) yields:

$$\vec{I}_N = -\vec{I}(1+h)$$

$$\vec{I}_N = -\left(\frac{\vec{I}_N Z_2 - \vec{E}}{Z_1}\right)(1+h)$$

## Norton's Theorem – Example 2 (dependent source controlled within network)

$$\vec{I}_N = - \left( \frac{\vec{I}_N \vec{Z}_2 - \vec{E}}{\vec{Z}_1} \right) (1+h)$$

Expanding to solve for  $\mathbf{I_N}$  in terms of the network values:

$$\begin{aligned} \vec{I}_N \vec{Z}_1 &= - (1+h) (\vec{I}_N \vec{Z}_2 - \vec{E}) \\ &= -\vec{I}_N \vec{Z}_2 + \vec{E} - h \vec{I}_N \vec{Z}_2 + \vec{E}h \end{aligned}$$



$$\vec{I}_N \vec{Z}_1 + \vec{I}_N \vec{Z}_2 + h \vec{I}_N \vec{Z}_2 = \vec{E}(1+h)$$

$$\vec{I}_N = \vec{E} \frac{(1+h)}{\vec{Z}_1 + \vec{Z}_2 + h \vec{Z}_2}$$

$$\vec{I}_N = \vec{E} \frac{(1+h)}{\vec{Z}_1 + \vec{Z}_2(1+h)}$$

**Step 3:** Find  $\mathbf{Z_N}$  by

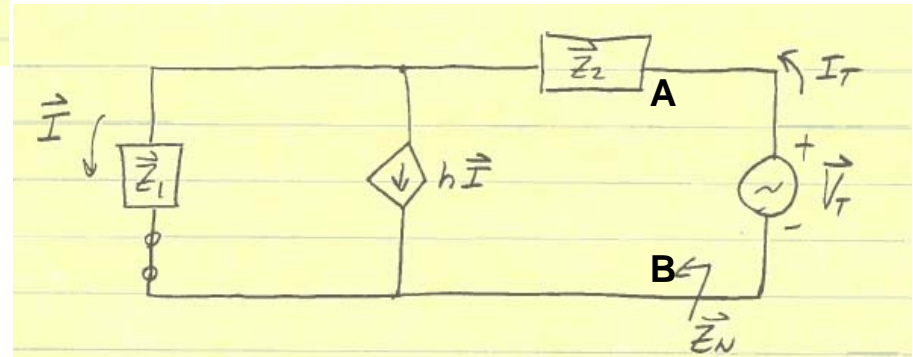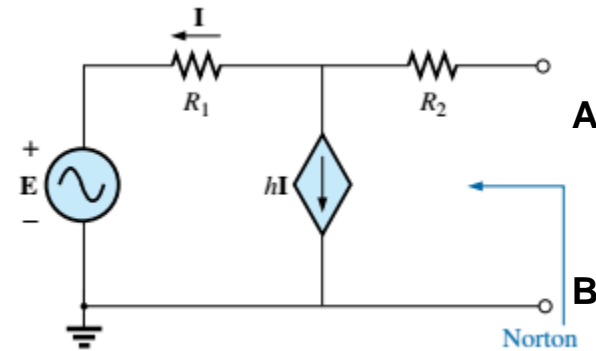
- Relaxing the independent sources ( $\mathbf{E}$ )
- Applying a test-source across A-B



$$\vec{Z}_N = \frac{\vec{V}_T}{\vec{I}_T}$$


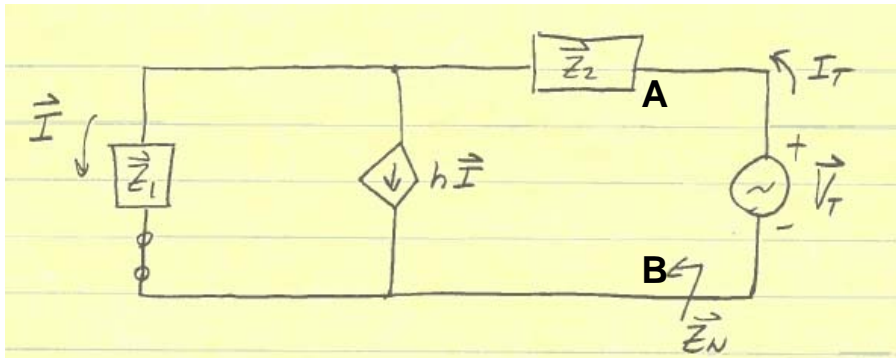
## Norton's Theorem – Example 2 (dependent source controlled within network)



KVL:

$$\vec{V}_T = \vec{I}_T \vec{Z}_2 + \vec{I} \vec{Z}_1 \quad (3)$$

KCL:

$$\vec{I}_T = \vec{I} + h \vec{I} \quad (4)$$

Solving (4) for  $\vec{I}$  and substituting into (3):

$$\vec{I} = \frac{\vec{I}_T}{1+h}$$


$$\vec{V}_T = \vec{I}_T \vec{Z}_2 + \vec{I}_T \left( \frac{1}{1+h} \right) \vec{Z}_1$$

Solving for  $\vec{V}_T/\vec{I}_T$  ( $\vec{Z}_N$ ):

$$\frac{\vec{V}_T}{\vec{I}_T} = \vec{Z}_N = \vec{Z}_2 + \vec{Z}_1 \left( \frac{1}{1+h} \right)$$

$$\boxed{\vec{Z}_N = \frac{\vec{Z}_2(1+h) + \vec{Z}_1}{1+h}}$$

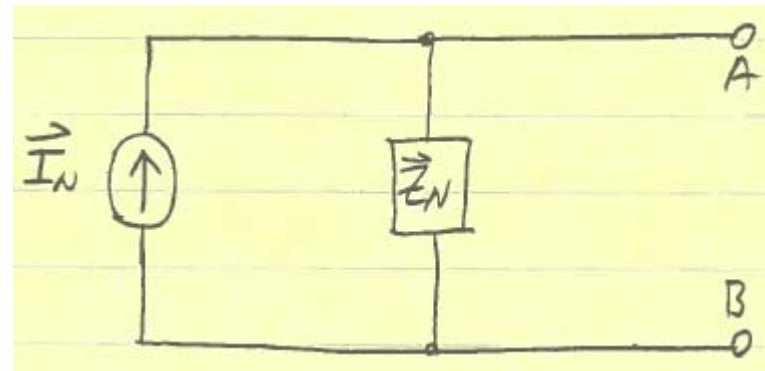
**Step 5:** Draw the Norton Equivalent Circuit



$$\boxed{\vec{I}_N = \vec{I} \frac{(1+h)}{\vec{Z}_1 + \vec{Z}_2(1+h)}}$$

## Maximum Power Transfer Theorem


- When applied to ac circuits, the maximum power transfer theorem states that maximum power will be delivered to a load when the load impedance is the conjugate of the Thévenin impedance across its terminals.

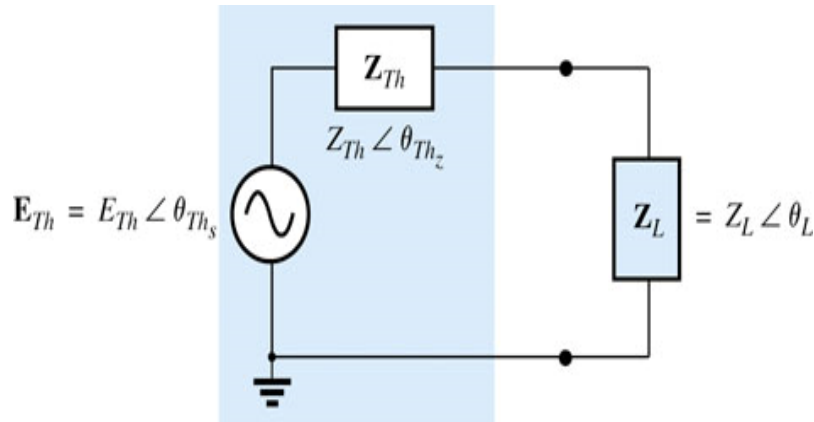

**FIG. 19.81** Defining the conditions for maximum power transfer to a load.


### NOTE:

When  $Z_L = Z_{Th}^*$ , the reactive components cancel and we have a series circuit with two equal value resistors... look familiar?

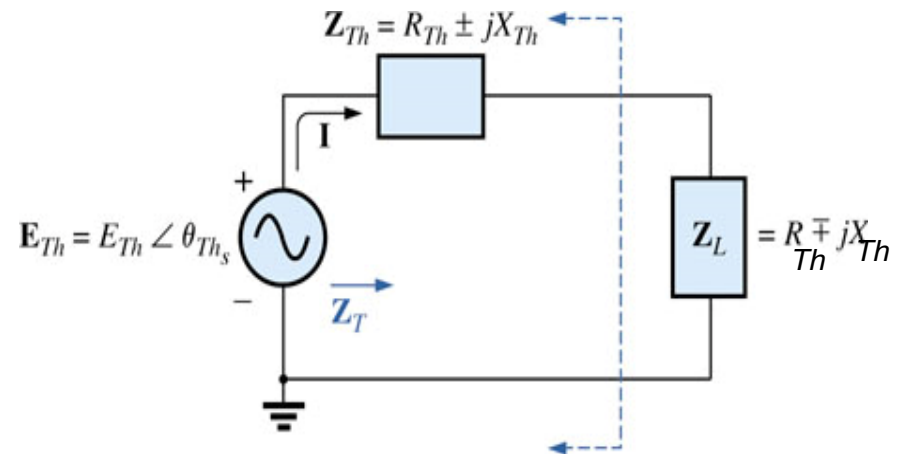

**FIG. 19.82** Conditions for maximum power transfer to  $Z_L$ .

## In Class Problem

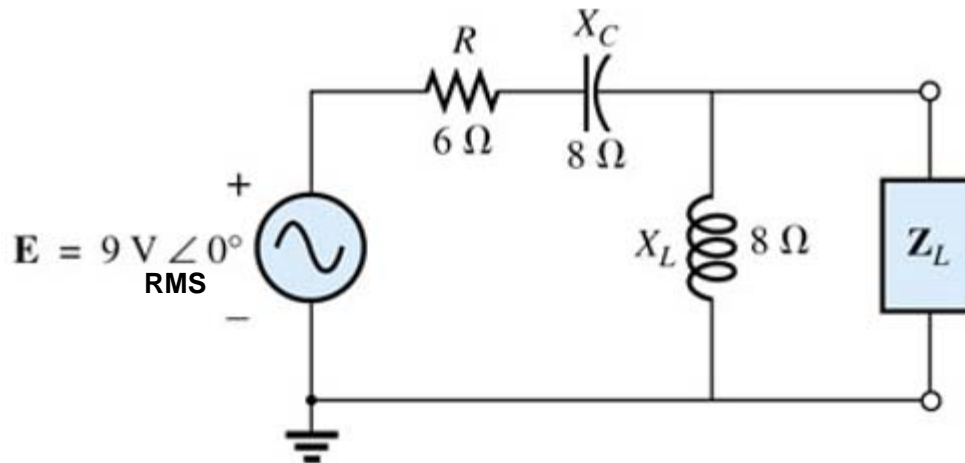

### Find:

- The Thevenin equivalent circuit for the network external to  $Z_L$
- The value of  $Z_L$  for maximum power transfer
- The average power dissipated by this load

### Approach:

- Standard Thevenin approach
- Set  $Z_L = Z_{TH}^*$
- $P_{ZL} = V_{RMS} I_{RMS} \cos(\Theta)$