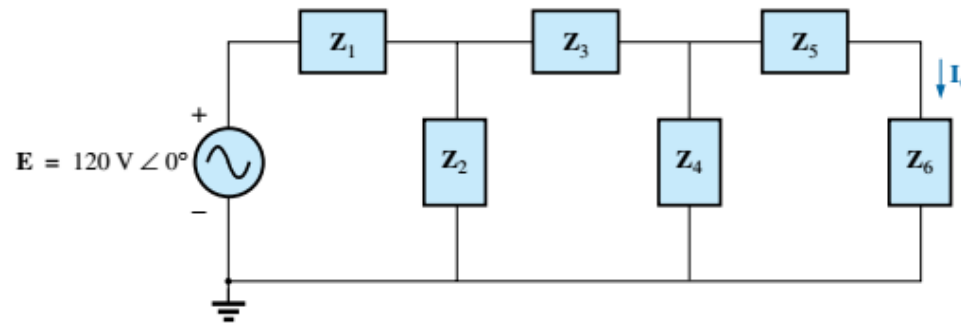


Ladder Networks and Grounding

- **Ladder Networks**
 - Approach from Wednesday
 - Current divider reminder
 - **In class problem**
- **Grounding**
 - Intro
 - Lab equipment example
 - AC line example


Ladder Networks – One Approach (same as in DC Circuits)




A specific series-parallel configuration

Analyze by:

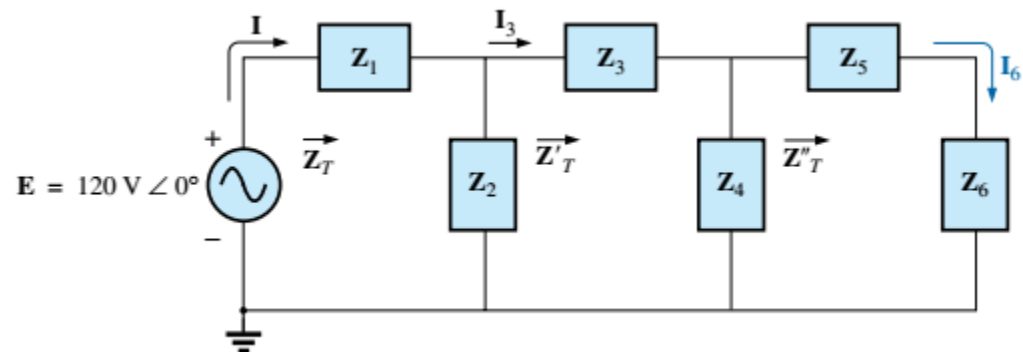- Collapse the circuit from the far end
- Find the source current
- Expand the circuit again, finding voltages or currents along the way
 - Successive application of voltage or current divider



Ladder Networks – One Approach

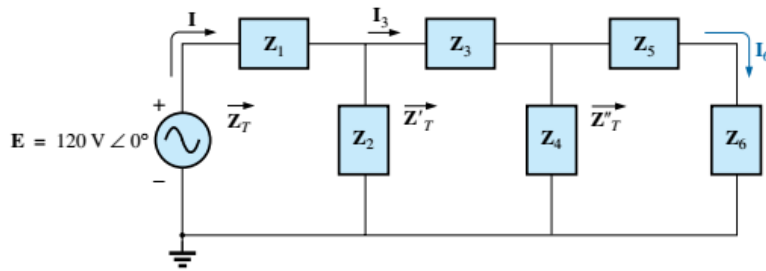

Finding Z_T

$$Z''_T = Z_5 + Z_6$$

and

$$Z'_T = Z_3 + Z_4 \parallel Z''_T$$

with

$$Z_T = Z_1 + Z_2 \parallel Z'_T$$

Finding I


$$I = \frac{E}{Z_T}$$

Current Divider (special case of 2 impedances)

$$I_3 = \frac{Z_2 I}{Z_2 + Z'_T}$$

$$I_6 = \frac{Z_4 I_3}{Z_4 + Z''_T}$$

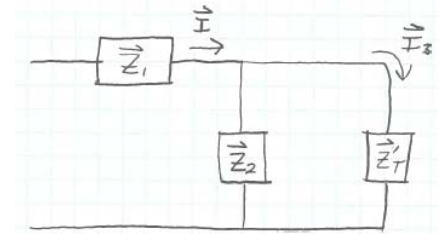Development of I_3 (special case equation)



GENERAL FORM:

$$I_x = I_T \left(\frac{Z_T}{Z_x} \right)$$

HERE:

$$I_3 = I \left(\frac{Z'_T \parallel Z_2}{Z'_T} \right)$$

$$\text{BUT } Z'_T \parallel Z_2 = \frac{Z'_T \cdot Z_2}{Z'_T + Z_2}$$

$$\therefore I_3 = I \left(\frac{Z'_T \cdot Z_2}{Z'_T + Z_2} \right) \left(\frac{1}{Z'_T} \right)$$

$$I_3 = I \frac{Z_2}{Z'_T + Z_2}$$

Ladder Networks – ICP (partial HW problem)


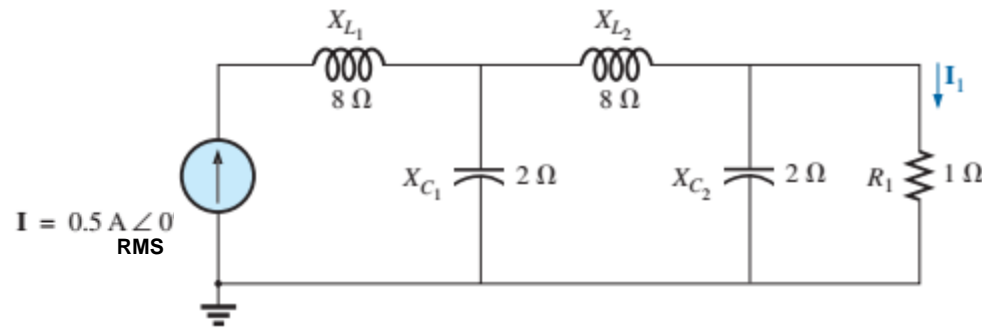


FIG. 17.54


Find: The voltage across L_2 , the current through C_2 (not I_1) and the average power delivered to the circuit by the source

Remember: Develop a strategy 1st and at least one check-point **BEFORE** starting the problem.

Grounding – In The Lab

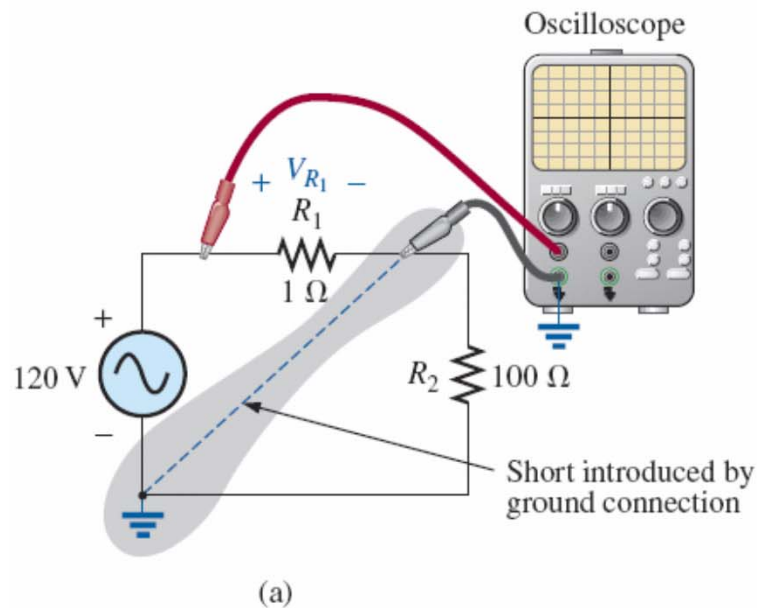


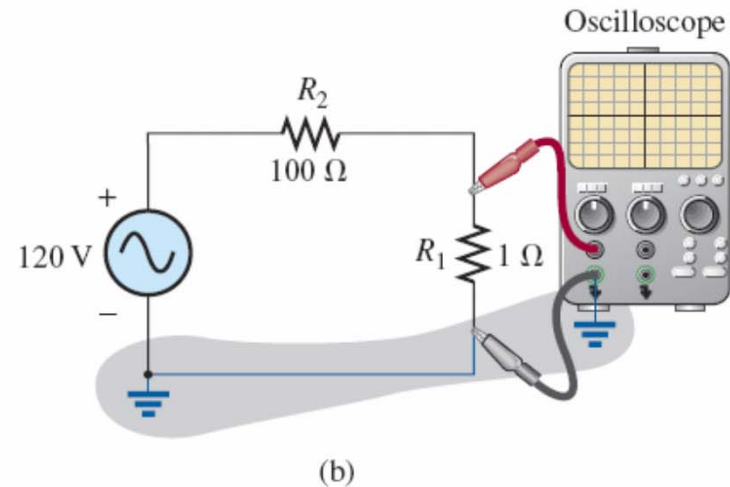What will the O'Scope read?
Is it the correct value?



effect of **What will the O'Scope read?**
across **Is it the correct value?**

Grounding – In The Lab

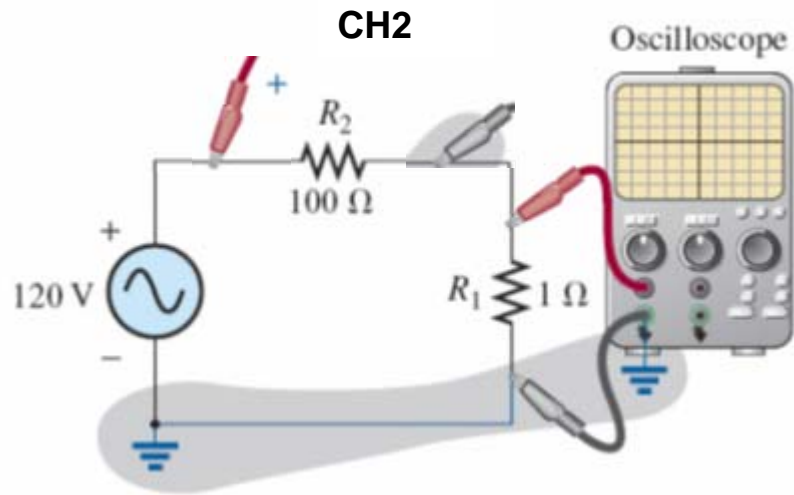

What will the O'Scope read?

CH1 and CH2?

**Are these the correct
measurements?**

Grounding – Electrical Outlets


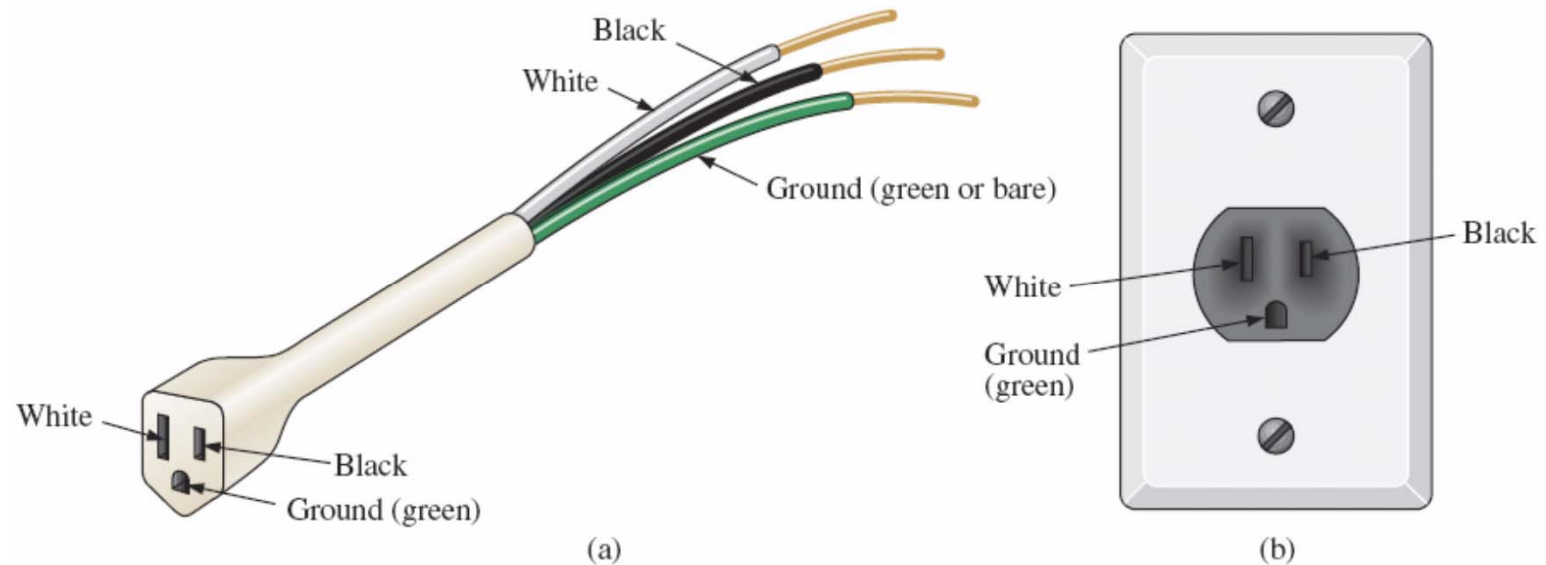


FIG. 17.24 Three-wire conductors: (a) extension cord; (b) home outlet.

Grounding – Electrical Outlets

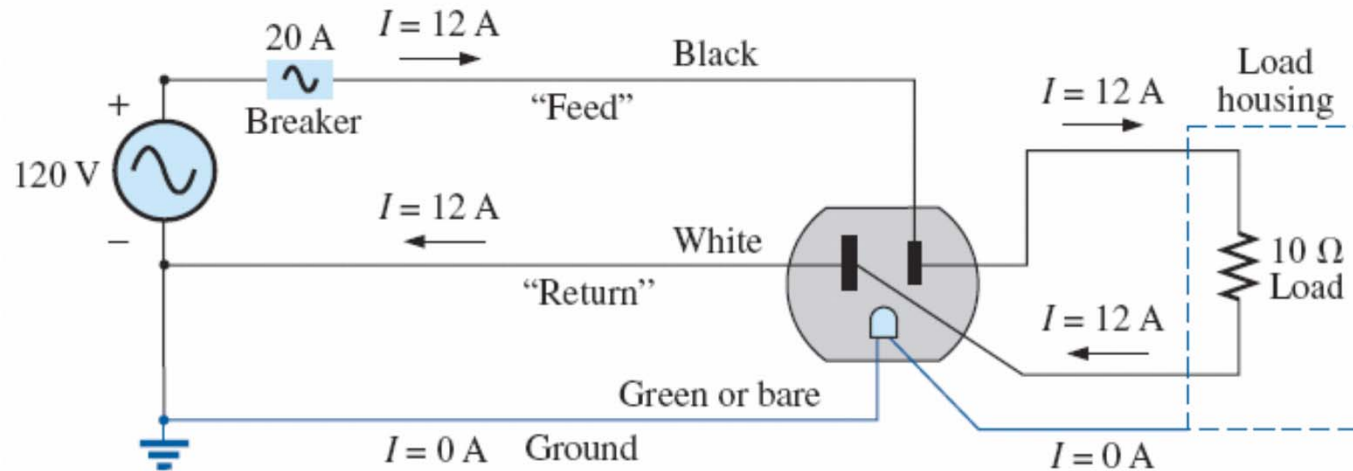

Note:

- No current is meant to flow through the green wire (earth ground)
- Return and ground are connected together

Grounding - Appliances

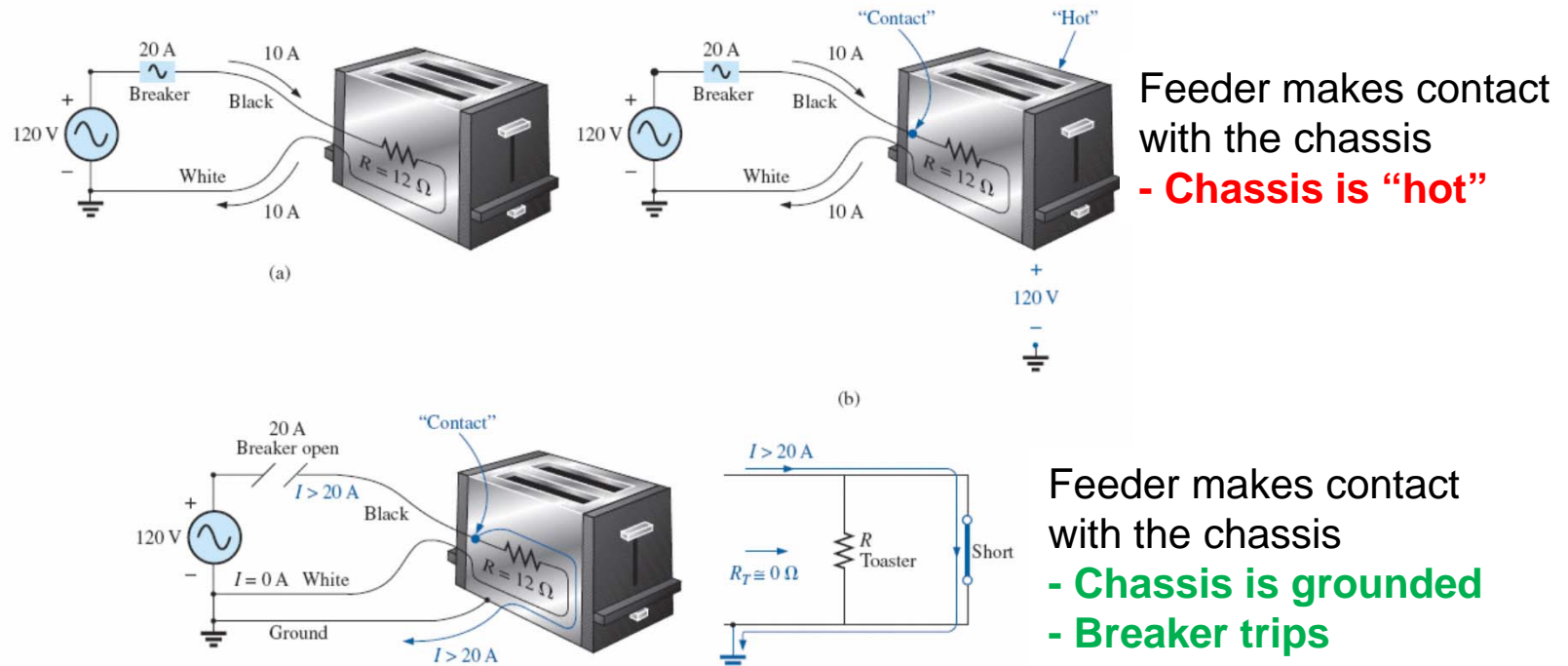


FIG. 17.26 Demonstrating the importance of a properly grounded appliance: (a) ungrounded; (b) ungrounded and undesirable contact; (c) grounded appliance with undesirable contact.