
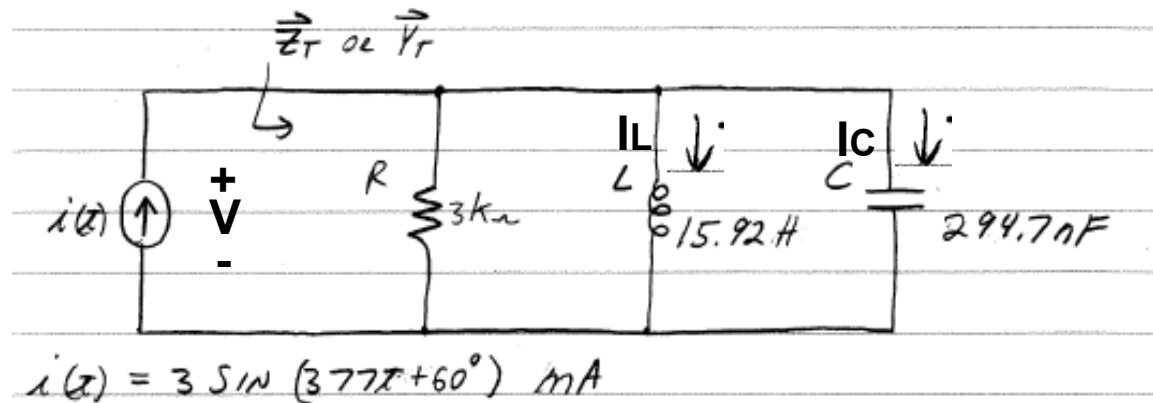


## ICP – Parallel AC Circuit Analysis

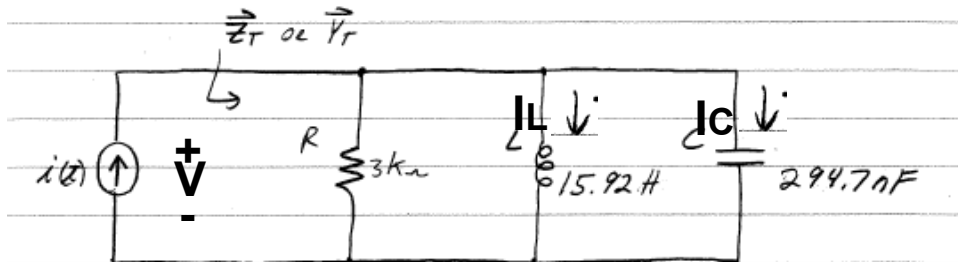


- 1 – Find the voltage  $V$  across the elements (use RMS)
- 2 – Find  $v(t)$ , the voltage across the elements
- 3 - Find  $I_L$  and  $I_C$  (use RMS)
- 4 - Find  $i_L(t)$  and  $i_C(t)$
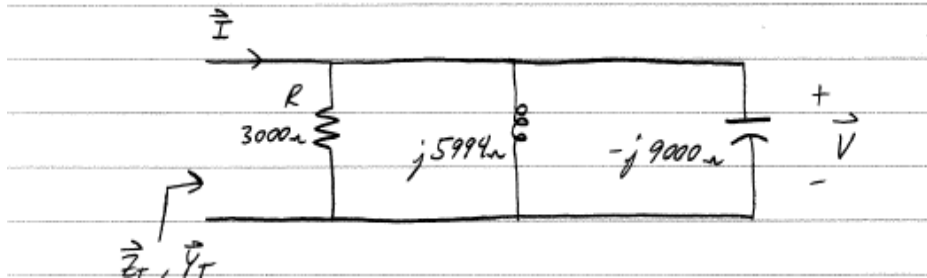
## ICP – Parallel AC Circuit Analysis



$$i(t) = 3 \sin(377t + 60^\circ) \text{ mA}$$





1 – Find the voltage  $V$  across the elements (use RMS)

$$\vec{V} = \vec{I} \vec{Z}_T = \frac{\vec{I}}{\vec{Y}_T} = \frac{3 \frac{1}{\sqrt{2}} \angle 60^\circ \text{ mA}}{337.9 \mu\text{S} \angle -9.49^\circ \text{ S}} \text{ RMS}$$

$$\boxed{\vec{V} = 6.28 \text{ V} \angle 69.49^\circ \text{ RMS}}$$

## ICP – Parallel AC Circuit Analysis

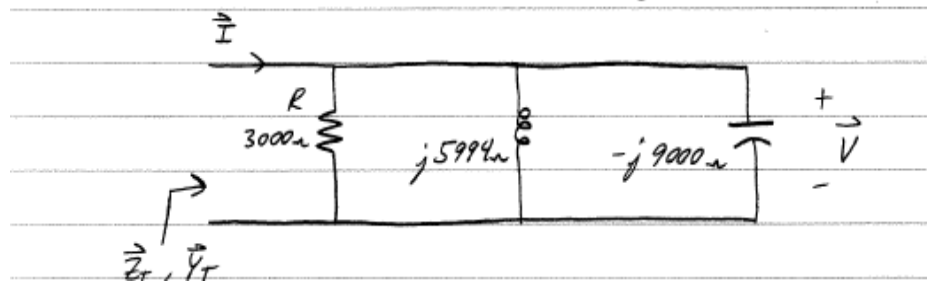
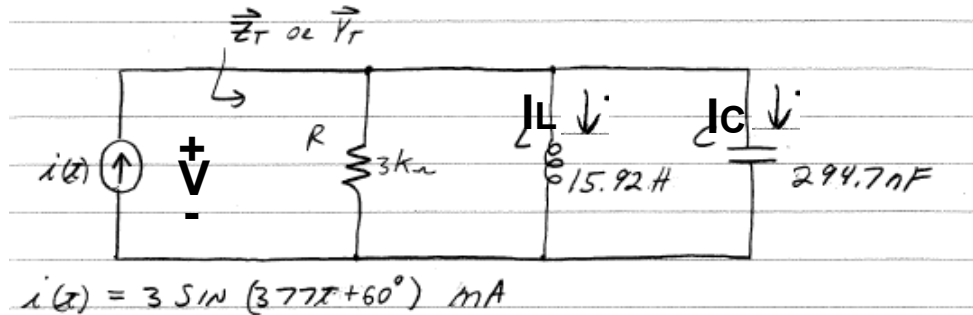


2 – Find  $v(t)$ , the voltage across the elements

$$\vec{V} = 6.28 \text{ V}_{\text{RMS}} \angle 69.49^\circ$$

$$v(t) = (6.28)\sqrt{2} \sin(377t + 69.5^\circ) \text{ V}$$

## ICP – Parallel AC Circuit Analysis

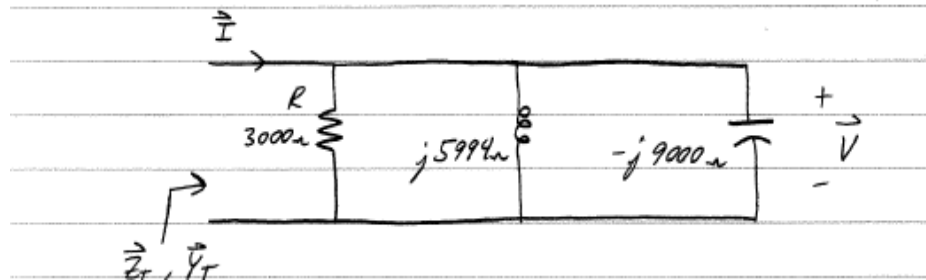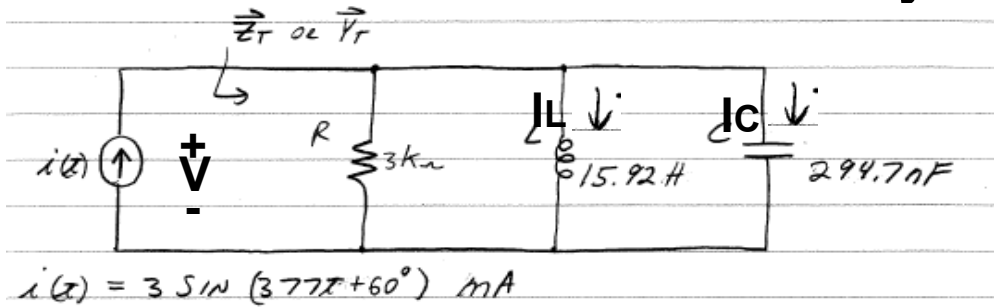

3 - Find  $I_L$  and  $I_C$  (use RMS)

Current Divider -  $I_L$

$$\vec{I}_L = \vec{I} \cdot \frac{\vec{Z}_r}{\vec{Z}_x \leftarrow \vec{Z}_L}$$

$$\vec{I}_L = 2.12 \text{ mA}_{\text{RMS}} \angle 60^\circ \cdot \frac{2959\Omega \angle 9.49^\circ}{5994\Omega \angle 90^\circ}$$

$$\boxed{\vec{I}_L = 1.047 \text{ mA}_{\text{RMS}} \angle -20.51^\circ}$$


Current Divider -  $I_C$

$$\vec{I}_C = \vec{I} \cdot \frac{\vec{Z}_r}{\vec{Z}_C}$$

$$= 2.12 \text{ mA}_{\text{RMS}} \angle 60^\circ \cdot \frac{2959\Omega \angle 9.49^\circ}{-j9000\Omega}$$

$$\therefore \boxed{\vec{I}_C = 697 \mu\text{A}_{\text{RMS}} \angle 159.5^\circ}$$

## ICP – Parallel AC Circuit Analysis

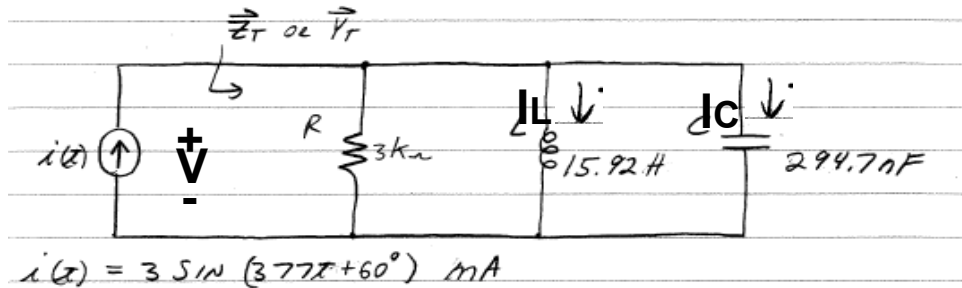

4 - Find  $i_L(t)$  and  $i_C(t)$

$$\vec{I}_L = 1.047 \text{ mA}_{\text{RMS}} \angle -20.51^\circ$$

$$\therefore i_L(t) = 1.48 \times 10^{-3} \sin(377t - 20.51^\circ) \text{ A}$$

check:  $v(t) = 8.88 \sin(377t + 69.5^\circ) \text{ V}$   $\nearrow$  ELI  
 $90^\circ$  PHASE SHIFT

$$\therefore \vec{I}_C = 697 \mu\text{A}_{\text{RMS}} \angle 159.5^\circ$$

$$i_C(t) = 985.7 \times 10^{-6} \sin(377t + 159.5^\circ) \text{ A}$$

check: ICE SATISFIED?  
YES