

Transformers – Impedance Matching and Simulation

☐ Impedance Transformation


- Analysis
- Example
- P_{max}

☐ Transformer Simulation

- Turns ratio and model
- Interpretation and Analysis

Transformers – Impedance Transformation

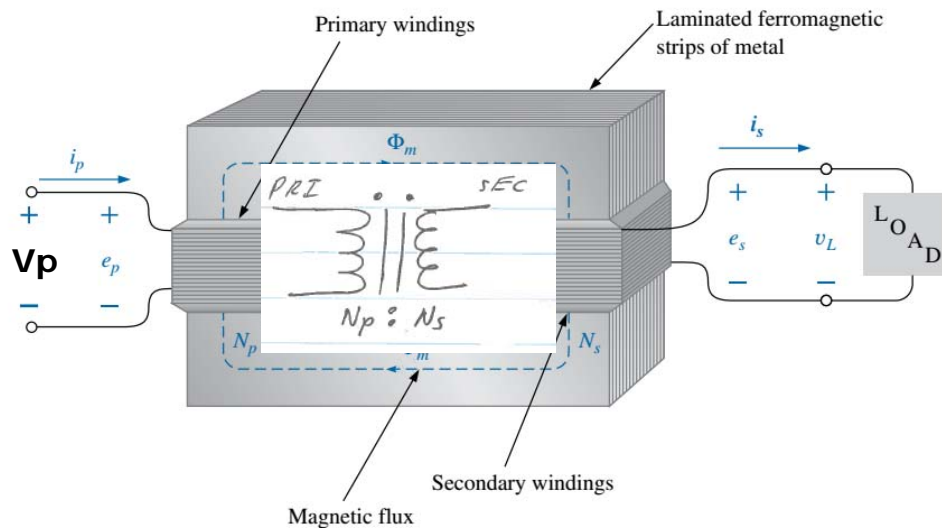Consider the following transformer
(ideal model, $k=1$):



Recall:

$$\frac{\vec{V}_p}{\vec{V}_s} = \frac{N_p}{N_s} = a \quad (1)$$

$$\frac{\vec{I}_s}{\vec{I}_p} = \frac{N_p}{N_s} = a \quad (2)$$

(1) MULTIPLIED BY (2)

$$\frac{\vec{V}_p}{\vec{V}_s} \cdot \frac{\vec{I}_s}{\vec{I}_p} = a^2$$


$$\vec{V}_p = a^2 \frac{\vec{V}_s}{\vec{I}_s}$$

OR $\boxed{\vec{Z}_p = a^2 \vec{Z}_L}$

REFLECTED
IMPEDANCE

Transformers – Impedance Transformation (example)

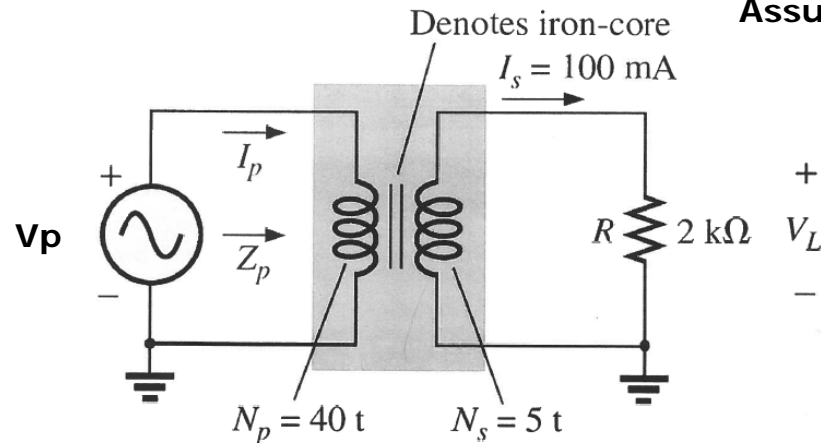Assume voltages and currents in RMS unless otherwise noted



Find: $|I_p|$, $|V_g|$, Z_p

$$a = \frac{40}{5} = 8$$

$$I_p = I_s / a = 100 \text{ mA} / 8 = 12.5 \text{ mA}$$


$$V_L = I_s \cdot R = (100 \text{ mA})(2 \text{ k}\Omega) = 200 \text{ V}$$

$$V_p = (8)(V_s) = (8)(200 \text{ V}) = 1600 \text{ V}$$

$$\vec{Z}_p = a^2 \vec{Z}_L$$

$$Z_p = 64(2 \text{ k}\Omega) = 128 \text{ k}\Omega$$

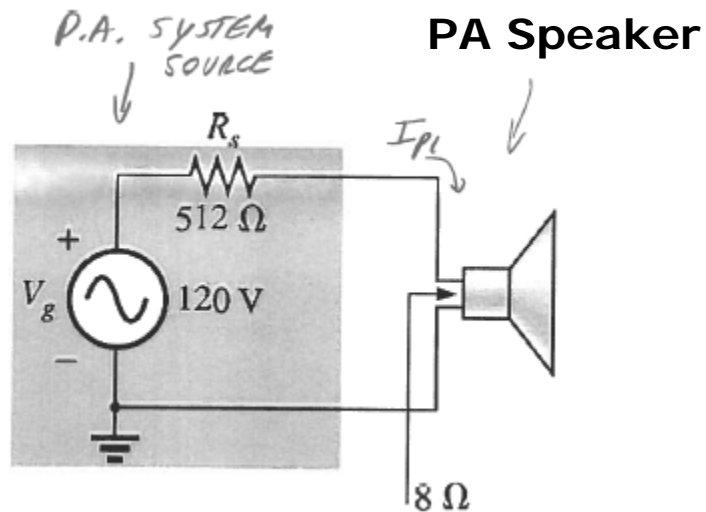Transformers – Impedance matching for Pmax (example)




$$P_{8\Omega} = (I_{pl})^2 (8\Omega)$$

$$I_{pl} = \frac{120V}{512\Omega} = 231mA$$

$$\therefore P_{8\Omega} = 426mW$$

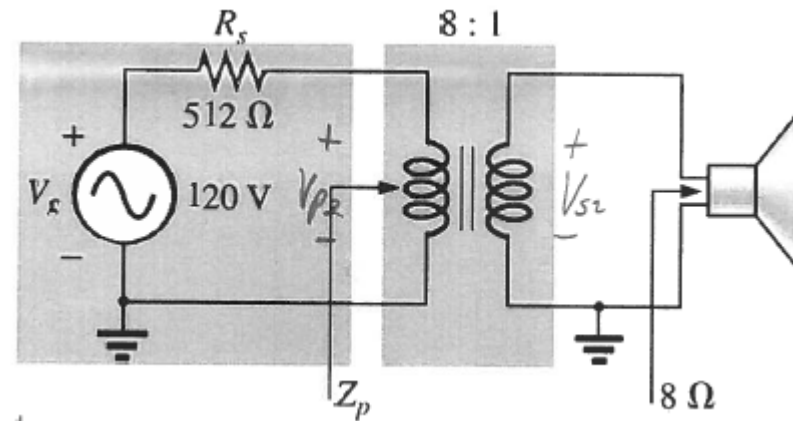Only 426mW into the speaker, 27.3W "lost" in R_s



$$Z_p = 8^2 (8\Omega) = 512\Omega$$

$$\therefore V_{p2} = 120V \left(\frac{512\Omega}{1024\Omega} \right) = 60V$$


$$\therefore P_{1N} = (60V)^2 / 512\Omega = 7.03W$$

$$\text{CHECK: } V_{s2} = 60V / 8 = 7.5V$$

$$\therefore P_{8\Omega} = \frac{(7.5V)^2}{8\Omega} = 7.03W$$

½ of the 14.06W available to the speaker ☺


Transformers - Simulation

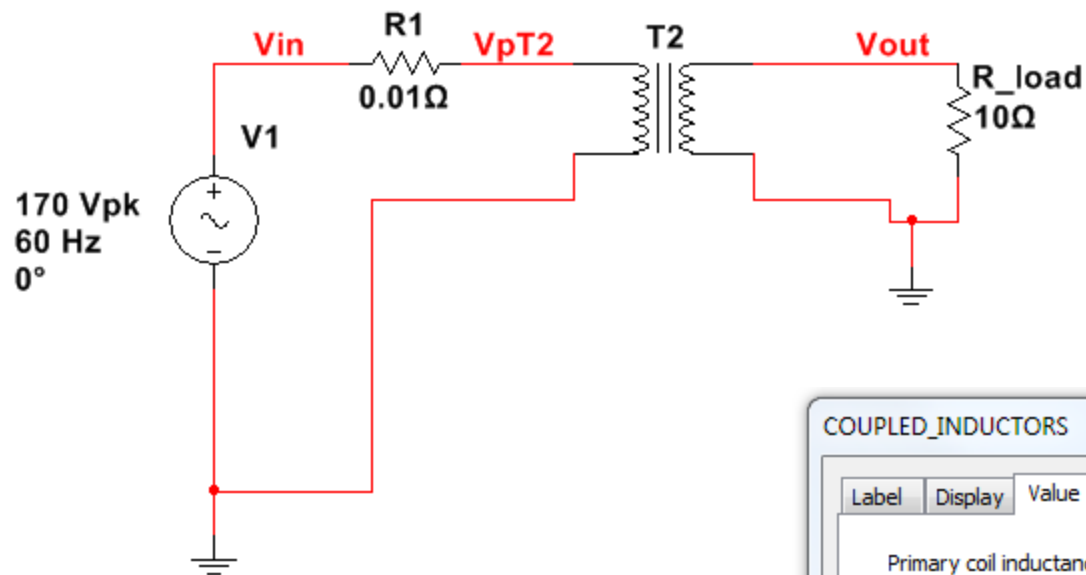

What is the turns ratio?

COUPLED_INDUCTORS				
Label	Display	Value	Fault	Pins
Primary coil inductance		100		H
Secondary coil inductance		1		H
Coefficient of coupling		1		

Transformers – Simulation (turns ratio)

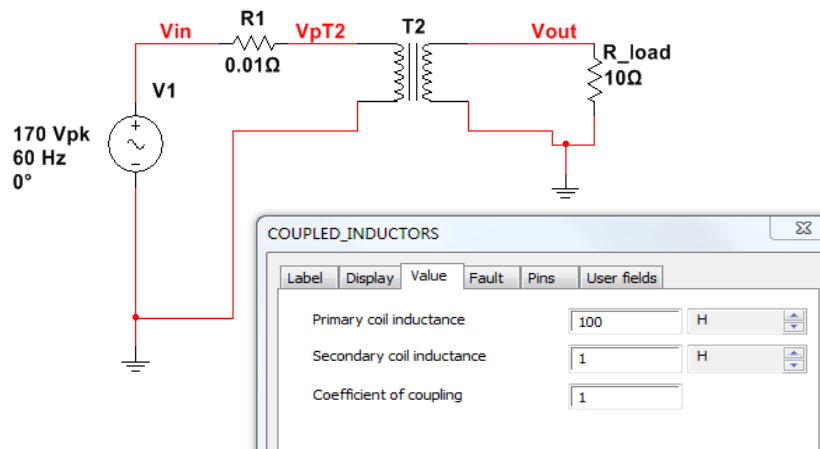

What is the turns ratio?

Recall:

$$L = N^2 \left(\frac{\mu A}{l} \right)$$

Therefore:


$$\frac{L_p}{L_s} = \frac{N_p^2 \left(\frac{\mu A}{l} \right)}{N_s^2 \left(\frac{\mu A}{l} \right)}$$

$$\text{or } \frac{L_p}{L_s} = \left(\frac{N_p}{N_s} \right)^2$$

Which yields:

$$\therefore \frac{N_p}{N_s} = \sqrt{\frac{L_p}{L_s}} = 10$$

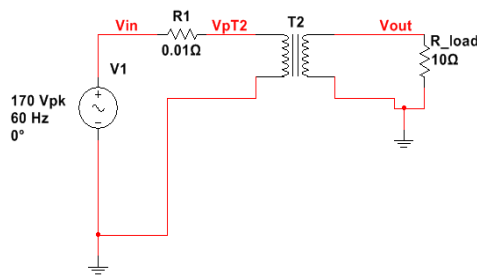Transformers – Turns Ratio (interpretation/analysis)



Notes: Voltages and currents all in-phase, R1
-> Sample resistor and for simulation

$$V_{in} = 170\text{Vpk} \sim 120\text{VRMS}$$

$$V_{out} = 17\text{Vpk} \sim 12\text{VRMS}$$

$$\text{So } N_p/N_s = V_{in}/V_{out} = 10$$

$$I_{in} = 174.6\text{pk}/1000 = 174.6\text{mApk} \sim 123\text{mARMS}$$

$$I_{out} = V_{out}/10 \text{ Ohms} = 1.2\text{ARMS}$$

$$P_{in} = V_{in} * I_{in} = 14.8\text{W}$$

$$P_{out} = V_{out} * I_{out} = 14.4\text{W}$$

$$Z_{in_exp} = a^2 * Z_L = 1000 \text{ Ohms}$$

$$Z_{in_sim} = V_{in}/I_{in} = 976 \text{ Ohms}$$

Minor errors due to winding inductance here (1H -> j377 Ohms at 60 Hz)

