

Basic Elements (Reactance and Freq Response)

■ The Derivative

- ☐ Intro and understanding (qualitative)
- ☐ Effects of frequency
- ☐ Calculus (the details)

■ Response of R,L,C to Sinusoids (as forcing functions)

- ☐ Resistor
- ☐ Inductor
- ☐ **Inductor ICPs**
- ☐ Capacitor
- ☐ **Capacitor ICPs**

■ R,L,C Over Frequency (Intro)

- ☐ Ideal vs “practical” models

Understanding the Derivative

Here: $x(t) = \sin(\omega t)$

$$\frac{dx}{dt} = 0$$

$dx/dt \rightarrow$ The rate of change of x wrt t
(wrt: with respect to)

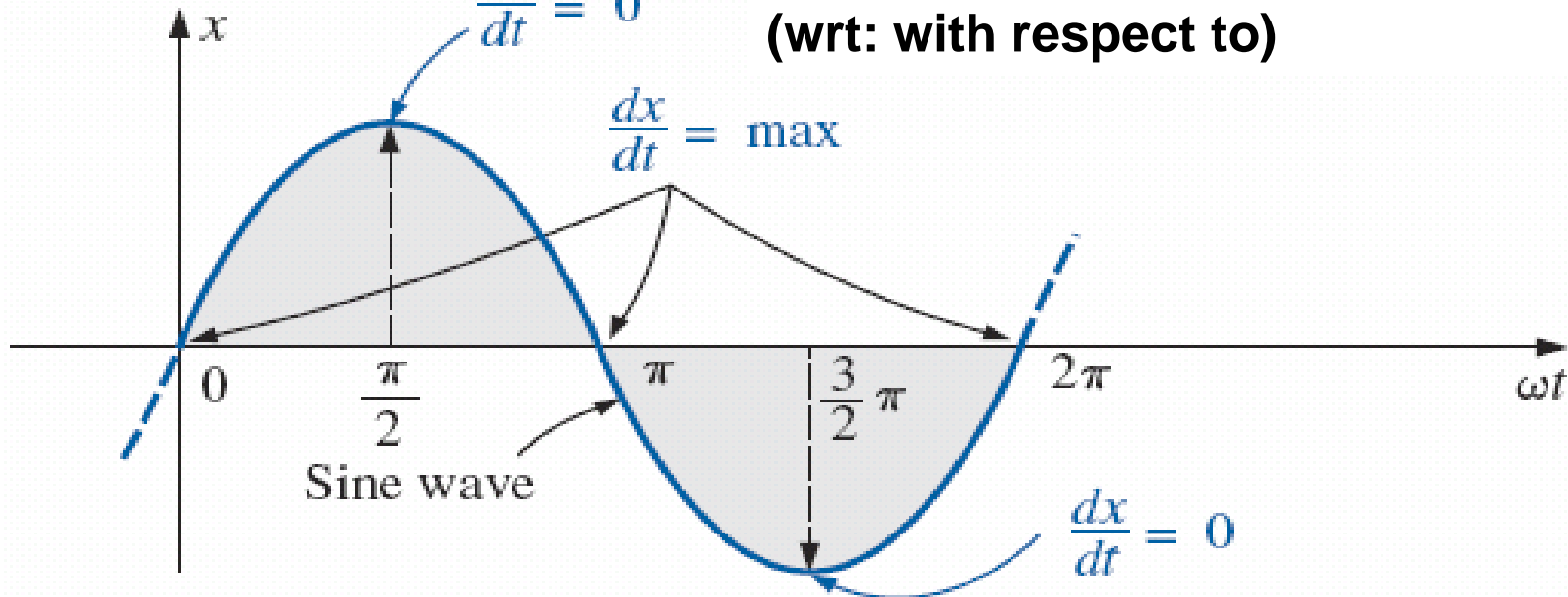


FIG. 14.1 *Defining those points in a sinusoidal waveform that have maximum and minimum derivatives.*

**Note max dx/dt at $\omega t = 0, \pi$ and 2π
And $dx/dt = 0$ at $\omega t = \pi/2$ and $3\pi/2$**

Understanding the Derivative

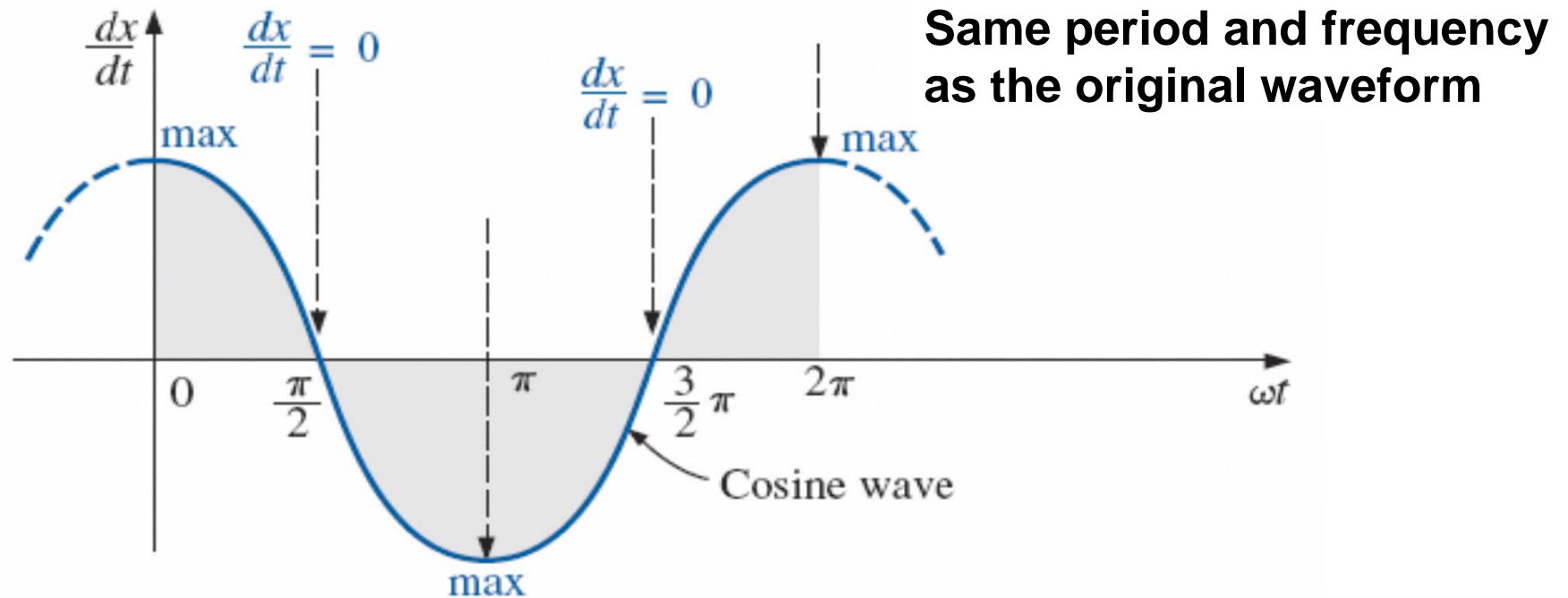


FIG. 14.2 *Derivative of the sine wave of Fig. 14.1.*

Notice that $x(t) = \cos(\omega t)$ and that
 $\frac{d}{dt}(\sin x) = \cos(x)$

Effect of Frequency on the Peak Value

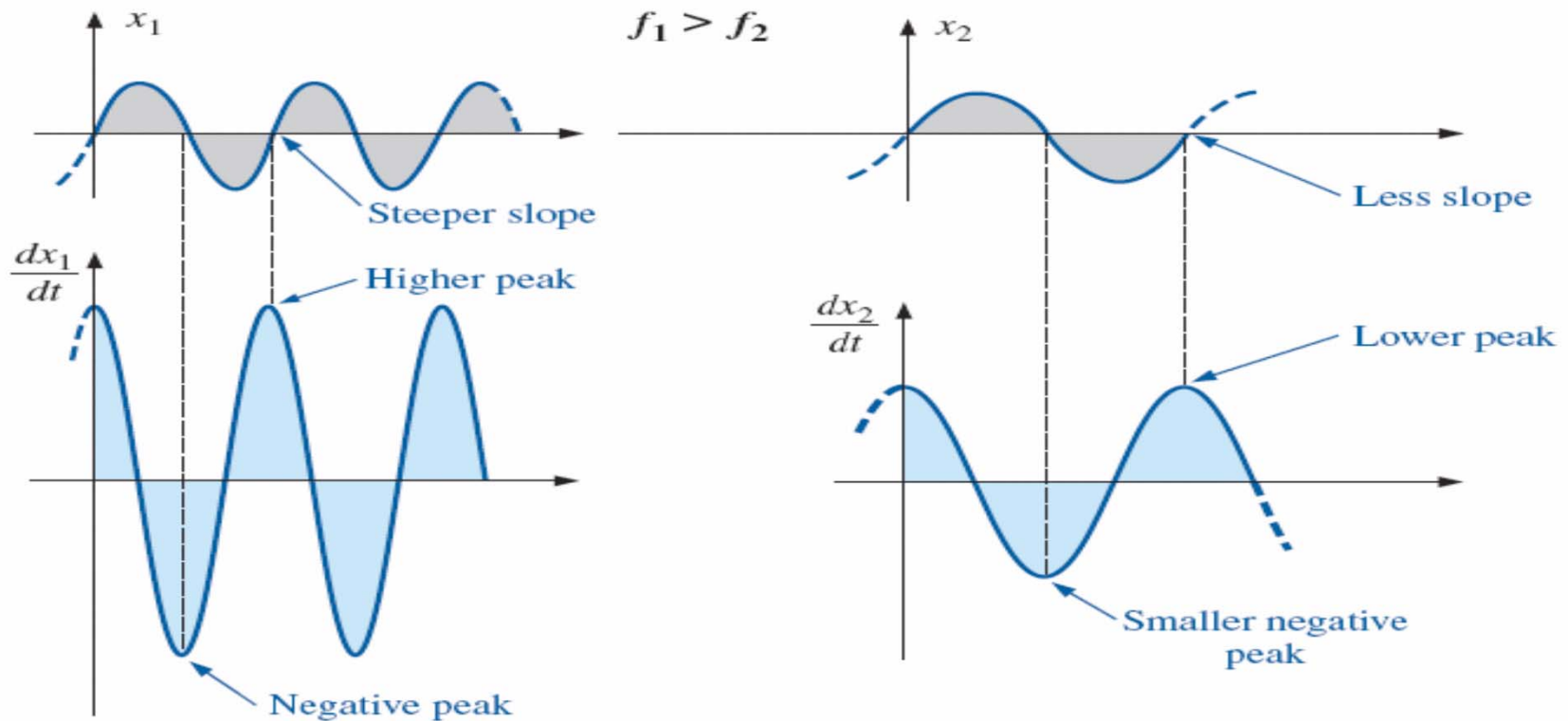


FIG. 14.3 *Effect of frequency on the peak value of the derivative.*

**Steeper slope = higher peak in the derivative or
Higher frequency = higher peak in the derivative**

Effect of Frequency on the Peak Value

CALCULUS

$$\rightarrow D_x \sin(u) = \cos(u) D_x u$$

$$\text{CONSIDER : } v(x) = E_m \sin(\omega x + \theta)$$

$$\frac{dv(x)}{dx} = E_m \cos(\omega x + \theta) \cdot \frac{d}{dx} (\omega x + \theta)$$

$$\boxed{v'(x) = E_m \omega \cos(\omega x + \theta)}$$

$$\rightarrow D_x \cos(u) = -\sin(u) D_x u$$

$$\text{CONSIDER : } v(x) = E_m \cos(\omega x + \theta)$$


$$\frac{dv(x)}{dx} = E_m (-\sin(\omega x + \theta)) \cdot \frac{d}{dx} (\omega x + \theta)$$

$$\boxed{v'(x) = -E_m \omega \sin(\omega x + \theta)}$$

RESPONSE OF R, L, C ELEMENTS TO A SINUSOIDAL VOLTAGE OR CURRENT

RESISTOR

RECALL: $\frac{E}{I/R}$

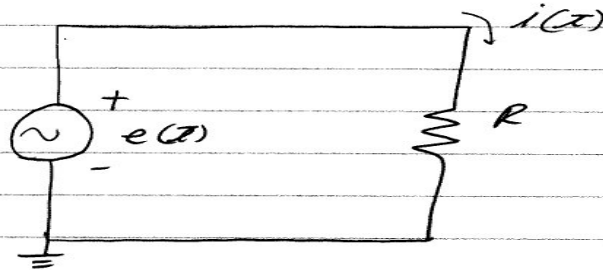


$$e(t) = V_m \sin(\omega t) \quad V$$

FIND $i(t)$:

$$i(t) = \frac{e(t)}{R} = \frac{V_m}{R} \sin(\omega t) \quad A$$

VOLTAGE &
CURRENT
IN-PHASE

INDUCTOR

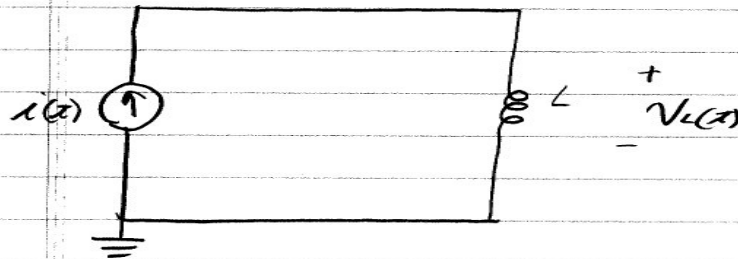

$$i(t) = I_m \sin(\omega t)$$

Response of the Inductor to a Sinusoidal Forcing Function

$$\begin{aligned} \text{RECALL: } V_L(t) &= L \frac{di}{dt} \\ \therefore V_L(t) &= L \frac{d}{dt} [I_m \sin(\omega t)] \\ V_L(t) &= \underbrace{I_m L \omega}_{V_m} \cos(\omega t) \end{aligned}$$

$$\begin{aligned} \text{RECALL: } \cos(\omega t) &= \sin(\omega t + 90^\circ) \\ \therefore V_L(t) &= \omega L I_m \sin(\omega t + 90^\circ) \end{aligned}$$

$$\begin{aligned} \text{COMPARE: } i_L(t) &= I_m \sin(\omega t) \\ V_L(t) &= \underbrace{\omega L I_m}_{V_m} \sin(\omega t + 90^\circ) \end{aligned}$$

$V_m = \omega L I_m$, PEAK VALUE OF $V_L(t)$
IS DIRECTLY RELATED TO
 ω & L

$\sin(\omega t + 90^\circ)$, THE PHASE ANGLE OF
 $V_L(t)$ LEADS THAT OF
 $i_L(t)$ BY 90°

$$\text{RECALL: } \frac{E}{I/R} \rightarrow \frac{V_m}{I_m} = \underline{\text{REACTANCE}} , X_L \text{ FOR THE } \text{INDUCTOR} \quad \text{INDUCTIVE REACTANCE}$$

$$X_L = \frac{V_m}{I_m} = \omega L , \text{ OHMS}$$

Response of the Inductor to a Sinusoidal Forcing Function

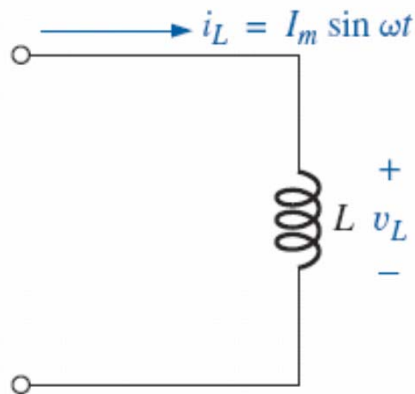


FIG. 14.6

Investigating the sinusoidal response of an inductive element.

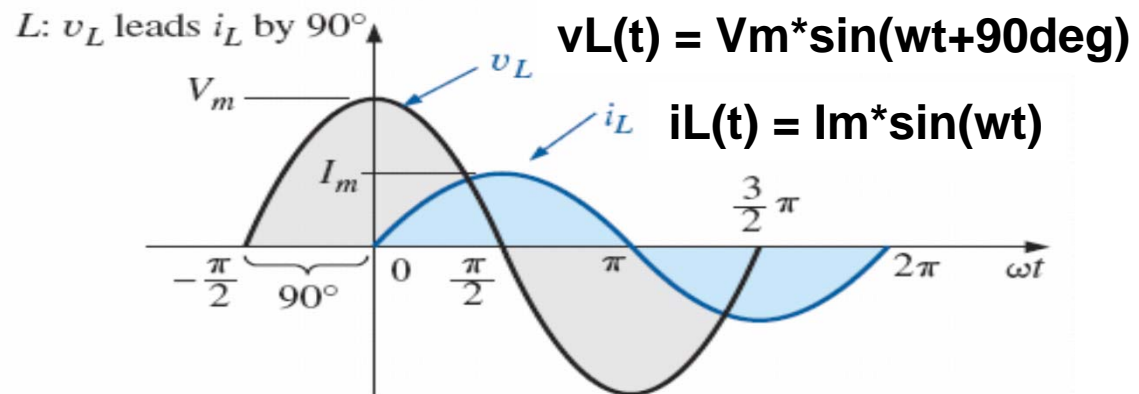


FIG. 14.7 *For a pure inductor, the voltage across the coil leads the current through the coil by 90° .*

ICPs – Inductive Reactance

P1 – Find the reactance of a 2H inductor at

- a) $F=60\text{Hz}$**
- b) $F=2\text{kHz}$**

P2 – Determine the inductance of a coil with a reactance of


- a) 20 Ohms @ 2Hz**
- b) 5280 Ohms @ 1000Hz**

P3 – Determine the frequency (in Hz) for a 10H inductor with

- a) $X_L = 50\text{ Ohms}$**
- b) $X_L = 3770\text{ Ohms}$**

Response of the Capacitor to a Sinusoidal Forcing Function

CAPACITOR

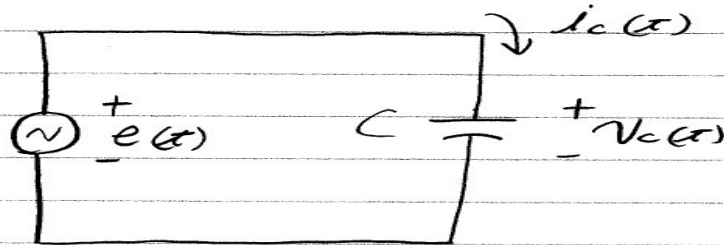

$$e(t) = V_m \sin(\omega t)$$

FIND $i_c(t)$:

$$\begin{aligned} i_c(t) &= C \frac{dv_c(t)}{dt} \\ &= C \frac{d}{dt} [V_m \sin(\omega t)] \end{aligned}$$

$$i_c(t) = \omega C V_m \cos(\omega t)$$

$$\therefore i_c(t) = \omega C V_m \sin(\omega t + 90^\circ)$$

COMPARE :


$$\begin{aligned} v_c(t) &= V_m \sin(\omega t) \\ i_c(t) &= \underbrace{\omega C V_m}_{I_m} \sin(\omega t + 90^\circ) \end{aligned}$$

$I_m = \omega C V_m$, PEAK VALUE OF $i_c(t)$ IS DIRECTLY RELATED TO ω & C

$\sin(\omega t + 90^\circ)$, THE PHASE ANGLE OF $i_c(t)$ LEADS THAT OF $v_c(t)$ BY 90°

$$\frac{E}{I/R} \rightarrow \frac{V_m}{I_m} = \boxed{X_C = \frac{1}{\omega C}} \text{ OHMS, FOR A CAPACITOR (CAPACITIVE REACTANCE)}$$

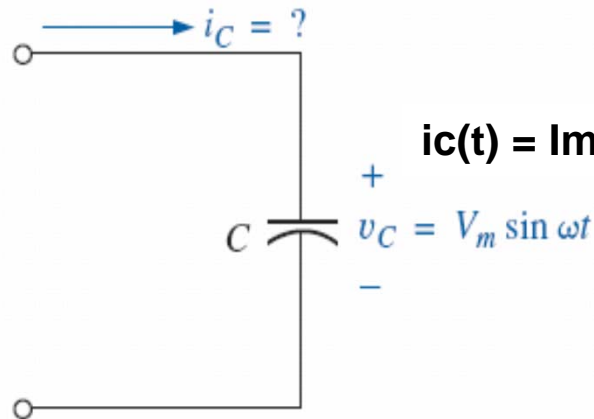Response of the Capacitor to a Sinusoidal Forcing Function



$$i_C(t) = I_m \sin(\omega t + 90^\circ)$$

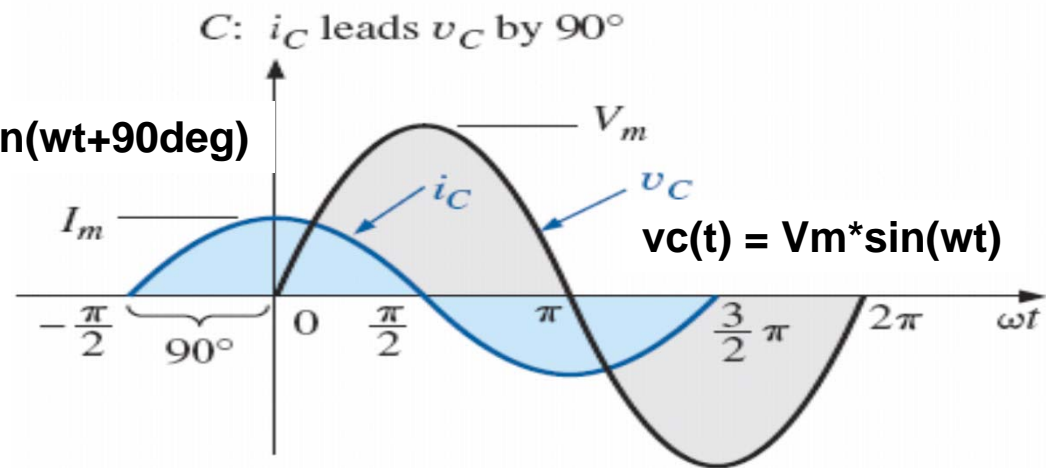


FIG. 14.8 Investigating the sinusoidal response of a capacitive element.

FIG. 14.9 The current of a purely capacitive element leads the voltage across the element by 90° .

* ELI the ICE Man *

ICPs – Capacitive Reactance

P1 – Find the reactance of a 5uF capacitor for

- a) $F=DC$**
- b) $F=60Hz$**
- c) $F=24kHz$**


P2 – Find the frequency at which a 50uF capacitor has

- a) $X_c = 342 \text{ Ohms}$**
- b) $X_c = 2000 \text{ Ohms}$**

P3 – Given $V_c(t) = 30 \cdot \sin(200t)$ Volts for a 1uF capacitor, find $i_c(t)$

Using an Oscilloscope to Determine Network Characteristics

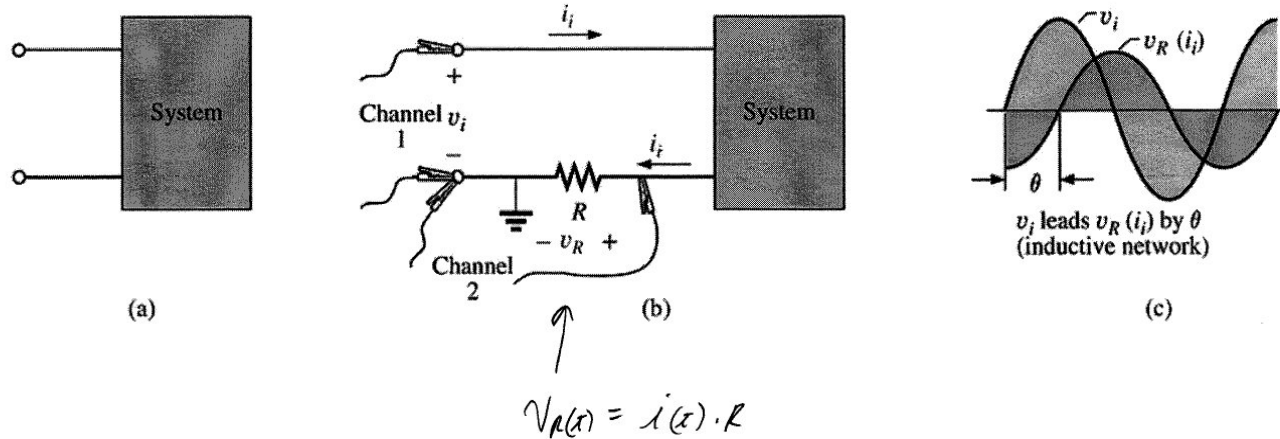The oscilloscope is a 2-channel volt-meter



By placing a “sense” resistor in series with the input current we can measure it indirectly

SUMMARY

	R	L	C
REACTANCE	X	ωL	$\frac{1}{\omega C}$
REACTANCE AT DC ($\omega = 0$)	X	0 (SHORT)	∞ (OPEN)
INCREASE FREQ ↓	NO CHANGE ↓	INCREASING REACTANCE ↓	DECREASING REACTANCE ↓
REACTANCE AT $\omega \rightarrow \infty$ (HIGH FREQ)	X	∞ (OPEN)	0

EXAMPLE

FIND THE REACTANCE OF A $1\mu F$ CAPACITOR & A $1\mu H$ INDUCTOR IF THE APPLIED VOLTAGE IS $30 \sin(400t - 30^\circ)$

$$\begin{aligned}
 X_L &= \omega L \\
 &= (400 \text{ r/s})(1\mu H) \\
 \boxed{X_L &= 400 \times 10^{-6} \Omega} \leftarrow \text{LOW}
 \end{aligned}$$

$$\begin{aligned}
 \omega &= 400 \text{ r/s} \\
 \therefore f &= 63.66 \text{ Hz}
 \end{aligned}$$

$$\begin{aligned}
 X_C &= \frac{1}{\omega C} = \frac{1}{(400 \text{ r/s})(1\mu F)} \\
 \boxed{X_C &= 2,500 \Omega} \leftarrow \text{HIGH}
 \end{aligned}$$

Frequency Response of The Basic Elements (ideal)

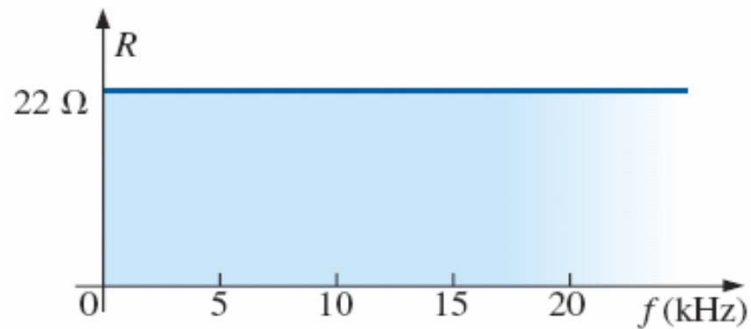


FIG. 14.16 R versus f for the range of interest.


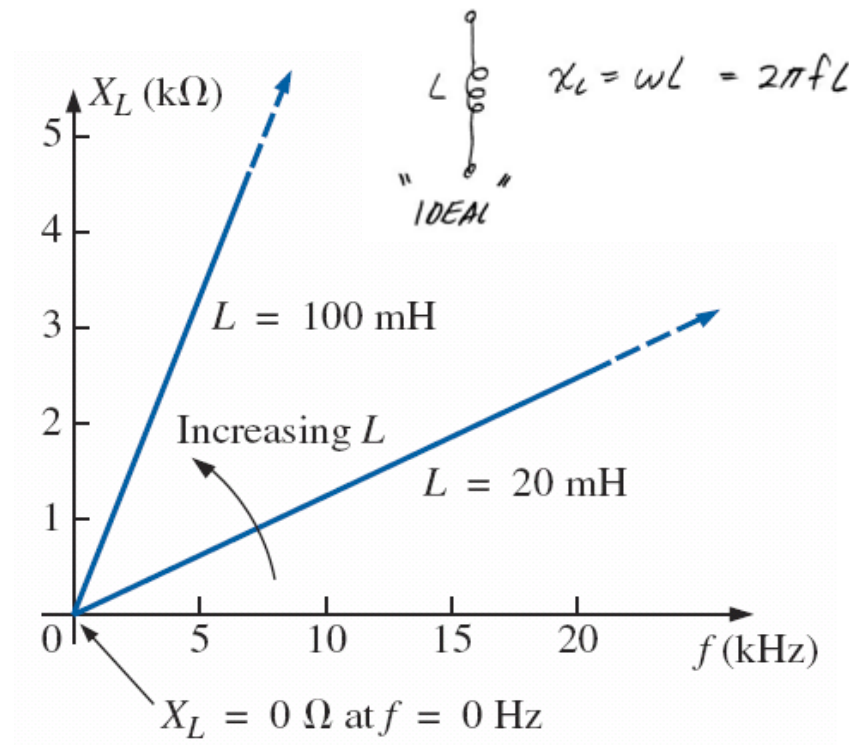


FIG. 14.17 X_L versus frequency.

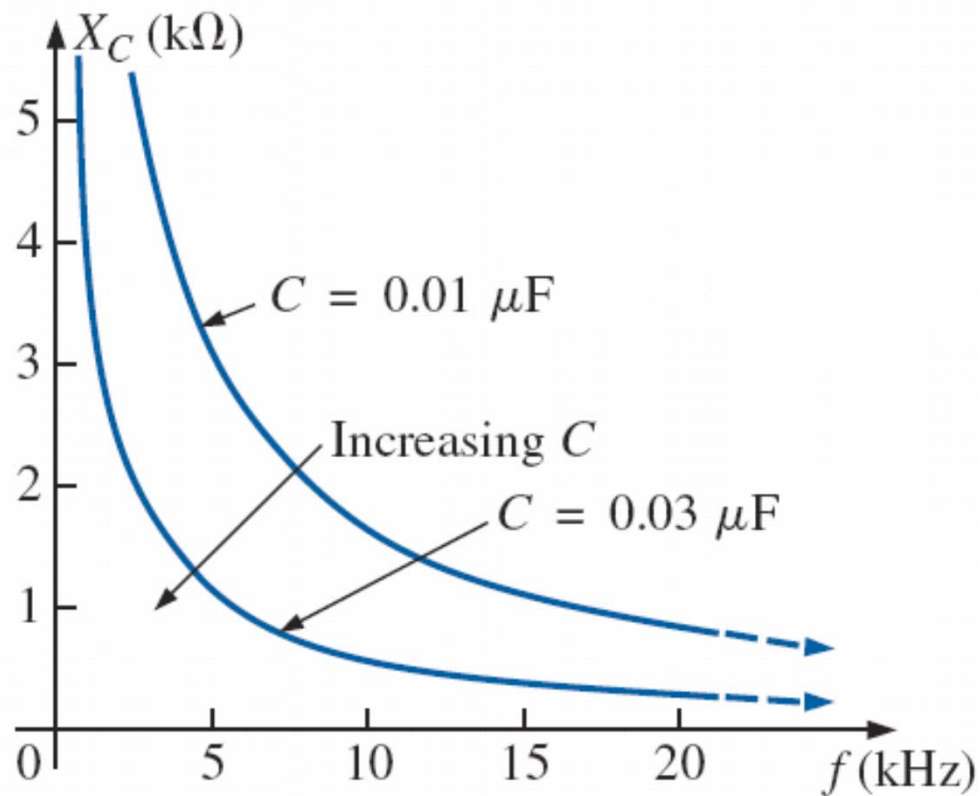Frequency Response of The Basic Elements (ideal)




C  $X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$
 "IDEAL"

FIG. 14.19 X_C versus frequency.

Frequency Response of The Basic Elements (more realistic)

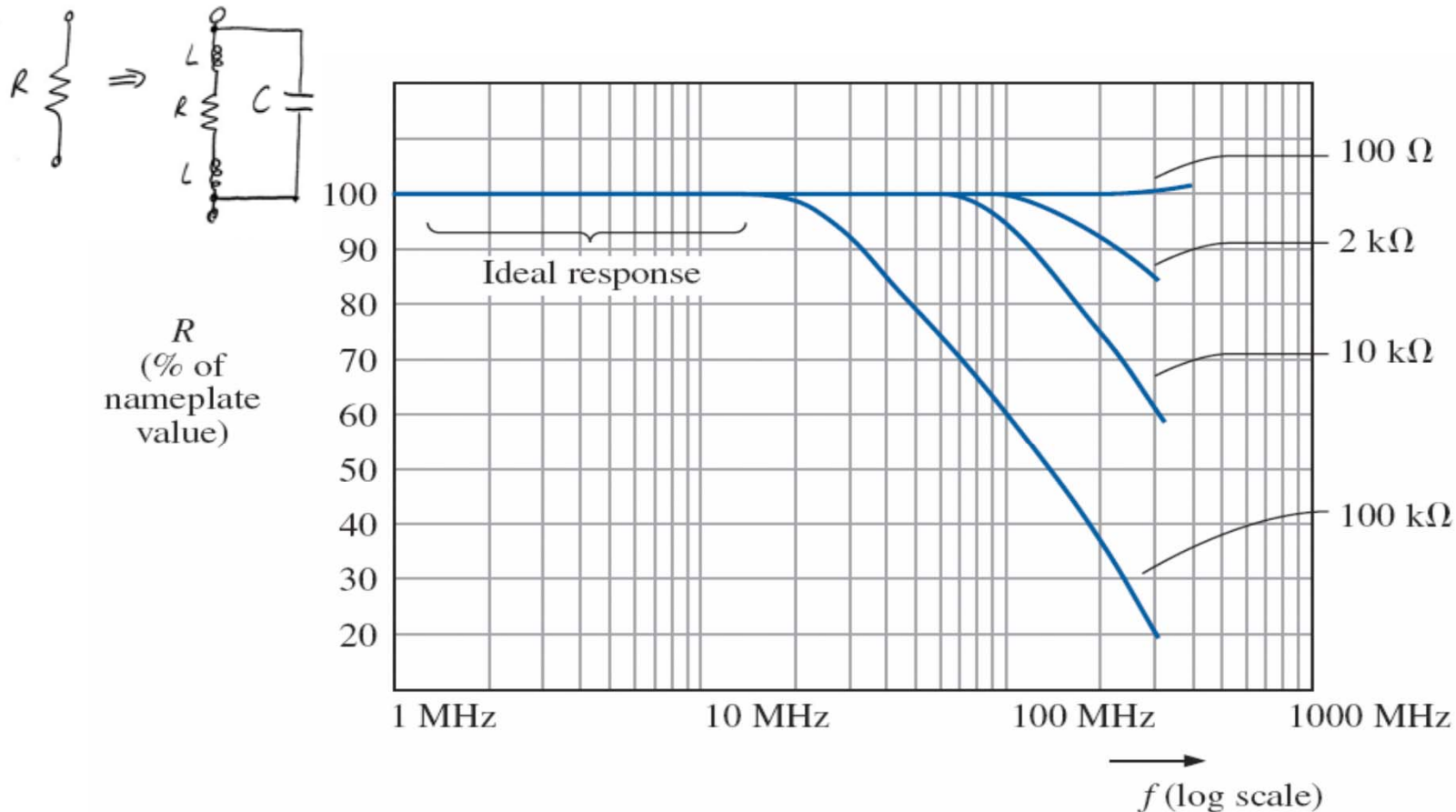


FIG. 14.21 Typical resistance-versus-frequency curves for carbon composition resistors.

Frequency Response of The Basic Elements (more realistic)

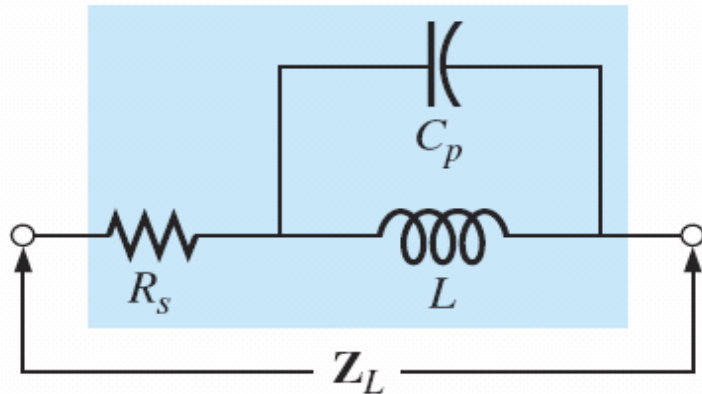


FIG. 14.22 *Practical equivalent for an inductor.*

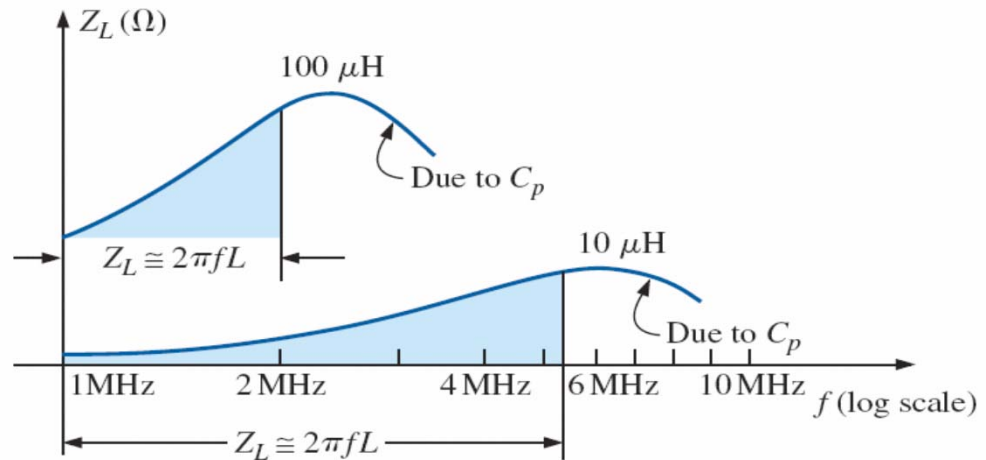


FIG. 14.23 Z_L versus frequency for the practical inductor equivalent of Fig. 14.22.

Frequency Response of The Basic Elements (more realistic)

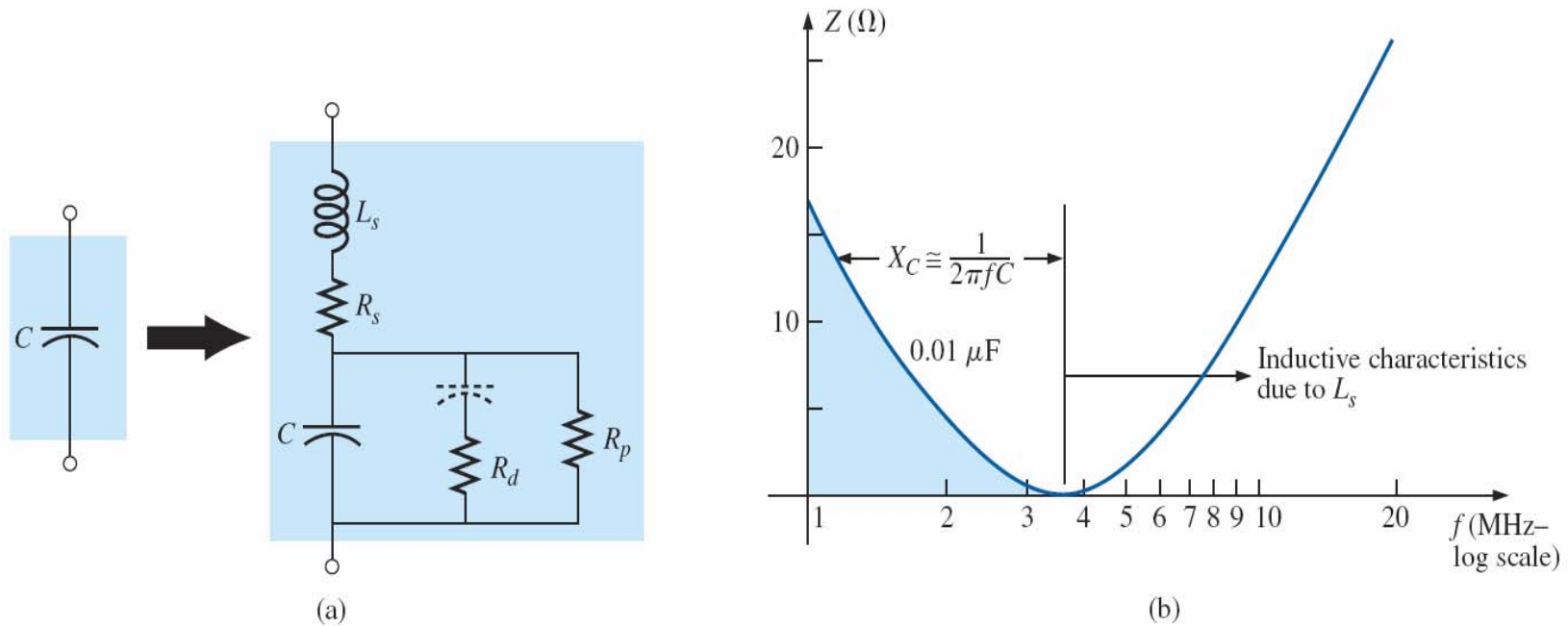


FIG. 14.24 Practical equivalent for a capacitor; (a) network; (b) response.