

## **Parallel Resonance**

- ☐ Introduction and General Circuit
- ☐ Resonant Frequency
- ☐ Quality Factor
- ☐  $Q \geq 10$  Case
- ☐ Selectivity and Branch Currents
- ☐ Example

## Parallel Resonance- Introduction and Circuit

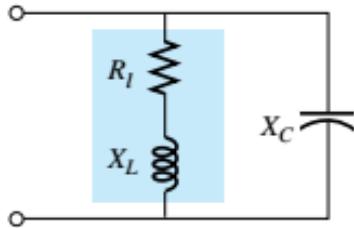


FIG. 21.23


Practical parallel L-C network.

Not just a simple R-L-C parallel network since practical inductors have to take into account series resistance


Taking the inverse of each component yields:

$$\vec{Z}_{TL} = \underbrace{\frac{R_L^2 + X_L^2}{R_L}}_{R_p} \parallel \underbrace{\frac{R_L^2 + X_L^2}{X_L}}_{X_{Lp}} \angle 90^\circ$$

So we have:

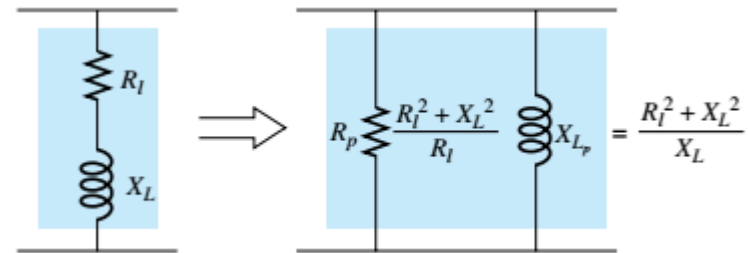

We will consider:

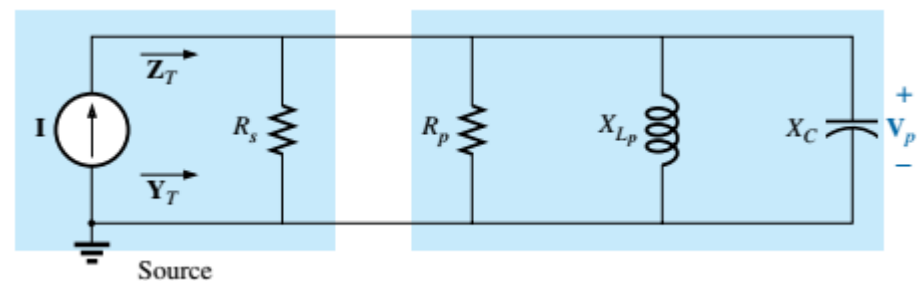


In rectangular form:

$$\vec{Y}_{TL} = \frac{R_L}{R_L^2 + X_L^2} - j \frac{X_L}{R_L^2 + X_L^2}$$

$\uparrow$   
 $G \angle 0^\circ (S)$        $B_L \angle -90^\circ (S)$

## Parallel Resonance - Resonant Frequency

Combining  $R_s$  and  $R_p$  yields:

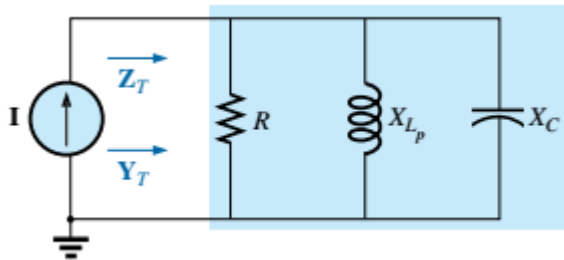

Analyzing

$$Y_T = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} = \frac{1}{R} + \frac{1}{jX_{L_p}} + \frac{1}{-jX_C}$$

$$= \frac{1}{R} - j\left(\frac{1}{X_{L_p}}\right) + j\left(\frac{1}{X_C}\right)$$

$$Y_T = \frac{1}{R} + j\left(\frac{1}{X_C} - \frac{1}{X_{L_p}}\right)$$

For  $F_p = 1$ , the imaginary component of  $Y_T$  must be equal to zero, therefore (at resonance):

$$\frac{1}{X_C} = \frac{1}{X_{L_p}}$$

$$X_{L_p} = X_C$$

Substituting for  $X_{L_p}$ , yields:

$$\frac{R_l^2 + X_L^2}{X_L} = X_C$$

$$R_l^2 + X_L^2 = X_C X_L = \left(\frac{1}{\omega C}\right) \omega L = \frac{L}{C}$$

Solving for  $f_p$ , reduces to (text section 21.10):

$$f_p = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{R_l^2 C}{L}}$$

For low  $R_L$  values,  
 $f_p \sim f_s$

$$f_p = f_s \sqrt{1 - \frac{R_l^2 C}{L}}$$

Looking closer at the  $(R_L^2 C/L)$  term:


$$\frac{R_l^2 C}{L} = \frac{1}{\frac{L}{R_l^2 C}} = \frac{1}{\frac{(\omega)}{(\omega)} \frac{L}{R_l^2 C}} = \frac{1}{\frac{\omega L}{R_l^2 \omega C}} = \frac{X_L X_C}{R_l^2}$$

At resonance,  $X_L = X_C$ , therefore:

$$\frac{1}{\frac{X_L X_C}{R_l^2}} = \frac{X_L^2}{R_l^2} = \frac{1}{Q_l^2}$$

$$f_p = f_s \sqrt{1 - \frac{1}{Q_l^2}} \quad Q_l \geq 10$$

## Parallel Resonance - Quality Factor

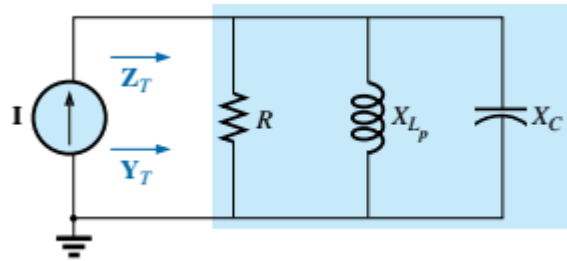

$$f_p = f_s \sqrt{1 - \frac{1}{Q_l^2}} \quad Q_l \geq 10$$

Or:

$$f_p \approx f_s = \frac{1}{2\pi\sqrt{LC}} \quad Q_l \geq 10$$

Recall:

$$Q_s = \frac{\text{reactive power}}{\text{average power}}$$

So here:

$$Q_p = \frac{V_p^2 / X_{L_p}}{V_p^2 / R}$$

$$Q_p = \frac{R}{X_{L_p}} = \frac{R_s \parallel R_p}{X_{L_p}}$$

But  $X_{L_p} = X_C$  at resonance, so we have:

$$Q_p = \frac{R_s \parallel R_p}{X_C}$$

$$\frac{R_l^2 + X_L^2}{R_L} \underbrace{\hspace{1cm}}_{R_p}$$


Expanding:

$$\begin{aligned} R_p &= \frac{R_l^2 + X_L^2}{R_l} = R_l + \frac{X_L^2}{R_l} \left( \frac{R_l}{R_l} \right) = R_l + \frac{X_L^2}{R_l^2} R_l \\ &= R_l + Q_l^2 R_l = (1 + Q_l^2) R_l \end{aligned}$$

Or, for  $Q \geq 10$ :

$$R_p \approx Q_l^2 R_l \quad Q_l \geq 10$$

## Parallel Resonance - $Q \geq 10$

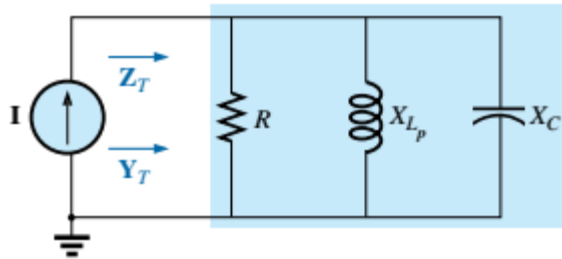

$$R_p \cong Q_l^2 R_l \quad Q_l \geq 10$$


Also, recall:

$$\begin{aligned} X_{L_p} &= \frac{R_l^2 + X_L^2}{X_L} \\ &= \frac{R_l^2(X_L)}{X_L(X_L)} + X_L \\ &= \frac{X_L}{Q_l^2} + X_L \\ &= X_L \left( \frac{1}{Q_l^2} + 1 \right) \end{aligned}$$

Therefore:

$$X_{L_p} \cong X_L \quad Q_l \geq 10$$

So, for  $Q \geq 10$ , we have:

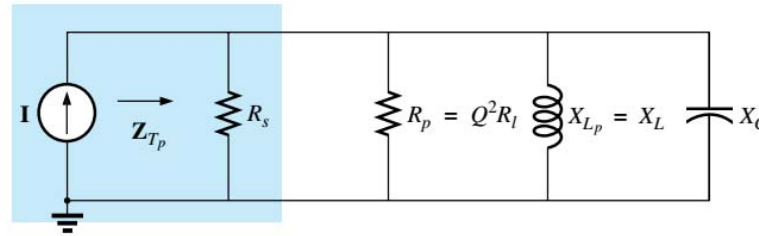

$$R_p \cong Q_l^2 R_l = \left( \frac{X_L}{R_l} \right)^2 R_l = \frac{X_L^2}{R_l}$$

But, at resonance  $X_L = X_C$ , so:


$$\frac{X_L^2}{R_l} = \frac{X_L X_C}{R_l} = \frac{2\pi f L}{R_l (2\pi f C)}$$

$$R_p \cong \frac{L}{R_l C} \quad Q_l \geq 10$$

$$Z_{T_p} \cong R_s \parallel R_p = R_s \parallel Q_l^2 R_l \quad Q_l \geq 10$$

$$Q_p = \frac{R}{X_{L_p}} \cong \frac{R_s \parallel Q_l^2 R_l}{X_L}$$
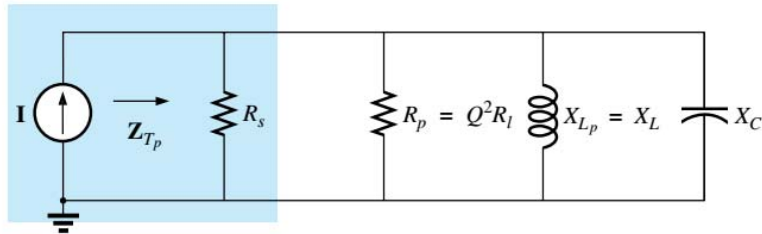
## Parallel Resonance – Selectivity and Branch Currents




As before, BW is defined as:

$$BW = f_2 - f_1 = \frac{f_p}{Q_p}$$

Or can be calculated as:

$$BW = f_2 - f_1 \cong \frac{1}{2\pi} \left[ \frac{R_l}{L} + \frac{1}{R_s C} \right]$$

Finally, consider:

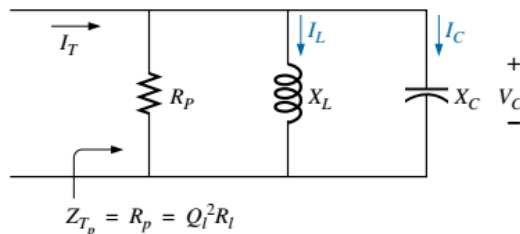

At resonance:

$$V_C = V_L = V_R = I_T Z_{T_p} = I_T Q_l^2 R_l$$

Finding  $I_C = |I_C|$ :

$$I_C = \frac{V_C}{X_C} = \frac{I_T Q_l^2 R_l}{X_C}$$

$$I_C = \frac{I_T Q_l^2 R_l}{X_L} = I_T \frac{Q_l^2}{\frac{X_L}{R_l}} = I_T \frac{Q_l^2}{Q_l}$$

Hence:

$$I_C \cong Q_l I_T \quad Q_l \geq 10$$


Similarly:

$$I_L \cong Q_l I_T \quad Q_l \geq 10$$


## Parallel Resonance – Example

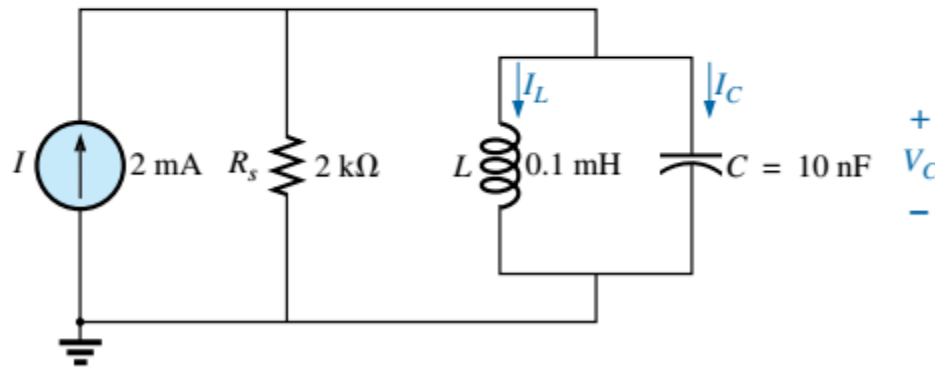13. For the “ideal” parallel resonant circuit in Fig. 21.54:

- Determine the resonant frequency ( $f_p$ ).
- Find the voltage  $V_C$  at resonance.
- Determine the currents  $I_L$  and  $I_C$  at resonance.
- Find  $Q_p$ .



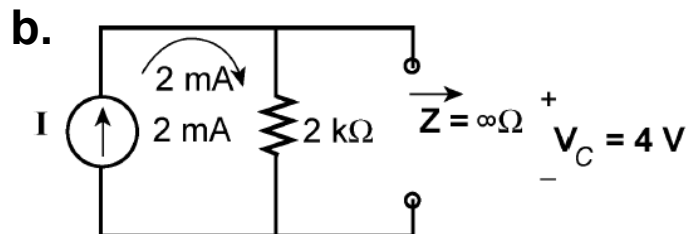a.  $f_p = \frac{1}{2\pi\sqrt{LC}} = \frac{2}{2\pi\sqrt{(0.1 \text{ mH})(10 \text{ nF})}} = 159.16 \text{ kHz}$



c.  $I_L = \frac{V_L}{X_L} = \frac{4 \text{ V}}{2\pi f_p L} = \frac{4 \text{ V}}{100 \Omega} = 40 \text{ mA}$

$$I_C = \frac{V_L}{X_C} = \frac{4 \text{ V}}{1/2\pi f_p C} = \frac{4 \text{ V}}{100 \Omega} = 40 \text{ mA}$$

Note that  $I_L = I_C > I$  at resonance

d.  $Q_p = \frac{R_s}{X_{L_p}} = \frac{2 \text{ k}\Omega}{2\pi f_p L} = \frac{2 \text{ k}\Omega}{100 \Omega} = 20$