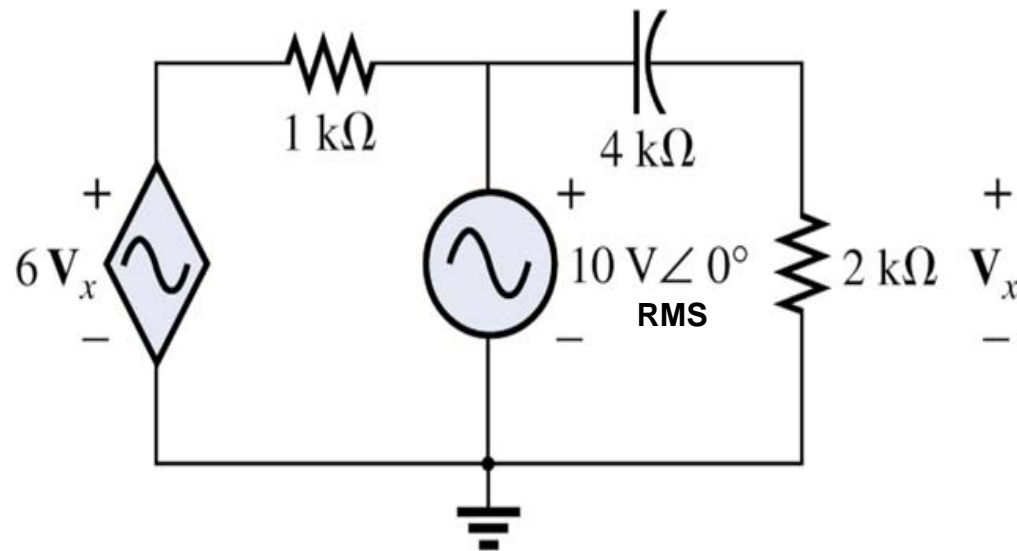


ICP – MESH Analysis w/Dependent Voltage Source




Find:

- The current through each resistor


Check:

- KVL on the LHS or RHS

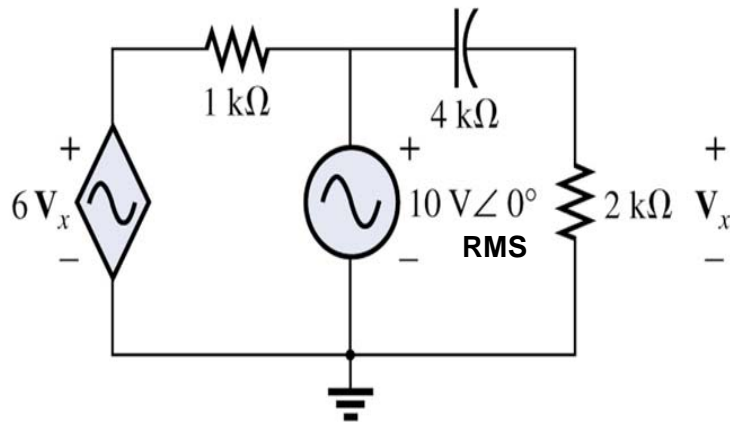ICP – MESH Analysis w/Dependent Voltage Source



Redraw and assign loop currents CW:

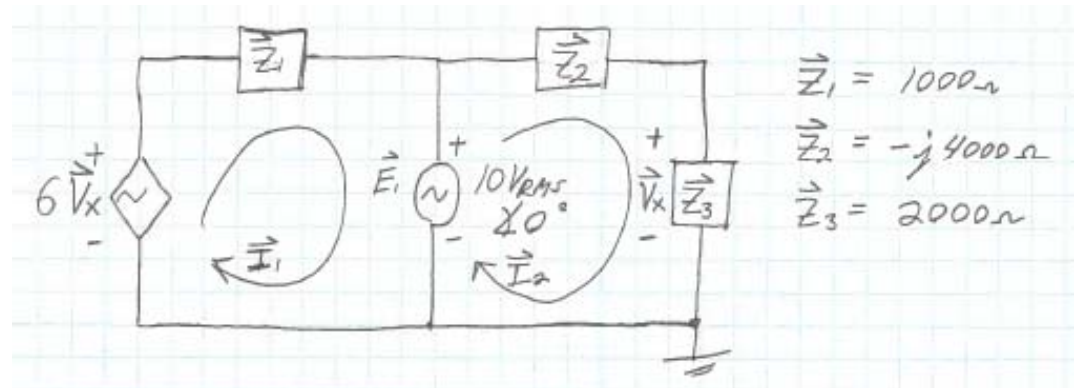

$$\text{Loop 1: } 6\vec{V}_x - \vec{I}_1 \vec{Z}_1 - \vec{E}_1 = 0$$

$$\text{But } \vec{V}_x = \vec{I}_2 \vec{Z}_3$$

$$\therefore 6 \vec{I}_2 \vec{Z}_3 - \vec{I}_1 \vec{Z}_1 = \vec{E}_1$$

$$\text{OR } -\vec{I}_1 \vec{Z}_1 + 6 \vec{Z}_3 \vec{I}_2 = \vec{E}_1 \quad (1)$$

$$\text{Loop 2: } \vec{E}_1 - \vec{I}_2 \vec{Z}_2 - \vec{I}_2 \vec{Z}_3 = 0$$

$$\text{OR } 0 \vec{I}_1 + (\vec{Z}_2 + \vec{Z}_3) \vec{I}_2 = \vec{E}_1 \quad (2)$$

SUBSTITUTING VALUES YIELDS:


$$-1000 \vec{I}_1 + 12,000 \vec{I}_2 = 10 \angle 0^\circ \quad (1)$$

$$0 \vec{I}_1 + (2000 - j4000) \vec{I}_2 = 10 \angle 0^\circ \quad (2)$$

$$A \cdot X = B$$

$$\therefore X = A^{-1} \cdot B = \begin{bmatrix} 24.1 \text{ mA} \angle 85.2^\circ \\ 2.24 \text{ mA} \angle 63.4^\circ \end{bmatrix} \begin{matrix} \vec{I}_1 \\ \vec{I}_2 \end{matrix}$$

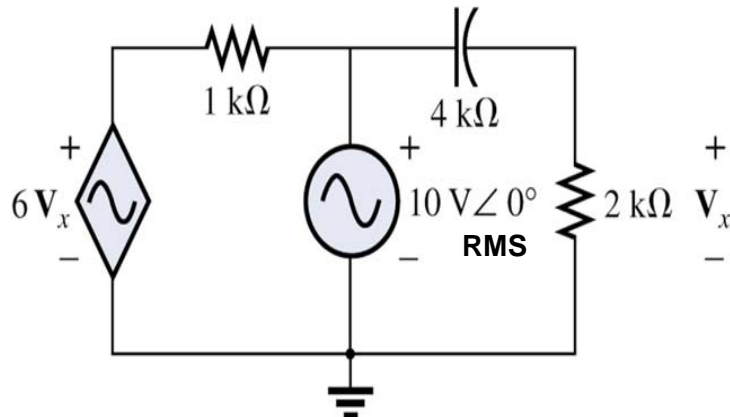ICP – MESH Analysis w/Dependent Voltage Source



LHS CHECK


$$6\vec{V}_x - \vec{I}_1 \vec{Z}_1 \stackrel{?}{=} \vec{E}_1$$

$$\text{But } \vec{V}_x = \vec{I}_2 \vec{Z}_3 = 4.48V_{RMS} \angle 63.4^\circ$$

So we have:

$$6(4.48V_{RMS} \angle 63.4^\circ) - 24.1V_{RMS} \angle 85.2^\circ \stackrel{?}{=} 10V_{RMS} \angle 0^\circ$$
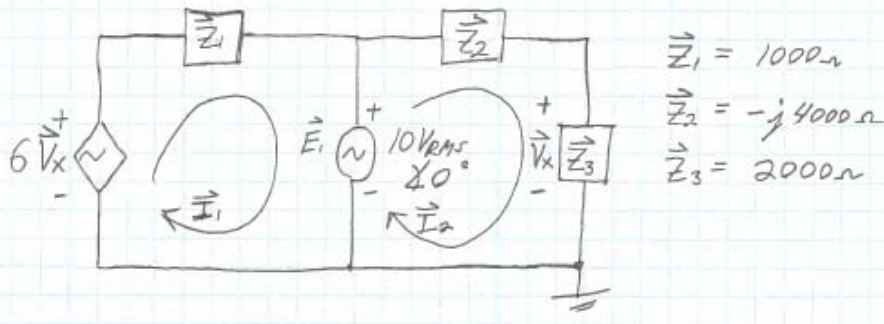
$$10.02V_{RMS} \angle 0.11^\circ \cong 10V_{RMS} \angle 0^\circ \checkmark$$



$$A \cdot X = B$$

$$\therefore X = A^{-1} \cdot B = \begin{bmatrix} 24.1mA_{RMS} \angle 85.2^\circ \\ 2.24mA_{RMS} \angle 63.4^\circ \end{bmatrix} \begin{matrix} \vec{I}_1 \\ \vec{I}_2 \end{matrix}$$