

## **Transformer Intro**

- Introduction
  - Objectives
  - Vocabulary and background
- Analysis/Equations
  - Schematic
  - Compare to inductors
  - Primary and secondary voltages
  - Coefficient of coupling
  - Mutual inductance
  - Example problem
- Transformer – In Class Problem

## **Transformer Intro - Objectives**

- Become familiar with the flux linkages that exist between the coils of a transformer and how the voltages across the primary and secondary are established (and related).
- Understand the operation of an iron-core and air-core transformer and know how to calculate the currents and voltages of the primary and secondary circuits.
- Be aware of how the transformer is used for impedance matching purposes to ensure a high level of power transfer.
- Become aware of all the components that make up the equivalent circuit of a transformer and how they affect its performance and frequency response. <- Machines and Transformers

## **Transformer Introduction**

- Mutual inductance is a phenomenon basic to the operation of the transformer, an electrical device used today in almost every field of electrical engineering.
- Transformers play an integral part in power distribution systems and can be found in many electronic circuits and measuring instruments.
- In this chapter, we discuss three of the basic applications of a transformer: to build up or step down the voltage or current, to act as an impedance matching device, and to isolate (no physical connection) one portion of a circuit from another.

# Transformer Analysis/Equations

## Review from Chapter 11 (inductors)


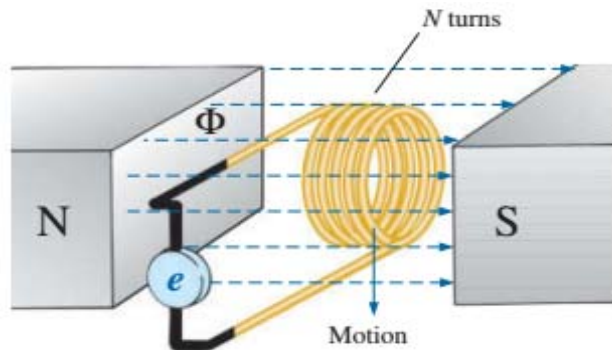


FIG. 11.29

Demonstrating Faraday's law.
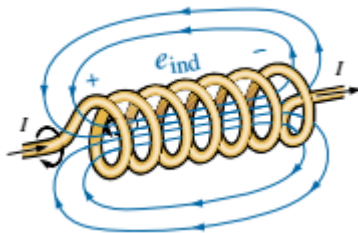
$$e = N \frac{d\phi}{dt} \quad (\text{volts, V})$$




$$L = N \frac{d\phi}{di_L} \quad (\text{henries, H})$$

$$e = N \frac{d\phi}{dt} = \left( N \frac{d\phi}{di_L} \right) \left( \frac{di_L}{dt} \right)$$

$$e_L = L \frac{di_L}{dt} \quad (\text{volts, V})$$

## Applying to a transformer

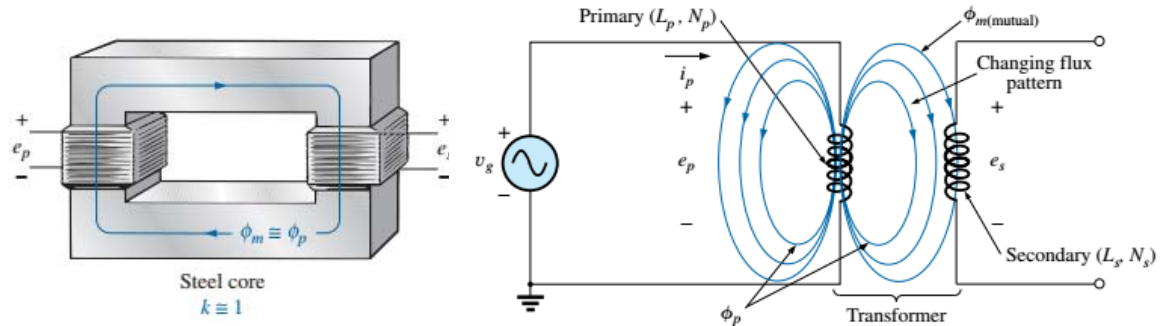

$$e_p = N_p \frac{d\phi_p}{dt} \quad (\text{volts, V})$$

$$e_p = L_p \frac{di_p}{dt} \quad (\text{volts, V})$$

$$e_s = N_s \frac{d\phi_m}{dt} \quad (\text{volts, V})$$

$$\text{If: } \phi_m = \phi_p$$


$$e_s = N_s \frac{d\phi_p}{dt} \quad (\text{volts, V})$$

k is defined:

$$k \text{ (coefficient of coupling)} = \frac{\phi_m}{\phi_p}$$

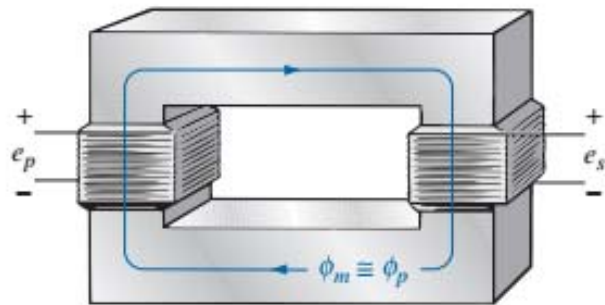
## Transformer Intro – Coefficient of Coupling

$$k \text{ (coefficient of coupling)} = \frac{\phi_m}{\phi_p}$$




Steel core

$$k \cong 1$$

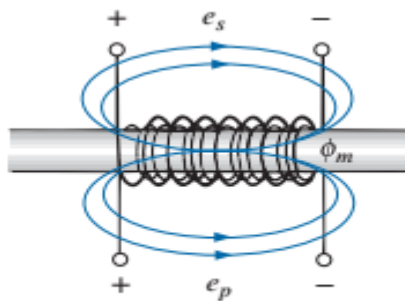

Any core

$$k \cong 1$$

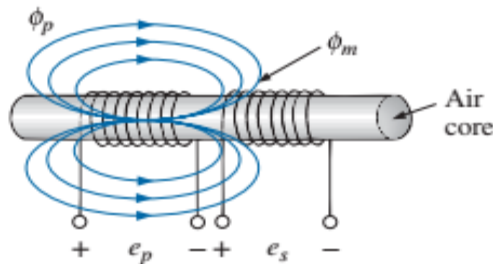


$$k = \frac{\phi_m}{\phi_p} \ll 1 \text{ (0.01} \rightarrow \text{0.3)}$$

Steel core:  $k \sim 1$ , most of the flux linking the primary also links the secondary

$k \sim 1$ , most of the flux linking the primary also links the secondary (same core, overlapping coils)


$k \ll 1$ , loosely coupled (non-ferromagnetic core AND coils are not overlapping)

## Transformer Intro – Mutual Inductance

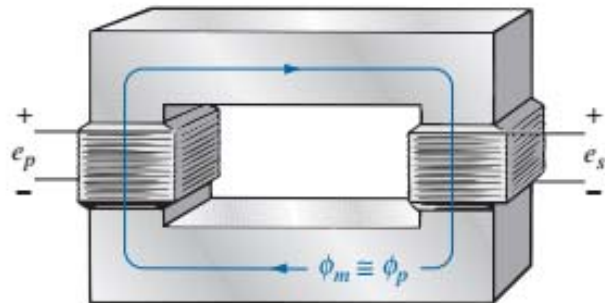

Steel core

$$k \equiv 1$$

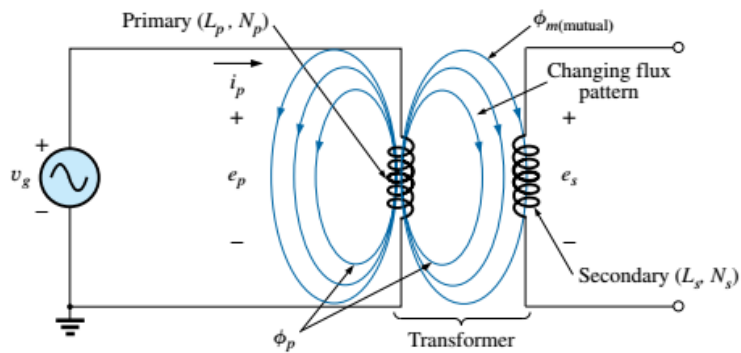

Recall:

$$e_s = N_s \frac{d\phi_m}{dt} \quad (\text{volts, V})$$

$$k \text{ (coefficient of coupling)} = \frac{\phi_m}{\phi_p}$$

Therefore, for any k:

$$e_s = kN_s \frac{d\phi_p}{dt} \quad (\text{volts, V})$$

*mutual inductance between two coils is proportional to the instantaneous change in flux linking one coil due to an instantaneous change in current through the other coil.*

The mutual inductance between the primary and secondary coils is given as:


$$M = N_s \frac{d\phi_m}{di_p} \quad (\text{henries, H})$$

$$M = N_p \frac{d\phi_m}{di_s} \quad (\text{henries, H})$$


In terms of the primary and secondary inductances, it can be shown that:

$$M = k\sqrt{L_p L_s} \quad (\text{henries, H})$$

## Transformer Intro – Mutual Inductance

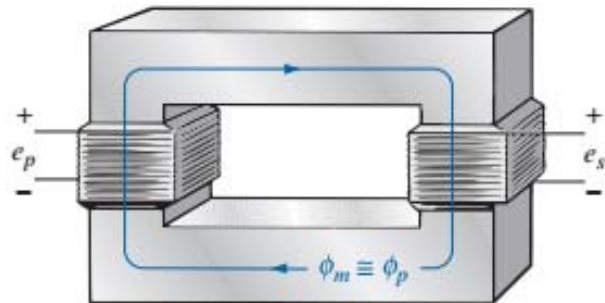

Steel core  
 $k \equiv 1$

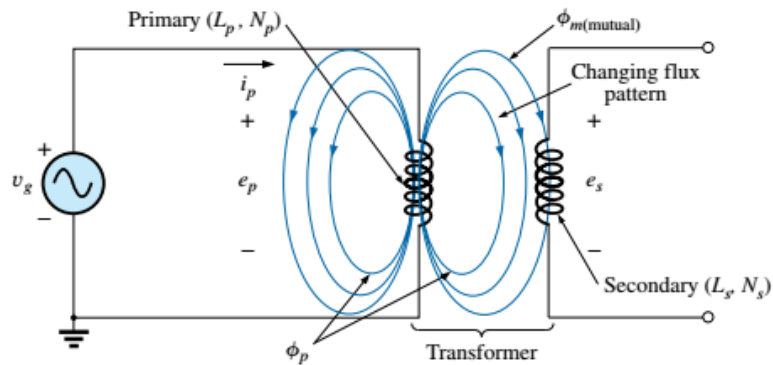

Recall:

$$e_s = N_s \frac{d\phi_m}{dt} \quad (\text{volts, V})$$

Rewriting:

$$e_s = N_s \left( \frac{d\phi_m}{di_p} \right) \left( \frac{di_p}{dt} \right)$$

And recall:

$$M = N_s \frac{d\phi_m}{di_p} \quad (\text{henries, H})$$


Combining, yields:

$$e_s = M \frac{di_p}{dt} \quad (\text{volts, V})$$

And similarly:

$$e_p = M \frac{di_s}{dt} \quad (\text{volts, V})$$

## Transformer Intro – Example

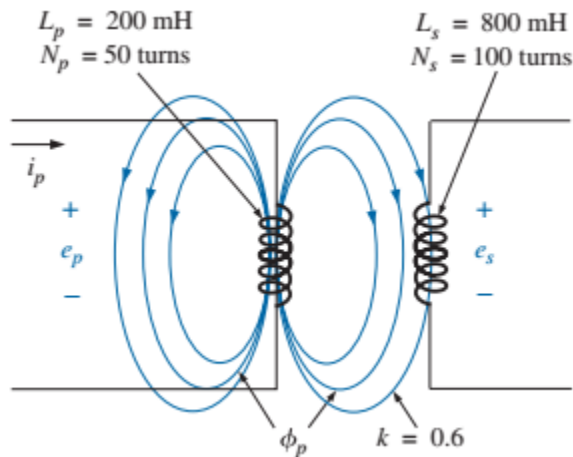

### Find:

- $e_p$  if the primary flux is changing at a rate of  $450 \text{ mWb/s}$
- $e_s$  given the same rate of change in primary flux
- $M$  in Henries
- $e_p$  and  $e_s$  if  $i_p$  changes at the rate of  $0.2 \text{ A/ms}$

$$e_p = N_p \frac{d\phi_p}{dt} = (50)(450 \text{ mWb/s}) = \mathbf{22.5 \text{ V}}$$

$$e_s = kN_s \frac{d\phi_p}{dt} = (0.6)(100)(450 \text{ mWb/s}) = \mathbf{27 \text{ V}}$$

$$M = k\sqrt{L_p L_s} = 0.6\sqrt{(200 \text{ mH})(800 \text{ mH})}$$

$$= 0.6\sqrt{16 \times 10^{-2}} = (0.6)(400 \times 10^{-3}) = \mathbf{240 \text{ mH}}$$


$$e_p = L_p \frac{di_p}{dt} = (200 \text{ mH})(0.2 \text{ A/ms})$$

$$= (200 \text{ mH})(200 \text{ A/s}) = \mathbf{40 \text{ V}}$$

$$e_s = M \frac{di_p}{dt} = (240 \text{ mH})(200 \text{ A/s}) = \mathbf{48 \text{ V}}$$



## Transformer Intro – In Class Problem

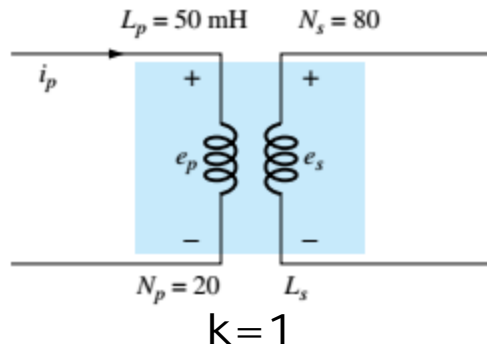

### Find:

- a)  $L_s$  if  $M = 200 \text{ mH}$
- b)  $e_p$  and  $e_s$  if the flux linking the primary coil changes at a rate of  $0.08 \text{ Wb/s}$
- c)  $e_p$  and  $e_s$  if  $i_p$  changes at a rate of  $0.3 \text{ A/ms}$