

Electrical Engineering Technology

Frequency Response For Series ac Circuits

Spring 2019 (2185)

Frequency Response For Series ac Circuits

- Frequency Response for Basic Elements
 - Introduction
 - RLC Series Circuit (qualitatively)
 - RLC Series Circuit Impedance Example/**ICP** – Find the equation and sketch
- Frequency Response for a Series RC Circuit
 - Total Impedance and example/**ICP**
 - Voltage V_C and example/**ICP**


How does the response of a series circuit change as the frequency changes?

■ Parameters of Interest

- ☐ Impedance, **Z**
- ☐ Voltage, **V**
- ☐ Current, **I**


Frequency Response of Basic Elements

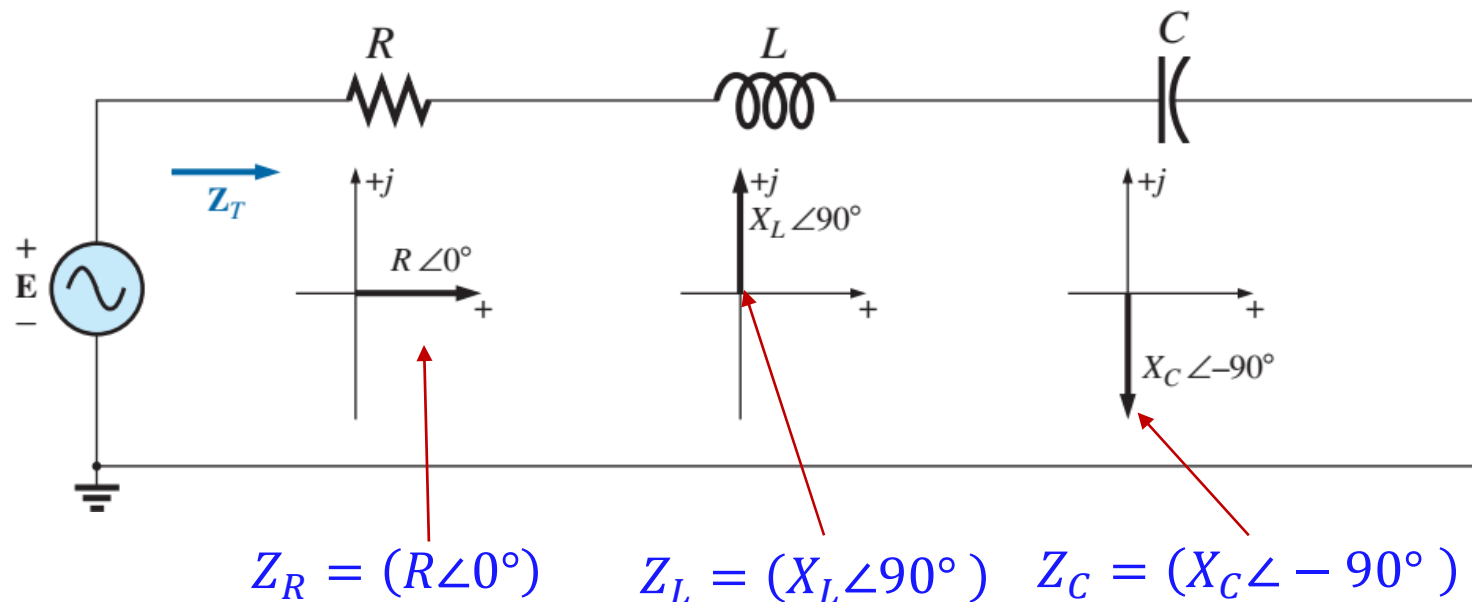- The impedance and impedance diagram of **ideal circuit elements** are shown in the RLC circuit below



Frequency Response of Basic Elements

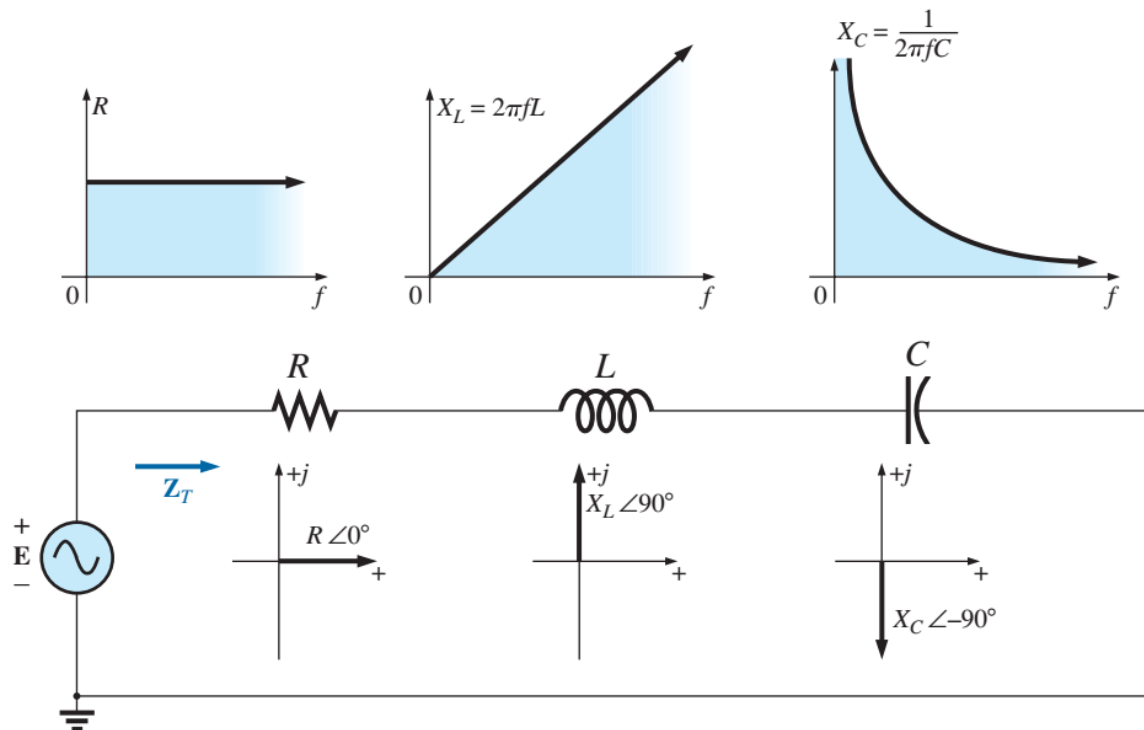- The response of the **ideal** elements to changes in frequency are shown below



Note:

	Low Freq. ($f = 0$)	High Freq. ($f \rightarrow \infty$)
Z_R	No changes	No changes
Z_L	Short-circuit	Open-circuit
Z_C	Open-circuit	Short-circuit

FIG. 15.49

Reviewing the frequency response of the basic elements.

Frequency Response of Basic Elements

- What do $|Z_T|$ and $|I_T|$ look like for a series RLC Circuit?



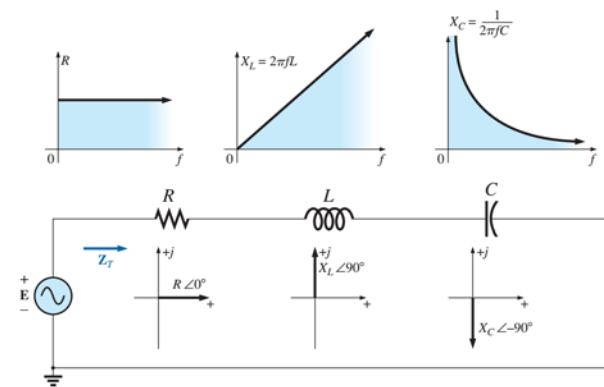
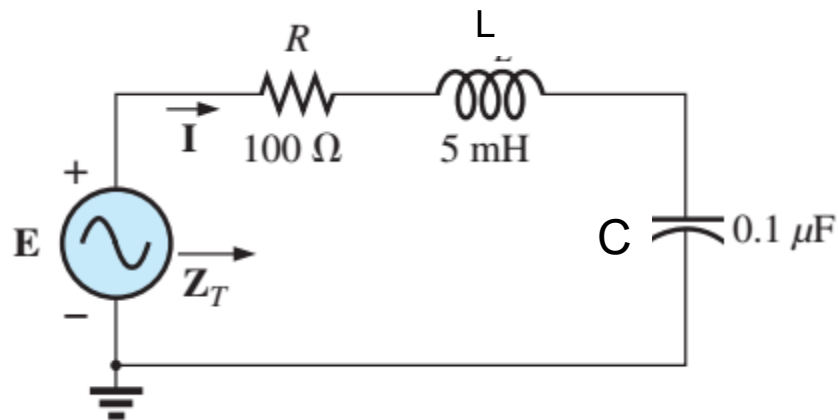
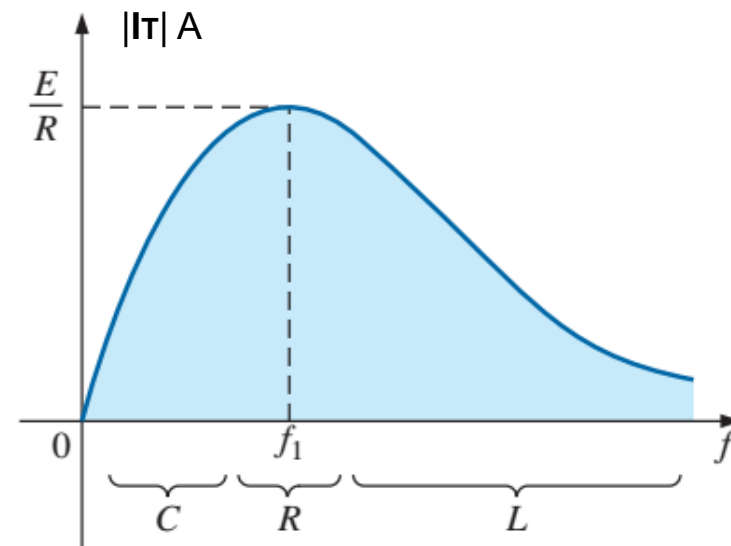
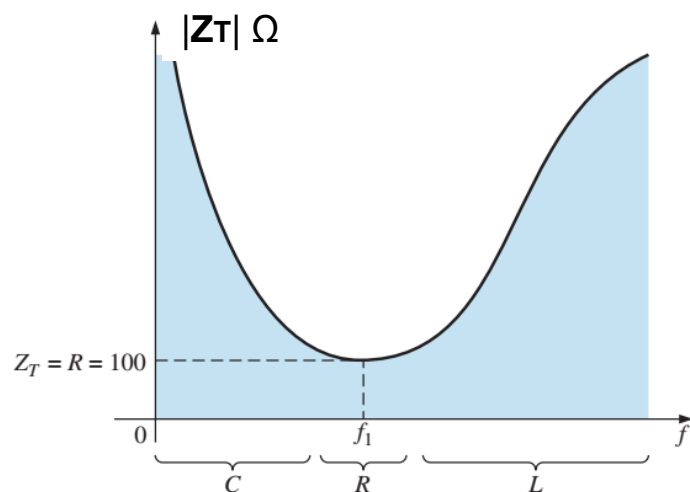


FIG. 15.49
Reviewing the frequency response of the basic elements.

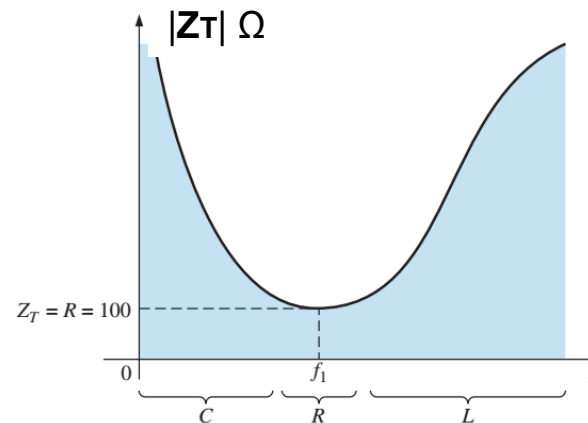

Frequency Response of Basic Elements

- Find $|Z_T|$ for this circuit as a function of frequency (as the frequency changes)

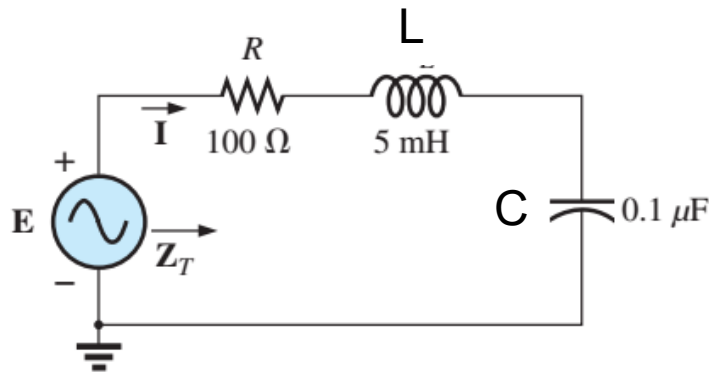

ICP:

- 1) Calculate $|Z_T|$ at 100Hz, 10kHz and 100kHz
- 2) At what frequency does $|Z_T|$ hit its minimum?
- 3) Sketch $|Z_T|$ as a function of frequency (calculator...)

Frequency Response of a Series R-C Circuit

- **Example:** Determine the frequency response of a series R-C circuit
 - Frequency range: 0 to 20 kHz
 - Frequency response of the individual elements are key
 - But - We are more interested in the frequency response of the entire circuit (Z_T and V_C here)

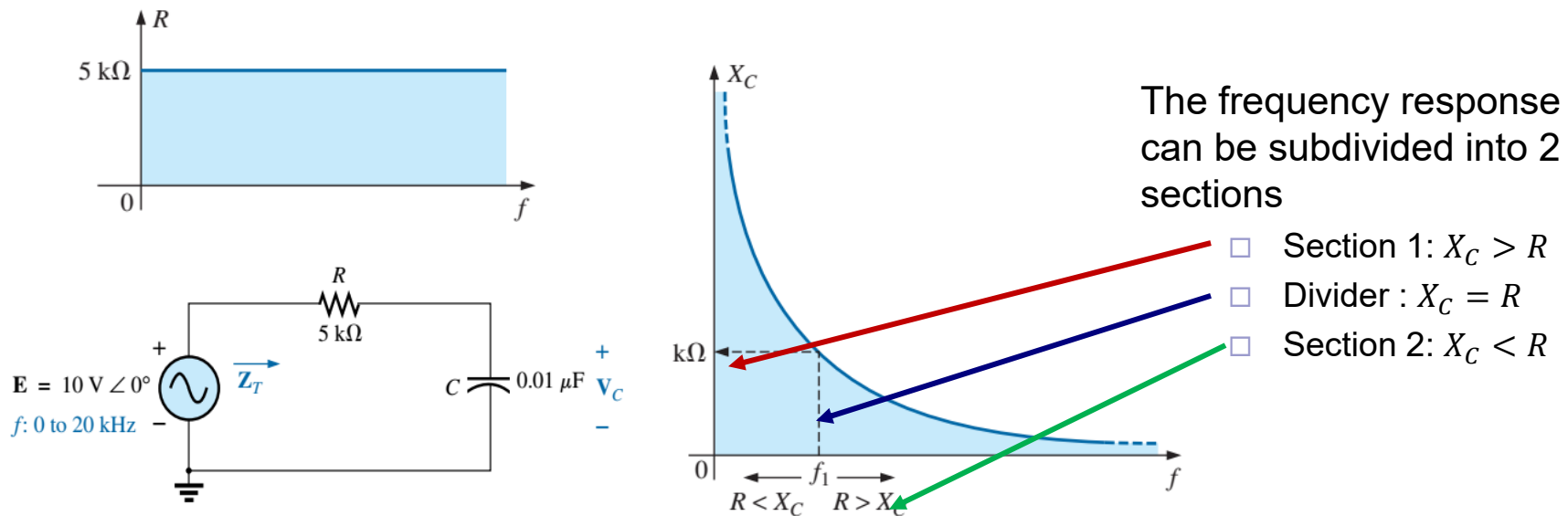


FIG. 15.51

Frequency Response of a Series R-C Circuit

- Frequency for $X_R = X_C$

$$X_C = \frac{1}{2\pi f_1 C} = R \quad \therefore f_1 = \frac{1}{2\pi RC}$$

- Total impedance, Z_T

- Rectangular form

$$Z_T = Z_R + Z_C$$


$$Z_T = (R + j0) + (0 - jX_C)$$

$$Z_T = R - jX_C$$

- Polar form

$$Z_T = Z_T \angle \theta$$
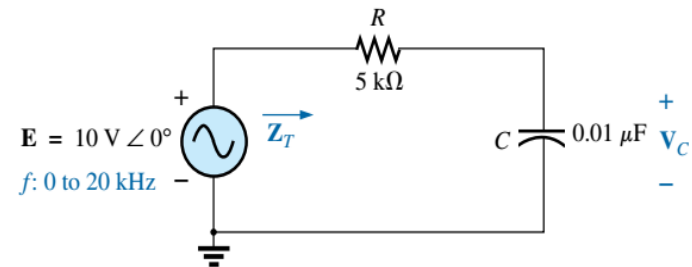
$$Z_T = \sqrt{(R^2 + X_C^2)} \angle -\tan^{-1}\left(\frac{X_C}{R}\right)$$




Frequency Response of a Series R-C Circuit


Magnitude: $\sqrt{(R^2 + X_C^2)}$

Z_T

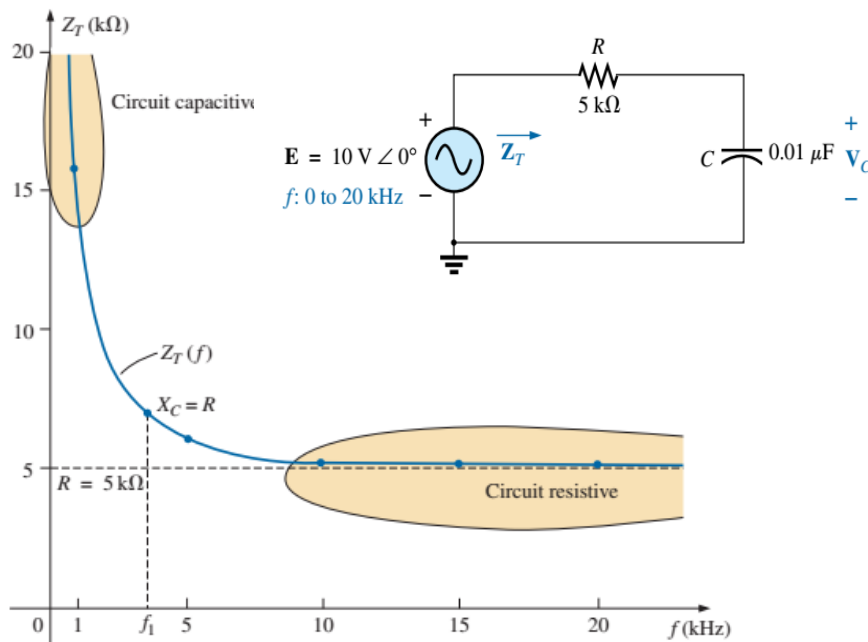Angle: $\angle -\tan^{-1}\left(\frac{X_C}{R}\right)$



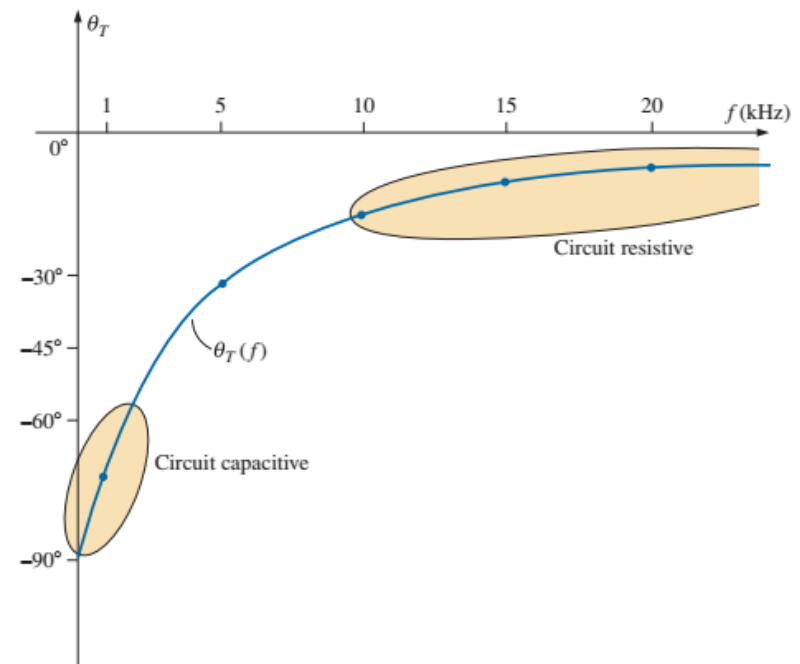The magnitude of the input impedance versus frequency for the circuit in Fig. 15.50.



The phase angle of the input impedance versus frequency for the circuit in Fig. 15.50.

ICP - Calculate $|Z_T|$ and $\angle Z_T$ at:
100Hz, 3.18kHz, 20kHz


frequency	Z_T
100 Hz	159.2KΩ < -88.2°
3.18 kHz	7.07KΩ < -45°
20 kHz	5.06KΩ < -9.04°

Frequency Response of a Series R-C Circuit

- Find the voltage V_C using voltage divider

$$V_C = \frac{Z_C E}{Z_T} = \frac{Z_C E}{Z_R + Z_C} = \frac{(X_C \angle -90^\circ)(E \angle 0^\circ)}{(R + j0) + (0 - jX_C)} = \frac{(X_C E \angle -90^\circ)}{(R - jX_C)}$$
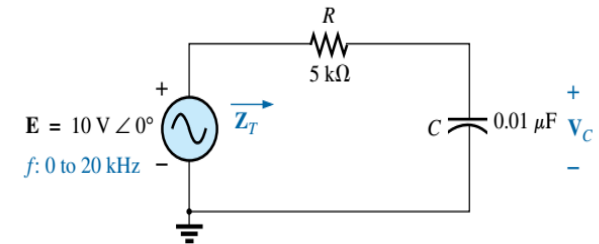
$$= \frac{(X_C E \angle -90^\circ)}{\sqrt{(R^2 + X_C^2)} \angle -\tan^{-1}\left(\frac{X_C}{R}\right)}$$



$$V_C = |V_C| \angle \theta_C = \frac{X_C E}{\sqrt{R^2 + X_C^2}} \angle -90^\circ - (-\tan^{-1}(X_C/R))$$

- Voltage V_C

□ Magnitude: $|V_C| = \frac{X_C E}{\sqrt{R^2 + X_C^2}}$

□ Angle: $\angle \theta_C = -90^\circ + \tan^{-1}(X_C/R) = -\tan^{-1}(R/X_C)$

Frequency Response of a Series R-C Circuit

Magnitude: $V_C = \frac{X_C E}{\sqrt{R^2 + X_C^2}}$

V_C

Angle: $\angle \theta_C$
 $= -90^\circ + \tan^{-1} (X_C / R)$
 $= -\tan^{-1} (R / X_C)$

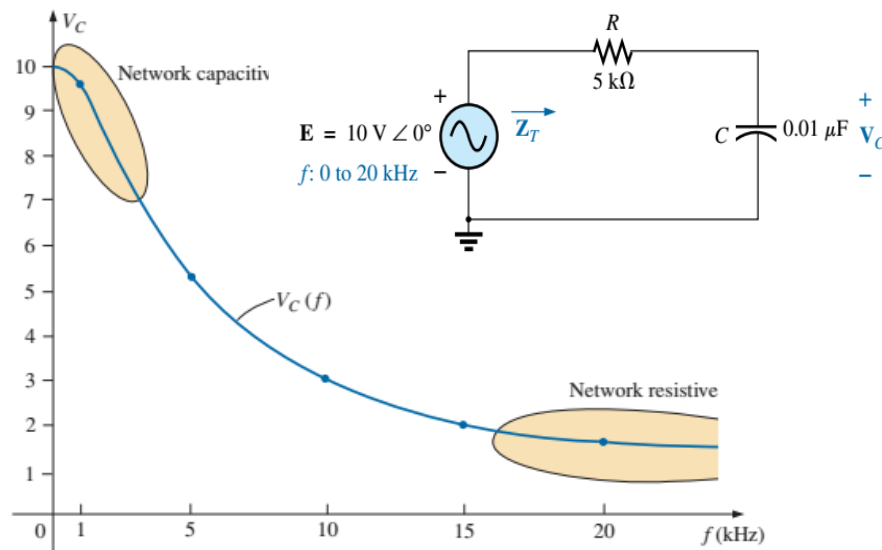


FIG. 15.58

The magnitude of the voltage V_C versus frequency for the circuit in Fig. 15.50.

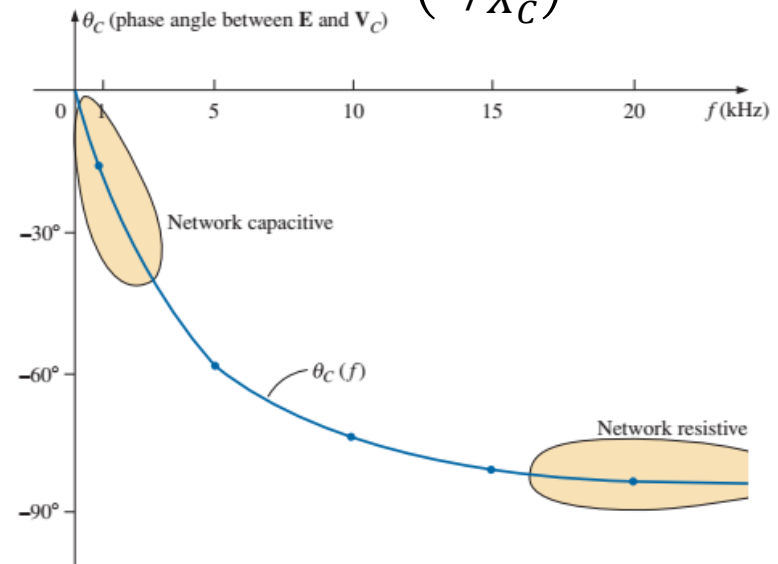


FIG. 15.59


The phase angle between E and V_C versus frequency for the circuit in Fig. 15.50.

Calculate $|V_C|$ and $\angle V_C$ at:
 100Hz, 3.18kHz, 20kHz

frequency	V_C
100 Hz	10.0V \angle -1.8°
3.18 kHz	7.07V \angle -45°
20 kHz	1.57V \angle -81.0°




Frequency Response of a Series R-C Circuit – Multisim

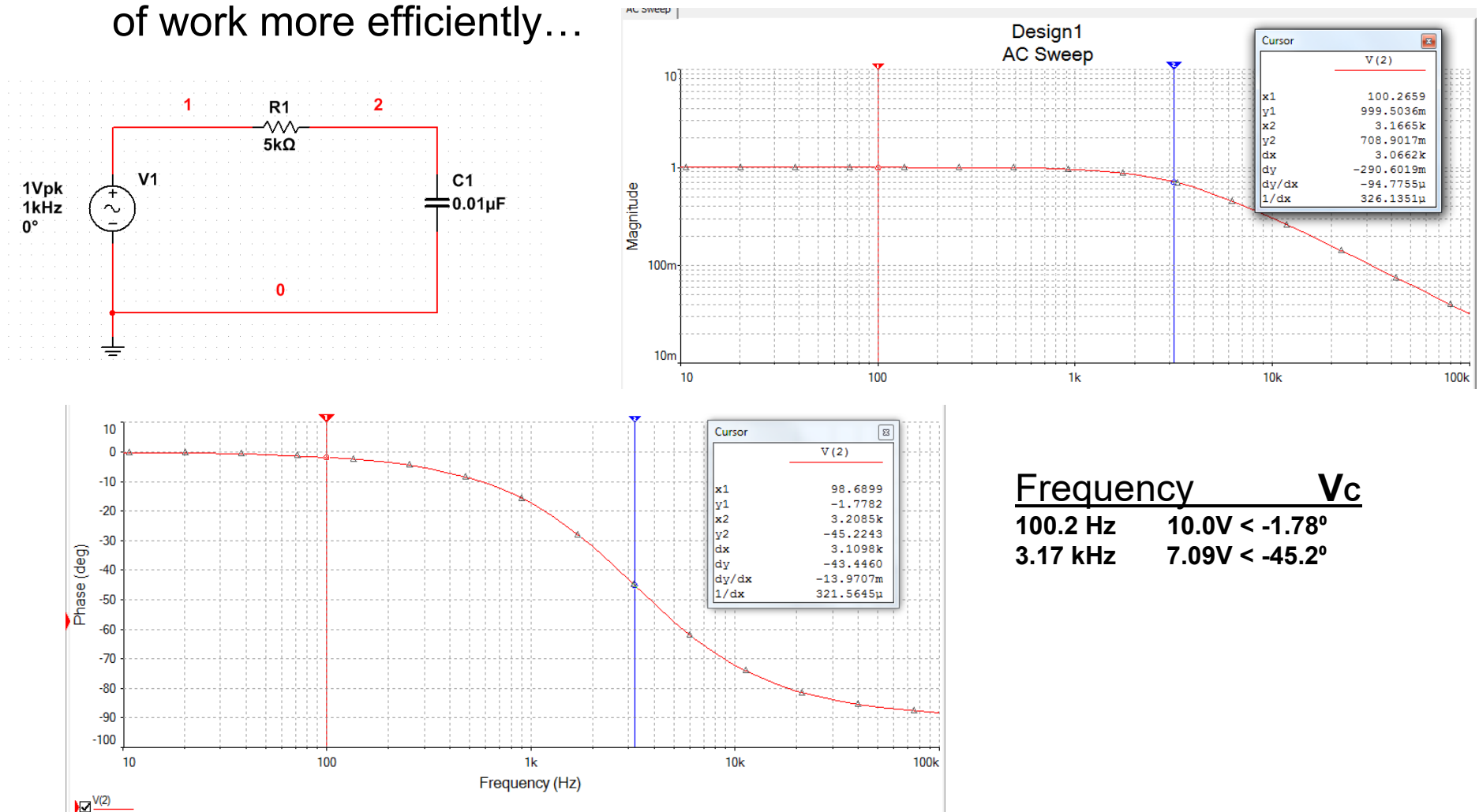- There is a great way to check your understanding and perform this kind of work more efficiently...



Frequency Response of a Series R-C Circuit – Multisim

What about Z_T ?

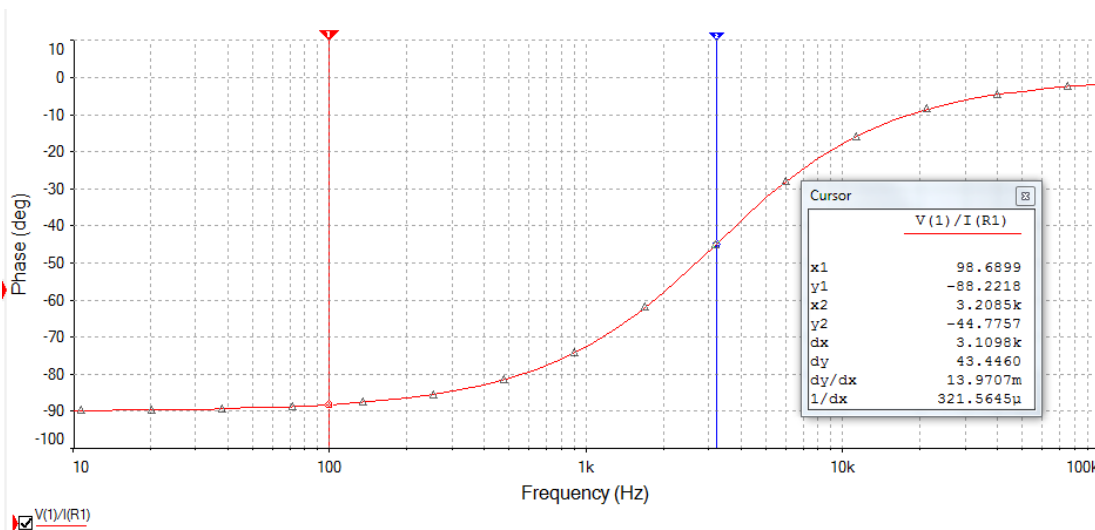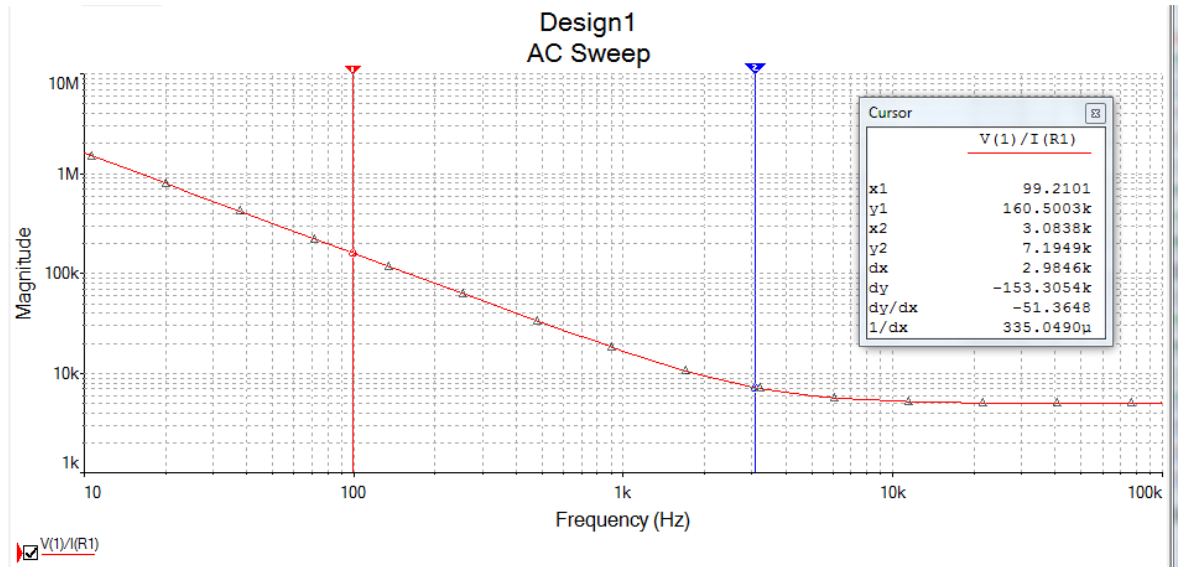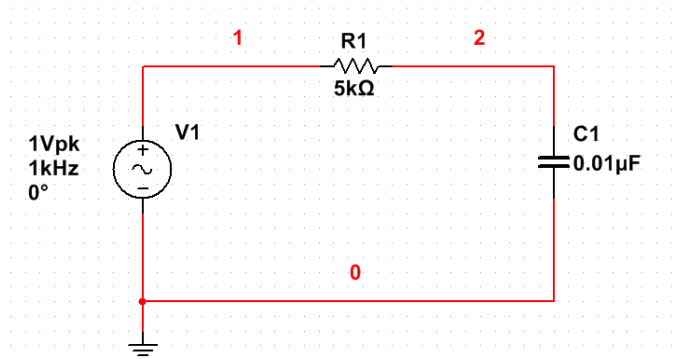

frequency	Z_T
~99 Hz	$160.5K\Omega < -88.2^\circ$
~3.1 kHz	$7.19K\Omega < -44.8^\circ$

Frequency Response of a Series R-C Circuit – Multisim

- Get familiar with Multisim for this kind of work
 - See the posted file to get started
 - Use Multisim to check your HW answers and text examples

