

Series Resonance

- Objectives
- Introduction
- Mechanical Example
- Series Circuit Resonance
 - Circuit properties
 - Quality factor
 - Z_T
 - Selectivity (bandwidth)
- In Class Problem
 - Similar to problems 1 and 3 (HW)

Series Resonance - Objectives

- Become familiar with the frequency response of a series resonant circuit and how to calculate the resonant frequency (f_s) and cutoff frequencies (f_1, f_2).
- Be able to calculate a tuned network's quality factor (Q), bandwidth (BW), and power levels at important frequency levels.
- Understand the impact of the quality factor on the frequency response of a series or parallel resonant network.


Some new vocabulary today

Series Resonance - Introduction

- Resonant (or tuned) circuits are fundamental to the operation of a wide variety of electrical and electronic systems in use today.
- The resonant circuit is a combination of R, L, and C elements having a frequency response characteristic.
- A resonant electrical circuit must have both inductance and capacitance. In addition, resistance will always be present due either to the lack of ideal elements or to control the shape of the resonance curve.
- When resonance occurs due to the application of the proper frequency (f_r), the energy absorbed by one reactive element is the same as that released by another reactive element within the system.

One example receiver architecture

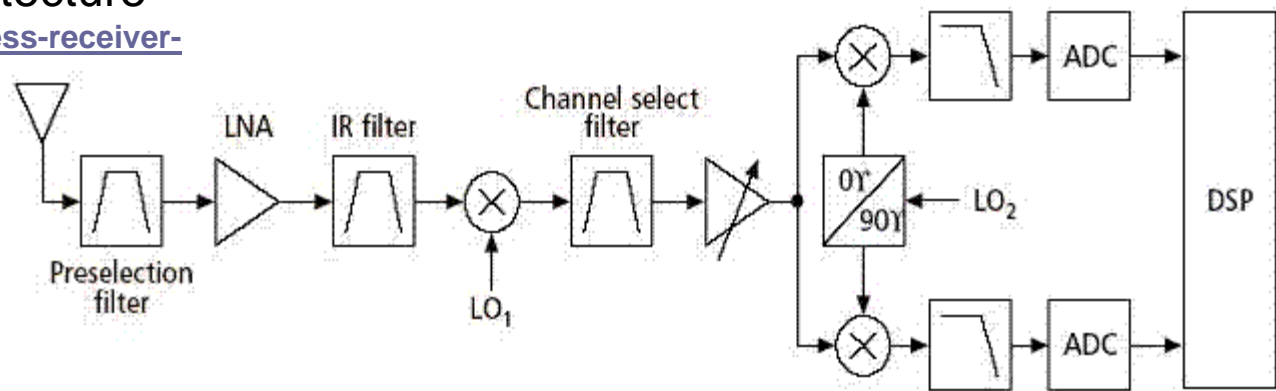(from <http://analog.intgckts.com/wireless-receiver-architectures/>)




Resonance – Mechanical Example (from the text)



<https://youtu.be/nFzu6CNtqec>

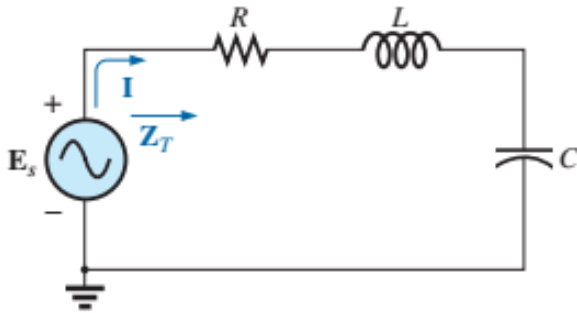Series Resonance – Circuit Properties at Resonance



The resonant frequency (ω for $X_L = X_C$) is:

$$\omega_s = \frac{1}{\sqrt{LC}} \text{ r/s}$$

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$

f = hertz (Hz)
 L = henries (H)
 C = farads (F)

At Resonance ($f = f_s$)

$$Z_{T_s} = R$$

$$F_{p_s} = 1$$

$$\mathbf{I} = \frac{E \angle 0^\circ}{R \angle 0^\circ} = \frac{E}{R} \angle 0^\circ$$

$$\left. \begin{aligned} V_L &= (I \angle 0^\circ)(X_L \angle 90^\circ) = IX_L \angle 90^\circ \\ V_C &= (I \angle 0^\circ)(X_C \angle -90^\circ) = IX_C \angle -90^\circ \end{aligned} \right\} 180^\circ \text{ out of phase}$$

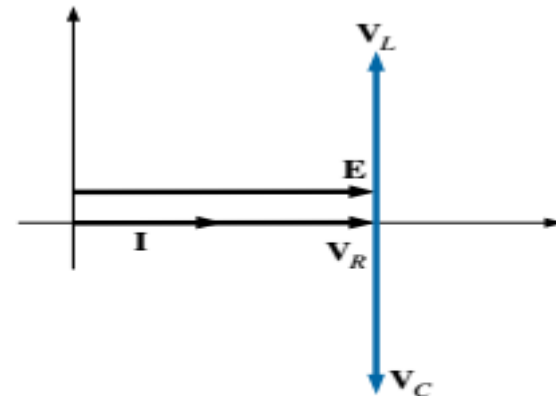


FIG. 21.4

Phasor diagram for the series resonant circuit at resonance.


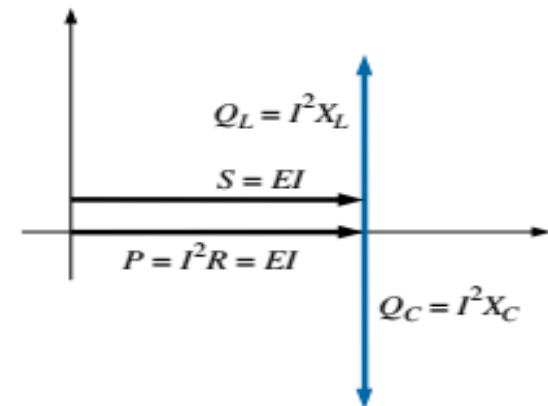


FIG. 21.5

Power triangle for the series resonant circuit at resonance.

Series Resonance –Quality Factor (Q)

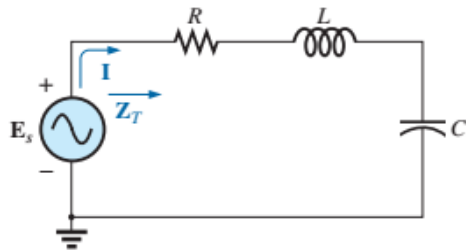

$$Q_s = \frac{\text{reactive power}}{\text{average power}}$$

Or (since X_L and X_C are equal at f_s)

$$Q_s = \frac{I^2 X_L}{I^2 R}$$

Hence:

$$Q_s = \frac{X_L}{R} = \frac{\omega_s L}{R}$$

For a coil (with a series resistance of R_l):

$$Q_s = Q_{\text{coil}} = Q_l = \frac{X_L}{R_l} \quad R = R_l$$

At higher frequencies Q drops off due to the skin effect (see chapter 20) and winding capacitance

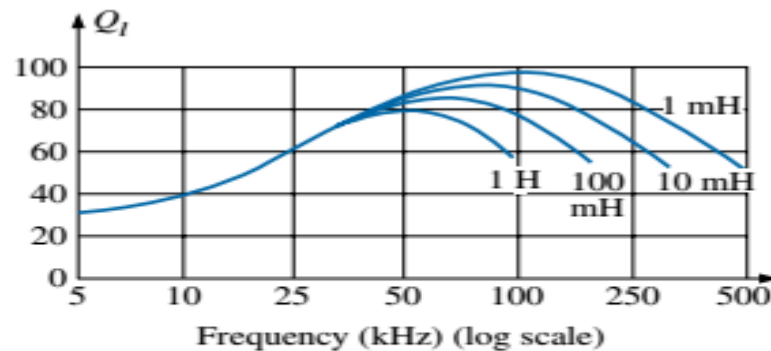


FIG. 21.7

The inductors used in Lab Project #2:



Features


- Current rating up to 1.2 A
- Dielectric strength: 500 VRMS
- RoHS compliant*

78F Series Conformal Coated

Electrical Specifications (@ 25 °C)

Part Number	Value (μH)	Q Min.	Test Frequency (MHz)	SRF (MHz) Min.	DCR (Ω) Max.	IDC (mA) Max.
78FR10K-RC	$0.10 \pm 10\%$	20	25	400	0.060	1200
78FR12K-RC	$0.12 \pm 10\%$	20	25	400	0.070	1200
78FR15K-RC	$0.15 \pm 10\%$	20	25	380	0.070	1200
78FR18K-RC	$0.18 \pm 10\%$	20	25	380	0.073	1150

Series Resonance – $Z_T(f)$

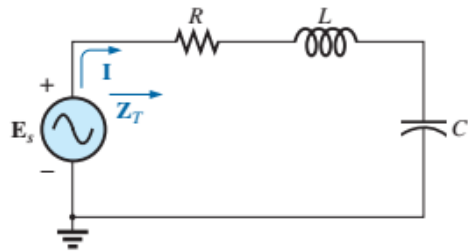

$$Z_T = R + jX_L - jX_C$$


$$Z_T = R + j(X_L - X_C)$$

So the magnitude of Z_T is:


$$Z_T = \sqrt{R^2 + (X_L - X_C)^2}$$

Or, as a function of frequency:
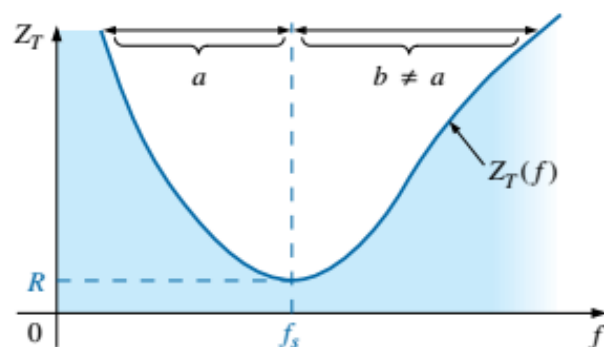
$$Z_T(f) = \sqrt{[R(f)]^2 + [X_L(f) - X_C(f)]^2}$$



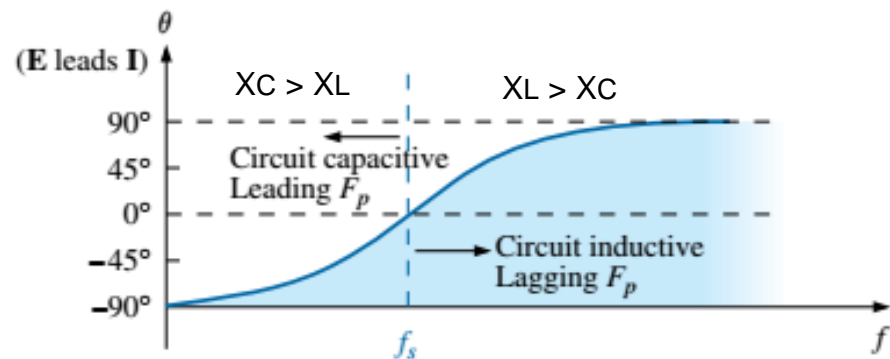
$$\theta_{Z_T} = \tan^{-1} \frac{(X_L - X_C)}{R}$$



$f < f_s$: network capacitive; **I** leads **E**
 $f > f_s$: network inductive; **E** leads **I**
 $f = f_s$: network resistive; **E** and **I** are in phase

In general, we consider R to remain constant over frequency (depends on the material and frequency range)

Series Resonance – Selectivity

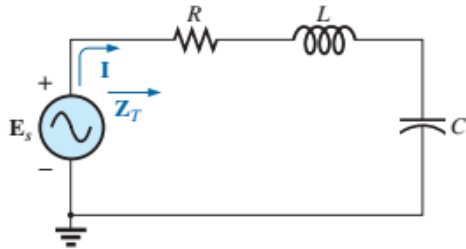

Looking at the current as a function of frequency:

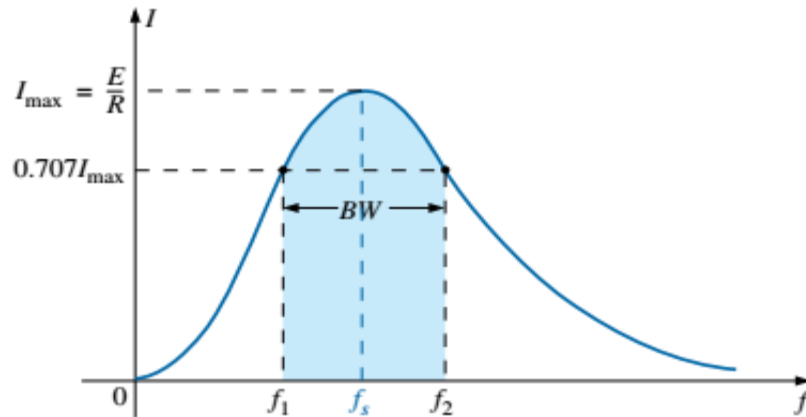


FIG. 21.15

I versus frequency for the series resonant circuit.

At f_1 and f_2 :

$$P_{\text{HPF}} = \frac{1}{2} P_{\text{max}}$$


$$\text{BW} == f_2 - f_1$$

Check:

$$P_{\text{max}} = I_{\text{max}}^2 R$$

$$P_{\text{HPF}} = I^2 R = (0.707 I_{\text{max}})^2 R = (0.5)(I_{\text{max}}^2 R) = \frac{1}{2} P_{\text{max}}$$

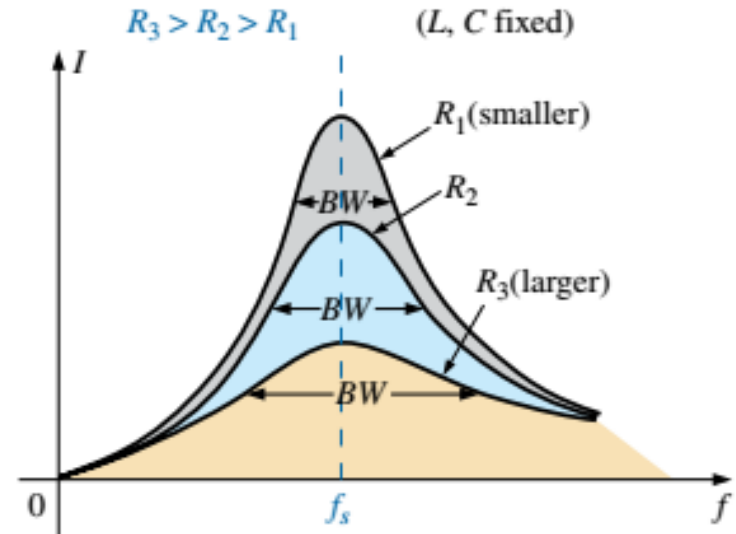Set of selectivity curves for different R values)



Lower Q (higher R):

- Larger BW
- Decreased selectivity

Higher Q (lower R):

- Smaller BW
- Increased selectivity

Series Resonance – Selectivity

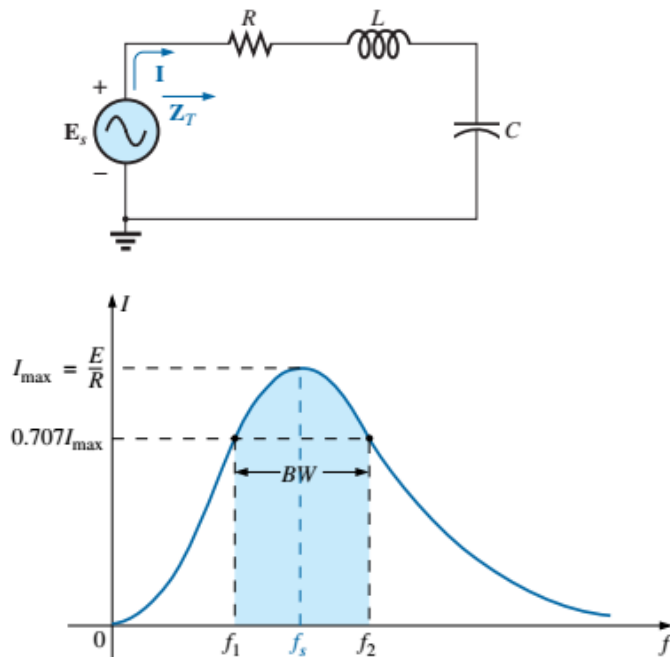


FIG. 21.15

I versus frequency for the series resonant circuit.

For $Q \geq 10$, assume symmetry about f_s
Text -> "High Q"

Values for f_1 and f_2 based on circuit elements (equations developed in the text):

$$f_2 = \frac{1}{2\pi} \left[\frac{R}{2L} + \frac{1}{2} \sqrt{\left(\frac{R}{L} \right)^2 + \frac{4}{LC}} \right] \quad (\text{Hz})$$

$$f_1 = \frac{1}{2\pi} \left[-\frac{R}{2L} + \frac{1}{2} \sqrt{\left(\frac{R}{L} \right)^2 + \frac{4}{LC}} \right] \quad (\text{Hz})$$

Subtracting the equations above yields:

$$BW = f_2 - f_1 = \frac{R}{2\pi L}$$

But, expanding and substituting yields:

$$BW = \frac{R}{2\pi L} = \left(\frac{1}{2\pi} \right) \left(\frac{R}{L} \right) = \left(\frac{f_s}{\omega_s} \right) \left(\frac{\omega_s}{Q_s} \right)$$


Hence:

$$BW = \frac{f_s}{Q_s}$$

$$\frac{f_2 - f_1}{f_s} = \frac{1}{Q_s}$$

So we can determine f_1 and f_2 based on knowing f_s and Q or determine Q knowing (measuring) f_s and f_1, f_2

Series Resonance – In Class Problem

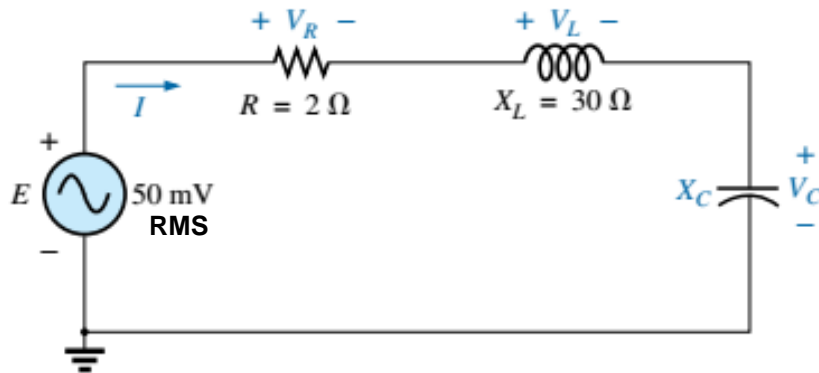

Find:

- a) X_C for resonance
- b) Z_T at resonance**
- c) $|I|$ at resonance
- d) $|V_R|$, $|V_L|$, $|V_C|$ at resonance
- e) Q , the quality factor
- f) The power dissipated by the circuit at resonance