

BPF with Loading

☐ Brief Review

- Parallel Resonance

☐ BPF with Source and Load (similar to lab project 2)

- Analysis (assumes $Q \geq 10$)

- ☐ f_p, Q_p, BW , voltage gain

- Simulation verification and interpretation


- Low frequency “tail” explanation

☐ BPF with Source and Load – In class problem


- Same circuit as above with matched impedances

Parallel Resonance – Review/Summary


General Parallel
R-L-C Circuit

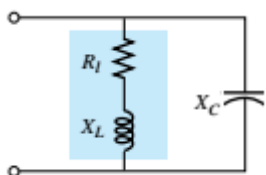

Converted to parallel equivalent

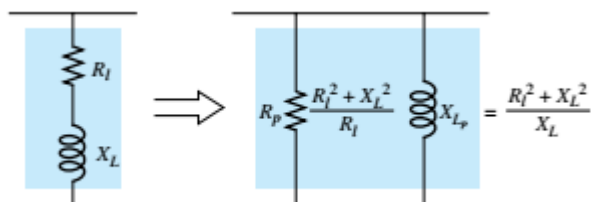

Simplified ($Q \geq 10$)

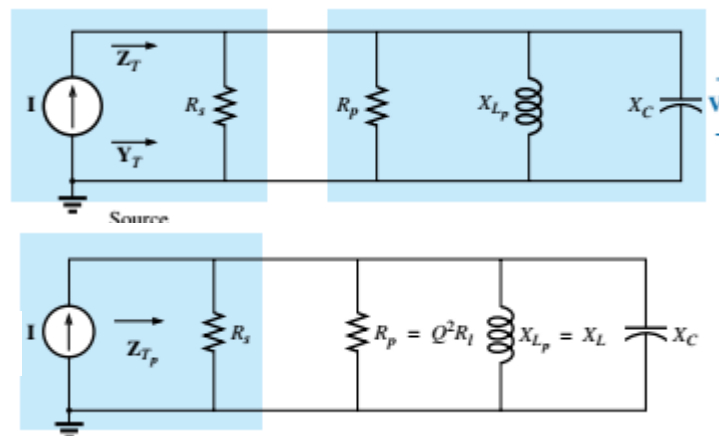


General circuit

TABLE 21.2

Parallel resonant circuit ($f_s = 1/(2\pi\sqrt{LC})$).

	Any Q_l	$Q_l \geq 10$	$Q_l \geq 10, R_s \gg Q_l^2 R_l$
f_p	$f_s \sqrt{1 - \frac{R_l^2 C}{L}}$	f_s	f_s
f_m	$f_s \sqrt{1 - \frac{1}{4} \left[\frac{R_l^2 C}{L} \right]}$	f_s	f_s
Z_{T_p}	$R_s \parallel R_p = R_s \parallel \left(\frac{R_l^2 + X_L^2}{R_l} \right)$	$R_s \parallel Q_l^2 R_l$	$Q_l^2 R_l$
Z_{T_m}	$R_s \parallel Z_{R-L} \parallel Z_C$	$R_s \parallel Q_l^2 R_l$	$Q_l^2 R_l$
Q_p	$\frac{Z_{T_p}}{X_{L_p}} = \frac{Z_{T_p}}{X_C}$	$\frac{Z_{T_p}}{X_L} = \frac{Z_{T_p}}{X_C}$	Q_l
BW	$\frac{f_p}{Q_p}$ or $\frac{f_m}{Q_p}$	$\frac{f_p}{Q_p} = \frac{f_s}{Q_p}$	$\frac{f_p}{Q_l} = \frac{f_s}{Q_l}$
I_L, I_C	Network analysis	$I_L = I_C = Q_l I_T$	$I_L = I_C = Q_l I_T$

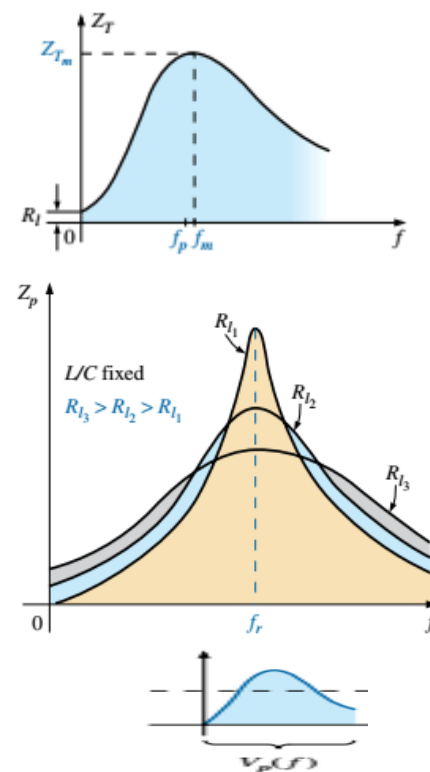

Parallel Resonance – Focus on $Q \geq 10$

Simplified Circuit
($Q \geq 10$)


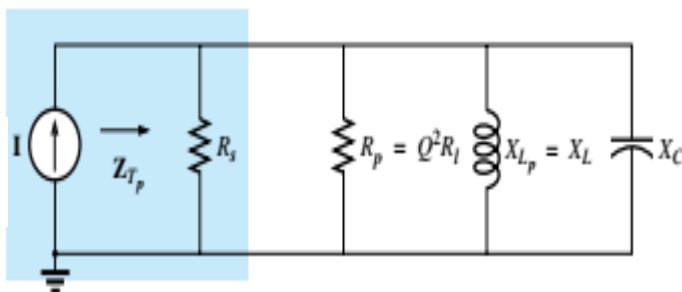


TABLE 21.2


Parallel resonant circuit ($f_s = 1/(2\pi\sqrt{LC})$).

	Any Q_l	$Q_l \geq 10$	$Q_l \geq 10, R_s \gg Q_l^2 R_l$
f_p	$f_s \sqrt{1 - \frac{R_l^2 C}{L}}$	f_s	f_s
f_m	$f_s \sqrt{1 - \frac{1}{4} \left[\frac{R_l^2 C}{L} \right]}$	f_s	f_s
Z_{T_p}	$R_s \parallel R_p = R_s \parallel \left(\frac{R_l^2 + X_L^2}{R_l} \right)$	$R_s \parallel Q_l^2 R_l$	$Q_l^2 R_l$
Z_{T_m}	$R_s \parallel Z_{R-L} \parallel Z_C$	$R_s \parallel Q_l^2 R_l$	$Q_l^2 R_l$
Q_p	$\frac{Z_{T_p}}{X_{L_p}} = \frac{Z_{T_p}}{X_C}$	$\frac{Z_{T_p}}{X_L} = \frac{Z_{T_p}}{X_C}$	Q_l
BW	$\frac{f_p}{Q_p}$ or $\frac{f_m}{Q_p}$	$\frac{f_p}{Q_p} = \frac{f_s}{Q_p}$	$\frac{f_p}{Q_l} = \frac{f_s}{Q_l}$
I_L, I_C	Network analysis	$I_L = I_C = Q_l I_T$	$I_L = I_C = Q_l I_T$


BPF with Source and Load (Analysis)

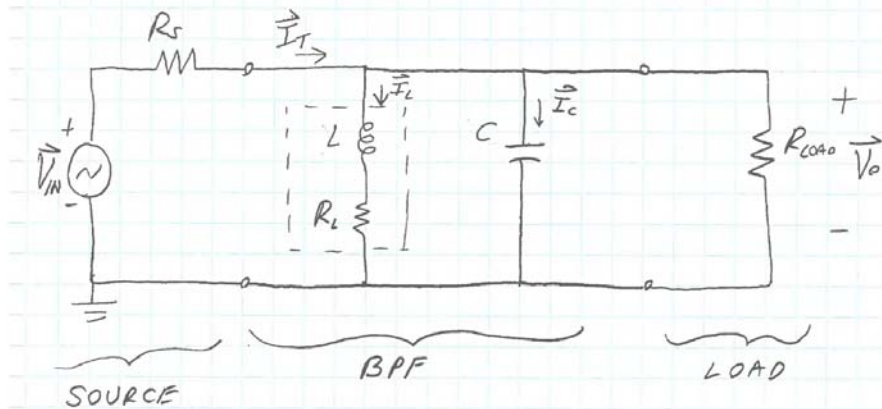

EQUIV TO: (For $Q_p \geq 10$)

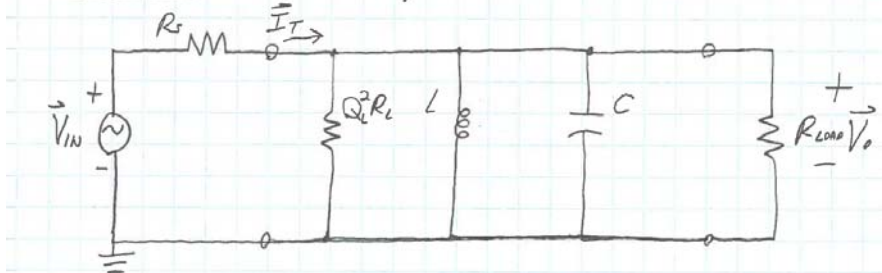

OR:

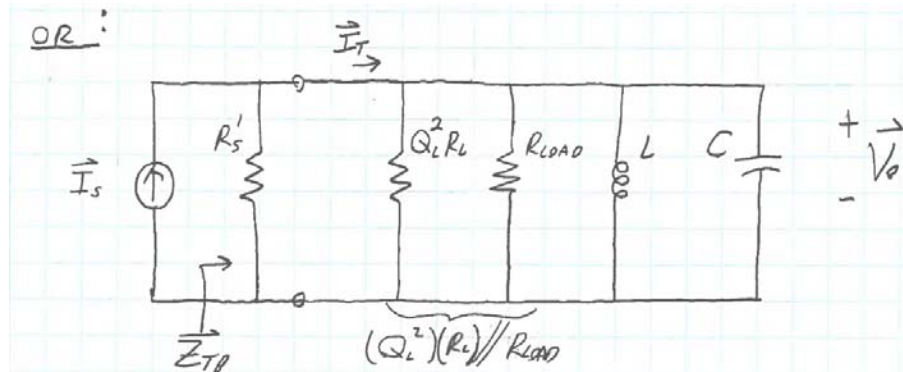

From the chart ($Q \geq 10$):

$$f_p \approx f_s = \frac{1}{2\pi\sqrt{LC}}$$

Defined below, at resonance ($X_L = X_C$)

$$\vec{Z}_{Tp} = R_S // Q_L^2 R_L \longrightarrow$$

For this circuit becomes:

$$R_S' // Q_L^2 R_L // R_{LOAD}$$

$$Q_L = \frac{X_L}{R_L}$$

From the chart ($Q \geq 10$):

$$Q_p = \frac{|\vec{Z}_{Tp}|}{X_L} = \frac{|\vec{Z}_{Tp}|}{X_C}$$

$$BW = \frac{f_p}{Q_p}$$


Also at resonance

$$|\vec{I}_L| = |\vec{I}_C| = Q_L |\vec{I}_T| \longrightarrow$$


For this circuit (at resonance):

$$\vec{I}_T = \frac{\vec{V}_{IN}}{R_S + (Q_L^2 R_L // R_{LOAD})}$$


BPF with Source and Load (Analysis)

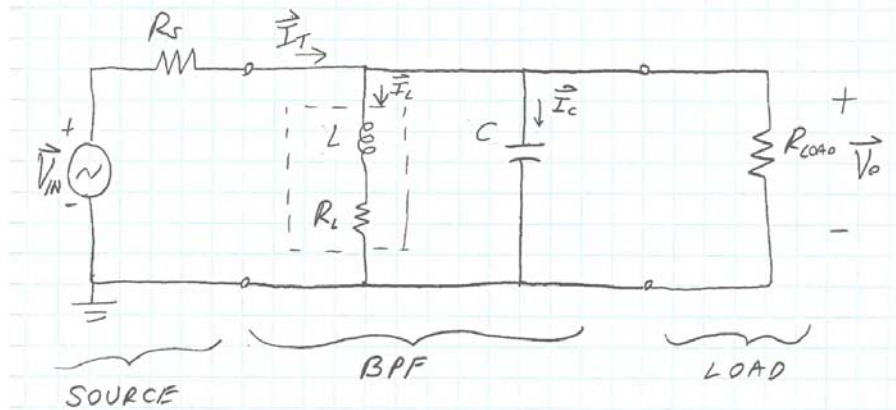

EQUIV TO : (For $Q_p \geq 10$)

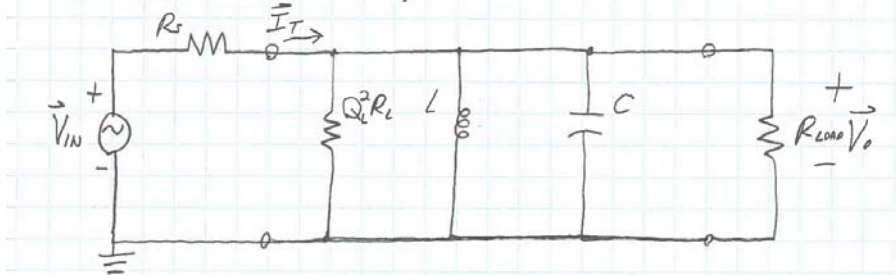

OR :

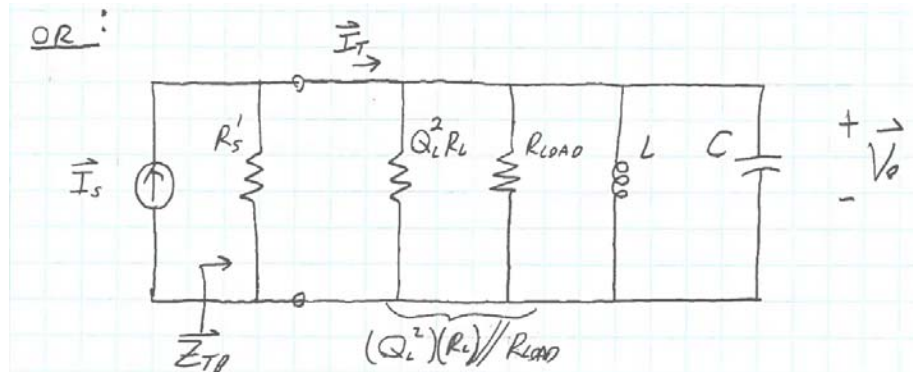

$$\frac{\vec{V}_O}{\vec{V}_{IN}} \text{ AT RESONANCE !}$$

Using the $Q > 10$ equivalent circuit:

$$\vec{V}_O = \vec{I}_T (Q_L^2 R_L // R_{LOAD})$$

Substituting for \vec{I}_T :

$$\vec{I}_T = \frac{\vec{V}_{IN}}{R_S + (Q_L^2 R_L // R_{LOAD})}$$



$$\vec{V}_O = \left[\frac{\vec{V}_{IN}}{R_S + (Q_L^2 R_L // R_{LOAD})} \right] (Q_L^2 R_L // R_{LOAD})$$

Therefore, we have:

$$\frac{\vec{V}_O}{\vec{V}_{IN}} = \frac{Q_L^2 R_L // R_{LOAD}}{R_S + Q_L^2 R_L // R_{LOAD}}$$

at resonance

BPF with Source and Load (Example)

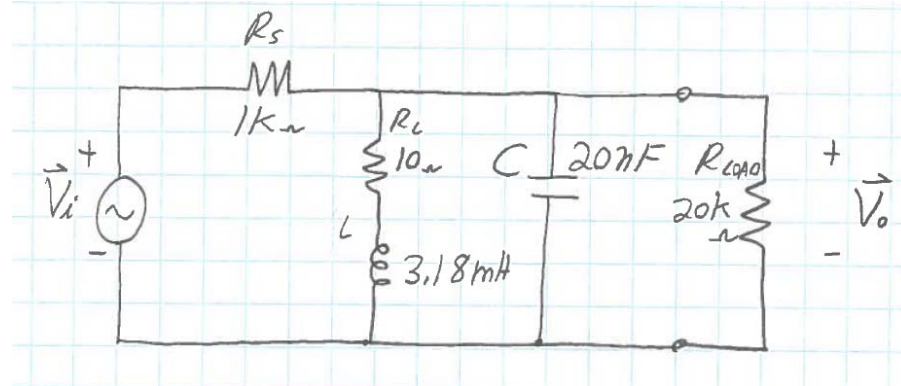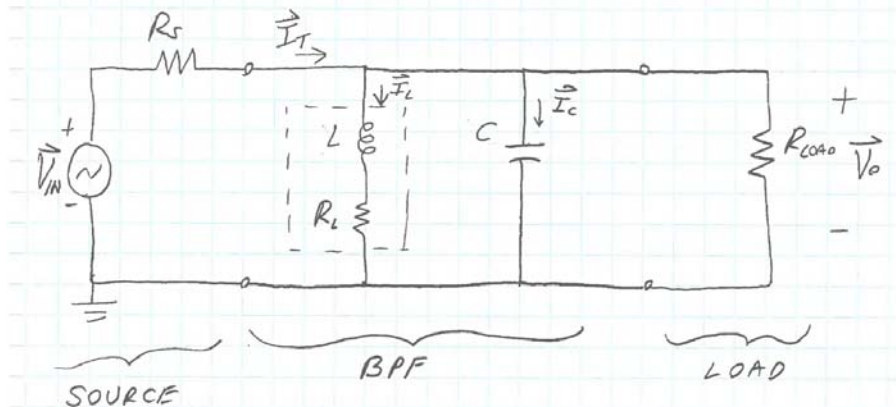

$$f_p = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{(3.18mH)(20nF)}} =$$

$$\boxed{19.96kHz}$$

$$\vec{Z}_{TP} = R_s' // Q_L^2 R_L // R_{LOAD}$$

But the inductor Q is:

$$Q_L = \frac{X_L}{R_L} = \frac{2\pi f L}{R_L} =$$

$$\frac{2\pi(19.96kHz)(3.18mH)}{10\Omega}$$

$$\underline{Q_L = 39.9}$$

So $\mathbf{Z_{TP}}$ becomes:

$$\therefore \vec{Z}_{TP} = 1000\Omega // (39.9)^2 (10\Omega) // 20k\Omega$$

$$= \boxed{898.6\Omega}$$



And the (loaded) circuit Q is:

$$Q_p = \frac{|\vec{Z}_{TP}|}{X_L} = \frac{898.6\Omega}{398.8\Omega}$$

$$= \boxed{2.25}$$

Note – Our assumption of $Q \geq 10$ **is NOT satisfied**, we'll check our results via simulation soon

BPF with Source and Load (Example)

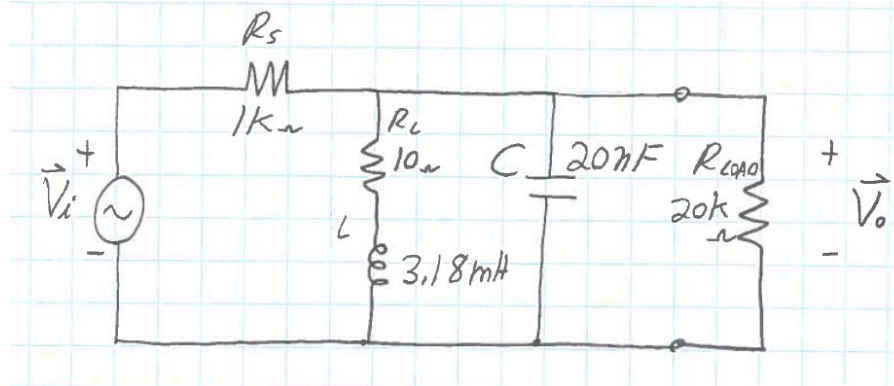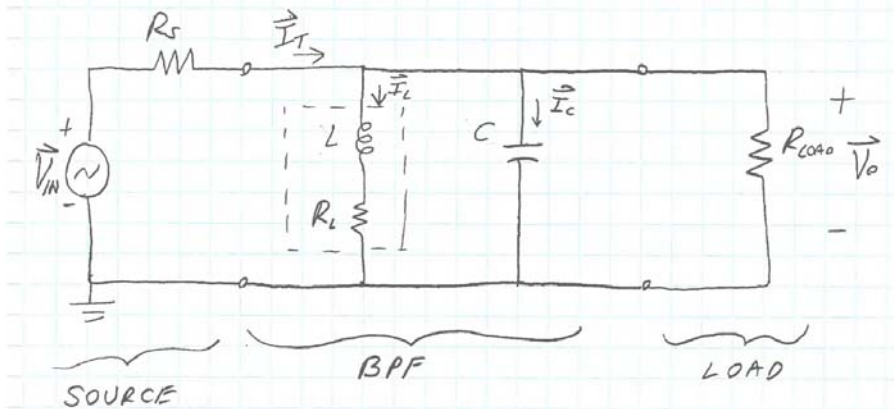

Calculating the BW and voltage gain:

$$BW = \frac{f_p}{Q_p} = \boxed{8.87 \text{ KHz}}$$

$$\frac{\vec{V}_o}{\vec{V}_i} = \frac{Q_p^2 R_L // R_{LOAD}}{R_s + Q_p^2 R_L // R_{LOAD}} =$$


$$\frac{8.85 k\Omega}{9.85 k\Omega} = \boxed{0.899}$$

In dB (taking $20\log_{10}(V_o/V_i)$):

$$\boxed{-0.92 \text{ dB}}$$

On to simulation to check our work...

BPF with Source and Load (Simulation)

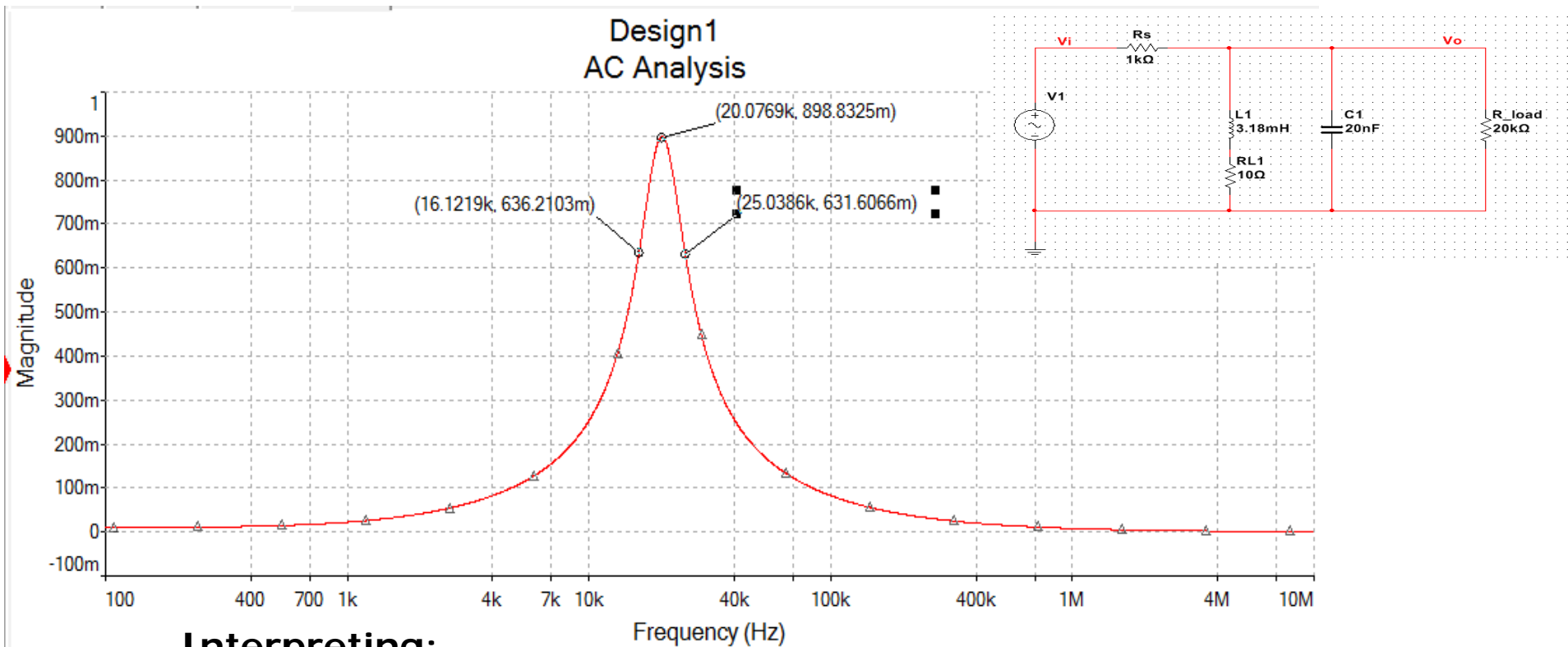

Interpreting:

$f_p = 20.08 \text{ kHz}$ $\frac{\bar{V}_o}{\bar{V}_i} = 0.899$

$BW = f_2 - f_1 \sim 25.04 \text{ kHz} - 16.12 \text{ kHz}$
 $= 8.92 \text{ kHz}$


$Q_p = \frac{f_p}{BW} = \frac{20.08 \text{ kHz}}{8.92 \text{ kHz}} = 2.25$

Compared to (calculations)

$f_p = 19.96 \text{ kHz}$, $V_o/V_i = 0.899$

$BW = 8.87 \text{ kHz}$, $Q_p = 2.25$

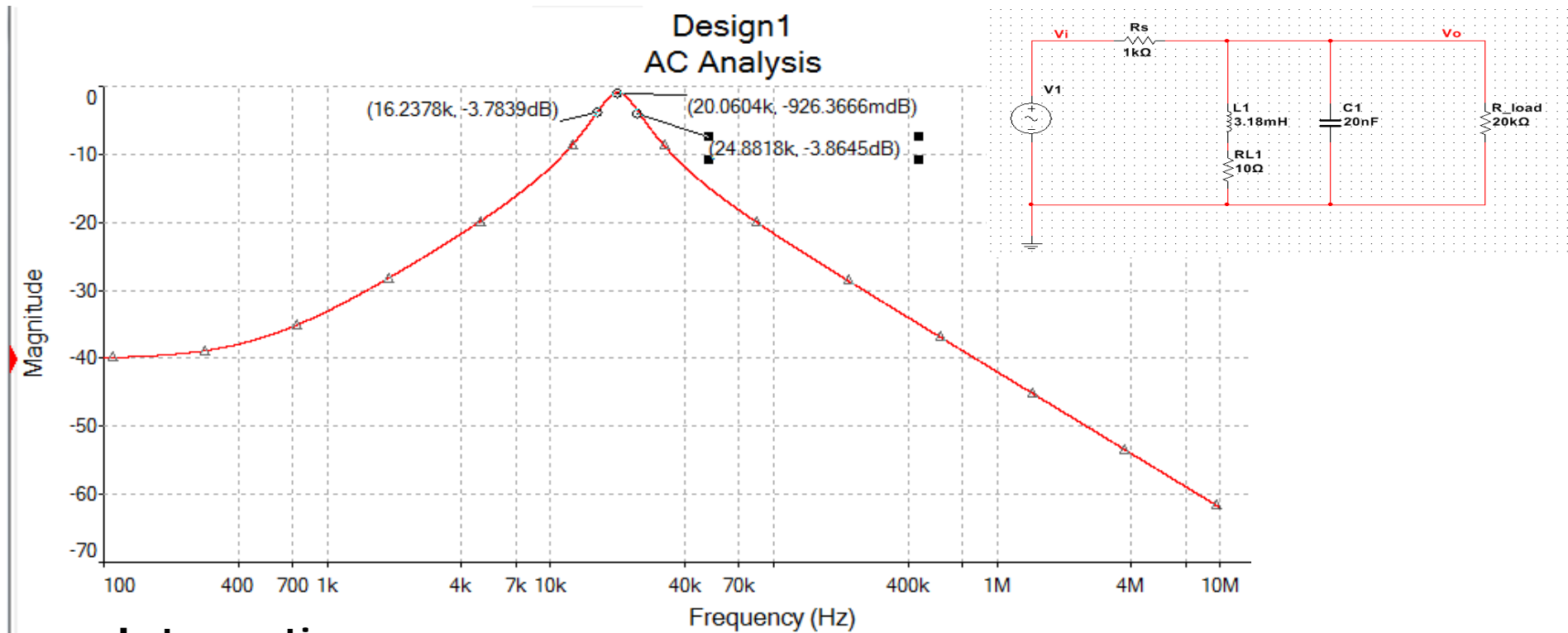BPF with Source and Load (Simulation in dB)



Interpreting:

$$f_p = 20.06 \text{ kHz}, V_o/V_i = -0.93\text{dB}$$

$$\text{BW} \sim f_2 - f_1 = 8.64 \text{ kHz}$$

$$Q_p = f_p/\text{BW} = 2.32$$

Explain:


-40dB voltage gain at low frequencies vs,
continuing decline in voltage gain at high frequencies

Compared to (calculations)

$$f_p = 19.96 \text{ kHz}, V_o/V_i = 0.899 \text{ (or } -0.92\text{dB)}$$

$$\text{BW} = 8.87 \text{ kHz}, Q_p = 2.25$$

BPF with Source and Load - ICP

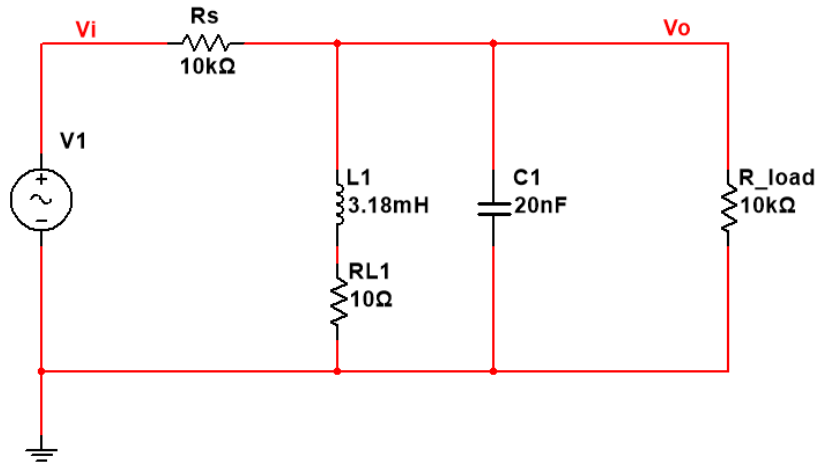

Find:

- a) f_p (resonant frequency)
- b) Q_p (circuit Q or "loaded" Q)
- c) Bandwidth
- d) V_o/V_i (voltage gain at resonance)