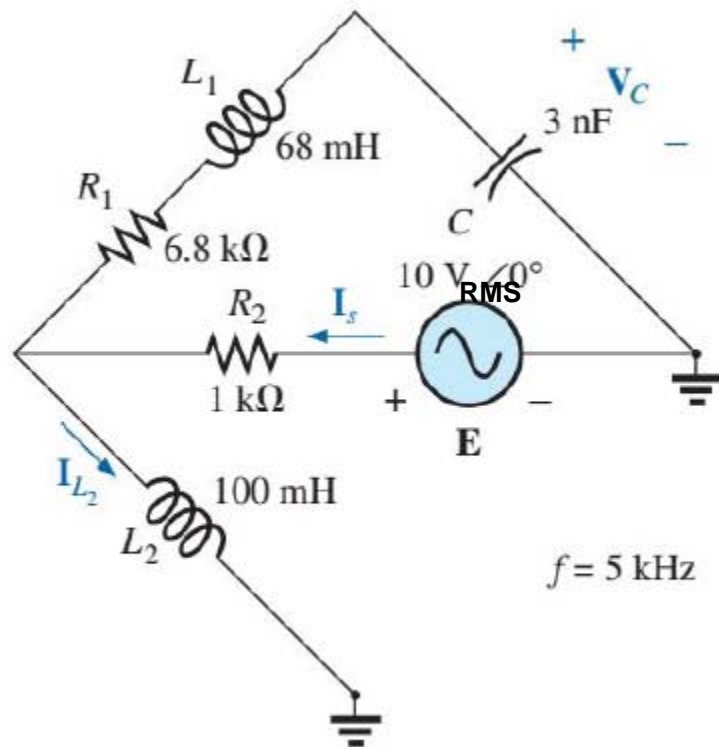


Ground – ICP (partial homework problem)



Find: The source current I_s and the voltage across L_2

FIG. 17.45