

Power-Factor Correction – In Class Problem

THE LOADING OF A FACTORY ON A 1000V,
60HZ SYSTEM INCLUDES:

20kW HEATING ($F_p = 1$)

10kW INDUCTION MOTORS ($F_p = 0.7$ LAGGING)

5kW LIGHTING ($F_p = 0.85$ LAGGING)

(a) ESTABLISH THE POWER TRIANGLE FOR THE TOTAL
LOADING ON THE SUPPLY

(b) FIND THE CAPACITOR REQUIRED TO CORRECT THE
POWER FACTOR TO $F_p = 1$

(c) FIND \vec{I}_s COMPENSATED & \vec{I}_s UNCOMPENSATED
(USE $\vec{S} = \vec{V} \vec{I}^*$)

Approach:

- (a) We know **S1** = 20kW + j0VAR, find **S2** and **S3** using the given F_p info and add to get **ST** and the power triangle
- (b) Use **S** = **V** **Is*** to find **Ic** and hence **Zc** and finally C
- (c) Use **S** = **V** **Is*** to find **Is** for each case

Power-Factor Correction – In Class Problem

THE LOADING OF A FACTORY ON A 1000V, 60Hz SYSTEM INCLUDES:

20kW HEATING ($F_p = 1$)

10kW INDUCTION MOTORS ($F_p = 0.7$ LAGGING)


5kW LIGHTING ($F_p = 0.85$ LAGGING)

(Q) ESTABLISH THE POWER TRIANGLE FOR THE TOTAL LOADING ON THE SUPPLY

$$\begin{aligned} \vec{S}_1 &= 20\text{kW} + j0 \\ \vec{S}_2 &= 10\text{kW} + j \frac{Q_{L2}}{10,000} \quad \text{--- } F_p = 0.7 \\ \vec{S}_3 &= 5\text{kW} + j \frac{Q_{L3}}{10,000} \quad \text{--- } F_p = 0.85 \end{aligned} \quad \left. \vphantom{\begin{aligned} \vec{S}_1 \\ \vec{S}_2 \\ \vec{S}_3 \end{aligned}} \right\} \begin{array}{l} \text{FILL IN} \\ \text{THE BLANKS} \end{array}$$

LOAD 2
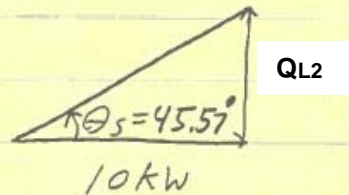
$$\begin{aligned} \theta_s &= \cos^{-1}(0.7) \\ &= \underline{45.57^\circ} \end{aligned}$$



$$\tan(\theta_s) = \frac{\text{OPP}}{\text{ADJ}} = \frac{Q_{L2}}{10,000}$$

LOAD 3 $\theta_s = \cos^{-1}(0.85) = \underline{31.79^\circ}$

$$Q_{L3} = (5\text{kW})(\tan(31.79^\circ))$$

$$\underline{Q_{L3} = 3.1\text{ kVAR}}$$

$$Q_{L2} = (10\text{kW})(\tan(45.57^\circ))$$

$$\underline{Q_{L2} = 10.2\text{ kVAR}}$$

Power-Factor Correction – In Class Problem

THE LOADING OF A FACTORY ON A 1000V, 60Hz SYSTEM INCLUDES:

20kW HEATING ($F_p = 1$)

10kW INDUCTION MOTORS ($F_p = 0.7$ LAGGING)

5kW LIGHTING ($F_p = 0.85$ LAGGING)

(Q) ESTABLISH THE POWER TRIANGLE FOR THE TOTAL LOADING ON THE SUPPLY

$$\begin{aligned} \vec{S}_1 &= 20\text{kW} + j0 \\ \vec{S}_2 &= 10\text{kW} + j \quad - F_p = 0.7 \\ \vec{S}_3 &= 5\text{kW} + j \quad - F_p = 0.85 \end{aligned} \left. \vphantom{\begin{aligned} \vec{S}_1 \\ \vec{S}_2 \\ \vec{S}_3 \end{aligned}} \right\} \begin{array}{l} \text{FILL IN} \\ \text{THE BLANKS} \end{array}$$

Becomes:

$$\vec{S}_1 = 20,000 + j0$$

$$\vec{S}_2 = 10,000 + j 10,200$$

$$\vec{S}_3 = 5,000 + j 3,100$$

$$\vec{S}_T = 35,000 + j 13,300$$

$$\downarrow$$


$$35\text{kW}$$

$$\downarrow$$

$$13.3\text{kVAR (L)}$$


$$\vec{S}_T = 37.44\text{kVA} \angle 20.81^\circ$$

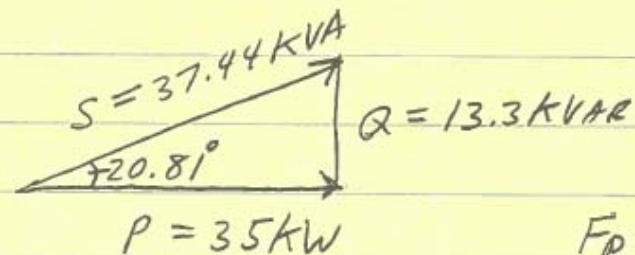So the power triangle for the uncompensated system is:




$$F_p = \cos(\theta_s) = 0.93$$

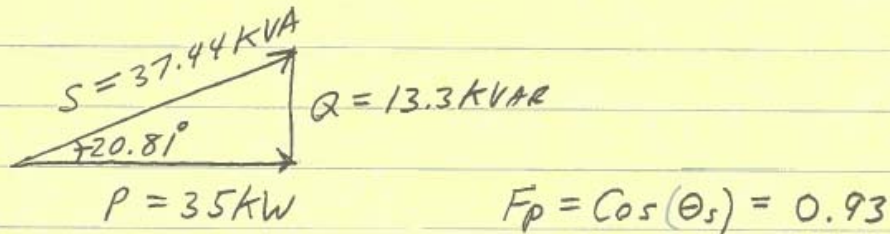Power-Factor Correction – In Class Problem



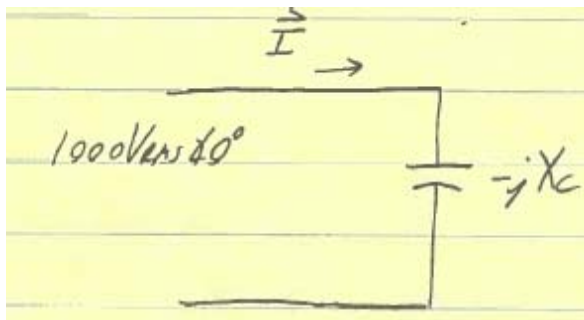(b) FIND THE CAPACITOR REQUIRED TO CORRECT THE POWER FACTOR TO $F_p = 1$

We need a 13.3KVAR (C) load to correct for or compensate for the 13.3KVAR (L):



$$\vec{I}^* = \frac{\vec{S}}{\vec{V}}$$

Using **I** and **V** to find **Zc**:

$$Z_c = \frac{\vec{V}}{\vec{I}} = \frac{1000 \text{ V}_{\text{rms}} \angle 0^\circ}{13.3 \text{ A}_{\text{rms}} \angle 90^\circ} = -j75.19 \Omega$$

Using **Zc** to find C:

$$X_c = 75.19 \Omega = \frac{1}{2\pi f C}$$

$$= \frac{1}{2\pi (60 \text{ Hz})(C)}$$

$$\vec{I}^* = \frac{(0 - j13,300) \text{ VA}}{1000 \text{ V}_{\text{rms}} \angle 0^\circ} = 13.3 \text{ A}_{\text{rms}} \angle -90^\circ$$

$$\vec{I} = 13.3 \text{ A}_{\text{rms}} \angle 90^\circ$$

$$C = \frac{1}{2\pi (60 \text{ Hz})(75.19 \Omega)} = \boxed{35.28 \mu\text{F}}$$

Power-Factor Correction – In Class Problem

(c) FIND \vec{I}_s COMPENSATED & \vec{I}_s UNCOMPENSATED
(USE $\vec{S} = \vec{V}\vec{I}^*$)

Uncompensated System (no C)

$$\vec{S}_T = 37.44 \text{ kVA} \angle 20.81^\circ$$

$$\therefore \vec{I}_s^* = \frac{37.44 \text{ kVA} \angle 20.81^\circ}{1000 \text{ V}_{\text{RMS}} \angle 0^\circ}$$

$$= 37.44 \text{ A}_{\text{RMS}} \angle 20.81^\circ$$

$$\boxed{\vec{I}_s = 37.44 \text{ A}_{\text{RMS}} \angle -20.81^\circ}$$

Compensated System (C = 35.28 μF)

$$\vec{S}_T = (37.44 \text{ kVA} \angle 20.81^\circ) + (0 - j 13.3 \times 10^3)$$

$$\therefore \vec{S}_T = 35 \text{ kVA} \angle 0^\circ$$

$$\vec{I}_s^* = \frac{35 \text{ kVA} \angle 0^\circ}{1000 \text{ V}_{\text{RMS}} \angle 0^\circ} = 35 \text{ A}_{\text{RMS}} \angle 0^\circ$$

$$\text{Hence } I_s = 35 \text{ A}_{\text{RMS}} < 0^\circ$$

Note the reduction in supply current from 37.44 A_{RMS} to 35 A_{RMS} while the loads experienced no differences in voltage or current.