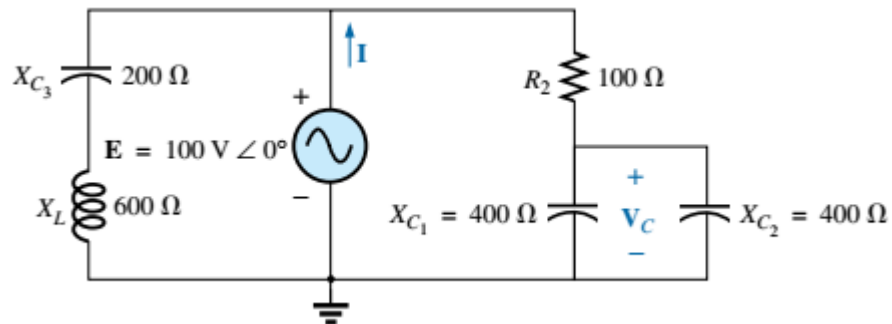


## In Class Problem



Find:  $I$ ,  $P_{R2}$

(one possible) Strategy/Plan 1<sup>st</sup>

- 1) Combine  $R_2$ ,  $C_1$ ,  $C_2 \rightarrow Z_1$
- 2) Combine  $C_3$ ,  $L \rightarrow Z_2$
- 3) Analyze the parallel circuit

- ☐  $I$
- ☐  $P_{R2}$


$$R_2, C_1, C_2 \Rightarrow Z_1 = 100 \Omega + (-j400 \Omega) // (-j400 \Omega)$$

$$(100 - j200) \Omega = 223.6 \Omega \angle -63.4^\circ$$

$$C_3, L \Rightarrow Z_2 = -j200 + j600$$

$$= j400 \Omega \text{ or } 400 \Omega \angle 90^\circ$$

ANALYZE :

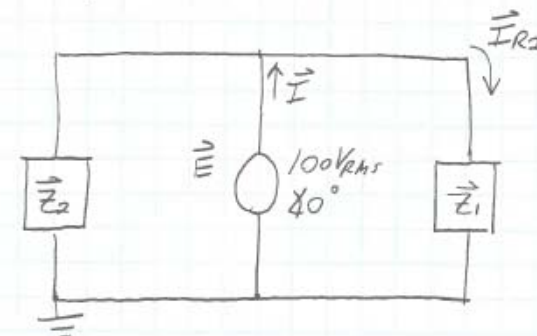

Finding  $I$ :


$$\vec{I} = \frac{\vec{E}}{\vec{Z}_1 // \vec{Z}_2}$$

$$\vec{I} = \frac{100 V_{rms} \angle 0^\circ}{(223.6 \Omega \angle -63.4^\circ) // (400 \Omega \angle 90^\circ)}$$

$$\vec{I} = \frac{100 V_{rms} \angle 0^\circ}{400 \Omega \angle -36.87^\circ}$$

$$\boxed{\vec{I} = 250 mA_{rms} \angle 36.9^\circ}$$

## In Class Problem

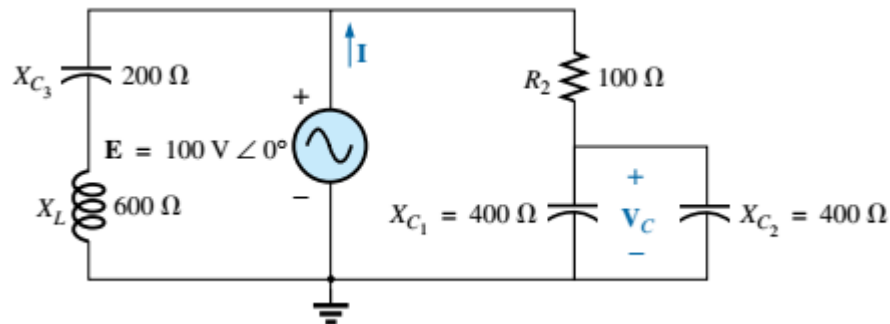


Find:  $I$ ,  $P_{R2}$

(one possible) Strategy/Plan 1<sup>st</sup>

- 1) Combine  $R_2$ ,  $C_1$ ,  $C_2 \rightarrow Z_1$
- 2) Combine  $C_3$ ,  $L \rightarrow Z_2$
- 3) Analyze the parallel circuit

- ☐  $I$
- ☐  $P_{R2}$

ANALYZE:

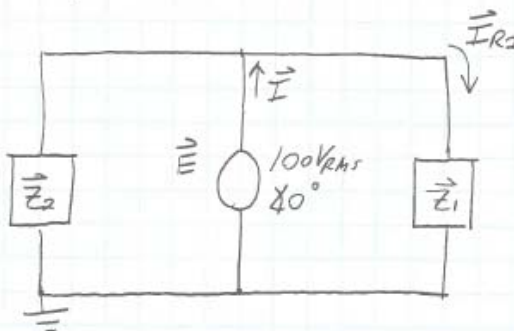

Finding  $P_{R2}$ :

$$P_{R2} = |\vec{I}_{R2_{RMS}}|^2 \cdot R_2$$

$$\vec{I}_{R2} = \vec{I} \left( \frac{\vec{Z}_1 // \vec{Z}_2}{\vec{Z}_1} \right)$$

$$= 250 \text{ mA}_{RMS} \angle 36.9^\circ \left( \frac{400 \Omega \angle -36.9^\circ}{223.6 \Omega \angle -63.4^\circ} \right)$$

$$\vec{I}_{R2} = 447.2 \text{ mA}_{RMS} \angle 63.4^\circ$$

$$\therefore P_{R2} = (447.2 \text{ mA}_{RMS})^2 \cdot 100 \Omega = \boxed{20 \text{ W}}$$

An easy way to check this result?

CHECK:  $P_{AVE} = |\vec{V}_{RMS}| \cdot |\vec{I}_{RMS}| \cdot \cos(\theta)$

$$= (100 \text{ V}_{RMS}) (250 \text{ mA}_{RMS}) \underbrace{\cos(0^\circ - 36.9^\circ)}_{0.8}$$

$$\boxed{P_{AVE} = 20 \text{ W}} \quad \checkmark$$