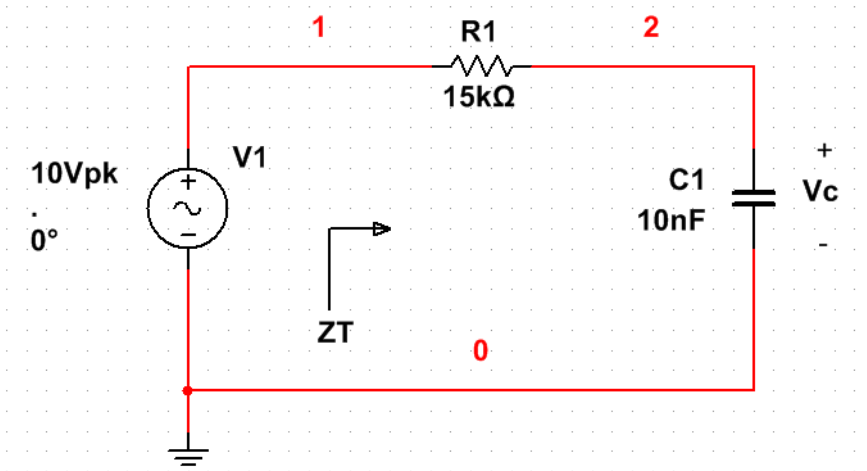


Series R-C Circuit Analysis (ICP)




- What is the source voltage, **V1** in phasor form?
- Write an **equation** for the capacitive reactance, X_{C1}
- Write an **equation** for the total impedance magnitude $|Z_T|$
- Write an **equation** for the total impedance phase θ_T
- Draw the impedance diagram for the circuit at 1 kHz.
- Write an **equation** for the series current **I**
- Find the corner frequency, f_1
- Write an **equation** for **Vc**
- Using your results, check the values in the table below AND complete it:

Table 1: Calculated Values for the Series RC Circuit

$f(\text{Hz})$	$X_C(\Omega)$	$Z_T(\Omega)$		$V_C(V_{pk})$	
		$ Z_T $	θ_T°	$ V_C $	θ_C°
10	$1.59 \cdot 10^6$	$1.59 \cdot 10^6$	-89.5	10	-0.54
1000					
10,000					
20,000	795.8	15,021	-3.04	0.53	-87.0

Series R-C Circuit Analysis (ICP)

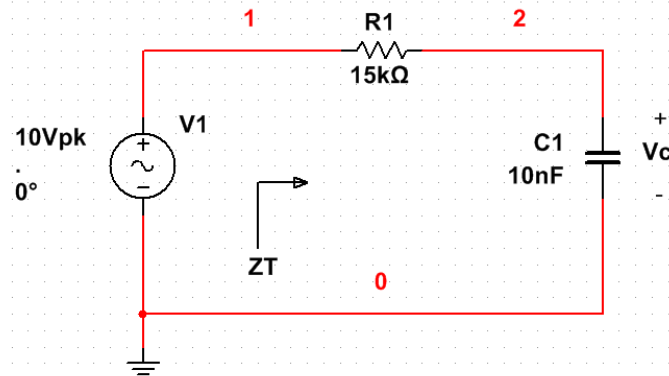

3. Write an equation for the total impedance magnitude $|Z_T|$

$$\vec{Z}_T = R_1 - jX_{C1}$$

$$\therefore |\vec{Z}_T| = \sqrt{(R_1)^2 + (X_{C1})^2} \quad (\text{EQ2})$$

1. What is the source voltage, **V1** in phasor form?

$$\vec{V}_1 = 10V_{pk} \angle 0^\circ$$

OR

$$7.07V_{RMS} \angle 0^\circ$$

2. Write an equation for the capacitive reactance, X_{C1}

$$X_{C1} = \frac{1}{2\pi f C_1} (\Omega) \quad (\text{EQ1})$$


4. Write an equation for the total impedance phase Θ_{ZT}

$$\tan(\Theta_{Z_T}) = \frac{X_{C1}}{R_1}$$


$$\therefore \Theta_{Z_T} = -\tan^{-1}\left(\frac{X_{C1}}{R_1}\right) \quad (\text{EQ3})$$

Θ_{Z_T} IS THE \angle MADE W/
POSITIVE X-AXIS
 Θ_{Z_T} IS "-" HERE.

Series R-C Circuit Analysis (ICP)

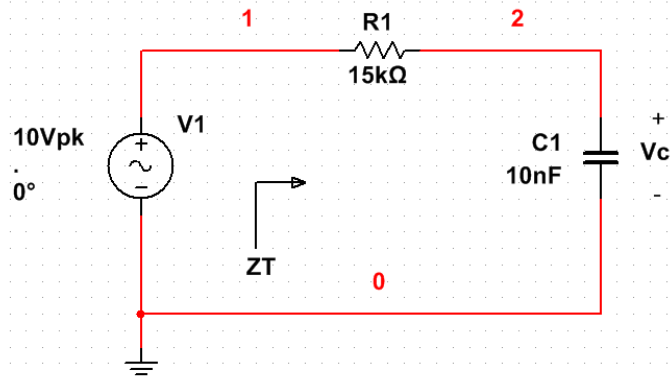

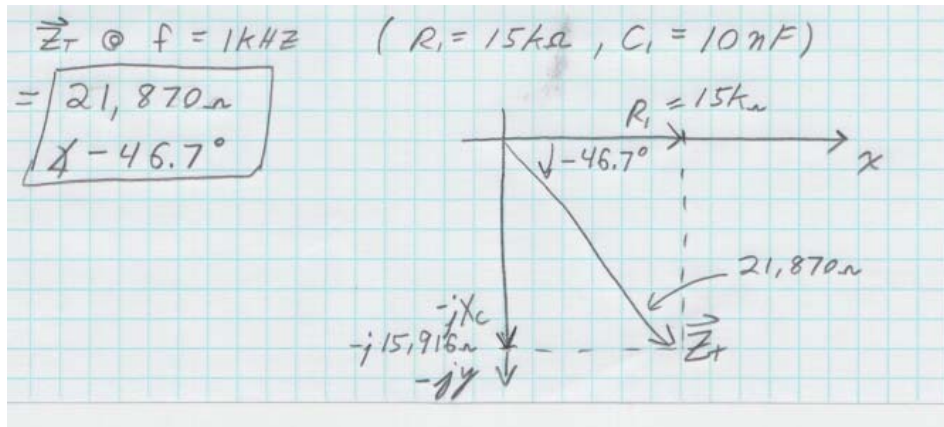5. Draw the impedance diagram for the circuit at 1 kHz.



6. Write an equation for the series current I

$$\vec{I} = \frac{\vec{V}_1}{\vec{Z}_T} = \frac{10\text{Vpk} \angle 0^\circ}{\vec{Z}_T}$$

$$\text{OR } \frac{10\text{Vpk} \angle 0^\circ}{\sqrt{R_1^2 + X_{C1}^2} \angle -\tan^{-1}\left(\frac{X_{C1}}{R_1}\right)}$$


7. Find the corner frequency, f_1

$$f_1 = \frac{1}{2\pi R_1 C_1}$$

$$= \frac{1}{(2)(\pi)(15\text{k}\Omega)(10\text{nF})}$$

$$= 1,061\text{ Hz}$$

Series R-C Circuit Analysis (ICP)

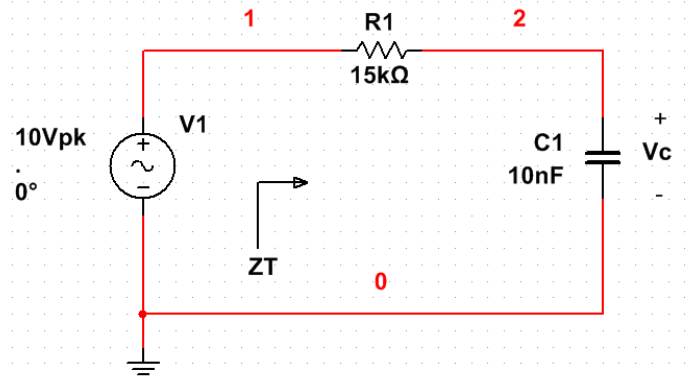

9. Using your results, check the values in the table below AND complete it:

Table 1: Calculated Values for the Series RC Circuit

$f(\text{Hz})$	$X_C(\Omega)$	$Z_T(\Omega)$		$V_C(\text{Vpk})$	
		$ Z_T $	θ_T°	$ V_C $	θ_C°
10	$1.59 \cdot 10^6$	$1.59 \cdot 10^6$	-89.5	10	-0.54
1000					
10,000					
20,000	795.8	15,021	-3.04	0.53	-87.0

8. Write an equation for V_c

$$\vec{V}_c = \vec{I} \cdot \vec{Z}_c$$

$$= \left(\frac{10\text{Vpk} \angle 0^\circ}{\vec{Z}_T} \right) (\vec{Z}_c) \quad \text{, SAME AS VOLTAGE DIVIDER}$$

SOLVING FOR : X_C , \vec{Z}_T + \vec{V}_c YIELDS:

$$\vec{V}_c = \frac{(10\text{Vpk} \angle 0^\circ)(X_C \angle -90^\circ)}{\vec{Z}_T}$$

$$|\vec{V}_c| = \frac{(10\text{Vpk})(X_C)}{\sqrt{R_1^2 + X_{C1}^2}} \quad (\text{EQ4})$$

$$\angle \vec{V}_c = -90^\circ - \theta_{ZT} \quad (\text{EQ5})$$

EQ1

EQ2,3

EQ4,5

$f(\text{Hz})$	$X_C(\Omega)$	\vec{Z}_T	\vec{V}_c
10	1.592×10^6	$1.592 \times 10^6 \angle -89.5^\circ$	$10.0\text{Vpk} \angle -0.54^\circ$
1,000	15,915	$21,870 \angle -46.7^\circ$	$7.28\text{Vpk} \angle -43.3^\circ$
10,000	1,592	$15,084 \angle -6.06^\circ$	$1.06\text{Vpk} \angle -83.9^\circ$
20,000	795.8	$15,021 \angle -3.04^\circ$	$0.530\text{Vpk} \angle -87.0^\circ$