

Electrical Engineering Technology

Transformers

Spring 2019 (2185)

Transformers

☐ Analysis


- Voltage ratio
- Current ratio
- Turns ratio
- Dot convention

☐ Transformer Example Problem

☐ Transformer In Class Problem

Transformer Analysis (voltage-ratio)

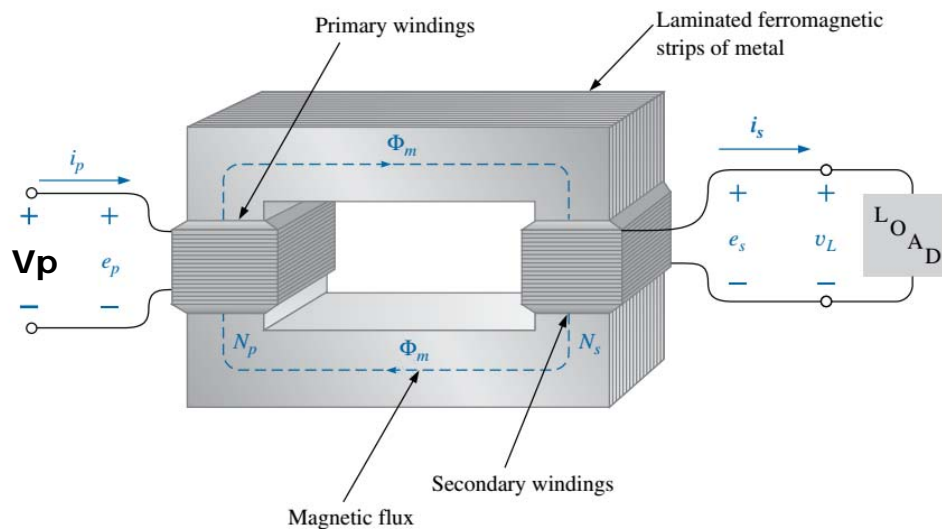Consider the following transformer
(ideal model, $k=1$):



$$\text{LET } I_p(x) = I_m \sin(\omega x)$$

"Ohm's Law" for magnetic circuits
(from Chapter 12):

Effect = cause/opposition

$$\phi = \frac{\mathcal{F}}{R} \quad \leftarrow \begin{array}{l} \text{MAGNETOMOTIVE} \\ \text{FORCE (A} \cdot \text{T)} \end{array} \quad (12.5)$$

\uparrow FLUX (WEBERS) \leftarrow RELUCTANCE (A·T/WEBER)

\therefore THE FLUX GENERATED BY \vec{V}_p, \vec{I}_p WILL HAVE THE FORM:

$$\phi = \frac{N_p \cdot I_p(x)}{R}$$

$$\text{OR } \phi = \left(\frac{N_p}{R} I_m \right) \sin(\omega x) \quad (\text{WEBERS})$$

Φ_m

$$\therefore e_p = N_p \frac{d\phi}{dx} \quad \text{BECOMES:}$$

$$e_p(x) = N_p \frac{d}{dx} \left[\Phi_m \sin(\omega x) \right] \quad \text{VOLTS}$$

$$\text{OR } e_p(x) = N_p \Phi_m \omega \cos(\omega x) \quad \text{VOLTS}$$


$$\text{BUT } \cos(\omega x) = \sin(\omega x + 90^\circ)$$

$$\therefore e_p(x) = N_p(2\pi f) \Phi_m \sin(\omega x + 90^\circ) \quad \text{VOLTS}$$

$$e_p(x) \approx (6.283)(f N_p) \Phi_m \sin(\omega x + 90^\circ) \quad \text{V}$$

Transformer Analysis (voltage-ratio)

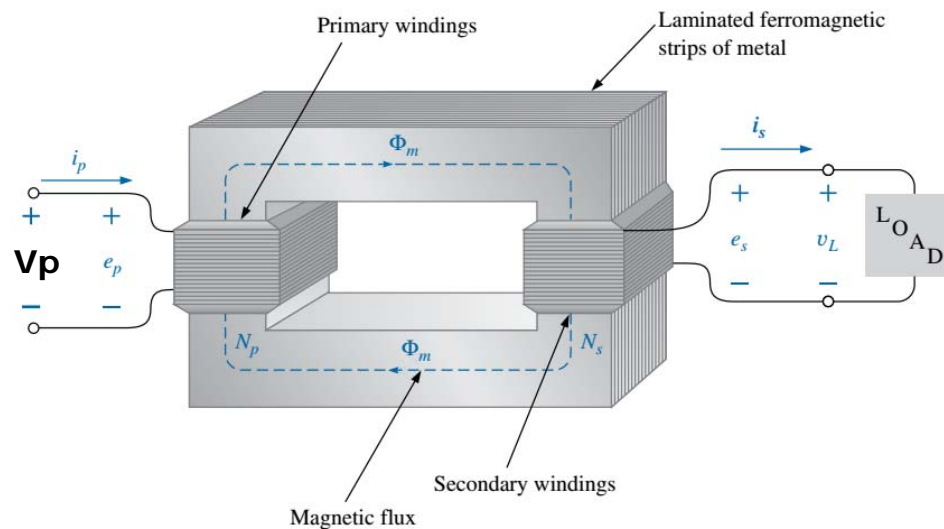Consider the following transformer
(ideal model, $k=1$):



Note:

\vec{V}_p LEADS \vec{I}_p BY 90° (ELI)

$|\vec{V}_p|$ IS DIRECTLY RELATED TO f, N_p + Φ_m

Looking at the secondary:

$$e_s = N_s \frac{d\Phi_m}{dt} \text{ BECOMES:}$$

$$e_s(t) = N_s (2\pi f) \Phi_m \sin(\omega t + 90^\circ) \text{ V}$$

$$\vec{V}_s \approx 4.44 f N_s \frac{\Phi_m}{\sqrt{2}} \angle 90^\circ$$

So we have the relationship:

$$\frac{\vec{V}_p}{\vec{V}_s} = \frac{N_p}{N_s}$$

$$I_p(t) = I_m \sin(\omega t)$$


$$e_p(t) \approx (6.283)(f N_p) \Phi_m \sin(\omega t + 90^\circ) \text{ V}$$

$$\text{So, } \vec{V}_p \approx (4.44 f N_p \frac{\Phi_m}{\sqrt{2}}) \angle 90^\circ$$

$$\vec{I}_p = \frac{I_m}{\sqrt{2}} \angle 0^\circ$$

Transformer Analysis (turns ratio, dot convention)

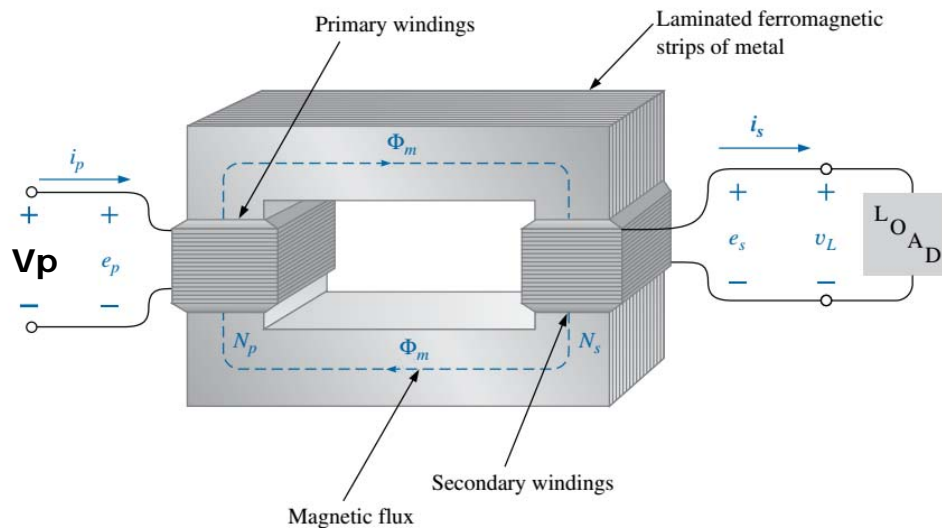
Consider the following transformer
(ideal model, $k=1$):




$$\frac{\vec{V}_p}{\vec{V}_s} = \frac{N_p}{N_s}$$

LET $a = \frac{N_p}{N_s}$, THE TURNS RATIO

$$\left. \begin{aligned} \vec{V}_p &= a \vec{V}_s \\ V_s &= \frac{\vec{V}_p}{a} \end{aligned} \right\} \begin{aligned} a < 1: |\vec{V}_s| &> |\vec{V}_p|, \text{ STEP UP} \\ a > 1: |\vec{V}_s| &< |\vec{V}_p|, \text{ STEP DOWN} \end{aligned}$$

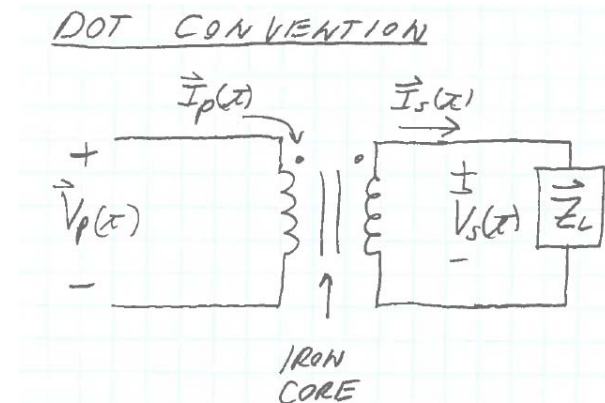

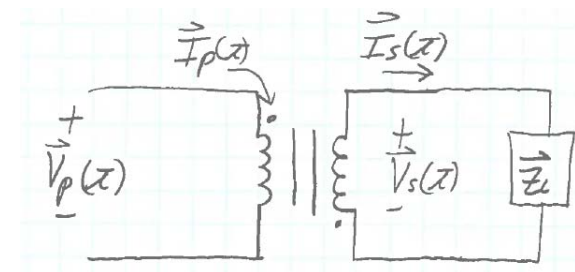
\vec{V}_p, \vec{V}_s IN PHASE
 \vec{I}_p, \vec{I}_s IN PHASE



\vec{V}_p, \vec{V}_s 180° OUT OF PHASE
 \vec{I}_p, \vec{I}_s 180° OUT OF PHASE

Transformer Analysis (current ratio)

EXAMPLE

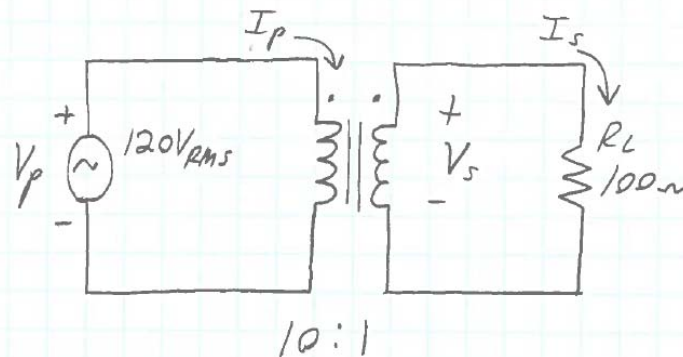

$$a = \frac{N_p}{N_s} = 10, \text{ STEP DOWN}$$

FIND: V_s , I_s , I_p (RMS VALUES)

$$V_s = \frac{V_p}{a} = \frac{120V_{rms}}{10} = \boxed{12V_{rms}}$$

$$I_s = \frac{V_s}{R_L} = \frac{12V_{rms}}{100\Omega} = \boxed{120mA_{rms}}$$

What about I_p ?

An iron-core, **lossless** transformer ($k=1$)

Therefore, **Pin = Pout**

$$P_{RL} = I_s^2 \cdot R_L$$

$$= (120mA)^2 \cdot 100\Omega = \underline{\underline{1.44W}}$$

$$\therefore P_{primary} = 1.44W$$

$$= (120V_{rms})(I_p)$$

$$\therefore \boxed{I_p = 12mA_{rms}}$$


$$\text{OR } I_p = \frac{I_s}{a}$$

So, we have established:

$$\boxed{\frac{V_p}{V_s} = \frac{N_p}{N_s} = a = \frac{I_s}{I_p}}$$

Transformer Analysis (example)

EXAMPLE

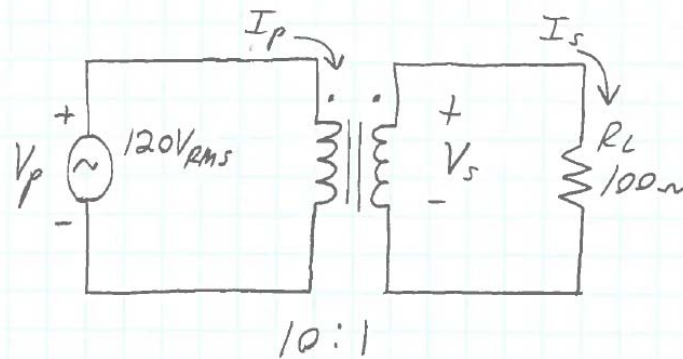

$$\therefore I_p = 12 \text{ mA}_{rms}$$


$$\frac{V_p}{V_s} = \frac{N_p}{N_s} = a = \frac{I_s}{I_p}$$

What's the magnitude of the input impedance?

$$\frac{V_p}{I_p} = \frac{120V_{rms}}{12 \text{ mA}_{rms}} = 10,000 \Omega$$

$$= a^2 \cdot R_L$$

Transformer Analysis (In Class Problem)

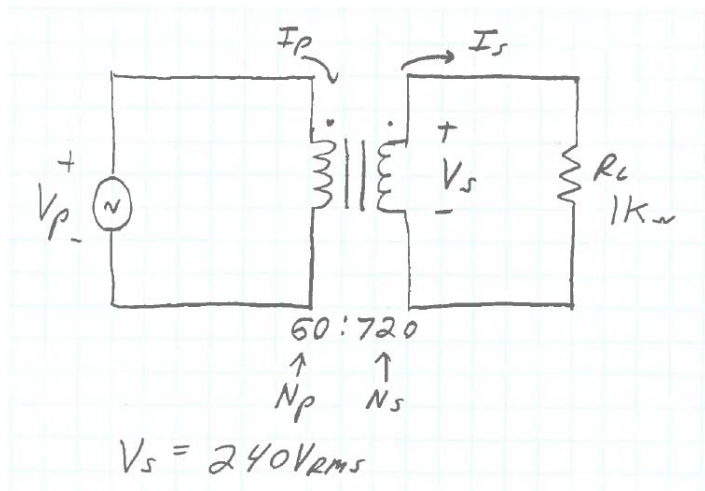

Find:

- a) V_p
- b) I_s
- c) I_p
- d) $P_{supplied}$ by V_p