
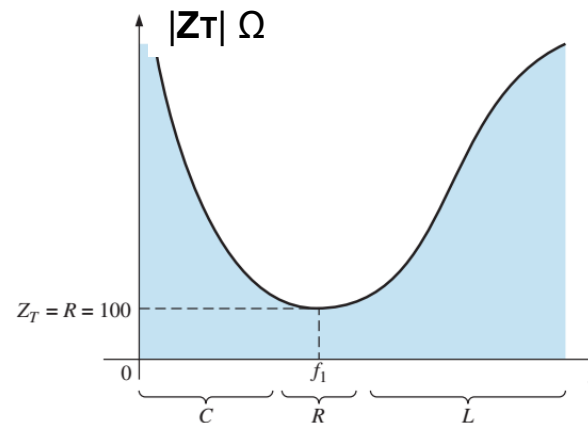


Frequency Response of Basic Elements

- Find $|Z_T|$ for this circuit as a function of frequency (as the frequency changes)

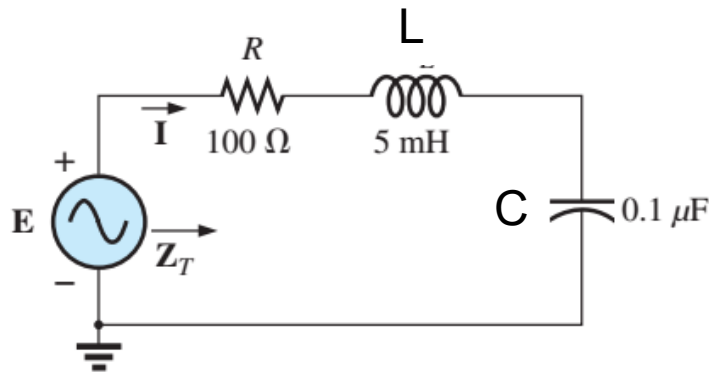


ICP:


- 1) Calculate $|Z_T|$ at 100Hz, 10kHz and 100kHz
- 2) At what frequency does $|Z_T|$ hit its minimum?
- 3) Sketch $|Z_T|$ as a function of frequency (calculator...)

Frequency Response of Basic Elements

- Find $|\vec{Z}_T|$ for this circuit as a function of frequency (as the frequency changes)

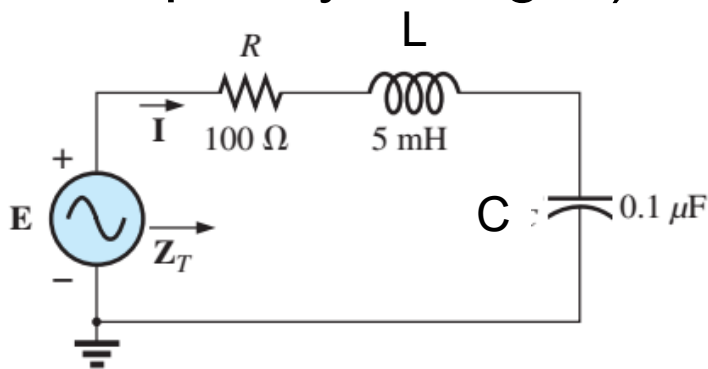

- Calculate $|\vec{Z}_T|$ at 100Hz, 10kHz and 100kHz

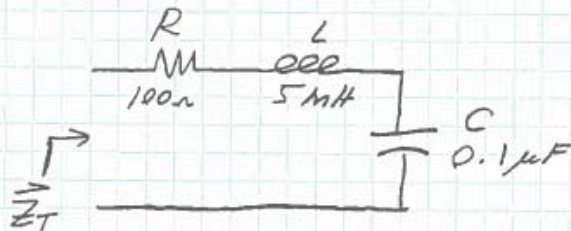

$$\vec{Z}_T = R + jX_L - jX_C$$

$$= R + j(X_L - X_C)$$

$$\therefore |\vec{Z}_T| = \sqrt{R^2 + (X_L - X_C)^2}$$

$$|\vec{Z}_T| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$= \sqrt{R^2 + \left(\frac{\omega L(\omega C)}{\omega C} - \frac{1}{\omega C}\right)^2}$$

$$|\vec{Z}_T| = \sqrt{R^2 + \left(\frac{\omega^2 LC - 1}{\omega C}\right)^2}$$

HERE

$$\omega = 2\pi f$$

$$C = 0.1 \mu F$$

$$L = 5 \text{ mH}$$


$$R = 100 \Omega$$

Solving for 100Hz, 10kHz and 100kHz yields:

f	$ \vec{Z}_T $
100Hz	15.9kΩ
10kHz	185Ω
100kHz	3.13kΩ

Frequency Response of Basic Elements

- Find $|\mathbf{Z}_T|$ for this circuit as a function of frequency (as the frequency changes)

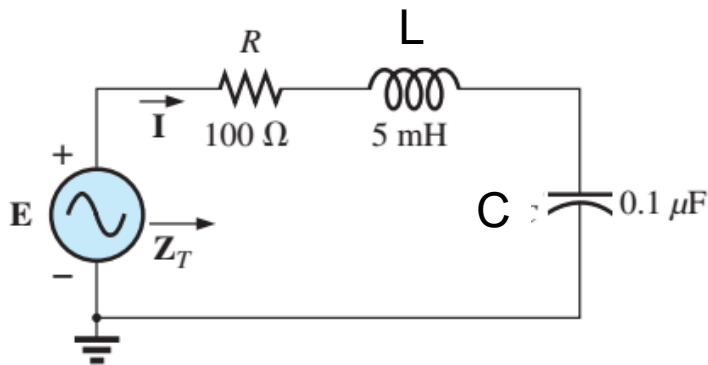

$$|\vec{Z}_T| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$= \sqrt{R^2 + \left(\frac{\omega L(\omega C)}{\omega C} - \frac{1}{\omega C}\right)^2}$$

$$|\vec{Z}_T| = \sqrt{R^2 + \left(\frac{\omega^2 LC - 1}{\omega C}\right)^2}$$

2) At what frequency does $|\mathbf{Z}_T|$ hit its minimum?

$$X_L = X_C$$

$$2\pi fL = \frac{1}{2\pi fC}$$

$$f^2 = \frac{1}{2\pi C(2\pi L)}$$

$$f^2 = \frac{1}{(2\pi \times 2\pi) CL}$$

$$\therefore f = \frac{1}{2\pi\sqrt{LC}}$$


f	$ \vec{Z}_T $
100 Hz	15.9 kΩ
10 kHz	185 Ω
100 kHz	3.13 kΩ
7.12 kHz	100 Ω

$|\mathbf{Z}_T| = 100 \text{ Ohms}$
at $f = 7.12 \text{ kHz}$

Or at $f = 7.12 \text{ kHz}$

Frequency Response of Basic Elements

- Find $|Z_T|$ for this circuit as a function of frequency (as the frequency changes)

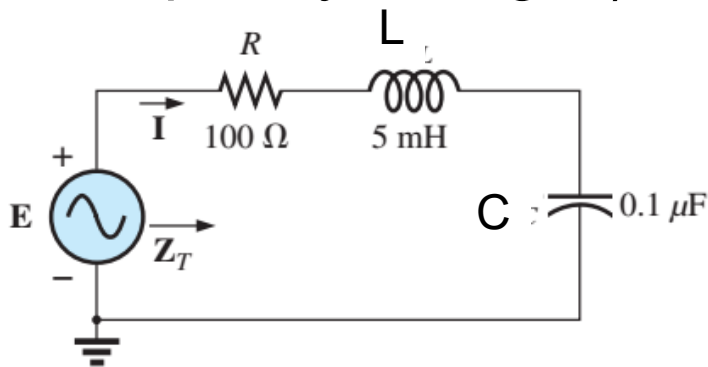

HP Prime Example - SOLVE App
(note: X is the variable that ranges, f in this case)

$$Z = \sqrt{R^2 + \left(\frac{(2\pi X)^2 * L * C - 1}{2\pi X * C} \right)^2}$$

- Sketch $|Z_T|$ as a function of frequency (calculator...)

$$|\vec{Z}_T| = \sqrt{R^2 + \left(\frac{\omega^2 LC - 1}{\omega C} \right)^2}$$

$$\begin{aligned} \omega &= 2\pi f \\ C &= 0.1 \mu F \\ L &= 5 \text{ mH} \\ R &= 100 \Omega \end{aligned}$$

Set R, L and C values (Num), then Plot:

