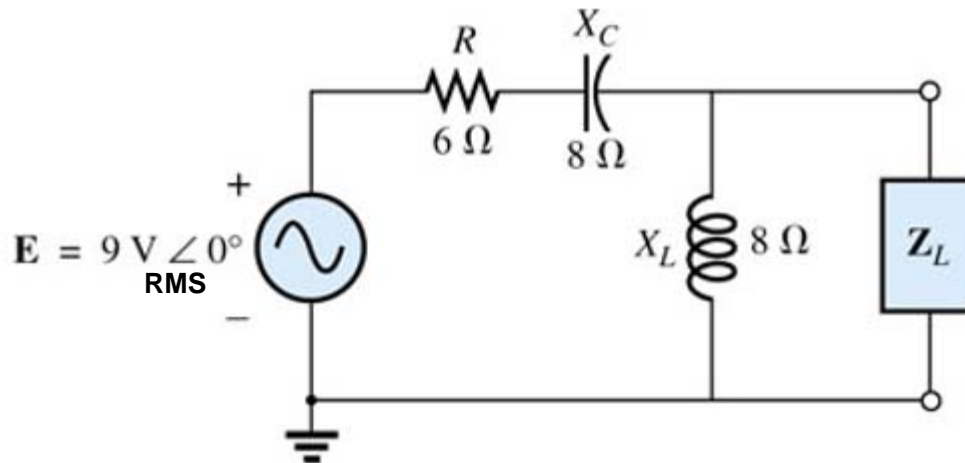


In Class Problem




Find:

- The Thevenin equivalent circuit for the network external to Z_L
- The value of Z_L for maximum power transfer
- The average power dissipated by this load


Approach:

- Standard Thevenin approach
- Set $Z_L = Z_{TH}^*$
- $P_{ZL} = V_{RMS} I_{RMS} \cos(\Theta)$

In Class Problem

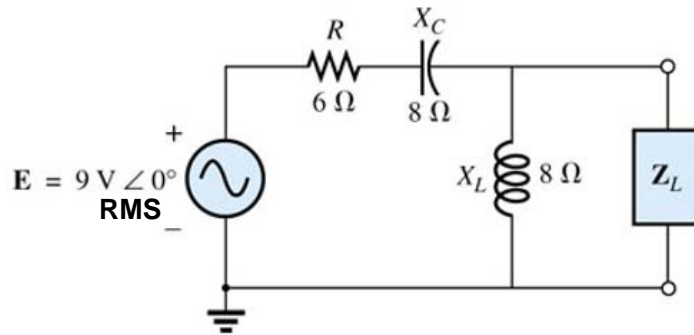

Redrawing and finding V_{TH} , Z_{TH} :

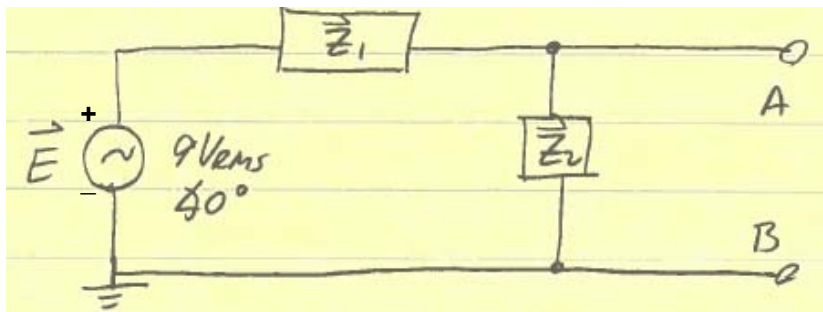

$$Z_1 = (6 - j8)\Omega$$

$$Z_2 = j8\Omega$$

$$\vec{V}_{TH} = \vec{E} \left(\frac{\vec{Z}_2}{\vec{Z}_1 + \vec{Z}_2} \right) = 9\text{ V}_{RMS} \angle 40^\circ \left(\frac{j8\Omega}{6\Omega} \right)$$


$$\underline{V_{TH} = 12\text{ V}_{RMS} \angle 90^\circ}$$

$$\vec{Z}_{TH} = \vec{Z}_1 // \vec{Z}_2$$


$$= (6 - j8)\Omega // (j8\Omega)$$

$$\underline{Z_{TH} = (10.67 + j8)\Omega}$$

Therefore, we now have:

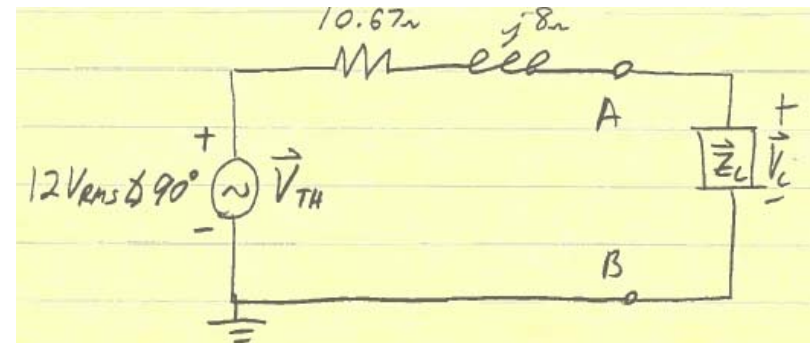


In Class Problem

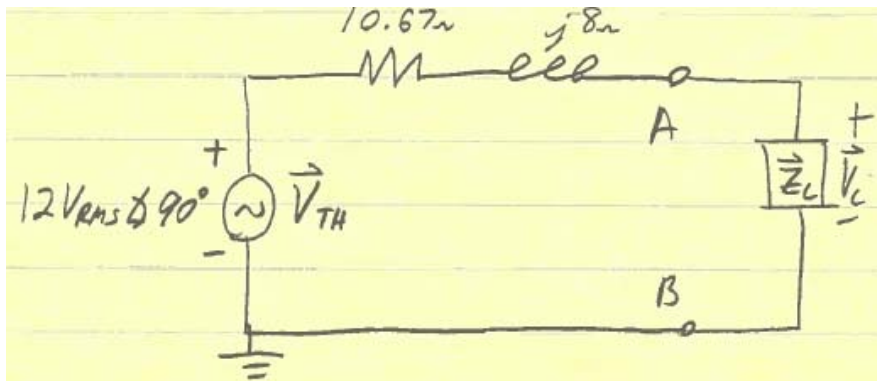

For MAX PWR

XFER

$$\vec{Z}_L = (10.67\Omega - j8\Omega)$$

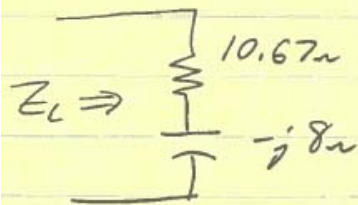

Finding \vec{V}_L , \vec{I}_L and P_L :

$$\vec{V}_L = \vec{V}_{TH} \left(\frac{\vec{Z}_L}{\vec{Z}_L + \vec{Z}_{TH}} \right)$$

$$= 12V_{RMS} \angle 90^\circ \left(\frac{10.67 - j8}{[10.67 - j8] + [10.67 + j8]} \right)$$

$$\vec{V}_L = 7.5V_{RMS} \angle 53.14^\circ$$

$$\vec{I}_L = \frac{\vec{V}_L}{\vec{Z}_L} = \frac{7.5V_{RMS} \angle 53.14^\circ}{(10.67 - j8)\Omega}$$


$$= 562.3 \text{ mA}_{RMS} \angle 90^\circ$$

$$P_L = (V_{L_{RMS}})(I_{L_{RMS}}) \cos(\theta)$$

$$= (7.5V_{RMS})(0.562A_{RMS}) \cos(|53.14^\circ - 90^\circ|)$$

$$P_L = (4.217)(0.8) = \boxed{3.37 \text{ W}}$$

In Class Problem

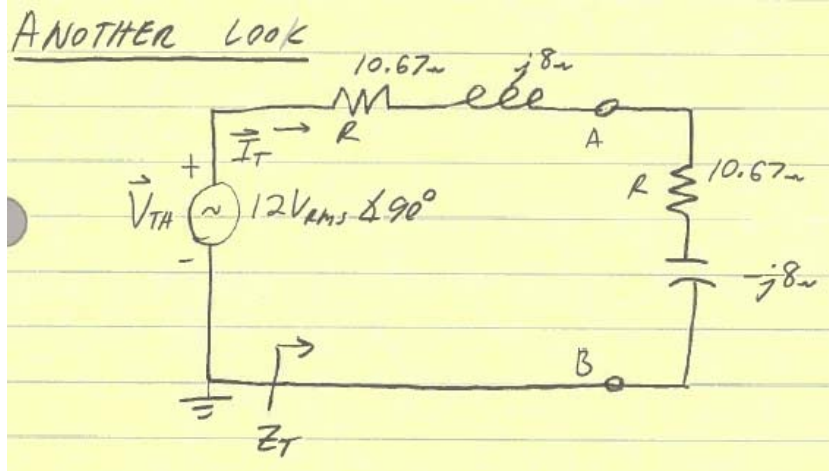

$$\vec{Z}_T = 2R = \underline{21.34\Omega}$$

$$\vec{I}_T = \frac{\vec{V}_{TH}}{\vec{Z}_T} = \frac{12V_{RMS} \angle 90^\circ}{21.34\Omega}$$

$$= \underline{0.562A_{RMS} \angle 90^\circ}$$

$$P_T = (V_{TH_{RMS}})(I_{T_{RMS}}) \cos(\theta)$$

$$= (12V)(0.562A) \cos(\theta)$$

$$= \underline{6.74W}$$

$$\therefore P_L = \frac{1}{2}P_T = \boxed{3.37W}$$