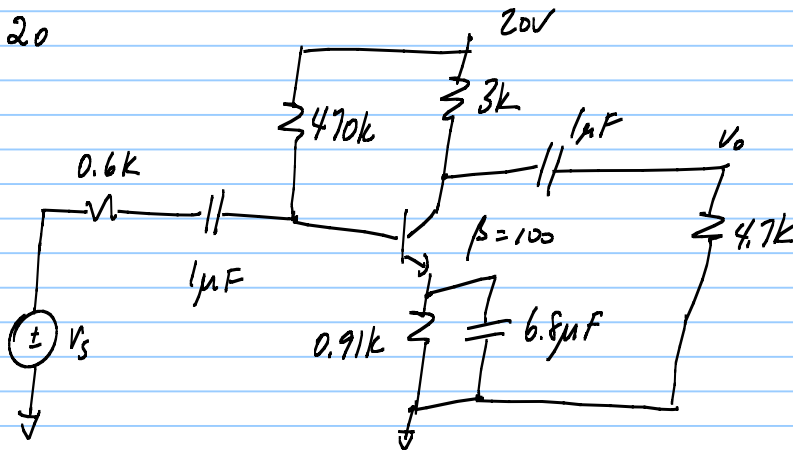


# Chapter 9 20 a-c, 23 a-c


Note Title

8/12/2018

20



DC

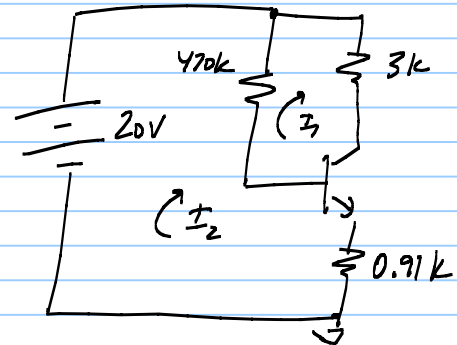

$$I_1 = 100(I_2 - I_1) \quad | \quad 0 = -101I_1 + 100I_2$$

$$20 - 0.7 = (I_2 - I_1)470k + 0.91kI_2$$

$$| \quad 19.3 = -470I_1 + 470.91I_2$$

$$I_1 = 3.435mA \quad | \quad I_2 = 3.469mA = I_E$$

$$r_e = \frac{0.026}{3.469mA} = 7.495\Omega$$

$$A_{v_{min}} = \frac{-R_c}{r_e} = \frac{-3k}{7.495} = -400$$

$$A_{v_L} = \frac{-R_c || R_L}{r_e} = \frac{-3k || 4.7k}{7.495} = -244.3$$

$$r_{in} = 470k || \beta r_e = 748\Omega$$

$$r_{out} = 3k$$

Determine  $f_{L_s}$ ,  $f_{L_e}$  &  $f_{L_c}$

$$f_{L_s} = \frac{1}{2\pi(600 + 748)(1\mu F)} = 118Hz \quad f_{L_c} = \frac{1}{2\pi(3k + 4.7k)(1\mu F)} = 20.7Hz$$


$$f_{L_e} = \frac{1}{2\pi R_e C_e} \quad R_c = 3k || \left( \frac{470k || 0.6k}{100} + 7.495 \right) = 3k || (6 + 7.495) = 13.43\Omega$$

$$f_{L_e} = \frac{1}{2\pi(13.43)(6.8\mu F)} = 1.742kHz$$

Lower Cutoff Frequency is the largest of  $f_{L_s}$ ,  $f_{L_e}$  and  $f_{L_c}$


$$f_1 = f_{L_e} = 1.742kHz$$

23)

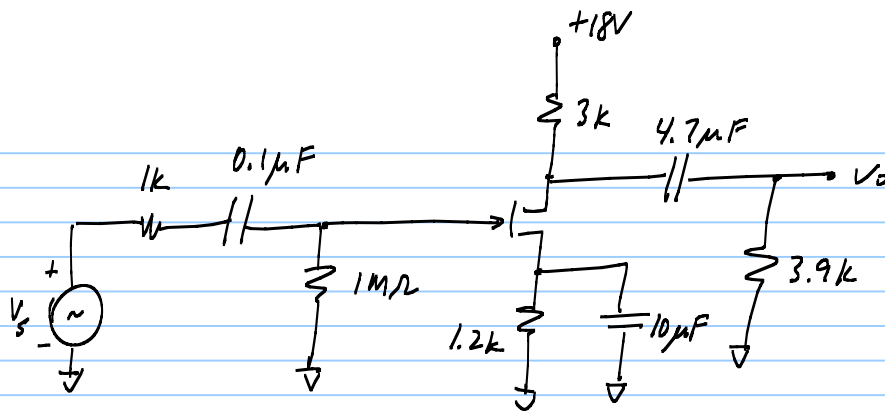

$$I_{DSS} = 6\text{mA}$$

$$V_p = -6, r_d = \infty\Omega$$

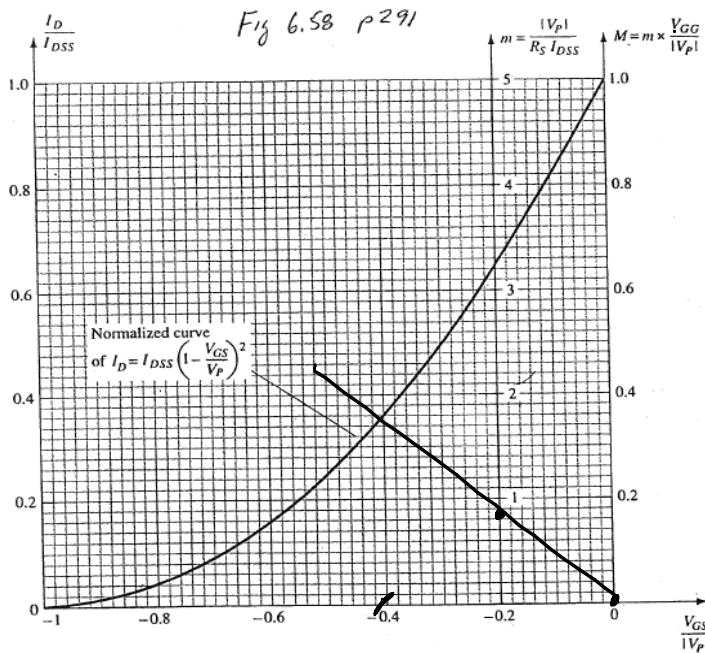

$$V_{GG} = 0V$$

$$m = \frac{6}{1.2K \cdot 6mA} = 0.833$$

$$M = 0.833 \frac{0}{6} = 0$$

$$V_{GSQ} = (-0.4)(6) = -2.4V$$

$$g_m = \left( \frac{2 I_{DSS}}{|V_p|} \right) \left( 1 - \frac{V_{GSQ}}{V_p} \right) = \frac{2(6mA)}{6} \left( 1 - \frac{-2.4}{-6} \right)$$

$$g_m = 1.2\text{ms}$$

$$A_{vL} = -g_m (R_o \parallel R_L) = -1.2m (3k \parallel 3.9k) = -2.03$$

$$Z_{in} = 1M\Omega$$

$$Z_{out} = 3k$$

find  $f_{Lg}$ ,  $f_{Lc}$  &  $f_{Ls}$

$$f_{Lg} = \frac{1}{2\pi(1M\Omega + 1k)(0.1\mu F)} = 1.59\text{Hz}$$

$$f_{Lc} = \frac{1}{2\pi(3k + 3.9k)(4.7\mu F)} = 4.91\text{Hz}$$

$$f_{Ls} = \frac{1}{2\pi R_{eq} C_s} = \frac{1}{2\pi(491.8)(10\mu F)}$$

$$R_{eq} = R_S \parallel 1/g_m = 1.2k \parallel 1/1.2m = 491.8\Omega$$

$$f_{Ls} = 32\text{Hz}$$

$$f_1 = 32\text{Hz}$$