

* include ac model, 41 & 43 require you to draw a transfer function and use it to find V_{GSQ}

Chapter 8 #1, 3, 7, 17*, 21*, 25*, 29*, 32*, 41*, 45*

Note Title

8/11/2018

1) Calculate g_{m0} for a JFET having device parameters $I_{DSS} = 12\text{mA}$ and $V_p = -4\text{V}$.

$$g_{m0} = \frac{2I_{DSS}}{|V_p|} = \frac{2(12\text{mA})}{4\text{V}} = 6\text{mA/V} = 6\text{mS}$$


3) For a JFET having device parameters $g_{m0} = 5\text{mS}$ and $V_p = -4\text{V}$, what is the device current at $V_{GS} = 0$?

$$g_{m0} = \frac{2I_{DSS}}{|V_p|} \quad 5\text{mS} = \frac{2I_{DSS}}{4} \quad I_{DSS} = 10\text{mA}, \quad I_{DSS} \text{ is the current when } V_{GS} = 0.$$

7) Determine the value of g_m for a JFET ($I_{DSS} = 8\text{mA}$, $V_p = -5\text{V}$) when biased at $V_{GSQ} = V_p/4$

$$g_m = \frac{2I_{DSS}}{|V_p|} \left(1 - \frac{V_{GS}}{V_p}\right) = \frac{2(8\text{mA})}{5} \left(1 - \frac{-5/4}{-5}\right) = \frac{2(8\text{mA})}{5} \left(\frac{3}{4}\right) = 2.4\text{mS}$$

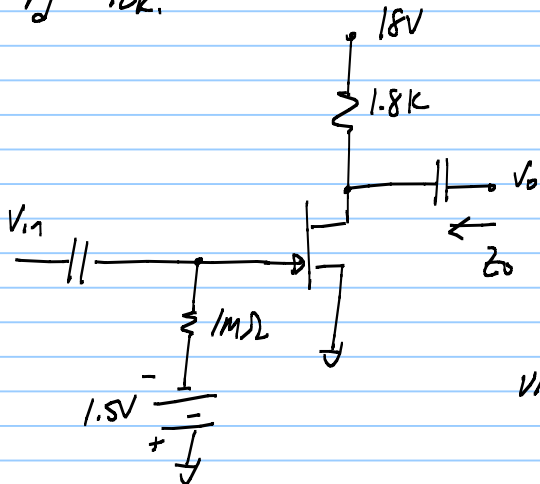
17) Determine Z_{in} , Z_{out} and A_v for the circuit below if $I_{DSS} = 10\text{mA}$ and $V_p = -6\text{V}$ and $R_D = 40\text{k}$.



Fixed bias. $V_{GSQ} = -1.5\text{V}$

$$g_m = \frac{2I_{DSS}}{|V_p|} \left(1 - \frac{V_{GS}}{V_p}\right) = \frac{2(10\text{mA})}{6} \left(1 - \frac{-1.5}{-6}\right)$$

$$g_m = 2.5\text{mS}$$



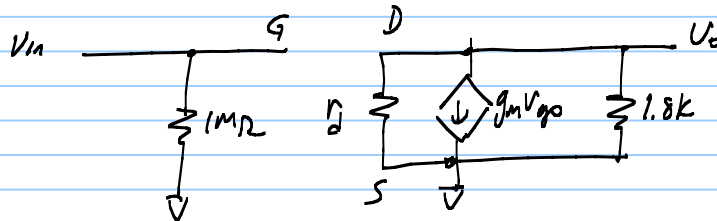


$$Z_{in} = 1\text{M}\Omega$$

$$Z_{out} = 1.8\text{k}\Omega \parallel 40\text{k}\Omega = 1.722\text{k}\Omega$$

$$A_v = -g_m (R_D \parallel R_o) = -2.5\text{mS} (40\text{k}\Omega \parallel 1.8\text{k}\Omega) = -4.3$$

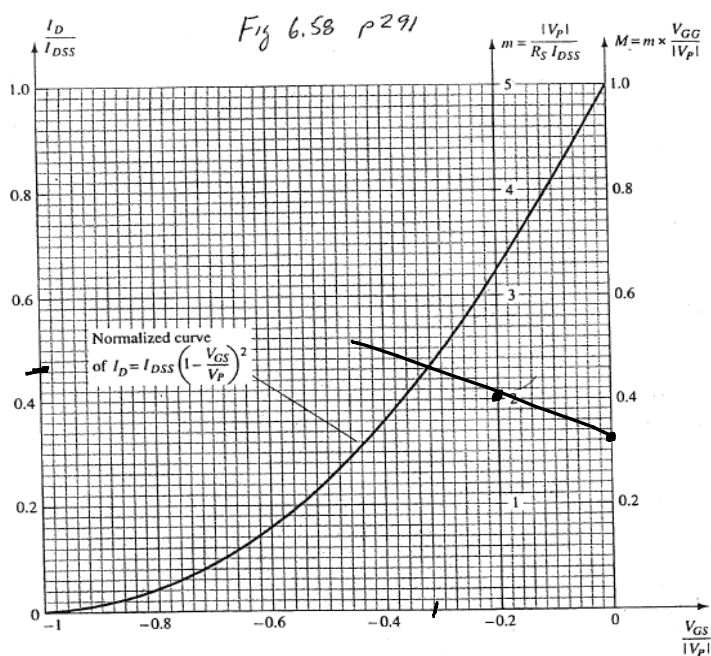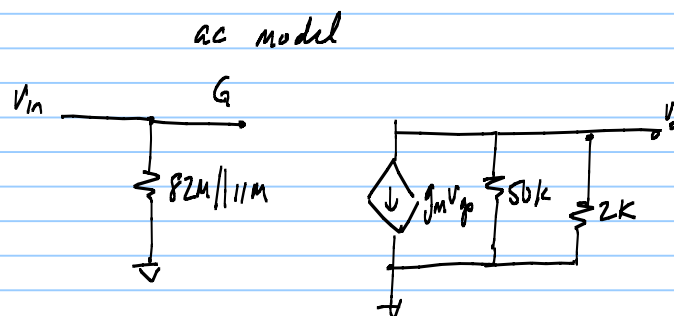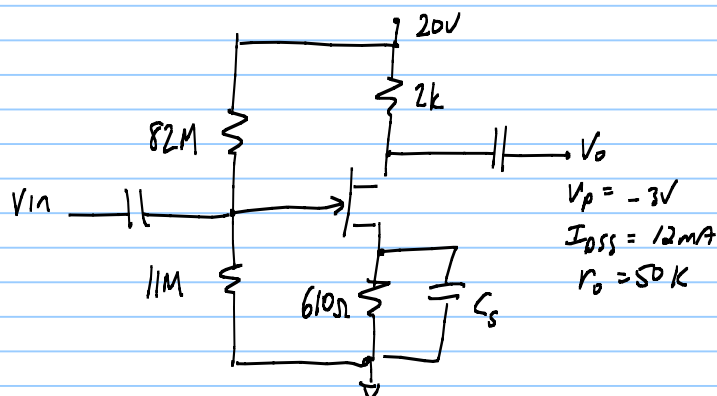25) Determine Z_{in} , Z_{out} & V_o for the circuit below given $v_{in} = 20 \text{ mV}$.



$$V_{GG} = \frac{11M}{82M + 11M} (20) = 2.37V$$

$$m = \frac{3V}{(610) 12mA} = 0.41$$

$$M = 0.41 \frac{2.37V}{3} = 0.324$$

$$V_{GSQ} = (-0.32)(3) = -0.96V$$

$$g_m = \left(\frac{2 I_{DSS}}{|V_p|} \right) \left(1 - \frac{V_{GSQ}}{V_p} \right) = \frac{2(12mA)}{3} \left(1 - \frac{-0.96}{-3} \right)$$




$$g_m = 5.44 \text{ mS}$$

$$Z_{in} = 82M \parallel 11M = 9.7M$$

$$Z_o = R_D \parallel r_o = 2k \parallel 50k = 1.92k\Omega$$

$$A_v = -g_m (r_o \parallel R_D) = -5.44 \text{ mS} (1.92k) = -10.46 \quad V_o = A_v v_{in} = -209.2 \text{ mV}$$

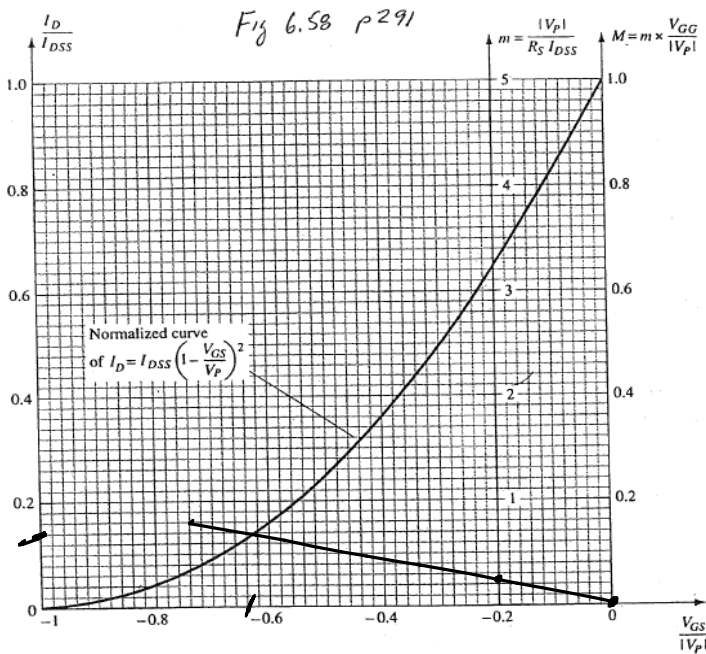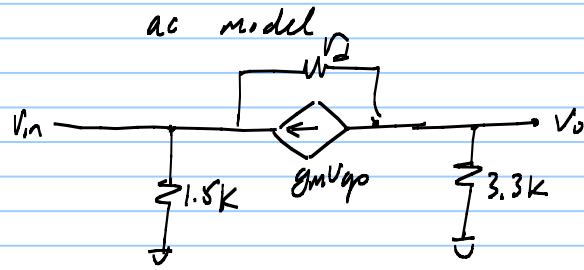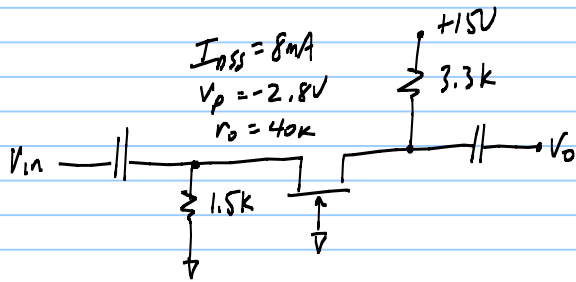2a) Determine Z_{in} , Z_{out} & V_o for the circuit below given $V_{in} = 4\text{mV}$.



$$V_{GG} = 0V$$

$$m = \frac{2.8}{(1.5k) 8mA} = 0.233$$

$$M = 0.233 \frac{0}{3} = 0$$

$$V_{GSQ} = (-0.64)(2.8) = -1.8V$$

$$g_m = \left(\frac{2 I_{DSS}}{|V_p|} \right) \left(1 - \frac{V_{GSQ}}{V_p} \right) = \frac{2(8mA)}{2.8} \left(1 - \frac{-1.8}{-2.8} \right)$$

$$g_m = 2.04\text{mS}$$




$$Z_{in} = R_s \parallel \left[\frac{r_d + R_o}{1 + g_m r_d} \right] = 1.5 \parallel \left[\frac{40 + 3.3k}{1 + (2.04)(40)} \right] = 388\Omega$$

$$Z_{out} = R_o \parallel r_d = 3.3k \parallel 40k = 3.04k$$

$$A_v = \frac{g_m R_o + \frac{R_o}{r_d}}{1 + \frac{R_o}{r_d}} = \frac{(2.04m)(3.3k) + \frac{3.3k}{40k}}{1 + \frac{3.3k}{40k}} = \frac{6.8145k}{1.083} = 6.29$$

$$V_o = A_v V_{in} = 25.2\text{mV}$$

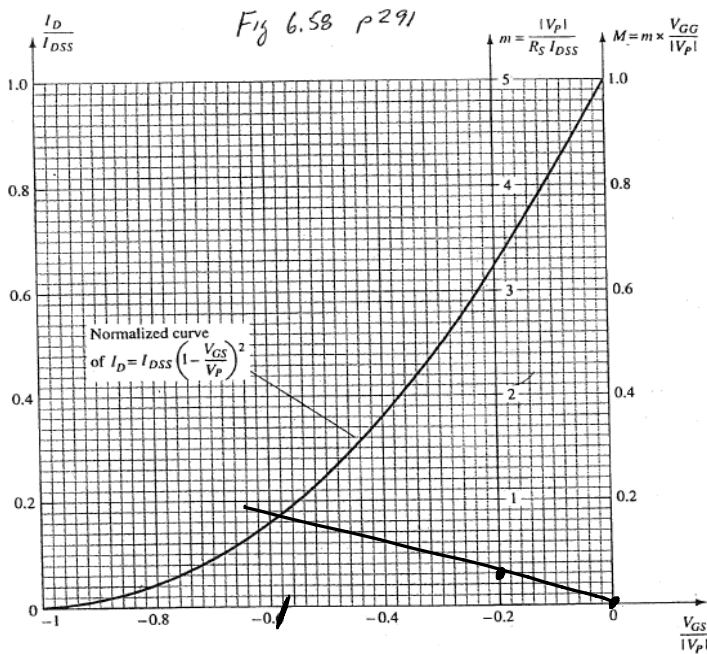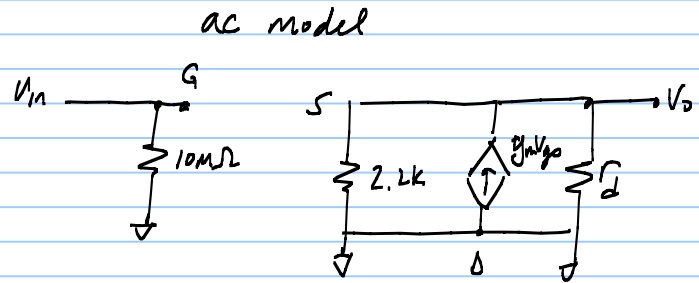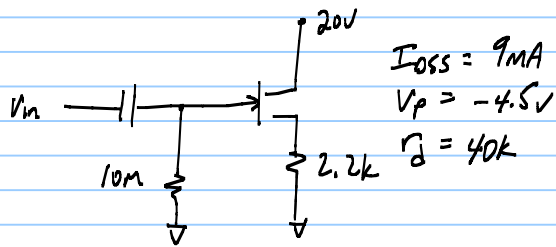32) Determine Z_{in} , Z_{out} & A_v for the circuit below



$$V_{GG} = 0V$$

$$m = \frac{4.5}{(2.2k)(9mA)} = 0.227$$

$$M = 0.227 \frac{0}{3} = 0$$

$$V_{GSQ} = (-0.58)(4.5) = -2.61$$

$$g_m = \left(\frac{2 I_{DSS}}{|V_p|} \right) \left(1 - \frac{V_{GSQ}}{V_p} \right) = \frac{2(9mA)}{4.5} \left(1 - \frac{-2.61}{-4.5} \right)$$


$$g_m = 1.68mS$$

$$Z_{in} = 10M\Omega$$



$$Z_o = r_d \parallel R_S \parallel 1/g_m = 40k \parallel 2.2k \parallel 1/1.68mS = 463\Omega$$

$$A_v = \frac{g_m (r_d \parallel R_S)}{1 + g_m (r_d \parallel R_S)} = \frac{1.68m (40k \parallel 2.2k)}{1 + 1.68m (40k \parallel 2.2k)} = \frac{3.5}{1 + 3.5} = 0.778$$

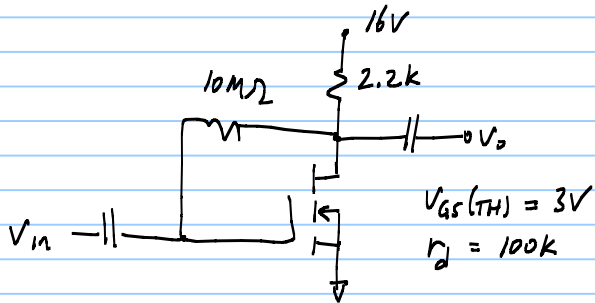41) Determine Z_{in} , Z_{out} & A_v for the circuit below given $k = 0.3 \times 10^{-3}$



ac model

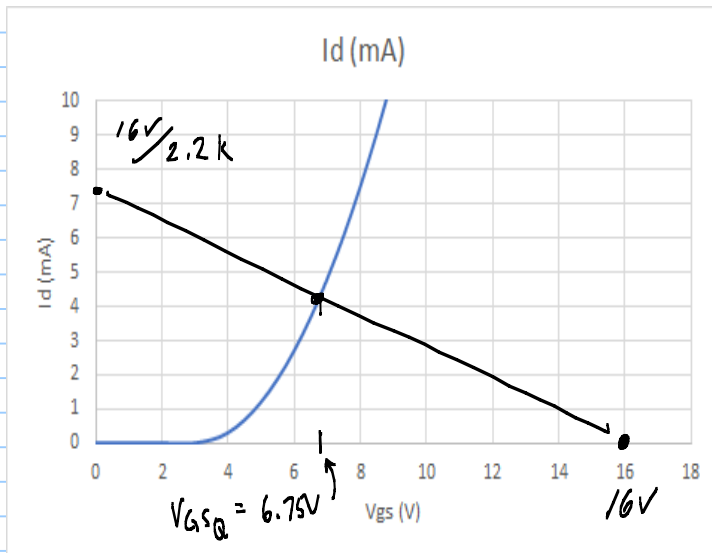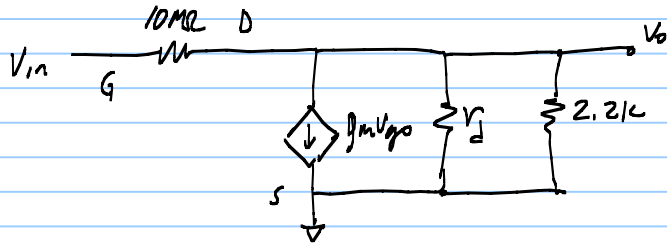

$$g_m = 2k(V_{GS} - V_{GS(TH)})$$

$$= 2(0.3m)(6.75 - 3) = 2.25mS$$


$$Z_{in} = \frac{R_F + r_d \parallel R_D}{1 + g_m(r_d \parallel R_D)} = \frac{10M + \cancel{100k} \parallel \cancel{2.2k}}{1 + 2.25m(100k \parallel 2.2k)} = \frac{10M}{5.84}$$

$$Z_{in} = 1.71M\Omega$$




$$Z_o = R_F \parallel r_d \parallel R_D = 10M \parallel 100k \parallel 2.2k = 2.15k$$

$$A_v = -g_m(R_F \parallel r_d \parallel R_D) = -4.84$$

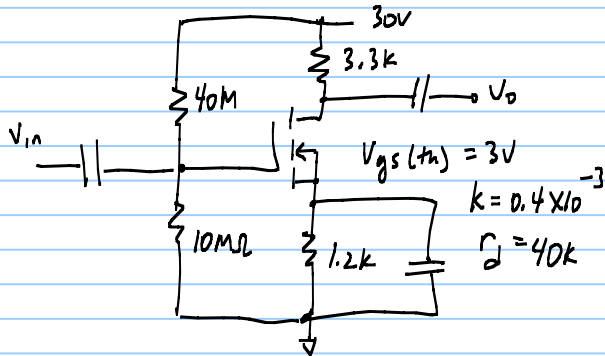45) Determine v_o when $v_{in} = 0.8 \text{ mV}$.



ac model

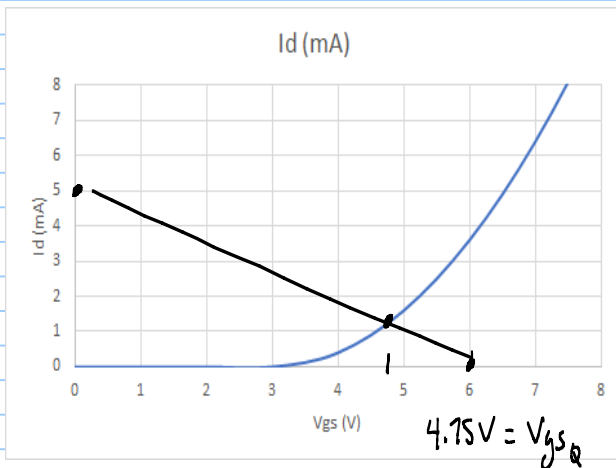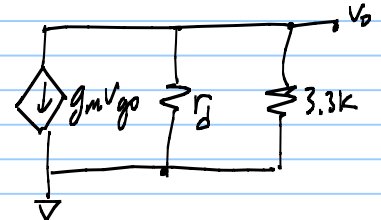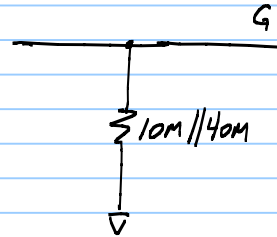

$$V_g = \frac{30\text{V}(10\text{M})}{10\text{M} + 40\text{M}} = 6\text{V} \quad V_{gs} = 6\text{V} \text{ when } I_D = 0$$

$$I_D = \frac{6\text{V}}{1.2\text{k}} = 5\text{mA} \text{ when } V_{gs} = 0$$

$$V_{gsQ} = 4.75\text{V}$$

$$g_m = 2k(V_{gs} - V_{gs(th)}) = 2(0.4\text{mA}) (4.75 - 3) = 1.4\text{mA/V}$$

$$A_v = -g_m(r_d \parallel R_o) = 1.4\text{mA/V} (40\text{k} \parallel 3.3\text{k}) = 4.27$$

$$v_o = A_v v_{in} = -3.41\text{mV}$$