
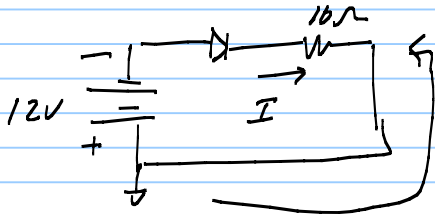


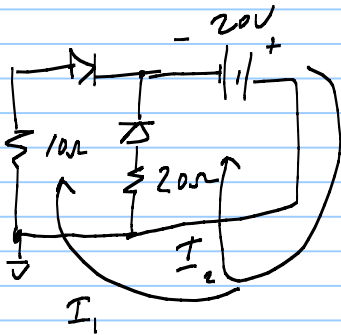
5) Determine the current I for each using the approx. diode model



Current wants to flow CCW. Diode open $I = 0$



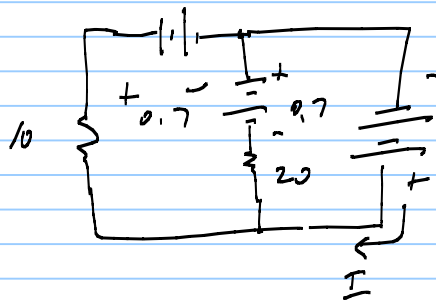Current wants to flow CW. Both diodes 0.7V




20V across each branch.

$$I_{10\Omega} = \frac{20 - 0.7}{10\Omega} = 1.93A$$

$$I_{20\Omega} = \frac{20 - 0.7}{20} = .965A$$





$$I_{10} + I_{20} = I = 2.895A$$

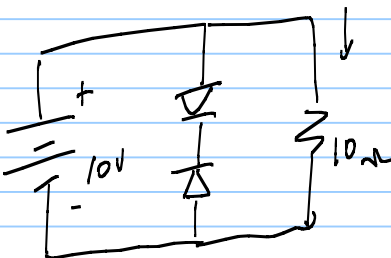


10V across both branches. Opposing diodes cannot be on simultaneously

$$I = \frac{10V}{10\Omega} = 1A$$

8) Determine I_D & V_o .

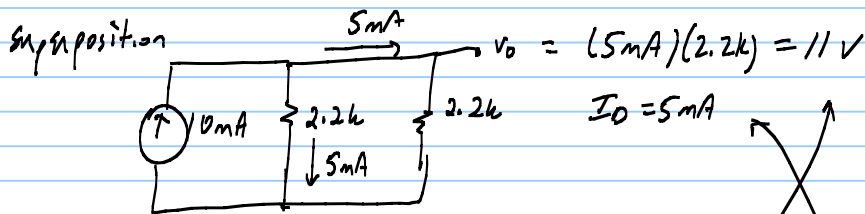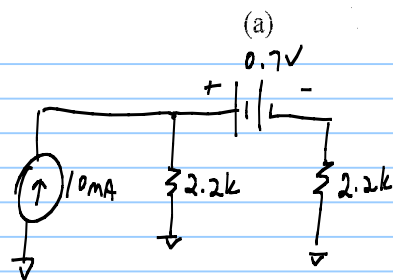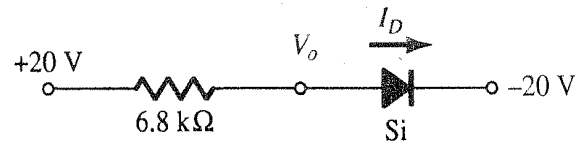
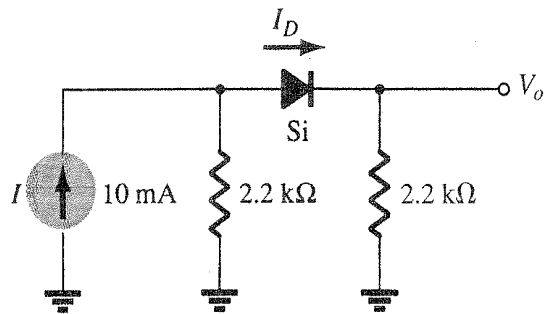


10 mA splits in $\frac{1}{2}$.

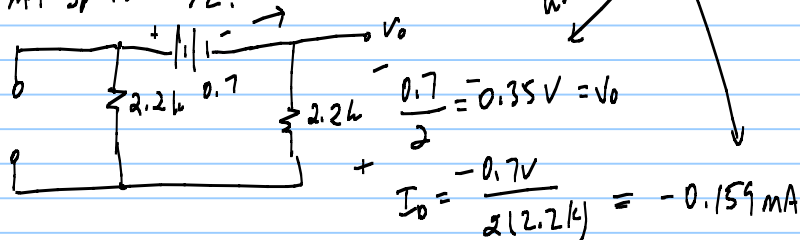

$$I_D = 5 \text{ mA} - 0.159 \text{ mA} = 4.84 \text{ mA}$$

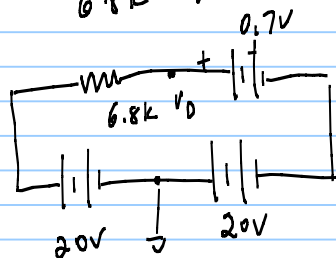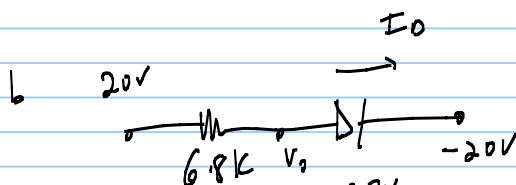
$$V_o = 11 \text{ V} - 0.35 = 10.65 \text{ V}$$



$$I_D = \frac{40 - 0.7}{6.8 \text{ k}} = 5.78 \text{ mA}$$


$$V_o = -20 + 0.7 = -19.3 \text{ V}$$

10

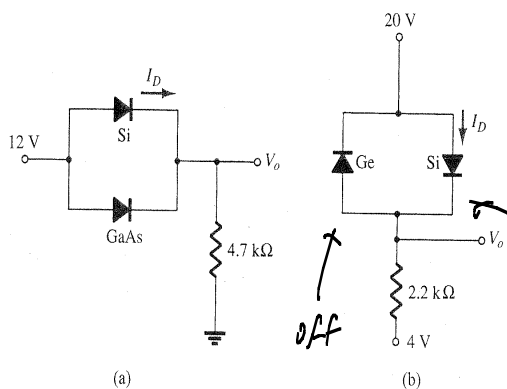

off

turns on

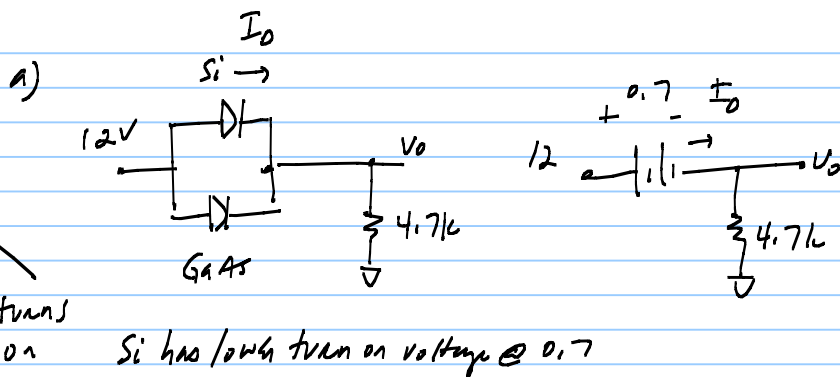


Si has lower turn on voltage @ 0.7

$$V_o = 12 - 0.7 = 11.3V$$

Find current using resistor.

$$11.3V / 4.7k = 2.4mA$$

b)


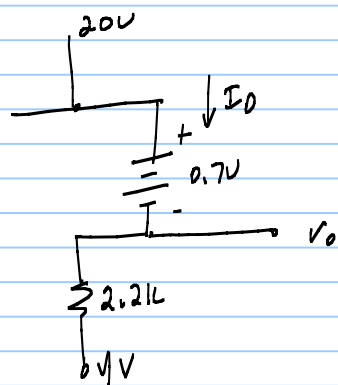


$$V_o = 20 - 0.7 = 19.3V$$


$$I_o = \frac{19.3 - 4}{2.2k} = 6.95mA$$

10.59 I_o

11

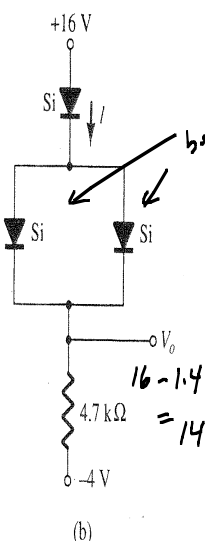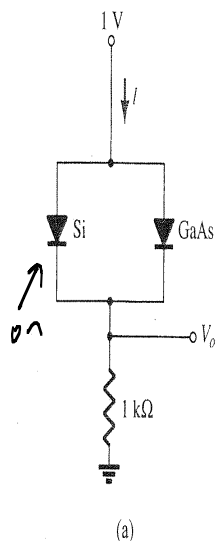

a) Si turns on before others.


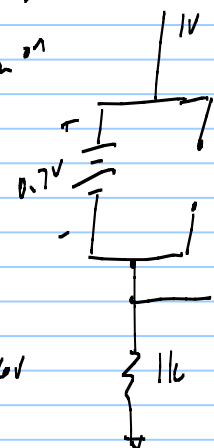


$$16 - 1.4 = 14.6V$$

$$I = \frac{0.3V}{1k} = 300\mu A$$

$$b) I = \frac{14.6 + 4}{4.7k} = 3.96mA$$

13)

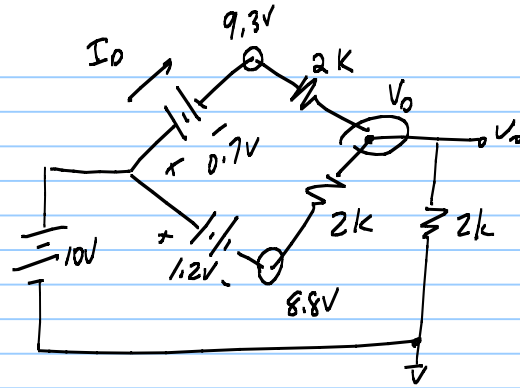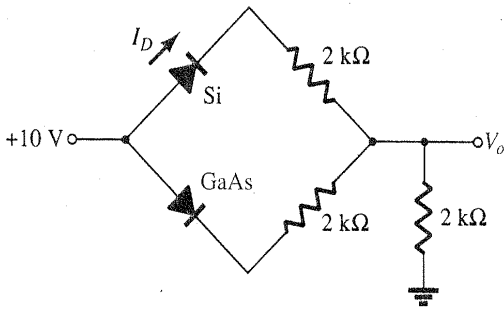

KCL @ V_o node.

$$\frac{9.3 - V_o}{2k} + \frac{8.8 - V_o}{2k} = \frac{V_o}{2k}$$


$$9.3 - V_o + 8.8 - V_o = V_o$$

$$18.1 = 3V_o$$

$$V_o = 6.033V$$

$$I_D = \frac{9.3 - V_o}{2k} = \frac{9.3 - 6.033}{2k} = 1.64 \text{ mA} = I_D$$

21.)

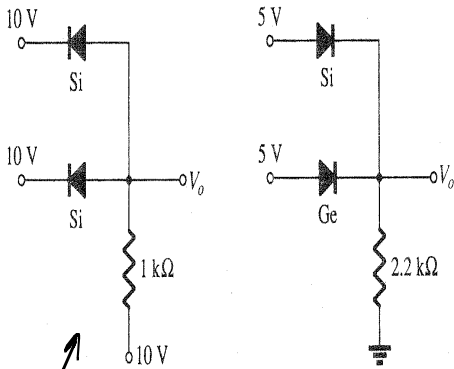


no voltage difference



both end 10V. No current.

$$V_o = 10V$$

Si cannot turn on.

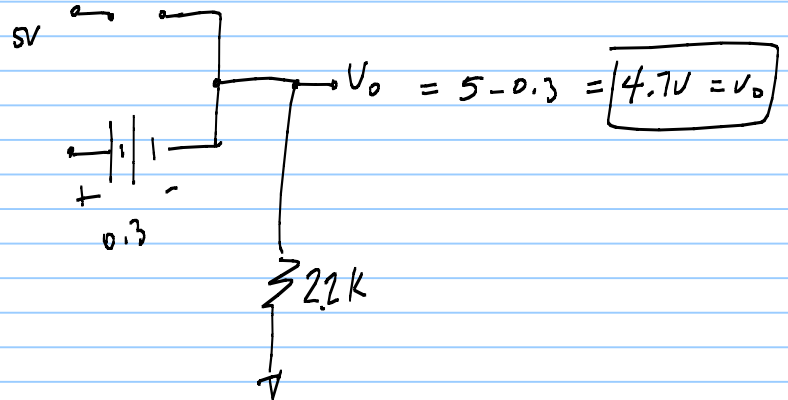

27

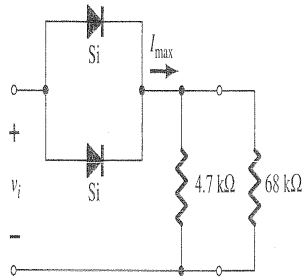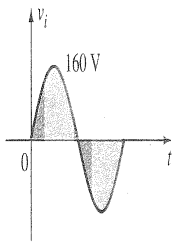

a) Given $P_{max} = 14 \text{ mW}$ for each diode determine the maximum current rating of each diode ($V_D = 0.7 \text{ V}$)

b) Determine I_{max} for parallel diodes

c) Determine the current through each diode at $v_{i,max}$

d) If only one diode were present, which would be the expected result.

$$a) I_{D,max} = \frac{P_{D,max}}{0.7 \text{ V}} = 20 \text{ mA}$$

$$b) I_{max} = 2 I_{D,max} = 40 \text{ mA}$$


$$c) I = \frac{160 - 0.7}{4.7 // 68 \text{ k}} = \frac{159.3 \text{ V}}{4.396 \text{ k}\Omega} = 36.236 \text{ mA}$$

$$I_D = I/2 = 18.1 \text{ mA}$$

d) The current rating would be exceeded & the smoke would be let out.

29] Determine v_o and the required PIV rating of each diode. In addition, determine the maximum current through each diode.

positive cycle

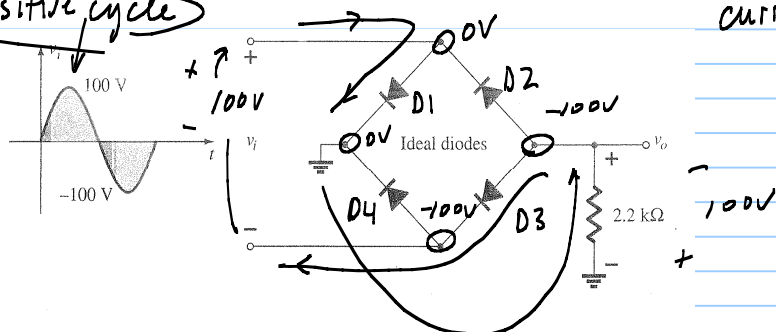


$$v_o = -100V$$

Diodes that are off must withstand a reverse voltage of

100V. So the minimum PIV rating is 100V. (D2 & D4 reverse biased)

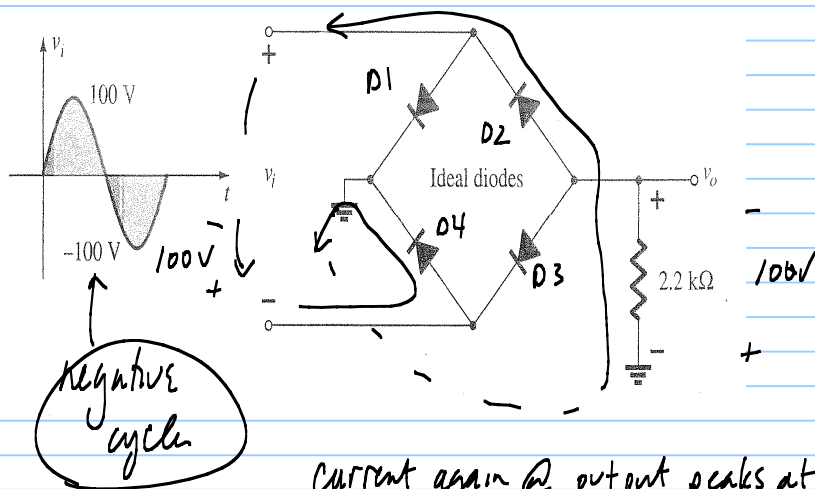The peak current is $\frac{100V}{2.2k} = 45.46mA$, in D1 & D3







negative cycle

current again @ output peaks at -100V.

This time D2 & D4 conduct. D1 & D3 are reverse biased.

33] Determine v_o for each circuit.

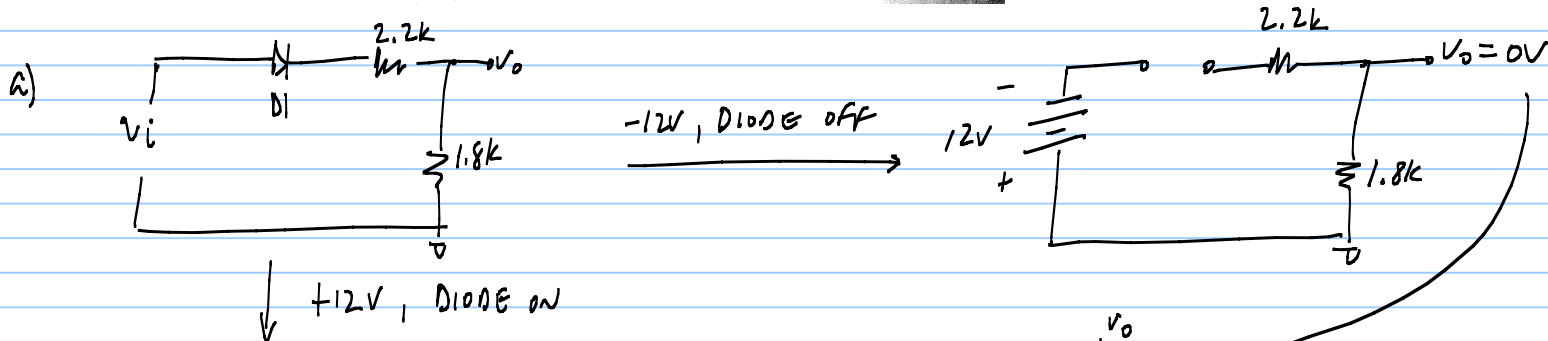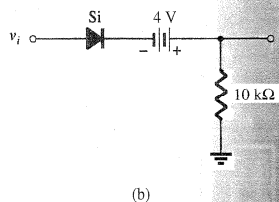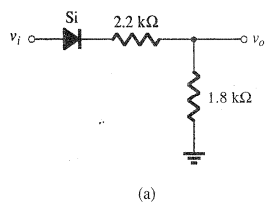
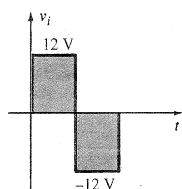


$$12V - 0.7V - 2.2kI - 1.8kI = 0$$


$$11.3V = 4I$$

$$I = 2.825mA$$




$$v_o = (1.8k)(2.825mA) = 5.09V$$

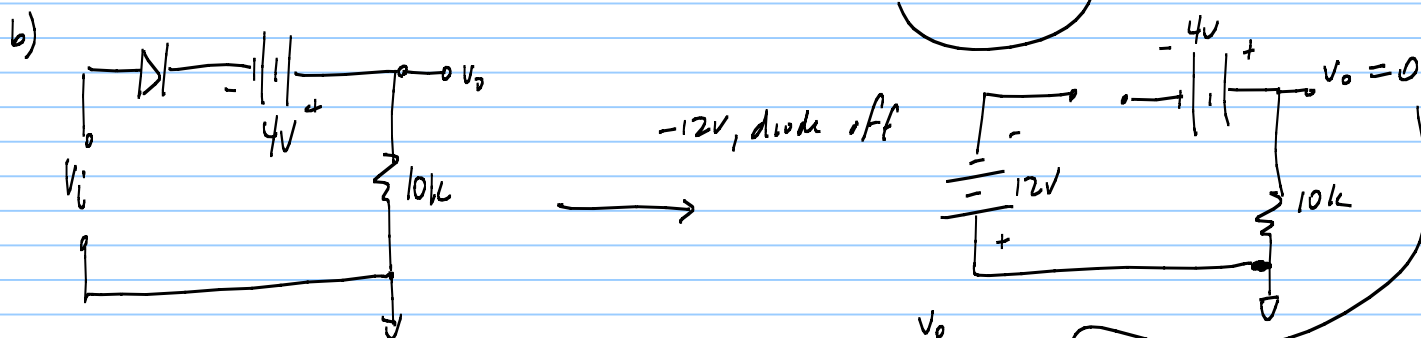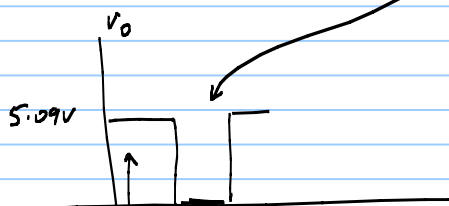

$$v_o = 12 - 0.7 + 4 = 15.3V$$

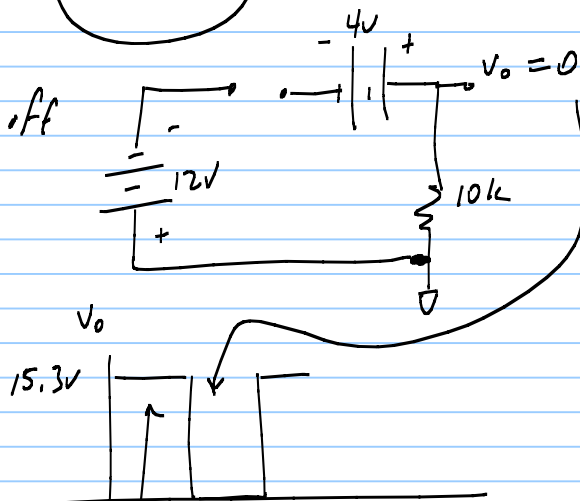

35

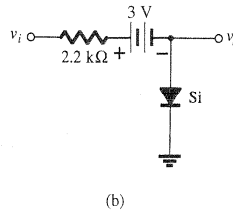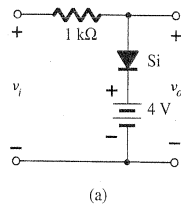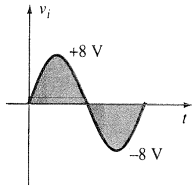

a) $v_i - v_d - 4 = 0$

$v_i - 4 = v_d$ $v_d > 0.7$ on

so $v_i - 4 > 0.7$




$\frac{1}{2} v_i > 4.7V$ diode on.


$v_i - v_d - 4 = 0$

$v_d < 0.7$ off

so $v_i - 4 < 0.7$

$\frac{1}{2} v_i < 4.7$ diode off

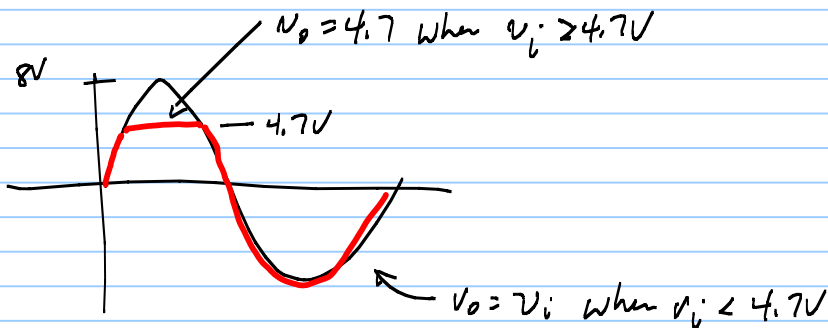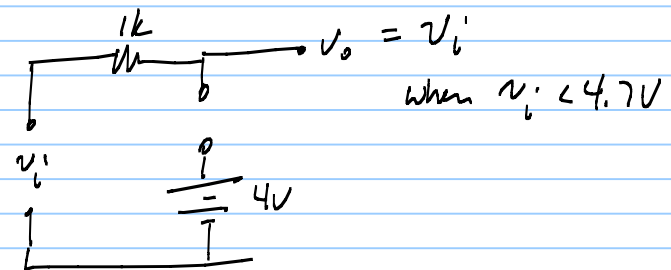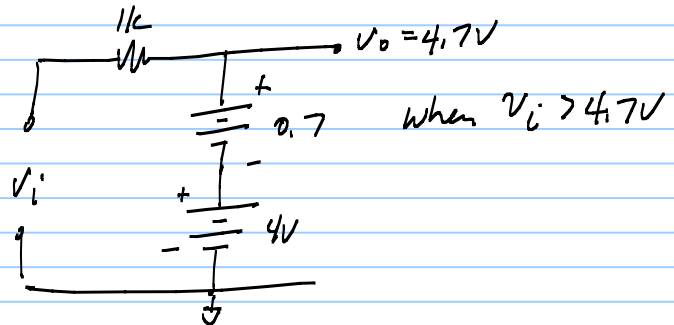

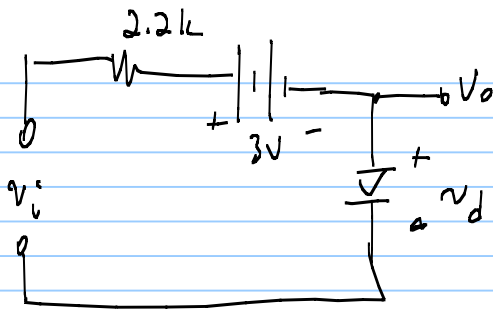

a) $v_i - 3 - v_d = 0$

$v_i - 3 = v_d$ $v_d > 0.7$ on

so $v_i - 3 > 0.7$

if $v_i > 3.7V$ diode on.

$v_i - 3 - v_d = 0$

$v_d < 0.7$ off

so $v_i - 3 < 0.7$

if $v_i < 3.7$ diode off

