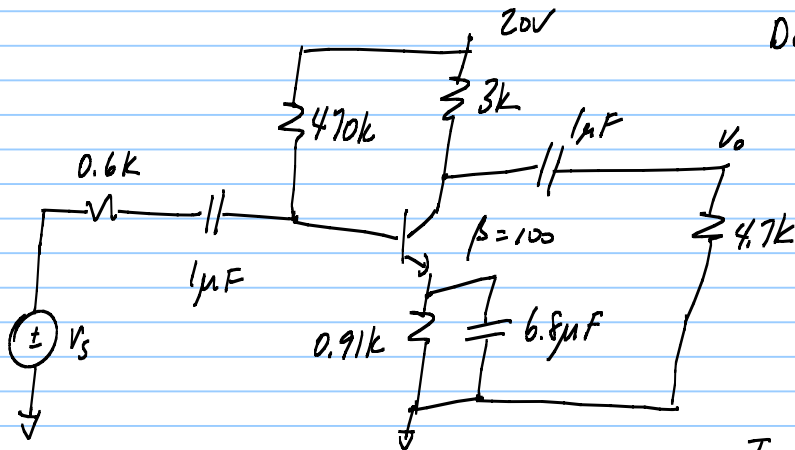


Chapter 9 #28a,b, 31a-c


Note Title

8/12/2018

28)



DC

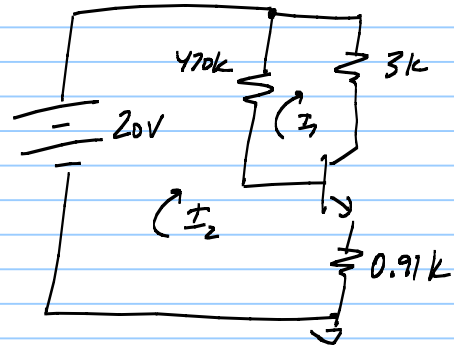

$$A_{v_{mid}} = \frac{-R_c}{r_e} = \frac{-3k}{7.495} = -400$$

$$A_{v_L} = \frac{-R_c \parallel R_L}{r_e} = \frac{-3k \parallel 4.7k}{7.495} = -244.3$$

$$r_{in} = 470k \parallel \beta r_e = 748\Omega$$

$$r_{out} = 3k$$

$$I_1 = 100(I_2 - I_3) \quad | \quad 0 = -101I_1 + 100I_2$$

$$20 - 0.7 = (I_2 - I_1)470k + 0.91kI_2$$

$$| 19.3 = -470I_1 + 470.91I_2$$

$$I_1 = 3.435mA \quad | \quad I_2 = 3.469mA = I_E$$

$$r_e = \frac{0.026}{3.469mA} = 7.495\Omega$$

$$C_{w_i} = 7pF$$

$$C_{bc} = 6pF$$

$$C_{m_i} = (1 - A_{v_L})C_{bc}$$

$$C_{m_o} \approx C_{bc}$$

$$C_{w_o} = 11pF$$

$$C_{be} = 20pF$$

$$= (245.3)(6pF)$$

$$C_{m_o} = 6pF$$

$$C_{ce} = 10pF$$

$$C_{m_i} = 1472pF$$


determine f_{H_i} & f_{H_o} & f_β

$$f_{H_i} = \frac{1}{2\pi(R_s \parallel r_{in})(C_{w_i} + C_{be} + C_{m_i})} = \frac{1}{2\pi(600 \parallel 748)(7pF + 20pF + 1472pF)} = 318.9KHz$$

$$f_{H_o} = \frac{1}{2\pi(r_o \parallel R_L)(C_{w_o} + C_{ce} + C_{m_o})} = \frac{1}{2\pi(3k \parallel 4.7k)(11pF + 10pF + 6pF)} = 3.22MHz$$


$$f_\beta = \frac{1}{2\pi\beta r_e(C_{be} + C_{bc})} = \frac{1}{2\pi(100)(7.5)(20pF + 6pF)} = 8.16MHz$$

31)

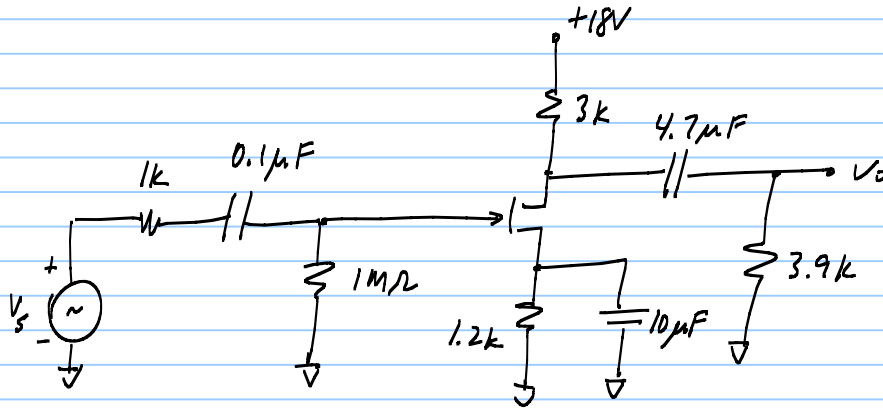

$$I_{DSS} = 6\text{mA}$$

$$V_p = -6, r_d = \infty \Omega$$

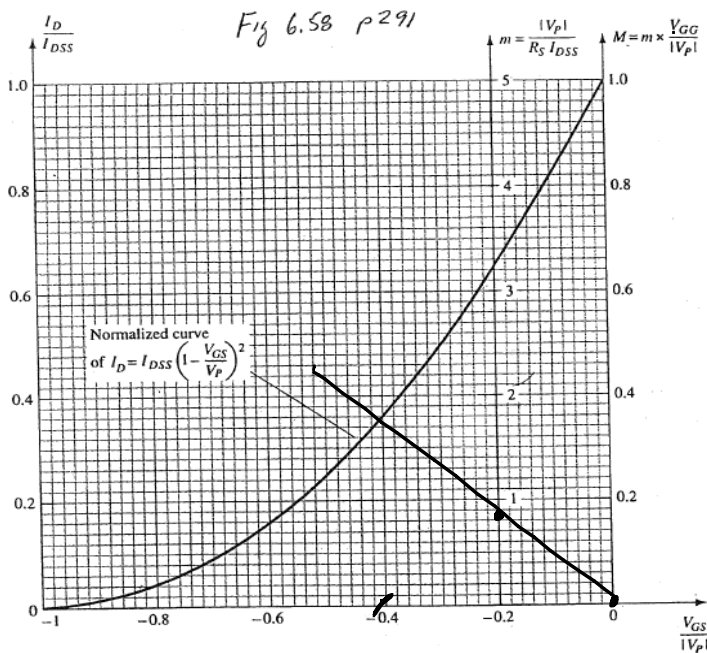

$$V_{GG} = 0V$$

$$m = \frac{6}{1.2K \cdot 6mA} = 0.833$$

$$M = 0.833 \cdot \frac{0}{6} = 0$$

$$V_{GSQ} = (-0.4)(6) = -2.4V$$

$$g_m = \left(\frac{2 I_{DSS}}{|V_p|} \right) \left(1 - \frac{V_{GSQ}}{V_p} \right) = \frac{2(6mA)}{6} \left(1 - \frac{-2.4}{-6} \right)$$

$$g_m = 1.2\text{mS}$$

$$A_{v_L} = -g_m(R_o \parallel R_L) = -1.2m(3k \parallel 3.9k) = -2.03$$

$$Z_{in} = 1M\Omega$$

$$Z_{out} = 3k$$

$$C_{w_L} = 3pF \quad C_{gd} = 4pF$$

$$C_{w_0} = 5pF \quad C_{gs} = 6pF$$

$$C_{ds} = 1pF$$

$$C_{m_i} = (1 - A_{v_L})C_{gd} = (1 + 2)(4pF) = 12pF$$

$$C_{m_0} = \left(1 - \frac{1}{A_{v_L}} \right) C_{gd} = \left(1 + \frac{1}{2} \right) (4pF) = 6pF$$

$$f_{H_i} = \frac{1}{2\pi(R_s \parallel r_{in})(C_{m_i} + C_{gs} + C_{m_0})} = \frac{1}{2\pi(1k \parallel 1M)(3pF + 6pF + 12pF)} = 7.59\text{MHz}$$

$$f_{H_0} = \frac{1}{2\pi(R_o \parallel R_L)(C_{w_0} + C_{ds} + C_{m_0})} = \frac{1}{2\pi(3k \parallel 3.9k)(5pF + 1pF + 6pF)} = 7.82\text{MHz}$$