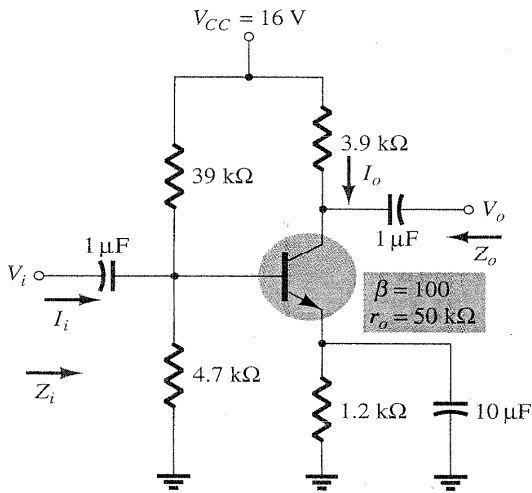


15)




a) Determine  $r_e$ . Requires DC analysis.

$$V_{TH} = \frac{16(4.7k)}{4.7k + 39k} = 1.721V$$

Thevenin analysis quickest.

$$R_{TH} = 39k // 4.7k = 4.195k$$

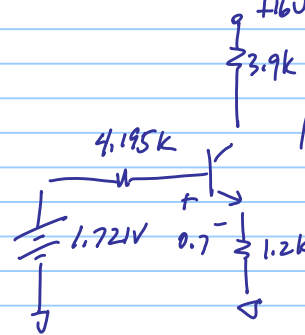

KVL:

$$\beta = 100 \quad 0 = 1.721 - I_B(4.195k) - 0.7 - 1.2k I_E$$

$$1.021 = I_B(4.195k) + (\beta + 1)I_B(1.2k)$$

$$1.021 = I_B(4.195k + (101)(1.2k))$$

$$1.021 = I_B(4.195k + 121.2k)$$

$$I_B = 1.021 / (4.195k + 121.2k)$$



$$I_B = 8.142 \mu A$$

$$I_E = (\beta + 1)I_B = (101)(8.142 \mu A)$$



$$I_E = 0.822 mA$$


$$\text{Finally } r_e = \frac{0.026}{I_E} = \boxed{31.6 \Omega = r_e}$$

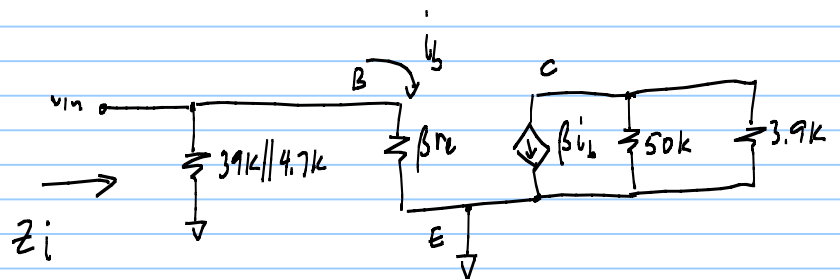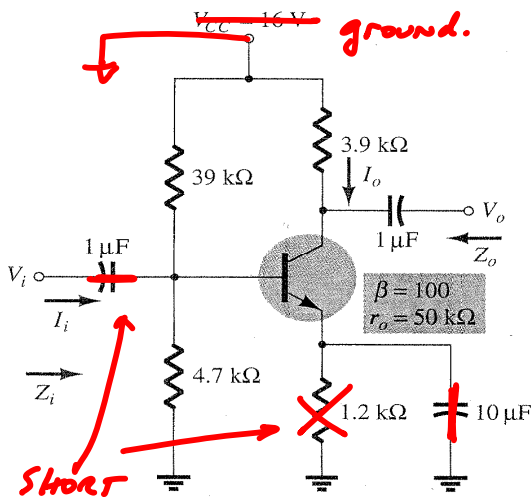b) Use  $r_e$ . Now draw ac model. Red shows shorts for ac model.



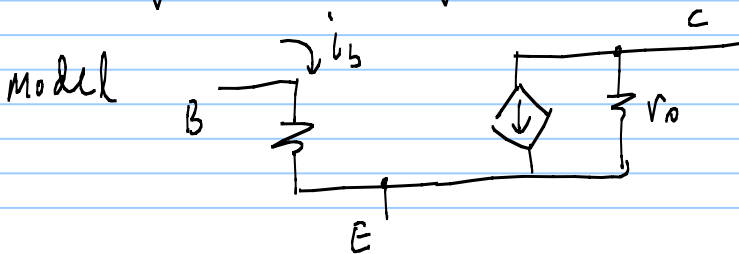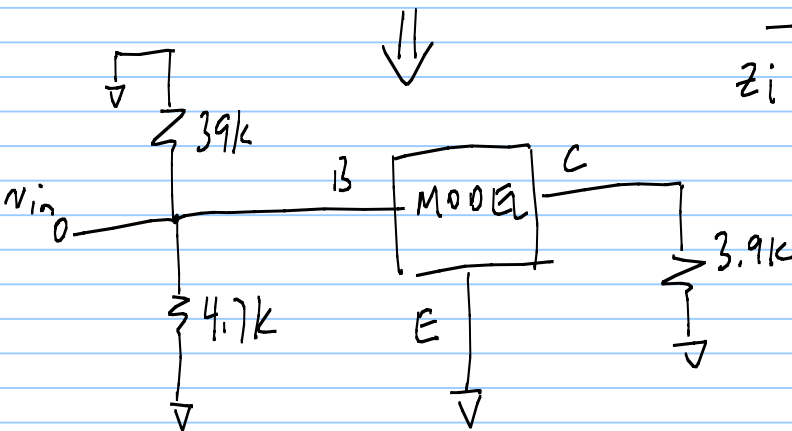plugged in transistor model.  
39k in parallel to 4.7k.



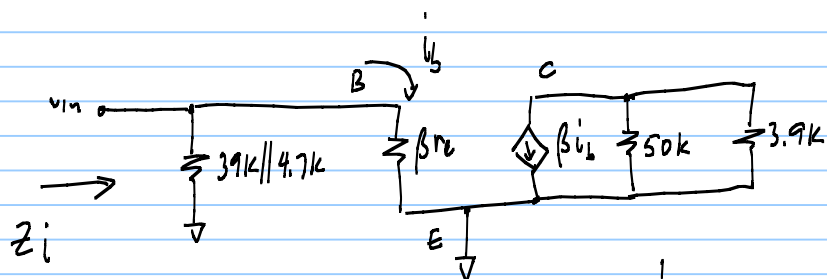


$$z_i = 39k \parallel 4.7k \parallel \beta r_e = \frac{1}{\frac{1}{39k} + \frac{1}{4.7k} + \frac{1}{(100)(31.6)}} = 1.802k$$

\* Using approx. method instead of Thevenin.

$$V_B = 1.721V, V_E = 1.021V \quad \therefore I_E = \frac{1.021}{1.2k} = 0.851mA \quad \therefore r_e = \frac{0.026}{I_E} = 30.56\Omega$$

$$z_i = \frac{1}{\frac{1}{39k} + \frac{1}{4.7k} + \frac{1}{(100)(30.56)}} = 1.77k, \text{ slightly different}$$

Output resistance

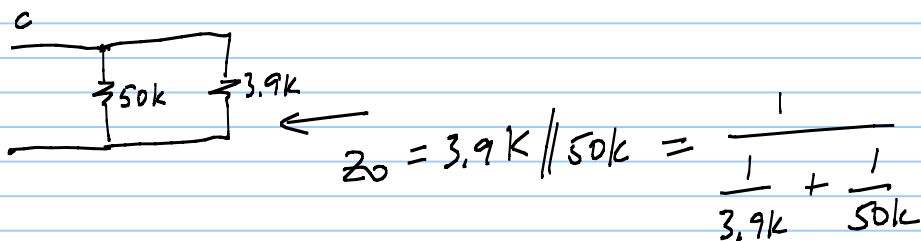

$$z_o = 3.62k\Omega$$


\* if  $r_o$  ignored,  $z_o = 3.9k$

Gain:

$$A_v = \frac{-R_c \parallel r_o}{r_e} = \frac{-3.9k \parallel 50k}{31.6} = -114.5$$

Repeat for  $r_o = 25k$ . Does not change  $r_e$  or  $Z_{in}$ .  $Z_{out}$  &  $A_v$  changed.

output resistance

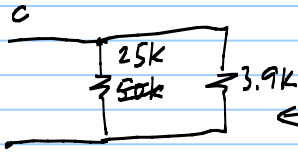


$$Z_o = 3.9k \parallel 25k = \frac{1}{\frac{1}{3.9k} + \frac{1}{25k}}$$

$$Z_o = 3.37k$$


Gain:

$$A_v = \frac{-R_c \parallel r_o}{r_e} = \frac{-3.9k \parallel 25k}{31.6} = -106.8$$

19)

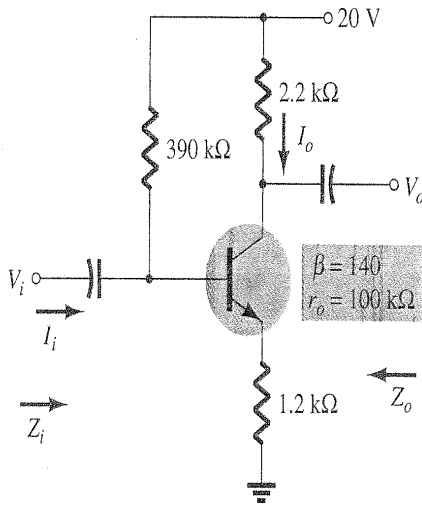

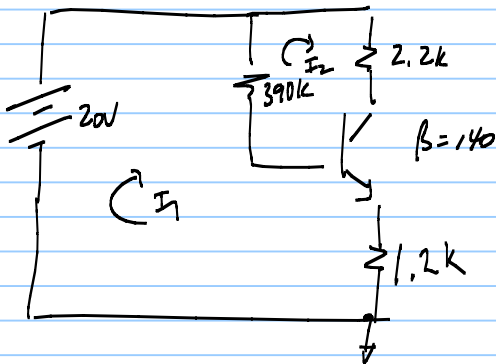a) Determine  $r_e$ . Requires DC analysis.



MESH  
#1

$$20 - 390k I_1 + 390k I_2 - 0.7 - I_1(1.2k) = 0$$

$$19.3 = 391.2k I_1 - 390k I_2$$

MESH

$$\#2 \quad I_C = \beta I_B$$

$$I_2 = \beta (I_1 - I_2)$$

$$I_2 = \beta I_1 - \beta I_2 \quad I_2 + \beta I_2 = \beta I_1$$

$$\beta I_1 - (\beta + 1) I_2 = 0$$

$$140 I_1 - 141 I_2 = 0$$

$$\#1 \quad 19.3 = 391.2k I_1 - 390k I_2$$




$$+ \quad 0 = -387.23k I_1 + 390k I_2$$

$\times -390k$  to make  $I_2$  go away.  
 $\frac{141}{140}$


$$19.3 = 3.966k I_1$$

$$I_1 = 4.866mA = I_E \Rightarrow r_e = \frac{0.026}{I_E} = 5.34\Omega$$

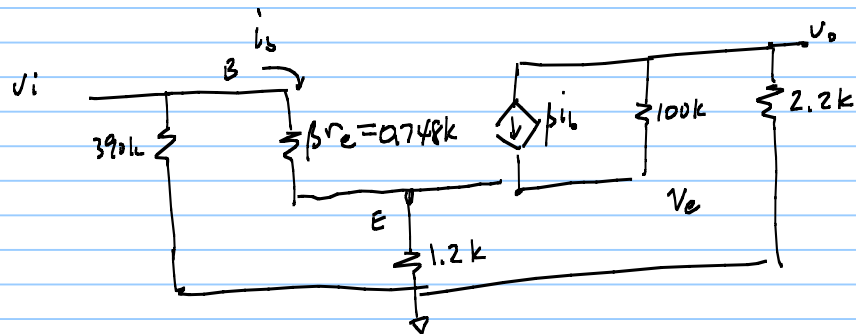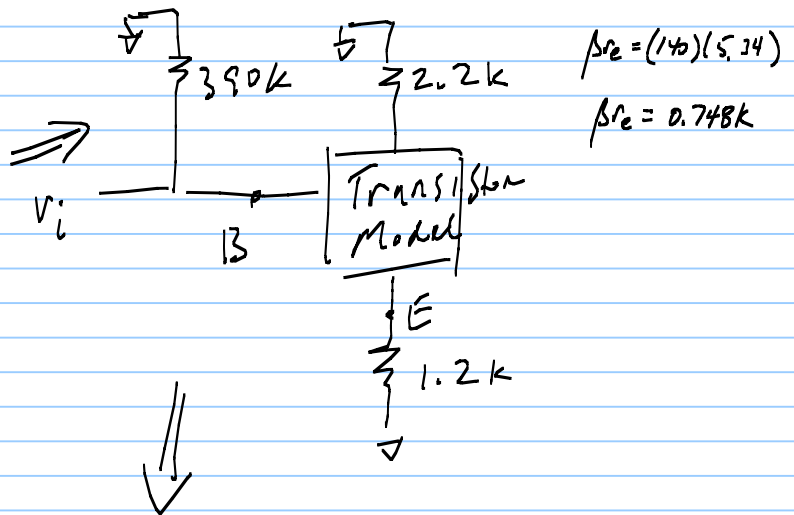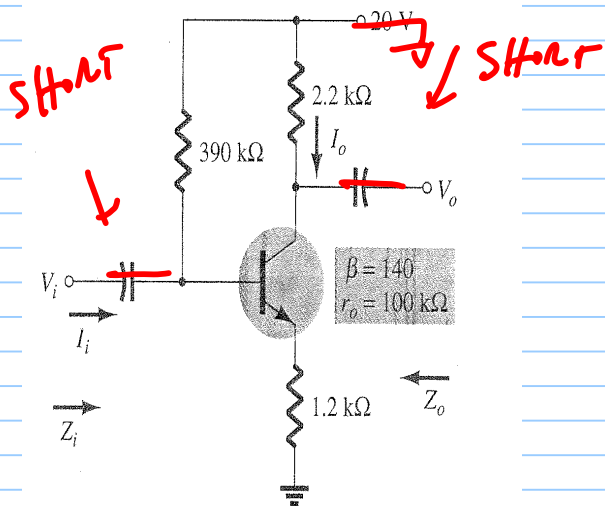
b) next,  $z_i$  &  $z_o$  requires ac model



25)

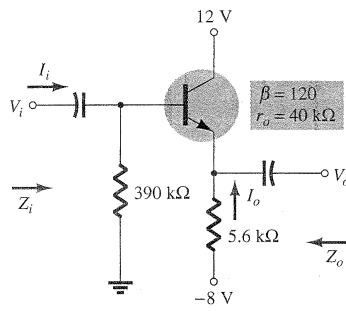

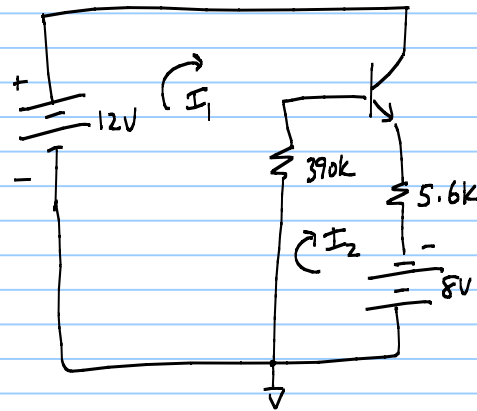As with all others, find  $r_e$  first. Requires DC analysis.



#1  $I_c = \beta I_B$

$$I_1 = \beta(I_2 - I_1) = \beta I_2 - \beta I_1$$

$$(1 + \beta) I_1 - \beta I_2 = 0$$

$$121 I_1 - 120 I_2 = 0$$

$$\rightarrow \times \frac{395.6k}{121}$$

#2

$$8 - 0.7 = I_1(390k + 5.6k) - I_2(390k)$$

$$7.3 = 395.6k I_1 - 390k I_2$$


$$7.3 = 395.6k I_1 - 390k I_2$$

$$0 = -395.6k I_1 + 392.33k I_2$$


$$7.3 = 2.331k I_2 \Rightarrow I_2 = 3.132mA \Rightarrow r_e = \frac{0.026}{I_E}$$

$$\text{w/ } I_c = I_E, \quad r_e = 8.301\Omega$$

multiply by 1/4 add.


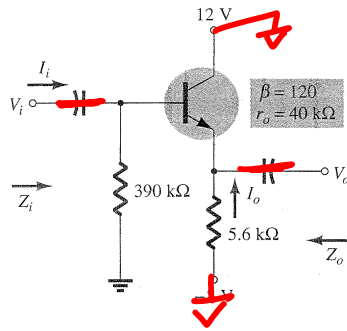

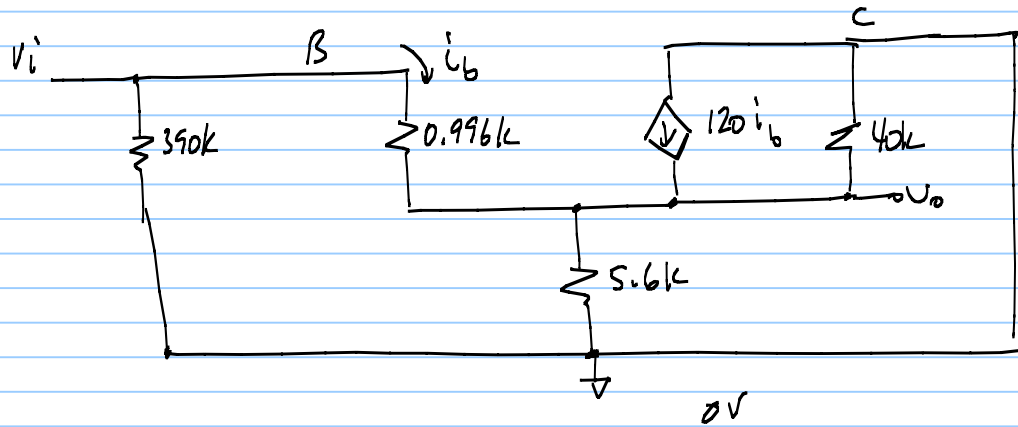
$$\beta r_o = (120)(8.301 \Omega) = 0.996 \text{ k}\Omega$$



← ground  
for whole  
node!

29)

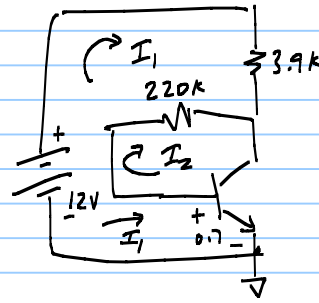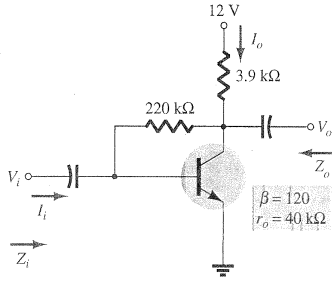

#1  $12 - I_1(3.9k) - 220k I_1 + 220k I_2 - 0.7 = 0$

$11.3 = 223.9k I_1 - 220k I_2$

#2  $I_C = \beta I_B$   $I_2 = \beta(I_1 - I_2) = \beta I_1 - \beta I_2 = 120 I_1 - 120 I_2$

$0 = 120 I_1 - 121 I_2$

$\rightarrow 11.3 = 223.9k I_1 - 220k I_2$

$0 = -218.182k I_1 + 220k I_2$

$11.3 = 5.718k I_1$

$I_1 = 1.976mA = I_E$

$r_c = 26mV / 1.976mA = 13.156\Omega = r_e$

$\beta r_c = (120)(13.15) = 1.578k$

AC model: short 12V, short caps.

