


Chapter 7 # 2a, 35-37 (use universal curve to find I_{DQ} & V_{GSQ} . Then find V_{DSQ})

26, 27, 28

Note Title

8/11/2018

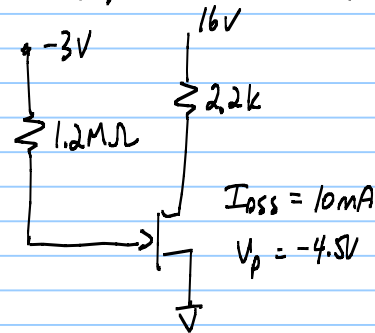2a) For the fixed-bias configuration below find I_{DQ} and V_{GSQ} using a purely mathematical approach.



$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$= 10\text{mA} \left(1 - \frac{-3}{-4.5}\right)^2 = 1.11\text{mA}$$



$$V_{DSQ} = 16 - I_{DQ}(2.2\text{k}) = +13.6\text{V}$$

Verify in sat:

$$|V_{DS}| > |V_p| - |V_{GS}|$$

$$13.6 > 4.5 - 3 = 1.5 \quad \checkmark$$

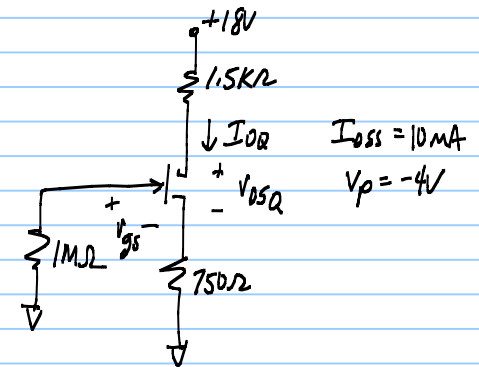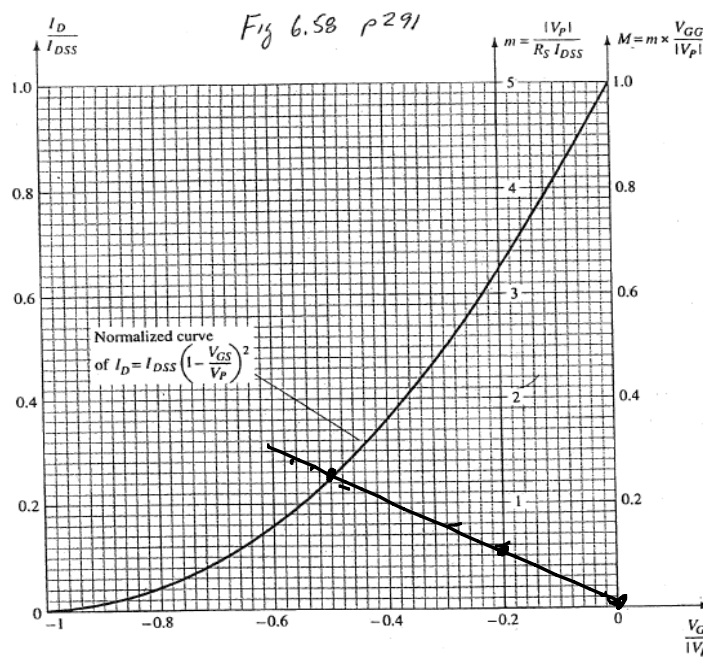35 → #6 w/ universal curve. Find I_{DQ} & V_{GSQ} . Then find V_{DSQ} .



$$m = \frac{4}{750 \cdot 10\text{mA}} = 0.533$$

$$M = 0.533 \cdot \frac{0}{4} = 0$$



$$\frac{I_D}{I_{DSS}} = 0.26 \quad I_{DQ} = 2.6\text{mA}$$

$$\frac{V_{GS}}{|V_p|} = -0.5 \quad V_{GSQ} = -2\text{V}$$

$$V_{DSQ} = 18 - 2.6\text{mA}(1.5\text{k} + 0.75\text{k}) = 12.15\text{V}$$

$$\text{check } |V_{DS}| > |V_p| - |V_{GS}| \quad 12.5 > 4 - 2 \quad \checkmark \text{ SAT}$$

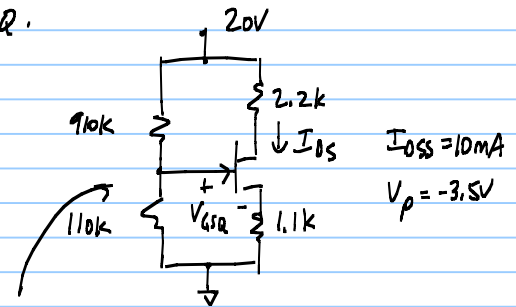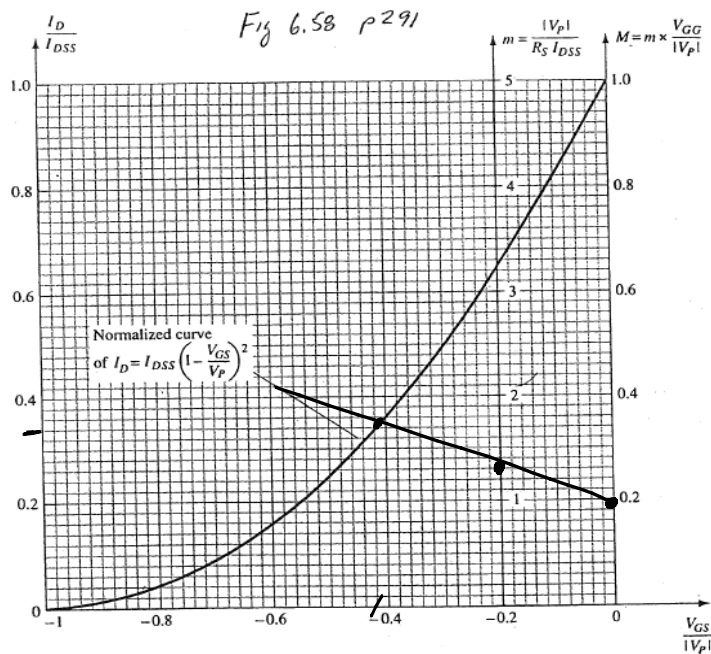36 → #12 w/ universal curve. Find I_{DQ} & V_{GSQ} . Then find V_{DSQ} .



$$V_{GG} = \frac{20(110k)}{90k + 110k} = 2.15V$$

$$m = \frac{3.5V}{(1.1k)(10mA)} = 0.318$$

$$M = 0.318 \frac{(2.15)}{3.5} = 0.195$$

$$I_{DQ} = (0.34)(10mA) = 3.4mA$$


$$V_{GSQ} = (-0.42)(3.5) = -1.47V$$

$$V_{DSQ} = 20 - 3.4mA(2.2k + 1.1k) = 8.78V$$

$$\text{Check sat. } |V_{DSQ}| > |V_P| - |V_{GSQ}|$$


$$8.78 > 3.5 - 1.47 \quad \checkmark$$

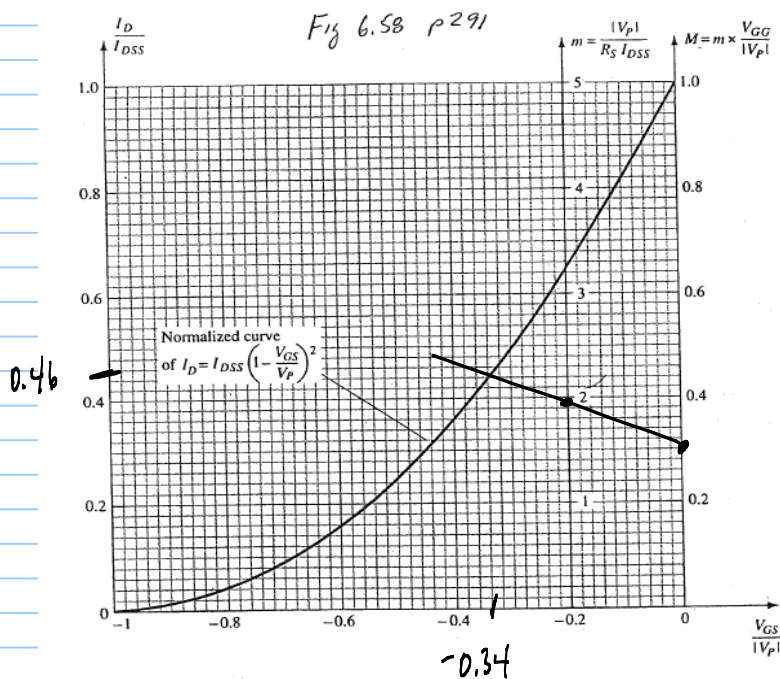37 → #16 w/ universal curve. Find I_{DQ} & V_{GSQ} . Then find V_{DSQ} .



$$V_{DSQ} = 16 + 4 - 2.76 \text{ mA} (2.2 \text{ k} + 2.2 \text{ k})$$
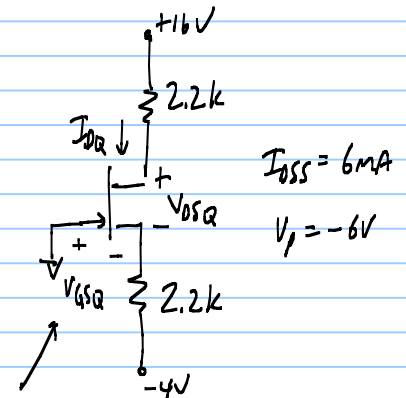
$$V_{DSQ} = 7.86 \text{ V} \quad (> 6 - 2.04 \quad \checkmark)$$



error
in book.
they labeled
as V_{DSQ} .

$$V_{GG} = V_{GS} \text{ when } I_D = 0$$

$$V_{GG} = 4 \text{ V}$$


$$m = \frac{6}{(2.2 \text{ k}) 6 \text{ mA}} = 0.45$$

$$M = 0.45 \frac{4}{6} = 0.3$$

$$I_{DQ} = (6 \text{ mA})(0.46) = 2.76 \text{ mA}$$

$$V_{GSQ} = (6 \text{ V})(-0.34) = -2.04 \text{ V}$$

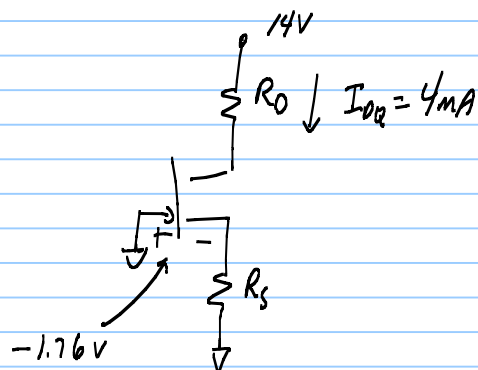- *26 Design a self-biased network using a JFET transistor with $I_{DSS} = 8\text{mA}$ and $V_p = -6\text{V}$ to have a Q point at $I_{DQ} = 4\text{mA}$ using a supply of 14V . Assume that $R_D = 3R_S$ and use standard values.



$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$4\text{mA} = 8\text{mA} \left(1 - \frac{V_{GS}}{6}\right)^2$$

$$\sqrt{0.5} = 1 - \frac{V_{GS}}{6}$$

$$\frac{V_{GS}}{6} = 1 - 0.707 \quad V_{GSQ} = -1.76\text{V}$$

So voltage across R_S is also 1.76

$$R_S = \frac{1.76}{4\text{mA}} = 440\Omega$$

$$\boxed{\text{use } R_S = 470\Omega}$$


Closest

$$R_D = 3R_S = 1410$$

$$\boxed{\text{use } R_D = 1.2\text{k}}$$

went down because R_S went up. Balance it out.

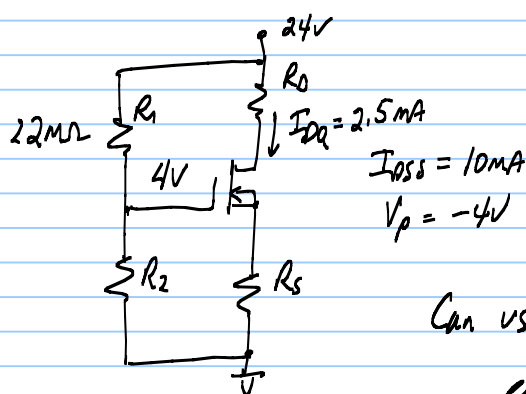- *27 Design a voltage divider bias network using a depletion type MOSFET with $I_{DSS} = 10\text{mA}$ and $V_p = -4\text{V}$ to have a Q-point at $I_{DQ} = 2.5\text{mA}$ using a supply of 24V . In addition, set $V_G = 4\text{V}$ and $R_D = 2.5R_S$ with $R_1 = 22\text{M}\Omega$. Use standard values.




$$\text{Current in } R_1 = \frac{24 - 4}{22\text{M}} = 0.91\mu\text{A}$$

$$R_2 = \frac{4\text{V}}{0.91\mu\text{A}} = 4.4\text{M}\Omega$$

↑ same current as R_1 since $I_G = 0$

Can use plot or equation to convert I_{DQ} to V_{GSQ} . Last problem used

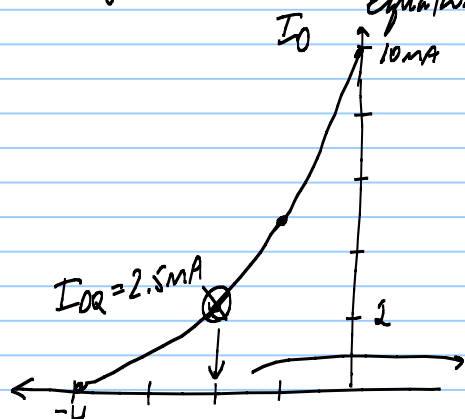equation so I will use a plot on this one




V_{GS}	I_D
-4	0
-2	2.5mA
-1.2	5mA
0	10mA

$$R_S = \frac{2\text{V}}{2.5\text{mA}} = 2.4\text{k} \quad \text{pick } \underline{\underline{2.2\text{k}}}$$

$$R_D = 2.5R_S = 6\text{k} \quad \text{pick } \underline{\underline{5.6\text{k}}}$$
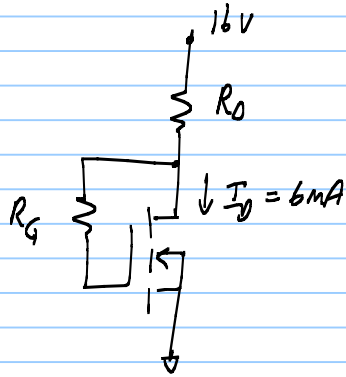
#28 Design the network below using an Enhancement type MOSFET with $V_{GS(TH)} = 4V$ and $K = 0.5 \times 10^{-3} A/V^2$ to have a Q point of $I_{DQ} = 6mA$. Use a supply of 16V and standard values.



Draw drain curve to solve OR use equation.

Equation easier.

$$I_D = K (V_{GS} - V_{GS(TH)})^2$$

$$4mA = 0.5mA/V^2 (V_{GS} - 4)^2$$

$$\sqrt{8} = V_{GS} - 4 \quad V_{GSQ} = 6.83V = V_{GSQ}$$

$$R_D = \frac{16 - 6.83}{6mA} = 1.53K \Rightarrow \text{use } \boxed{1.8K = R_D}$$

R_G can be any $M\Omega$ resistor.