


- 4) What is the reactance of a  $10\text{-}\mu\text{F}$  capacitor at a frequency of  $1\text{ kHz}$ ? For networks in which the resistor levels are typically in the kilohm range, is it a good assumption to use the short-circuit equivalence for the conditions just described? How about at  $100\text{ kHz}$ ?

$X_C$  is reactance  $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi (1\text{ kHz}) (10\text{ }\mu\text{F})} = 15.92\Omega$

yes,  $\sim 1.5\%$  of the resistor values.



$X_C @ 100\text{ kHz} \Rightarrow X_C = \frac{1}{2\pi (100,000) (10\text{ }\mu\text{F})} = 0.1592\Omega$  less than  $1\Omega$   
Totally insignificant

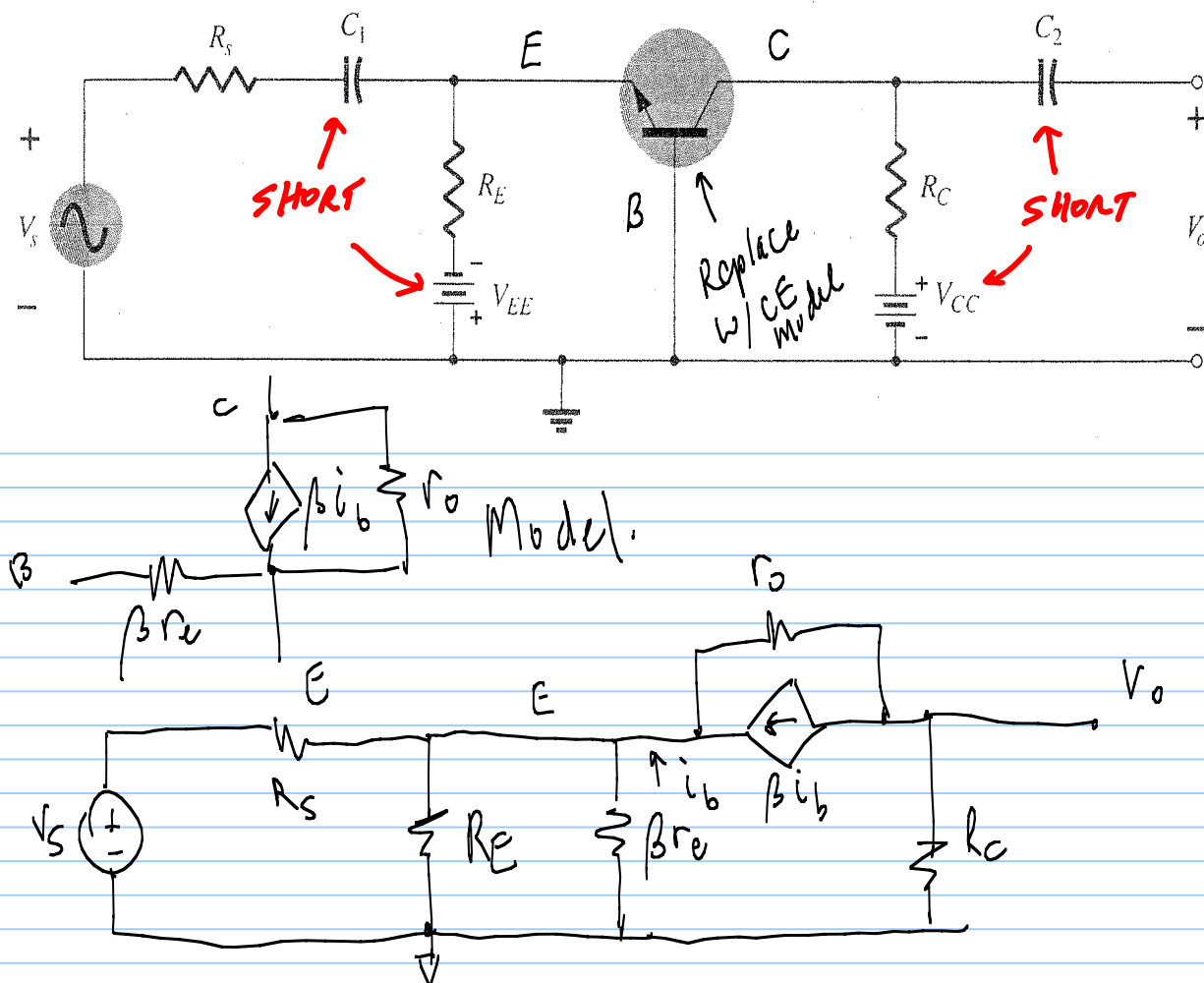- 5) Sketch the ac equivalent of the common base circuit. Use the model in 5.16.




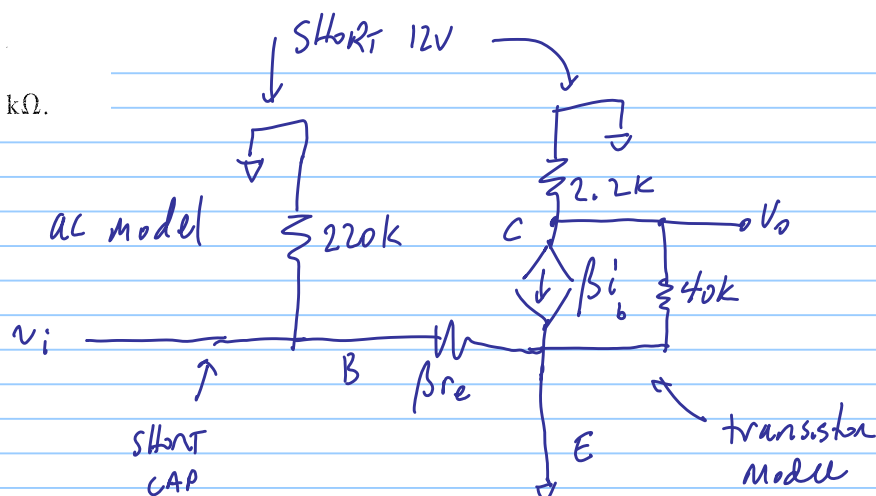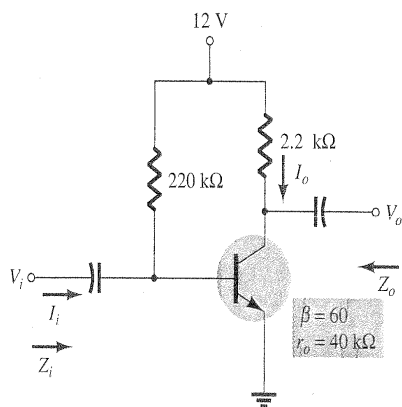11)

- Determine  $Z_i$  and  $Z_o$ .
- Find  $A_v$ .
- Repeat parts (a) and (b) with  $r_o = 20 \text{ k}\Omega$ .




clean up.

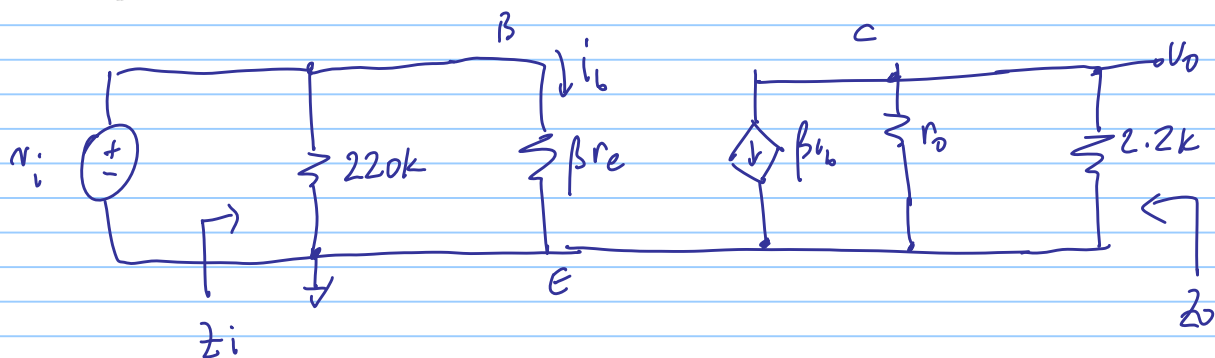

DC analysis to find  $I_E$  & then  $r_e$ .

$$I_B = \frac{12 - 0.7}{220k} = 51.36 \mu A \quad I_E = (\beta + 1) I_B = 3.133 \text{ mA} \quad r_e = \frac{0.026}{I_E} = 8.3 \Omega$$

$$\beta r_e = 498 \Omega$$

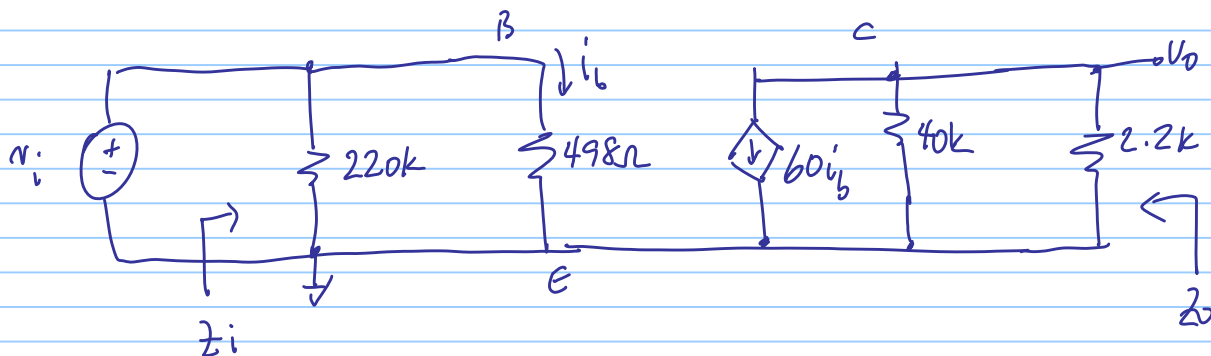

$$Z_i = R_B \parallel \beta r_e = 220k \parallel 498 \Omega = 492 \Omega$$

$$Z_o = R_C \parallel r_o = 40k \parallel 2.2k = 2.09k$$

$$A_v = \frac{-R_c \parallel r_o}{r_e} = \frac{-40k \parallel 2.2k}{8.3} = -251$$

c) Repeat w/  $r_o = 20k$

$Z_i$  unchanged.  $497\Omega$

$$Z_o = 2.2k \parallel 20k = 1.98k$$

$$v_o = \frac{(20k \parallel 2.2k)}{8.3} = -238$$