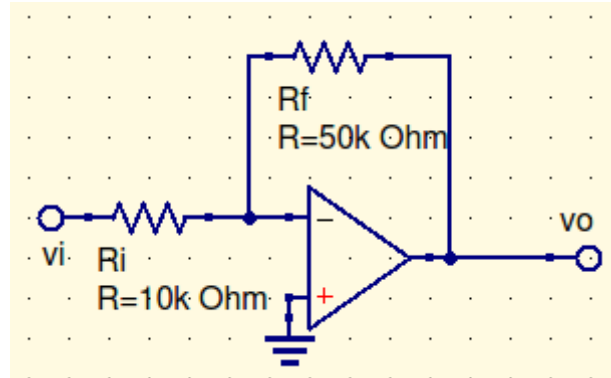


Skyler MacDougall

Homework 1: Due 1/20/2020

Chapter 2

1. Consider the circuit of Figure P2-1 with $R_i = 10k\Omega$ and $R_f = 50k\Omega$



1. Determine the closed-loop voltage gain.

$$A_{CL} = \frac{V_o}{V_i} = \frac{R_f}{R_i} = -5 \quad (1)$$

2. Determine the input impedance of the circuit.

$$r_i = R_i = 10k\Omega \quad (2)$$

3. Determine the ideal output impedance of the circuit.

$$r_o = 0\Omega \quad (3)$$

4. Determine the peak input voltage v_i (peak) for which linear operation is possible.


$$V_{ipk} = \frac{V_{sat}}{|A_{CL}|} = \left(\frac{13}{5}\right) \text{ or } \left(2\frac{3}{5}\right) \quad (4)$$

5. Determine the output voltage for each of the following values for the following input voltages.

$$V_o = A_{CL} v_i \quad (5)$$

v_i (V)	v_o (V)
0	0
-1	5
2	-10
-3	15
4	-20

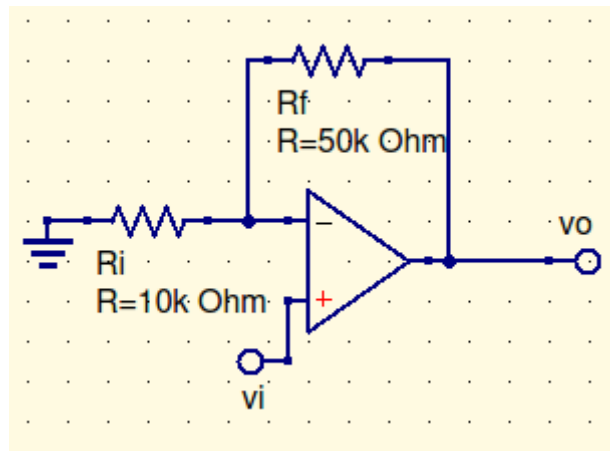3. Consider the circuit of Figure P2-3 with $R_i = 10k\Omega$ and $R_f = 50k\Omega$



1. Determine the closed-loop voltage gain.

$$A_{CL} = \frac{V_o}{V_i} = \frac{R_f + R_i}{R_i} = \frac{6}{5} \quad (6)$$

2. Determine the input impedance of the circuit.

$$r_i = R_i = 10k\Omega \quad (7)$$

3. Determine the ideal output impedance of the circuit.

$$r_o = 0\Omega \quad (8)$$

4. Determine the peak input voltage v_i (peak) for which linear operation is possible.

$$V_{ipk} = \frac{V_{sat}}{|A_{CL}|} = \left(\frac{13(5)}{6}\right) \text{ or } \left(10\frac{5}{6}\right) \quad (9)$$

5. Determine the output voltage for each of the following values for the following input voltages.

$$V_o = A_{CL} v_i \quad (10)$$

v_i (V)	v_o (V)
0	0
-1	$-\frac{6}{5}$
2	$\frac{12}{5}$
-3	$-\frac{18}{5}$
4	$\frac{24}{5}$

5. For the circuit of Problem 2-1 with $v_i = -2V$, assume an external load of $R_L = 2k\Omega$ is connected to the output. Determine the total op-amp output current.

$$A_{CL} = -10 \quad (11)$$

$$v_i = 2V$$

$$v_o = -20V$$

$$\frac{V}{R} = I$$

$$\frac{20V}{2k\Omega} = I = \frac{1}{100} A = 10mA$$