

Electronics 2

TEST 2

Professor Cliver ENT-2156

(EEET-221 15442)

Name: _____

Class time (ex. 1 p.m.): _____

1. If $V_{IN1} = 6V$, $V_{IN2} = 2V$, $V_{O(SAT)} = \pm 13V$ and, $R_L = 5K\Omega$ in figure 1, determine the output voltage V_O of the comparator.
 - (a) -13 V
 - (b) 13 V
 - (c) 4 V
 - (d) 4.0 V
2. If $V_{IN1} = 6V$, $V_{IN2} = 1V$, $V_{O(SAT)} = \pm 13V$ and, $R_L = 4K\Omega$ in figure 1, determine the output current I_L of the comparator (the current through R_L).
 - (a) 1.25 mA
 - (b) 3.25 mA
 - (c) 0.88 mA
 - (d) -3.25 mA

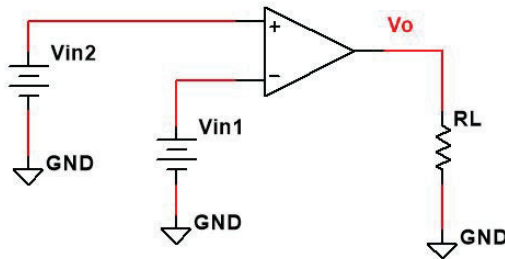



Figure 1

3. For a non-inverting amplifier with $R_f = 9K\Omega$, $R_i = 5K\Omega$ and the total RMS noise level referred to the input is $7\mu V$. Select the output noise level.
 - (a) $12.60\text{ }\mu V$
 - (b) $19.60\text{ }\mu V$
 - (c) $7.00\text{ }\mu V$
 - (d) $-12.60\text{ }\mu V$


4. An amplifier has a common mode gain of 30 dB and a differential gain of 110 dB. What is the CMRR (common mode rejection ratio)?
- (a) 110.00 dB
 - (b) 80.00 dB
 - (c) 3.67 dB
 - (d) 30.00 dB
5. An op-amp has a slew-rate of $5 \frac{V}{\mu s}$ and is configured as a non-inverting amplifier $R_F = 9.6K\Omega$ and $R_I = 4.2K\Omega$. If a 8.00mV peak sine wave is applied to the non-inverting input, determine the slew rate limiting frequency (maximum sine wave frequency).
- (a) 99.5 MHz
 - (b) 30.3 MHz
 - (c) 190.2 MHz
 - (d) 227.4 MHz
6. An op-amp has a unity gain frequency of 4 MHz and is configured as a non-inverting amplifier $R_f = 10.0K\Omega$ and $R_i = 4.4K\Omega$. Calculate the rise time (t_{CL}) associated with the amplifier.
- (a) 818.18 ns
 - (b) 1.22 ns
 - (c) 4.00 ns
 - (d) 286.36 ns

The problems on this page both use the same figure.

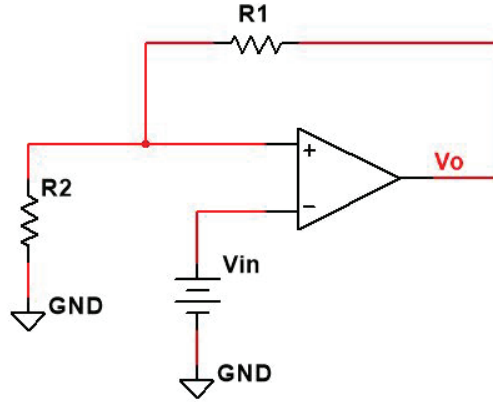7. Sketch the input-output characteristic curve given $R_1 = 8.1K\Omega$, $R_2 = 3.1K\Omega$ and $V_{O(SAT)} = \pm 13V$.




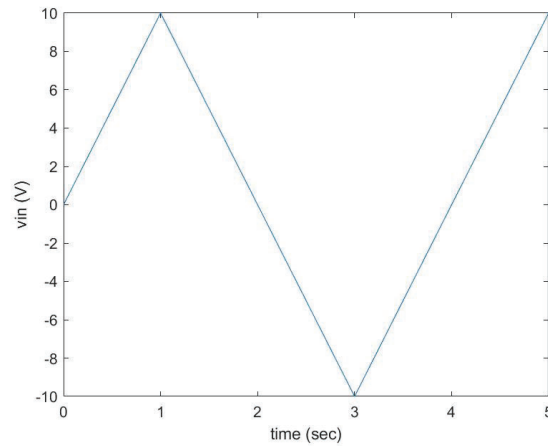8. Sketch the output curve given the input curve and $R_1 = 8.2K\Omega$, $R_2 = 4.6K\Omega$ and $V_{O(SAT)} = \pm 14V$.




The problems on this page both use the same figure.

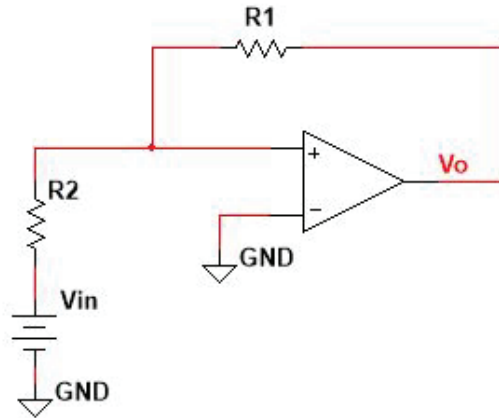9. Sketch the input-output characteristic curve given $R_1 = 9.4K\Omega$, $R_2 = 3.3K\Omega$ and $V_{O(SAT)} = \pm 13V$.




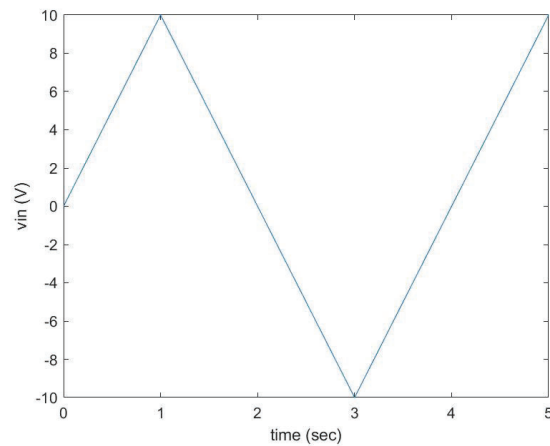10. Sketch the output curve given the input curve and $R_1 = 9.0K\Omega$, $R_2 = 4.9K\Omega$ and $V_{O(SAT)} = \pm 13V$.




The problems on this page both use the same figure.

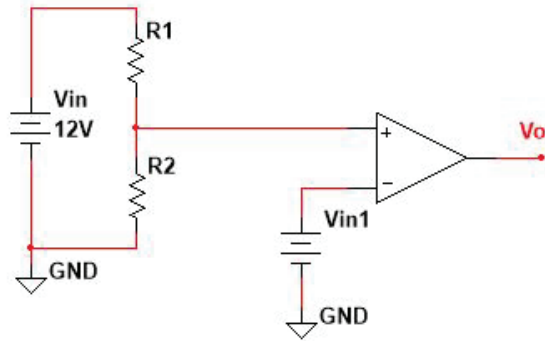11. Sketch the input-output characteristic curve (input is V_{in1}) given $R_1 = 9.6K\Omega$, $R_2 = 3.9K\Omega$ and $V_{O(SAT)} = \pm 13V$.



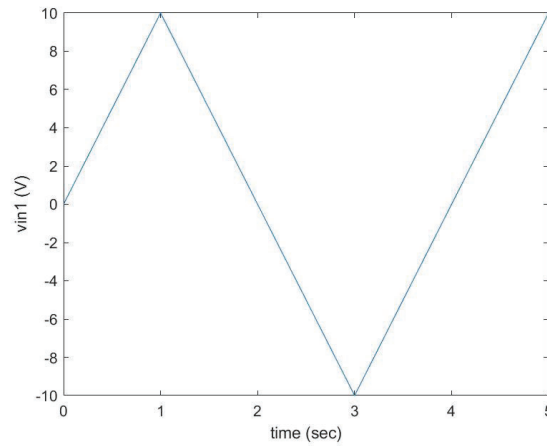12. Sketch the output curve given the input (V_{in1}) curve and $R_1 = 9.7K\Omega$, $R_2 = 3.2K\Omega$ and $V_{O(SAT)} = \pm 12V$.



13. What has been the most confusing point so far in the class?

This image shows a single sheet of white paper with horizontal blue or grey ruling lines. The lines are evenly spaced and run across the width of the page. There are approximately 20 lines visible. The paper has a slight shadow on the right side, suggesting it's resting on a surface.