

# Skyler MacDougall

## Exam 2

Due April 22<sup>nd</sup> at 8pm

1. If  $V_{IN1} = 6V$ ,  $V_{IN2} = 2V$ ,  $V_{O(SAT)} = \pm 13V$ ,  $R_L = 5k\Omega$  in the following image, determine the output voltage  $V_O$  of the comparator.

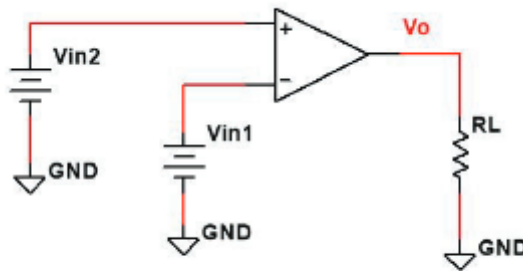


Figure 1

$$V_{IN1} > V_{IN2}; V_{IN1} = \text{inverting input} \quad (1)$$

$\therefore$

$$\boxed{|V_O = -13V = (a)|}$$

2. If  $V_{IN1} = 6V$ ,  $V_{IN2} = 1V$ ,  $V_{O(SAT)} = \pm 13V$ ,  $R_L = 4k\Omega$ , determine the output current  $I_L$  (the current through  $R_L$ ) of the comparator. (Using the comparator noted in question 1)

$$V_{IN1} > V_{IN2}; V_{IN1} = \text{inverting input} \quad (2)$$

$\therefore$

$$V_O = -13V$$

$$I_L = \frac{V_O}{R_L} = \frac{-13V}{4k\Omega}$$

$$\boxed{|I_L = -3.25mA = (d)|}$$

3. For a non-inverting amplifier with  $R_f = 9k\Omega$ ,  $R_i = 5k\Omega$  and the total RMS noise level referred to the input is  $7\mu V$ , select the noise level.

$$A = 1 + \frac{R_f}{R_i} = 1 + \frac{9k\Omega}{5k\Omega} = 2.8 \quad (3)$$

$$V_o = V_i * A = V_i = 7\mu V * 2.8$$

$$\boxed{|V_o \text{ Noise} = 19.6\mu V = (b)|}$$

4. An amplifier has a common mode gain of  $30dB$  and a differential gain of  $110dB$ . What is the common mode rejection ratio?

$$CMRR = 20\log\left(\frac{A_d}{|A_{cm}|}\right) \quad (4)$$

$$CMRR = 20\log\left(\frac{110dB}{|30dB|}\right)$$

$$CMMR = 11.28dB$$

🧑 (c)

5. An op-amp has a slew-rate of  $5 \frac{V}{\mu s}$  and is configured as a non-inverting amplifier, with  $R_f = 9.6k\Omega$ ,  $R_i = 4.2k\Omega$ . If an  $8.00mV$  peak sine wave is applied to the non-inverting input, determine the slew-rate limiting frequency.

$$f_{sr} = \frac{S}{2\pi V_o}; V_o = V_i * (1 + \frac{R_f}{R_i}) \quad (5)$$

$$f_{sr} = \frac{S}{2\pi V_i * (1 + \frac{R_f}{R_i})}$$

$$f_{sr} = \frac{5 \frac{V}{\mu s}}{2 * \pi * 8mV * (1 + \frac{9.6k\Omega}{4.2k\Omega})}$$

$$f_{sr} = \frac{5}{2 * \pi * 0.0008 * 3.28} MHz$$

$$|f_{sr} = 30.27 MHz \approx 30.3 MHz = (a)|$$

6. An op-amp has a unity gain frequency of  $4MHz$  and is configured as a non-inverting amplifier with  $R_f = 10.0k\Omega$ ,  $R_i = 4.4k\Omega$ . Calculate the rise time ( $t_{CL}$ ) associated with the amplifier.

$$T_{sr} = \frac{0.35}{BW}; BW = \frac{B}{k_n}; k_n = 1 + \frac{R_f}{R_i} \quad (6)$$

$$T_{sr} = \frac{0.35}{\frac{B}{1 + \frac{R_f}{R_i}}}$$

$$T_{sr} = \frac{0.35}{\frac{4MHz}{1 + \frac{10.0k\Omega}{4.4k\Omega}}}$$

$$T_{sr} = \frac{0.35}{\frac{4}{3.27}} \mu s$$


$$|T_{sr} = 286.36 ns = (d)|$$


7. Sketch the input characteristic curve given the below image and:

$$R_1 = 8.1k\Omega \quad (7)$$

$$R_2 = 3.1k\Omega$$

$$V_{O(STAT)} = \pm 13V$$

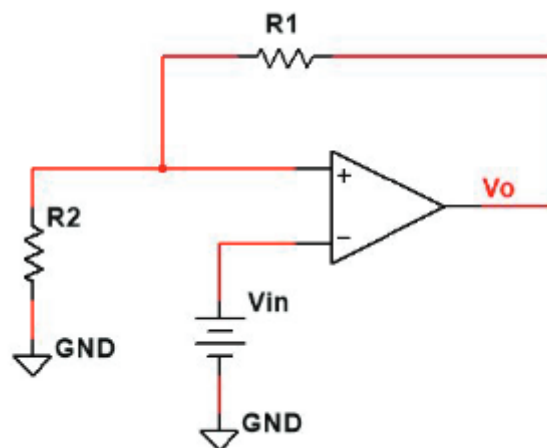

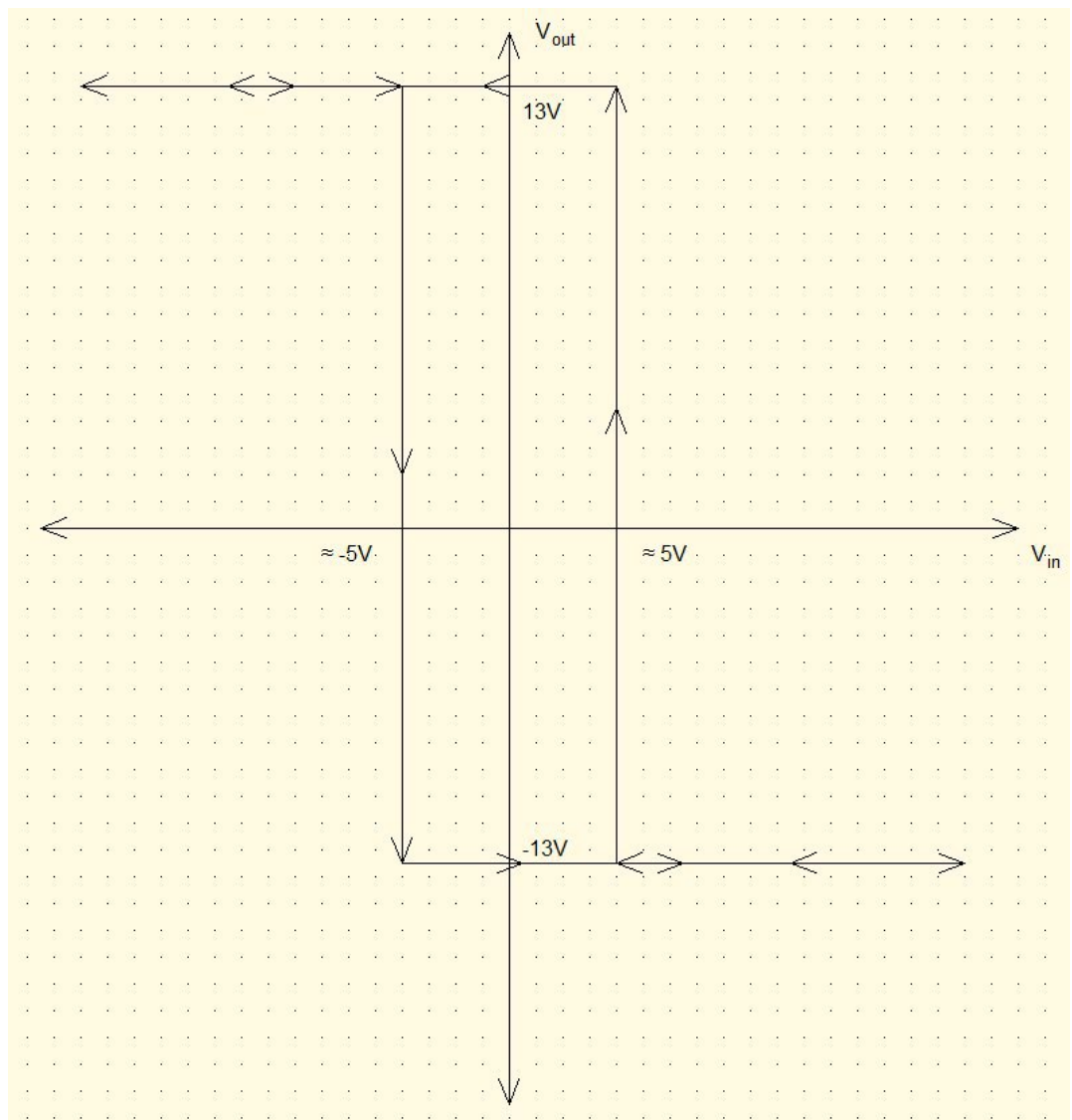



8. Sketch the output curve given the input curve shown below and the following:

$$R_1 = 8.2k\Omega \quad (8)$$

$$R_2 = 4.6k\Omega$$

$$V_{O(SAT)} = \pm 14V$$

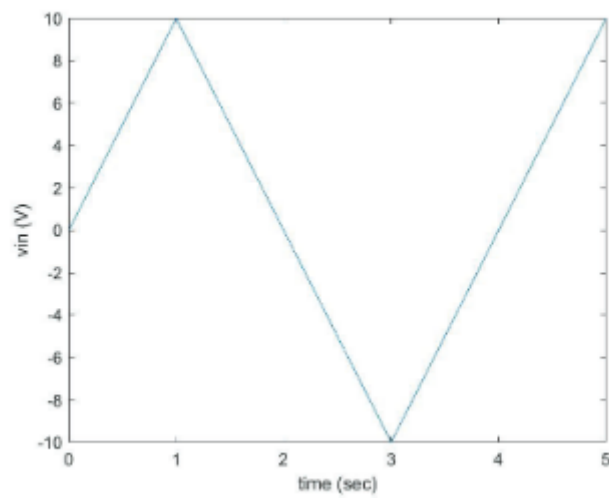

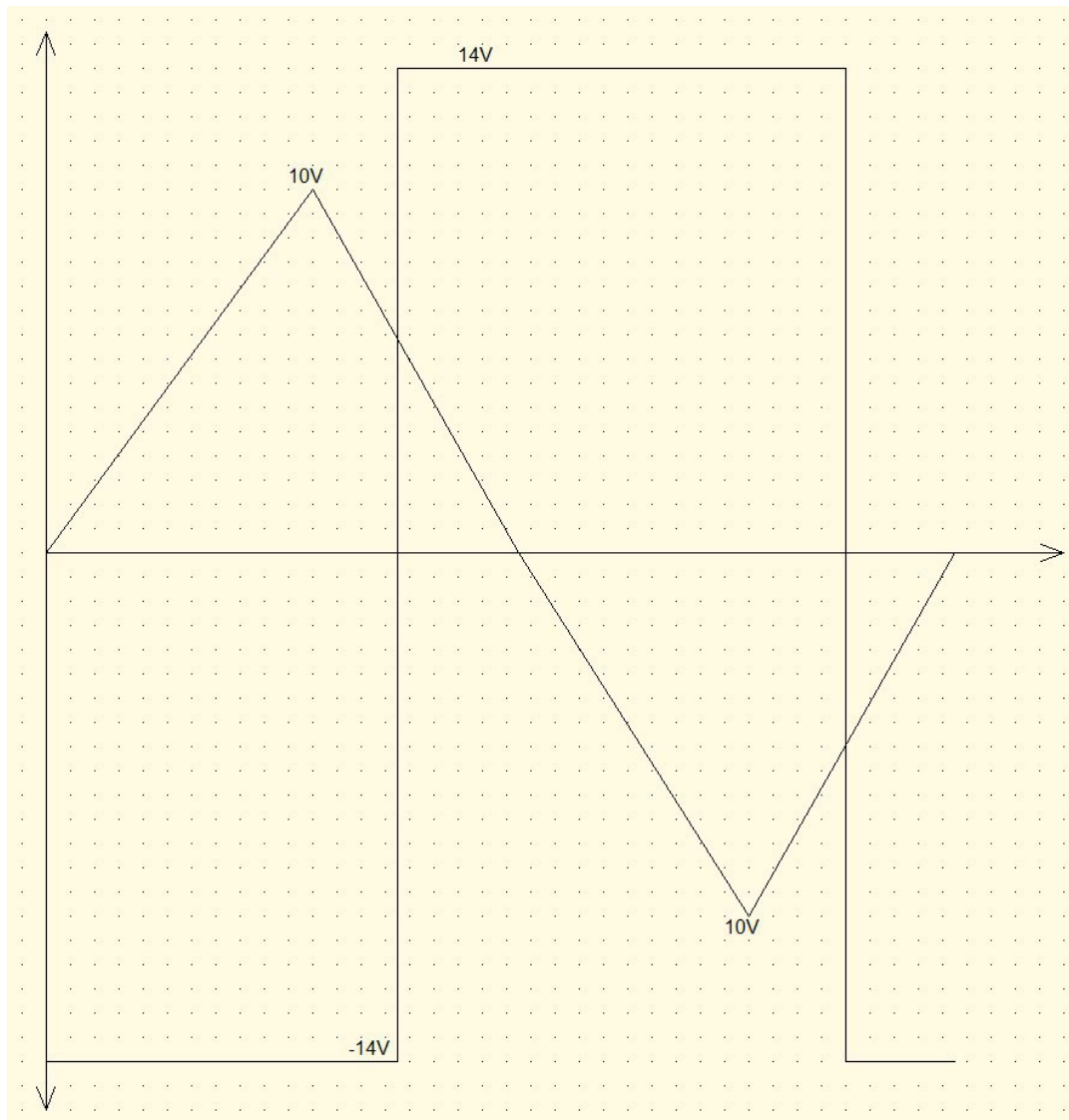


9. Sketch the input-output characteristic curve given the image below and the following:


$$R_1 = 9.4k\Omega$$

(9)

$$R_2 = 3.3k\Omega$$

$$V_{O(SAT)} = \pm 13V$$

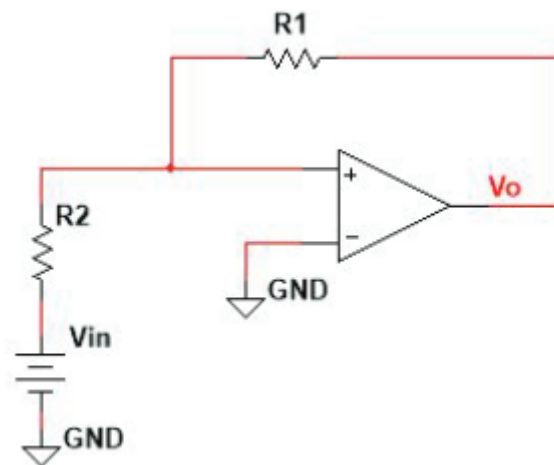

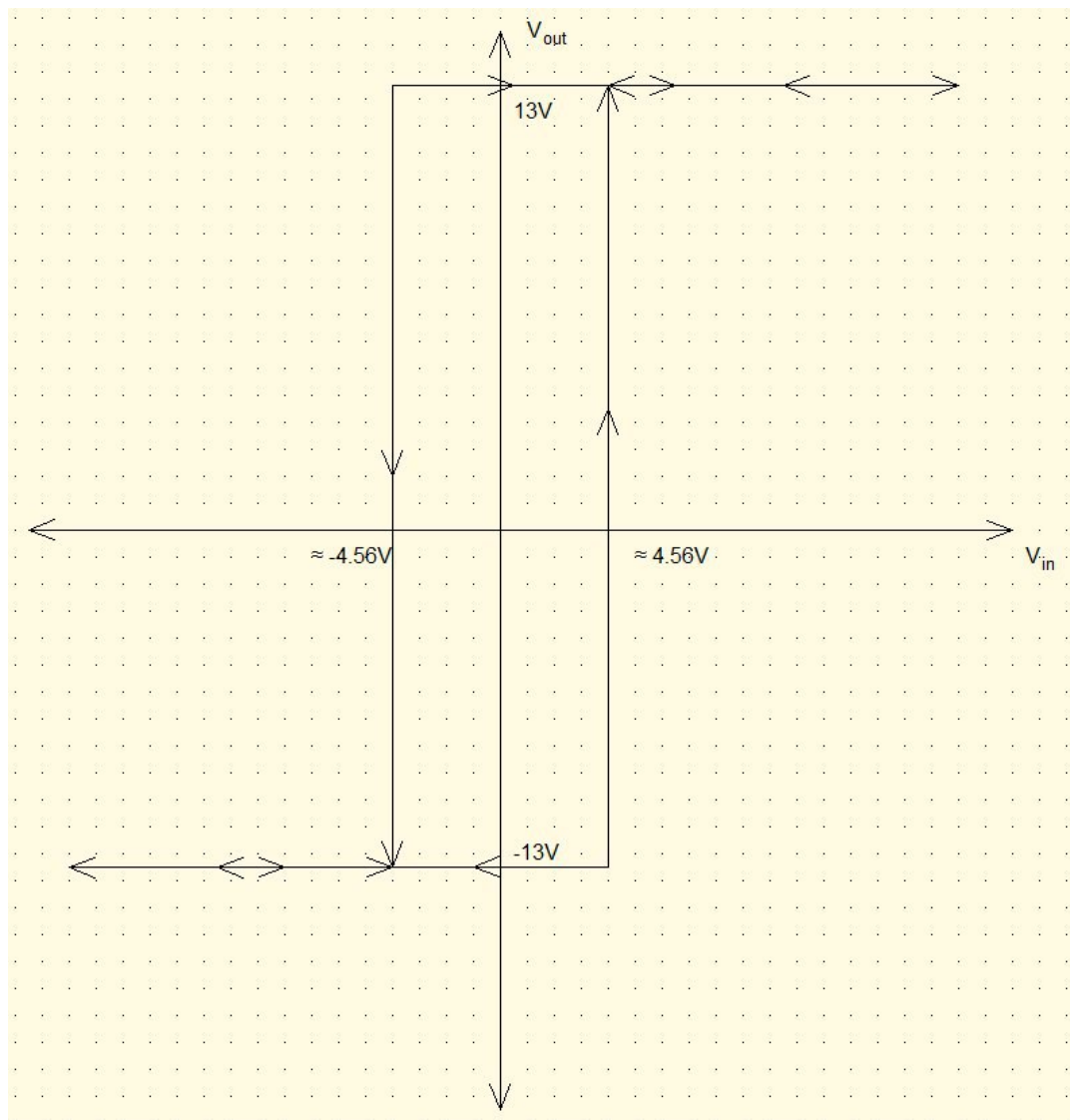



10. Sketch the output curve given the input curve below and the following:

$$R_1 = 9.0k\Omega \quad (10)$$

$$R_2 = 4.9k\Omega$$

$$V_{O(SAT)} = \pm 13V$$

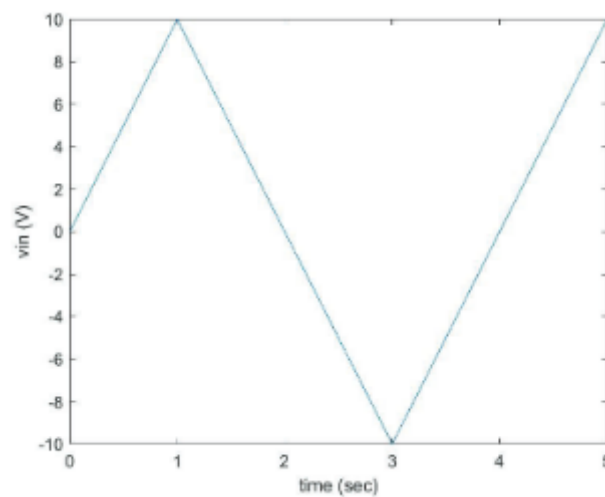

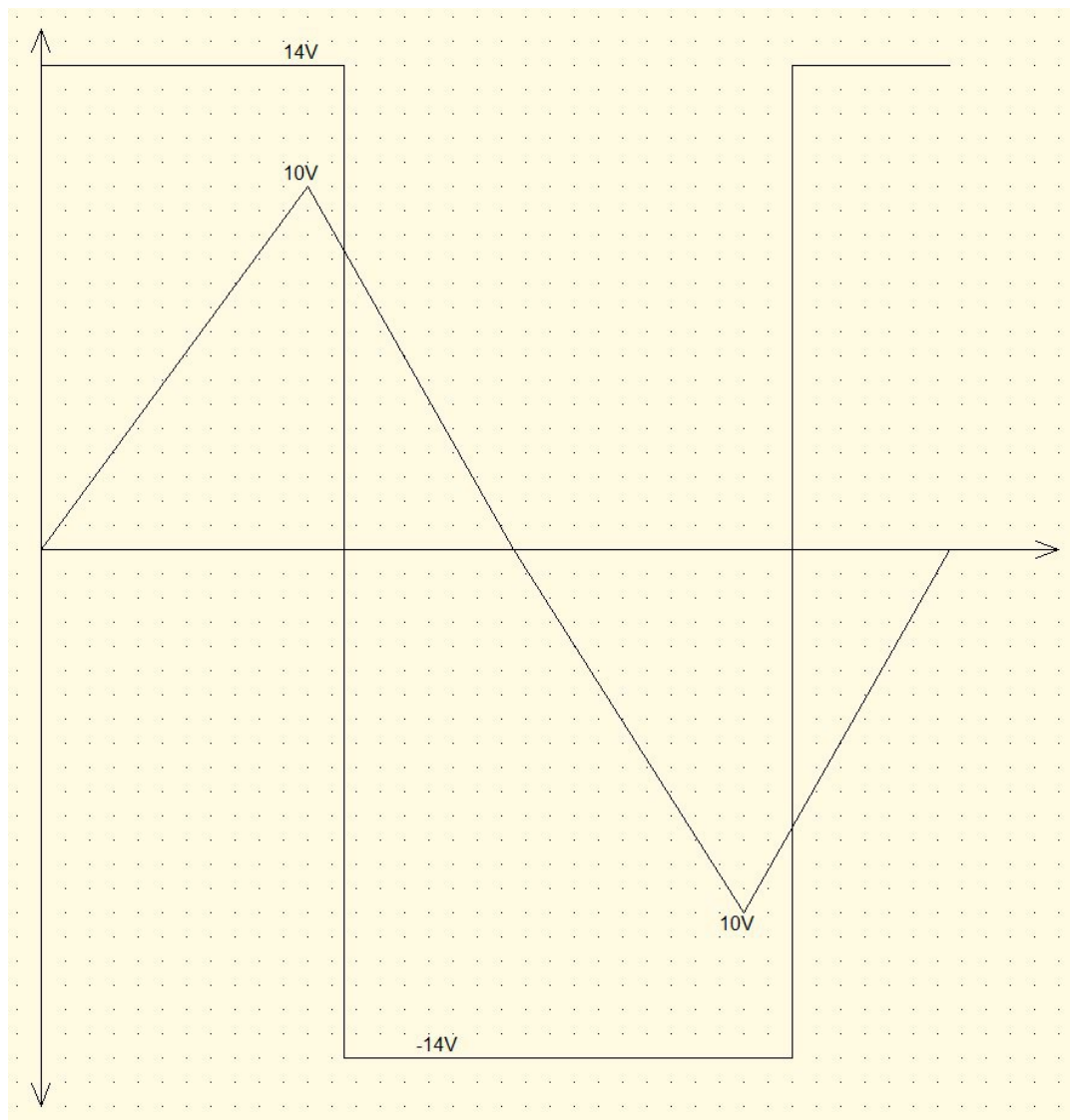



11. Sketch the input-output characteristic curve given the below image and the following:

$$R_1 = 9.6k\Omega \quad (11)$$

$$R_2 = 3.9k\Omega$$


$$V_{O(SAT)} = \pm 13V$$

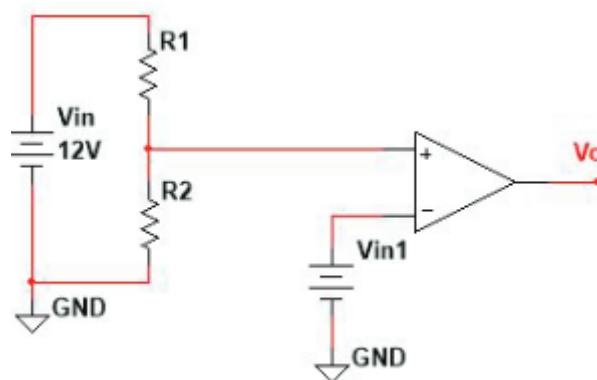


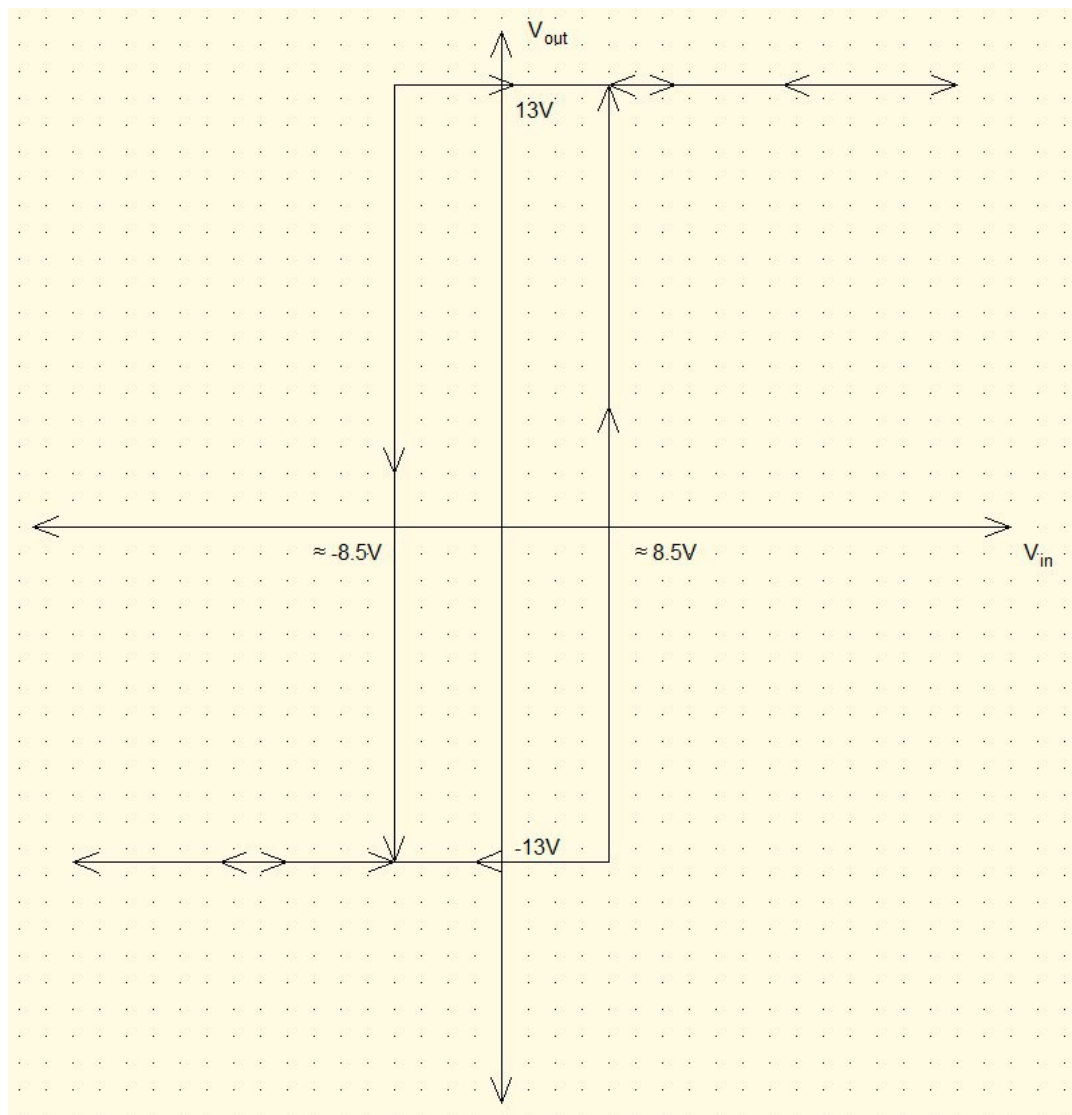

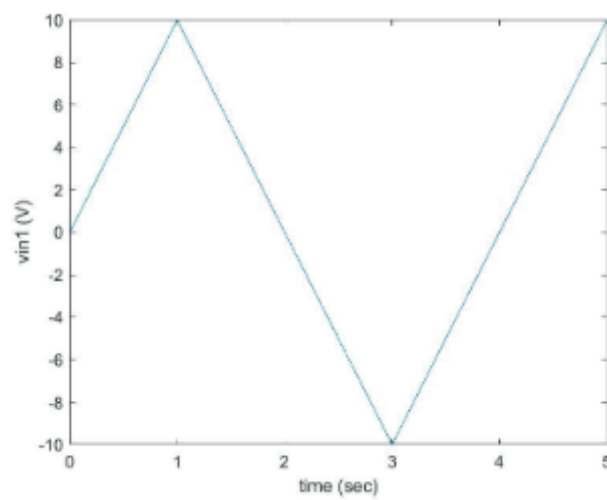12. Sketch the output curve given the input ( $V_{in1}$ ) curve and the following:

$$\begin{aligned} R_1 &= 9.7k\Omega \\ R_2 &= 3.2k\Omega \\ V_{O(SAT)} &= \pm 12V \end{aligned} \quad (12)$$



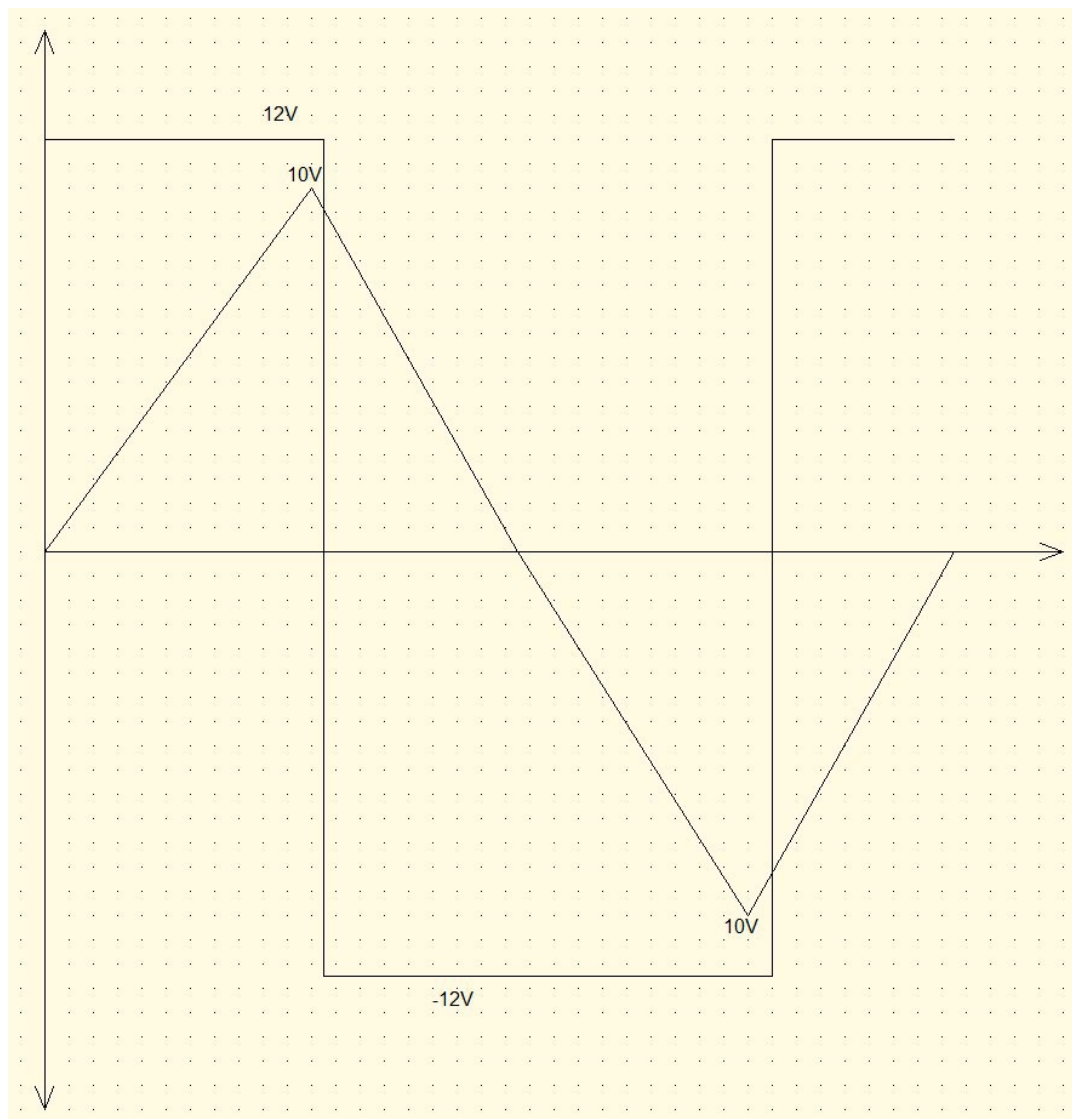

13. What has been the most confusing point so far in this class?

Nothing much in particular, although I may have missed the last couple problems on this exam due to misunderstanding how triggers work.