

Skyler MacDougall

Homework 6: Due 2/24/2020

5. Calculate the rise time T_{CL} associated with the following gain values:

1. $A_{CL} = 500$

$$A_{CL} = \frac{V_o}{V_i} = 1 - e^{-2\pi B_{CL}t} \quad (1)$$

$$A_{CL} - 1 = e^{-2\pi B_{CL}t}$$

$$\ln(A_{CL} - 1) = -2\pi B_{CL}t$$

$$\frac{\ln(A_{CL} - 1)}{-2\pi B_{CL}} = t; B_{CL} = 4kHz$$

$$\frac{\ln(499)}{-2\pi(4kHz)} = t$$

$$\underline{|t = 247.2\mu s|}$$

2. $A_{CL} = 50$

$$\frac{\ln(A_{CL} - 1)}{-2\pi B_{CL}} = t; B_{CL} = 40kHz \quad (2)$$

$$\frac{\ln(49)}{-2\pi(40kHz)} = t$$

$$\underline{|t = 15.5\mu s|}$$

3. $A_{CL} = 5$

$$\frac{\ln(A_{CL} - 1)}{-2\pi B_{CL}} = t; B_{CL} = 400kHz \quad (3)$$

$$\frac{\ln(4)}{-2\pi(400kHz)} = t$$

$$\underline{|t = 551.6ns|}$$

4. $A_{CL} = 1$

$$\frac{\ln(A_{CL} - 1)}{-2\pi B_{CL}} = t; B_{CL} = 2MHz \quad (4)$$


$$\frac{\ln(0)}{-2\pi(2MHz)} = t$$

$$\ln(0) = -\infty$$

$$\therefore$$

$$\underline{|t = unknown|}$$

9. Consider the following circuit:

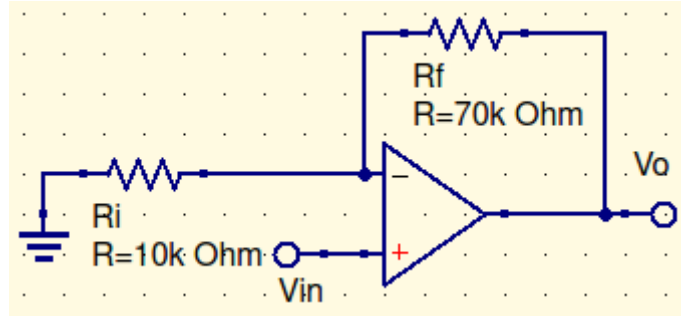

If the unity-gain frequency of the op amp is 1.6MHz, determine the closed loop 3-dB bandwidth.

$$A_{CL} = 1 + \frac{R_i}{R_f} = 1 + \frac{10k\Omega}{70k\Omega} = 1.1428 \quad (5)$$

$$B_{CL} = \frac{B}{A_{CL}} = \frac{1.6MHz}{1.1428}$$

$$\boxed{B_{CL} = 1.12MHz}$$


13. Calculate the rise time T_{CL} for the circuit stated above.

$$\frac{\ln(A_{CL} - 1)}{-2\pi B_{CL}} = t; B_{CL} = 1.12MHz \quad (6)$$

$$\frac{\ln(0.1418)}{-2\pi(1.12MHz)} = t$$

$$\boxed{t = 276.5ns}$$

19. Consider the circuit below:

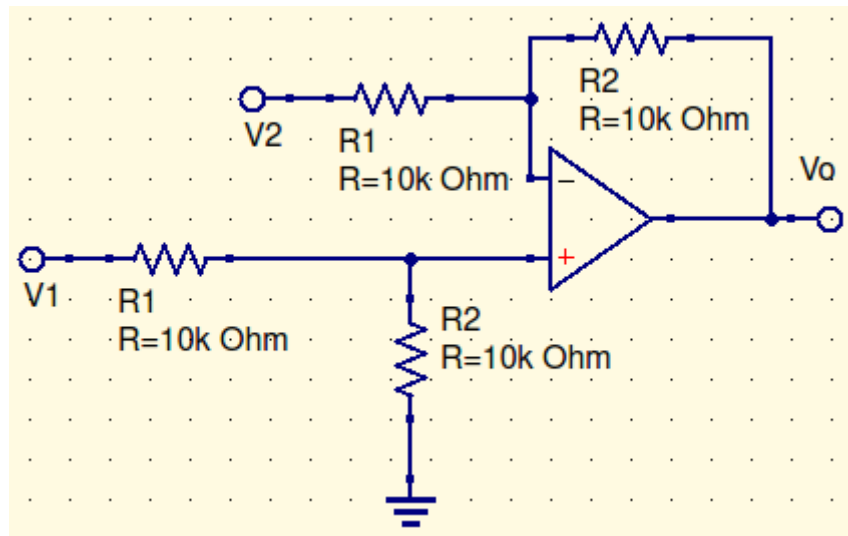

If the unity-gain frequency of the op-amp is 1MHz, determine the closed-loop 3-dB bandwidth.


$$B_{CL} = \frac{B}{A_{CL}} \quad (7)$$

$$A_{CL} = \frac{R_2}{R_1} = \frac{10k\Omega}{10k\Omega} = 1$$

$$B_{CL} = \frac{1MHz}{1}$$

$$\boxed{B_{CL} = 1MHz}$$

21. Consider the following circuit:

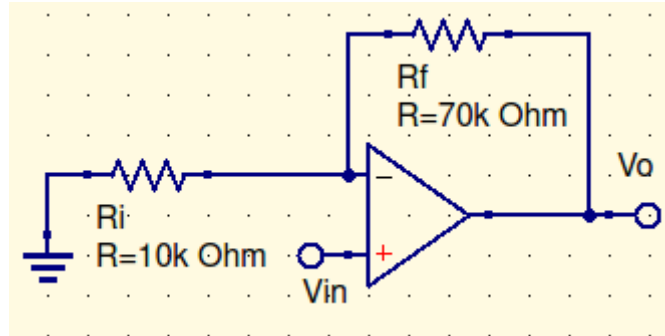

Assume that the op-amp slew rate is $0.6V/\mu s$. Calculate the rise time T_{SR} due to the slew rate when the input is a pulse that changes from zero to the following values:

1. 10mV

$$T_{SR} = \frac{V_o}{S} \quad (8)$$

$$T_{SR} = \frac{V_i A_{CL}}{0.6V/\mu s}$$

$$A_{CL} = 1 + \frac{R_i}{R_f} = 1 + \frac{10k\Omega}{70k\Omega}$$

$$T_{SR} = \frac{(10mV)(1.1428)}{0.6V/\mu s}$$

$$\boxed{T_{SR} = 23.8ns}$$

2. 0.1V

$$T_{SR} = \frac{V_i A_{CL}}{0.6V/\mu s} \quad (9)$$

$$T_{SR} = \frac{(100mV)(1.1428)}{0.6V/\mu s}$$

$$\boxed{T_{SR} = 238ns}$$


3. 1V

$$T_{SR} = \frac{V_i A_{CL}}{0.6V/\mu s} \quad (10)$$

$$T_{SR} = \frac{(1V)(1.1428)}{0.6V/\mu s}$$

$$\boxed{T_{SR} = 2.38\mu s}$$

23. Consider the following circuit:

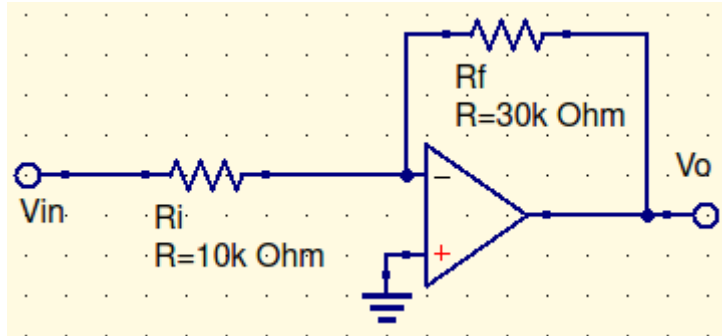

Assume that the op-amp slew rate is $0.5V/\mu s$. Calculate the rise time T_{SR} due to the slew rate when the input is a pulse that changes from zero to each of the following values:

1. 0.2V

$$T_{SR} = \frac{V_o}{S} \quad (11)$$

$$T_{SR} = \frac{V_i A_{CL}}{0.5V/\mu s}$$

$$A_{CL} = -\frac{R_f}{R_i} = \frac{-3}{1} = -3$$

$$T_{SR} = \frac{(0.2V)(-3)}{0.5V/\mu s}$$

$$\boxed{T_{SR} = 1.2\mu s}$$

2. 1V

$$T_{SR} = \frac{V_i A_{CL}}{0.5V/\mu s} \quad (12)$$

$$T_{SR} = \frac{(1V)(-3)}{0.5V/\mu s}$$

$$\boxed{T_{SR} = 6\mu s}$$

3. 3V

$$T_{SR} = \frac{V_i A_{CL}}{0.5V/\mu s} \quad (14)$$

$$T_{SR} = \frac{(3V)(-3)}{0.5V/\mu s}$$

$$\boxed{T_{SR} = 18\mu s}$$