

Skyler MacDougall

Homework 5: Due 2/17/2020

1. A certain op-amp has a unity-gain frequency of 2MHz. For a *noninverting* amplifier, calculate the closed-loop 3-dB bandwidth for each of the following ideal values of closed loop gain:

1. $A_{CL} = 500$

$$B_{CL} = B\beta; A_{CL} = \frac{1}{\beta} = K_n \quad (1)$$

$$\begin{aligned} \therefore \\ B_{CL} &= \frac{B}{A_{CL}} = \frac{2MHz}{500} \\ \underline{|B_{CL} = 4kHz|} \end{aligned}$$

2. $A_{CL} = 50$

$$B_{CL} = B\beta; A_{CL} = \frac{1}{\beta} = K_n \quad (2)$$

$$\begin{aligned} \therefore \\ B_{CL} &= \frac{B}{A_{CL}} = \frac{2MHz}{50} \\ \underline{|B_{CL} = 40kHz|} \end{aligned}$$

3. $A_{CL} = 5$

$$B_{CL} = \frac{B}{A_{CL}} = \frac{2MHz}{5} \quad (3)$$

$$\underline{|B_{CL} = 400kHz|}$$

4. $A_{CL} = 1$

$$B_{CL} = B\beta; A_{CL} = \frac{1}{\beta} = K_n \quad (4)$$

$$\begin{aligned} \therefore \\ B_{CL} &= \frac{B}{A_{CL}} = \frac{2MHz}{1} \\ \underline{|B_{CL} = 2MHz|} \end{aligned}$$

3. A certain op-amp has a unity-gain frequency of 2MHz. For an inverting amplifier, calculate the closed-loop 3-dB bandwidth for each of the following ideal values of closed loop gain:

1. $|A_{CL}| = 500$

$$B_{CL} = B\beta; |A_{CL}| = \frac{R_f}{R_i}; \beta = \frac{R_i}{R_f + R_i} \quad (5)$$

$$A_{CL} = 500; \therefore \beta = \frac{1}{501}$$

$$B_{CL} = \frac{B}{\beta} = \frac{2MHz}{501}$$

$$\boxed{|B_{CL} = 3.99kHz \approx 4kHz|}$$

$$2. |A_{CL}| = 50$$

$$B_{CL} = B\beta; |A_{CL}| = \frac{R_f}{R_i}; \beta = \frac{R_i}{R_f + R_i} \quad (6)$$

$$A_{CL} = 50; \therefore \beta = \frac{1}{51}$$

$$B_{CL} = \frac{B}{\beta} = \frac{2MHz}{51}$$

$$\boxed{|B_{CL} = 39.2kHz \approx 40kHz|}$$

$$3. |A_{CL}| = 5$$

$$B_{CL} = B\beta; |A_{CL}| = \frac{R_f}{R_i}; \beta = \frac{R_i}{R_f + R_i} \quad (7)$$

$$A_{CL} = 5; \therefore \beta = \frac{1}{6}$$

$$B_{CL} = \frac{B}{\beta} = \frac{2MHz}{6}$$

$$\boxed{|B_{CL} = 333.\bar{3}kHz|}$$

$$4. |A_{CL}| = 1$$

$$B_{CL} = B\beta; |A_{CL}| = \frac{R_f}{R_i}; \beta = \frac{R_i}{R_f + R_i} \quad (8)$$

$$A_{CL} = 1; \therefore \beta = \frac{1}{2}$$

$$B_{CL} = \frac{B}{\beta} = \frac{2MHz}{2}$$

$$\boxed{|B_{CL} = 1MHz|}$$