

Skyler MacDougall

Homework 3: due 2/3/2020

12. A single-phase motor draws a current of $12A$ at a power factor of 60% . Calculate the in phase and quadrature components of current I_p and I_q with respect to the line voltage.

$$I_S = 12A; pf = 0.6 \quad (1)$$

$$I_p = I_S(pf); I_q = I_S(\sin(\cos^{-1}(pf)))$$

$$I_p = 12A \times 0.6$$

$$\underline{I_p = 7.2A}$$

$$I_q = 12A \times (\sin(\cos^{-1}(0.6))) = 12A \times 0.8$$

$$\underline{I_q = 9.6A}$$

15. Using only power triangle concepts and without drawing any phasor diagrams, calculate the impedance of the circuits below.

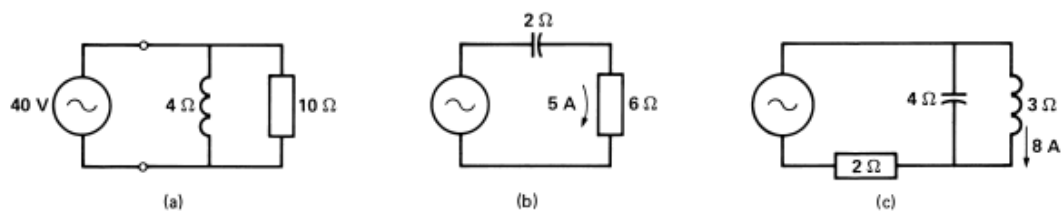


Figure 25
See Problem 15.

$$Q_L = \frac{V^2}{X_L} = \frac{(40V)^2}{4\Omega} = 400VAR \quad (2)$$

$$P = \frac{V^2}{R} = \frac{(40V)^2}{10\Omega} = 160W$$

$$S = \sqrt{P^2 + Q^2} = \sqrt{(160W)^2 + (400VAR)^2}$$

$$S \approx 431VA$$

$$Z = \frac{V^2}{S} \angle(\cos^{-1}(\frac{P}{S})) = \frac{(40V)^2}{431VA} \angle(\cos^{-1}(\frac{160W}{431VA}))$$

$$\underline{Z \approx 3.71\Omega \angle 68^\circ}$$

$$Q_L = I^2 X_C = (5A)^2 2\Omega = -50VAR \quad (3)$$

$$P = I^2 R = (5A)^2 6\Omega = 150W$$

$$S = \sqrt{P^2 + Q^2} = \sqrt{(150W)^2 + (-50VAR)^2}$$

$$S \approx 158VA$$

$$Z = \frac{S}{I^2} \angle(\cos^{-1}(\frac{P}{S})) = \frac{158VA}{(5A)^2} \angle(\cos^{-1}(\frac{150W}{158VA}))$$

$$\underline{Z \approx 6.3\Omega \angle 18^\circ}$$

$$\begin{aligned}
Q_L &= I^2 X_C = (5A)^2 2\Omega = -50VAR \\
P &= I^2 R = (5A)^2 6\Omega = 150W \\
S &= \sqrt{P^2 + Q^2} = \sqrt{(150W)^2 + (-50VAR)^2} \\
S &\approx 158VA \\
Z &= \frac{S}{I^2} \angle (\cos^{-1}(\frac{P}{S})) = \frac{158VA}{(5A)^2} \angle (\cos^{-1}(\frac{150W}{158VA})) \\
\boxed{Z \approx 6.3\Omega \angle 18^\circ}
\end{aligned} \tag{4}$$

20. If a $500VAR$ is put in parallel with a $3840VA$; $pf = 0.72$ motor, calculate

1. Active power.

The active power is unchanged at $2765W$, because the only thing we added was a capacitor, which is purely reactive power.

2. The apparent power of the system.

$$\begin{aligned}
S &= \sqrt{P^2 + Q^2}; P = 2765W; \\
Q_C &= -500VAR; Q_L \approx 2664VAR \\
S &= \sqrt{(2765W)^2 + (2664 - 500VAR)^2} \\
\text{sqrt}((2765^2) + (\text{answer}(18) - 500)^2) &\boxed{S \approx 3511VA}
\end{aligned} \tag{5}$$

3. The power factor of the system.

$$\begin{aligned}
pf &= \frac{P}{S}; P = 2765W; S = 3511VA \\
pf &= \frac{2765W}{3511VA} \\
\boxed{pf \approx 0.79}
\end{aligned} \tag{6}$$

21. A coil having a reactance of 10Ω and a resistance of 2Ω is connected in parallel with a capacitive reactance of 10Ω . If the supply voltage is $200V$, calculate

1. The reactive power generated by the coil

$$\begin{aligned}
Q &= \frac{V^2}{X_L} = \frac{(200V)^2}{10\Omega} \\
\boxed{Q = 4kVAR}
\end{aligned} \tag{7}$$

2. The reactive power generated by the capacitor

$$\begin{aligned}
Q &= \frac{V^2}{X_C} = \frac{(200V)^2}{10\Omega} \\
\boxed{Q = -4kVAR}
\end{aligned} \tag{8}$$

3. The active power dissipated by the coil

$$P = \frac{V^2}{R} = \frac{(200V)^2}{2\Omega} \quad (9)$$

$$\boxed{P = 20kW}$$

4. The apparent power of the circuit

$$S = \sqrt{P^2 + (\sum Q)^2} \quad (10)$$

$$S = \sqrt{(20kW)^2 + (4kVAR - 4kVAR)^2}$$

$$\boxed{S = 20kVA}$$

26. A capacitor bank has a resistor connected to it, to dissipate voltage after its been disconnected. It should have $\leq 50V$ after 1 minute of disconnection. Calculate the discharge resistance required for a $30kVAR$, $480V$ capacitor. Then, calculate the wattage rating for the resistor.

$$30kVAR; 480V; C \approx 345\mu F \quad (11)$$

$$V(0) = 480V; V_0 = 480V$$

$$V_0 e^{\frac{-t}{RC}} = V(t)$$

$$R = \frac{60}{\approx 345\mu F (\ln(\frac{5}{48}))}$$

$$R \approx 76k\Omega$$

$$P = \frac{V^2}{R} = \frac{480^2}{76k\Omega}$$

$$\boxed{R \approx 76k\Omega; P \approx 3W}$$