

# Skyler MacDougall

## Homework 5: due 2/19/2020

14. The primary of a transformer has twice as many turns as the secondary. ( $a = 2$ ) The primary voltage is  $220V$  and a  $5\Omega$  load is connected across the secondary. Calculate the power delivered by the transformer, as well as the primary and secondary current.

$$V_p = 220V; Z_s = 5\Omega \quad (1)$$

$$V_s = \frac{V_p}{a} = \frac{220V}{2} = 110V$$

$$P = \frac{V_s^2}{Z_s} = \frac{110V^2}{5\Omega}$$

$$P = 2420W$$

$$I_s = \frac{V_s}{Z_s} = \frac{110V}{5\Omega}$$

$$I_s = 22A$$

$$I_p = \frac{I_s}{a} = \frac{22A}{2}$$

$$I_p = 11A$$

$$\boxed{P = 2420W; I_s = 22A; I_p = 11A}$$

21. Explain why the secondary voltage of a practical transformer decreases with increasing resistive loads.

The voltage decreases, because there is more voltage going to the internal losses.

25. A 66.7MVA transformer has an efficiency of 99.3% when it delivers full power to a load having a power factor of 100%.

1. Calculate the losses in the transformer under these conditions.

$$efficiency = \frac{P_s}{P_p} \quad (2)$$

$$P_s = 66.7MW * 0.993 = 66.2331MW$$

$$losses = P_p - P_s = 66.7MW - 66.2331MW$$

$$\boxed{losses = 466.9kW}$$

2. Calculate the losses and efficiency when the transformer delivers 66.7MVA to a load having a power factor of 80%.

$$\text{losses are consistent} \quad (3)$$

$$\therefore$$

$$\text{losses} = 466.9kW$$

$$P_s = 66.2MW; S = \frac{P}{pf} = \frac{66.2MW}{0.8} = 82.75MVA$$

$$S_p = \frac{66.7MW}{0.8} = 83.375MVA$$

$$\text{efficiency} = \frac{S_s}{S_p} = \frac{83.375MVA}{82.75MVA}$$

$$\boxed{\text{losses} = 466.9kW; \text{efficiency} = 98.7\%}$$

30. During a short-circuit test on a 10MVA, 66kV-7.6kV transformer, the following results were obtained.

$$E_g = 2640V \quad (4)$$

$$I_{sc} = 72A$$

$$P_{sc} = 9.85kW$$

Calculate:

1. The total resistance and total leakage reactance referred to the 66kV primary side.

$$10MVA \gg 100kVA \quad (5)$$

$$\therefore$$

$$Z \approx X$$

$$Z = \frac{V}{I} = \frac{2640V}{72A} \approx 37\Omega$$

$$\boxed{R \approx 0\Omega; X \approx 37\Omega}$$

2. The nominal impedance of the transformer referred to the primary side.

$$Z_n = \frac{E^2}{S_n} = \frac{(66kV)^2}{10MVA} \quad (6)$$

$$\boxed{Z_n = 435.6\Omega}$$

3. The percent impedance of the transformer.

$$Z_p(pu) = \frac{Z_p}{Z_{n_p}} = \frac{37\Omega}{435.6\Omega} \quad (7)$$

$$\boxed{Z_p(pu) = 8.42\%}$$


31. In the above problem, if the iron losses at rated voltage are 35kW, calculate the full-load efficiency of the transformer if the power factor of the load is 85%.

$$35kW @ pf = 0.85; S = \frac{P}{pf} = \frac{35kW}{0.85} = 41.2kVA \quad (8)$$

$$efficiency = \frac{S_s}{S_p} = \frac{10MVA - 41.2kVA}{10MVA}$$

$$\boxed{efficiency = 99.5\%}$$

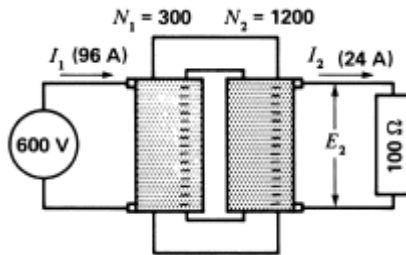33. If a transformer were actually built according to the below diagram, it would have very poor voltage regulation. Explain why, and propose a method for improving it.



When the load is reflected across the transformer, it becomes significantly smaller, where the internal losses are significant.

One can change this in as simple a step as changing the sides that the power and the load are connected to, although if current or voltage requirements exist, it may be more difficult.